

TRANSISTORIZED AMATEUR TRANSMITTER

RADIO & TELEVISION NEWS

FEBRUARY
1957
35 CENTS

World's Largest Electronics Magazine

ALCONY OR ORCHESTRA—
WHICH LOUDSPEAKER?

THE STRATEGY OF
COLOR SERVICING

MINIATURE SCOPE
FOR THE HAMSHACK

A COMPACT 6 WATT
POWER AMPLIFIER

COMMON-SENSE
TROUBLESHOOTING

FIELD-STRENGTH METER
THAT TESTS TUNERS

ELECTRONIC AGITATOR

5,000 MILES-PER-WATT
(See Page 37)



W10GU





Answers Independent Service Dealers' Questions About "Captive Service"

What is "Captive Service"?

It is the repair work done by service companies owned by set manufacturers — companies established by them to handle the profitable TV and radio set maintenance on receivers of their own manufacture — work that otherwise would be handled by Independent Service Dealers.

Will "Captive Service" affect my volume of business as an Independent Service Dealer?

A conservative estimate by service association spokesmen indicates that in 1957 Captive Service Companies could do close to \$250,000,000 worth of TV and radio repair work.

Does Raytheon compete with me through a "Captive Service" organization?

No, indeed! Raytheon does not have a captive TV-Radio service organization — does not now manufacture TV or radio receivers.

Raytheon believes service is your business — serving you is Raytheon's.

How can I compete with the "Captive Service" organizations of big national companies?

Raytheon helps you do this. If you can qualify as a RAYTHEON Bonded ELECTRONIC TECHNICIAN, your service and parts guarantee is backed by a bond — a bond issued through Continental Casualty Company, one of the country's largest insurance companies. Here is real prestige for you. What's more, your work on all makes and models of sets is bonded.



Will becoming a Raytheon Bonded Dealer mean I'll lose my "independence"?

Not at all. You become one of a group of TV-radio technicians known from coast-to-coast as the best in the business, yet you retain your own "independence." The Raytheon Bonded Program is nothing new. It's a proven program Raytheon has provided for more than 11 years — that has successfully helped build premium customer business for Independent "Bonded" Service Dealers. It's Raytheon's investment in your future.

How does being a Raytheon Bonded Dealer help me compete with "Captive Service" companies?

- (1) Your TV-radio repair service is nationally advertised by Raytheon in TV Guide Magazine.
- (2) Western Union "Operator 25" is retained in 23,000 cities and towns by Raytheon to send customers to Raytheon Bonded Dealers.
- (3) You are bonded to service all makes and models of sets — a big advantage.

Will I have other advantages over "Captive Service" organizations?

Yes, you'll be using Raytheon TV and Radio Tubes. They are perfect for your replacement work because Raytheon Tubes are designed to give quality performance in all Television and Radio sets.

How do I get the whole story on the Raytheon Bonded Program?

Ask your nearest Raytheon Sponsoring Bonded Tube Distributor.

RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, all these Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



Excellence in Electronics

N
t
N
Tube
Signa

S

The
Prof
pres
high
tice
Tech
be th
Serv
If yo
and
Tele
error
face
solve
you

N.R.


Over
recon
this
Serv
ing a
cond
TV
"tric
Serv
any
Yo

The
spec
know
vast

RAD
Chic
ment

Febru

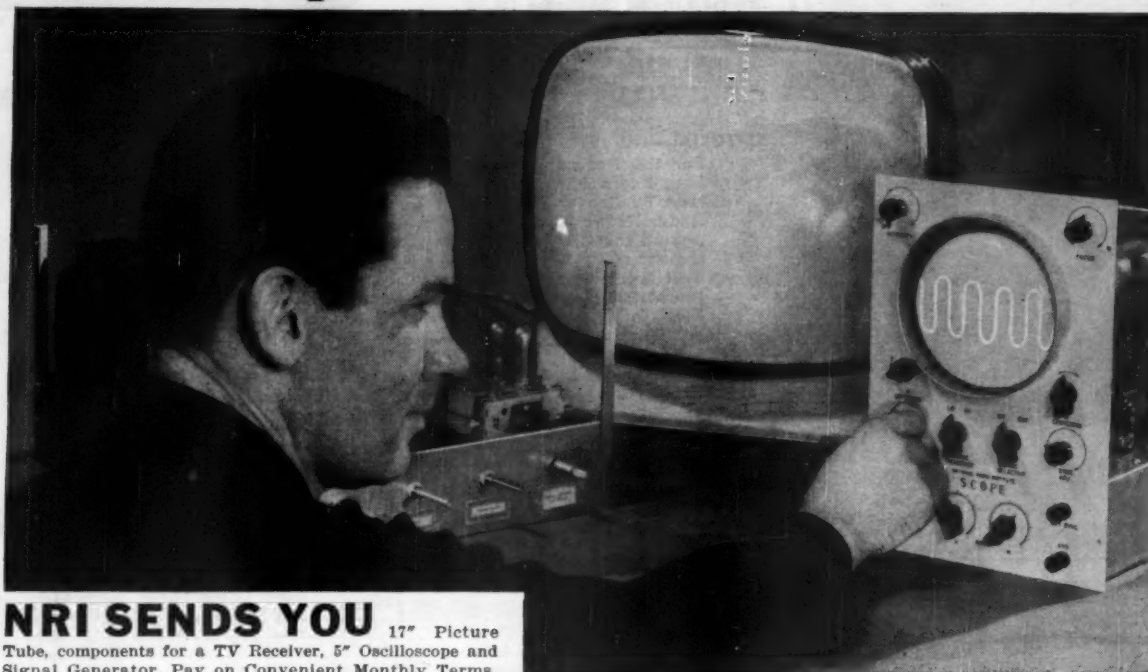NOW-A Faster Way to Reach the Top in TV SERVICING



NRI SENDS YOU 17" Picture Tube, components for a TV Receiver, 5" Oscilloscope and Signal Generator. Pay on Convenient Monthly Terms.

N.R.I. All-Practice Method Trains You at Home in Spare Time to Fix TV Sets Quickly, with Confidence

The man who knows the answers—the Professional TV Technician enjoys the prestige, gets the better jobs, the higher pay. Here is the learn-by-practice training to be a Professional TV Technician. It shows you the way to be the boss, to earn top pay. Television Servicing needs more well trained men. If you have a basic knowledge of radio and electronics you can make some Television repairs simply by trial and error. But sooner or later you will face TV Service problems you can not solve. And you can't get the training you need while customers wait.

N.R.I. is Oldest and Largest Home Study Radio-TV School

Over forty years experience and the record and reputation of NRI back up this learn-by-doing Professional TV Servicing Course. Instead of just reading about TV problems, you build and conduct experiments on circuits in a TV receiver. You learn methods, "tricks of the trade" proved by top TV Servicemen. You learn to fix any set, any model with confidence.

You Get COLOR TV Textbooks Early

The day you enroll, N.R.I. sends you special Color-TV books to speed your knowledge and understanding of this vast, growing phase of Television.

Many full color pictures and diagrams help you recognize defects and help you learn how to correct them quickly and properly. To cash in on the coming Color TV boom, you'll need the kind of knowledge and experience this NRI training gives.

This is 100% learn-by-doing, practical training. Here is a course for men who know basic theory, either from Radio or TV Servicing experience or planned training but realize the need for more knowledge to forge ahead. Here is what one graduate, G. G. STETHEM of Belpre, Ohio says, "I can not praise N.R.I.'s Professional TV Course highly enough. I have my own spare time

shop and all the Radio-TV work I can handle."

Another graduate, EDWARD RAVITSKY of Northumberland, Pa. says, "I have taken your course in Professional TV Servicing. It takes the kind of experience you offer to really learn." If you want to go places faster in TV servicing, make your future more secure as the industry develops, we invite you to find out what you get, what you practice, what you learn from NRI's Course in Professional TV Servicing. Mail the coupon now. There is no obligation. NATIONAL RADIO INSTITUTE, Dept. 7BET, WASHINGTON 9, D. C.



**Send for
FREE
BOOK**

NATIONAL RADIO INSTITUTE

Dept. 7BET, Washington 9, D.C.

Please send FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name.....Age.....

Address.....

City.....Zone.....State.....

Accredited Member, National Home Study Council.

RADIO & TELEVISION NEWS is published monthly by Ziff-Davis Publishing Company, William B. Ziff, Chairman of the Board (1946-1953), at 64 E. Lake St., Chicago 1, Ill. Entered as second-class matter July 21, 1945, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Authorized by Post Office Department, Ottawa, Canada, as second-class matter. SUBSCRIPTION RATES: Radio & Television News—one year U. S. and possessions, and Canada \$4.00; Pan-American Union countries \$4.50; all other foreign countries \$5.00.

Publisher
OLIVER READ, D.E., WIETI
Editor
WIL. A. STOCKLIN, B. S.
Technical Editor
MILTON S. SNITZER
Service Editor
SIDNEY C. SILVER
Associate Editor
P. B. HOFFER
Assistant Editor
J. JUSTER

Television Consultant
WALTER H. BUCHSBAUM

Art Editor
FRANK SAYLES

Art and Drafting Dept.
J. A. GOLANIK
W. K. VAHLING
JAMES A. ROTH

Advertising Director
L. L. OSTEN

Advertising Manager
MURRAY GOLDMAN

Midwest Adv. Manager
JOHN A. ROMAN, JR.

Western Adv. Manager
JOHN L. PAYNE



COVER PHOTO: Gus Fallgren tries out his history-making transmitter, the first to span the Atlantic on transistor power. Two Raytheon transistors are used. See article, page 37. (Ktichrome by G. E. Meyers, Raytheon)

ZIFF-DAVIS PUBLISHING COMPANY

President
B. G. DAVIS

Vice-President
H. J. MORGANROTH

Vice-President
M. H. FROELICH

Vice-President & Circulation Dir.
M. MICHAELSON

Secretary-Treasurer
G. I. CARNEY

Art Director
AL GRUEN

BRANCH OFFICES

CHICAGO (1)
64 E. Lake St., AN 3-5200
LOS ANGELES (14)
215 W. 7th St. (Phone 442) Tri-Union

First in radio- television-audio-electronics

Average Net Paid Circulation 258,780

Radio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U. S. Pat. Office.

RADIO & TELEVISION NEWS

Reg. U. S. Pat. Off.

CONTENTS

FEBRUARY, 1957

EDITORIAL—INDUSTRY NEWS

For the Record.....	O. Read	8
Spot Radio News.....	Washington Correspondent	12
New TV Grants Since Freeze Lift.....		12
Radar Network for Air Traffic Control.....		61
Behind the Giant Brains (Part 2).....	Frank Leary	70
Industrial TV Control System.....		94
B-52 Bomb-Navigation System.....		100
Rubberized Circuits for Guided Missiles.....		116
First Guidance System for Satellite Rocket.....		124
West Coast Hi-Fi Shows.....		159

HIGH FIDELITY AND AUDIO

A Plug-In "Presence" Equalizer.....	Allan M. Ferres	42
Balcony or Orchestra—which Loudspeaker?.....	Phil Bernheim	44
Certified Record Revue.....	Bert Whyte	50
Realistic High Fidelity—Audio Output Tubes and Circuits (Part 10).....	H. A. Hartley	51
A Compact 6 Watt Power Amplifier.....	E. Taylor Horton	62
A Simplified Automatic Tone Compensator.....	Ed. C. Miller	67
New Hi-Fi—Audio Equipment.....		153

SERVICING

Television-Radio

The Strategy of Color Servicing.....	Art Margolis	40
Sylvania Color TV Circuits.....	Walter H. Buchsbaum	54
Common-Sense Troubleshooting.....	Charles Garrett	58
Service Diversification.....	William Leonard	60
Component Checking.....	N. H. Crowhurst	64
Mac's Service Shop.....	John T. Frye	76
Curing TV I.F. Troubles.....	Donald Quaranta	110
Bench Puzzlers.....	James A. McRoberts	130
Antenna News.....		134
'56 G-E TV; Many Symptoms—One Cause.....	Lloyd B. Hust	145
Service Industry News.....		194

Test Equipment

A Portable Thyatron Tester.....	W. Philbrook	46
Portable 90-Degree Test CRT.....	John T. Jans	49
A Field-Strength Meter that Tests Tuners.....	Robert G. Middleton	56
New Tube Tester Data.....		98

AMATEUR AND COMMUNICATIONS

Transistorized Amateur Transmitter—45,000 Miles-per-Watt.....		
.....Gus Fallgren, W10GU & Al Hankinson, W10SF		37
Miniature Scope for the Hamshack.....	Rob Wagner, W6WGD	68

ELECTRONIC CONSTRUCTION AND THEORY

Electronic Agitator—For Color Film Processing.....	Arthur Ross, Jr.	43
Subminiature Construction Techniques for the Home Builder.....		
.....Louis E. Garner, Jr.		72
TV-to-Radio Wireless Oscillator.....	Harold Reed	150

DEPARTMENTS

Within the Industry.....	26	Manufacturers' Literature.....	172
Sales Aids.....	103	Technical Books.....	181
Calendar of Events.....	123	What's New in Radio.....	187



ZIFF-DAVIS PUBLISHING COMPANY
WILLIAM B. ZIFF (1898-1953) FOUNDER
Editorial and Executive Offices
344 Madison Ave., New York 17, N. Y.
MU 7-4080
VOLUME 57 • NUMBER 2




Copyright © 1957 by Ziff-Davis Publishing Company. All rights reserved.

SUBSCRIPTION SERVICE. All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Subscribers should allow at least four weeks for change of address. Include your old address as well as new—enclosing, if possible, an address label from a recent issue of this magazine.

CONTRIBUTIONS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's, and contestant's rights, title, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material purchased.

RADIO & TELEVISION NEWS

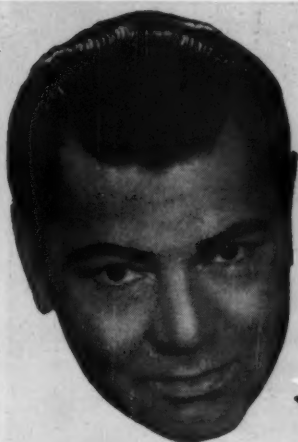

Jack Dempsey

The former world's heavyweight boxing champion says: "I know the value of good training, and believe me, for 25 years, DeVry has been one of America's outstanding electronics training centers! The Employment Service is 'tops' too!"

THESE DeVRY TECH GRADUATES VERIFY WHAT DEMPSEY SAYS



NICK BARTON, Illinois, a DeVry graduate, now has his own business and tells us he is "literally snowed with work."

GEORGE D. CROUCH, California, was a retail store clerk. He took the DeVry program, and today is in business for himself.



EDWARD HAHN, Illinois. Now an electronics technician with Televiso, Inc. DeVry Tech training helped him prepare for his present position.



"If You Want to Make More Money Full or Part Time in TELEVISION RADIO • ELECTRONICS DeVry Tech Has An Answer," SAYS JACK DEMPSEY

NO TECHNICAL EXPERIENCE NEEDED—YOU CAN LEARN IN YOUR OWN HOME!

Great opportunities are found in Electronics—one of today's top fields. Good jobs in modern plants, TV—Radio studios, offices and laboratories await trained men who can build, install, operate and service Electronic equipment. And equally exciting are the possibilities for starting your own servicing shop. The coupon below will bring you full details—Free!

HERE'S HOW TO GET STARTED!


You can get Television-Radio-Electronics training right in your own home. You don't need previous technical experience, advanced education, or exceptional "aptitude." And the training DeVry Tech provides is "tops." What's more, DeVry helps you get started toward a job, or a servicing shop of your own!

TOO GOOD TO BE TRUE?

Not at all! Our files show that many men—high school graduates, truck drivers, store clerks, unskilled workers—now have the better jobs they wanted because of their DeVry diplomas. Age is no barrier—DeVry trains men 17—55.

TWO GREAT TRAINING CENTERS—CHICAGO and TORONTO

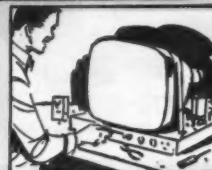If you can come to either of DeVry's training centers—Chicago or Toronto—you can prepare under the close guidance of friendly, experienced instructors. You can use valuable equipment similar to that found in the field. Write today for complete information.



EARN AS YOU LEARN—by servicing radio and TV sets at home before you complete the training.



LIVE-WIRE EMPLOYMENT SERVICE—puts you in touch with job opportunities—even helps you establish a service shop of your own.



BUILD TEST EQUIPMENT—You assemble your own high quality test equipment to help you earn money servicing Radio and TV sets in your spare time.

A SAMPLE LESSON IS YOURS

See for yourself how DeVry trains you for real opportunities in Electronics. We'll also give you a free copy of an interesting booklet, "Electronics and YOU."


FREE!



ARE YOU OF DRAFT AGE?

We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.

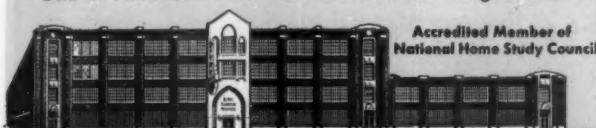"One of America's Foremost Electronics Training Centers"



Accredited Member of National Home Study Council

DEVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

FORMERLY

DEFOREST'S TRAINING, INC.



MAIL TODAY FOR FREE FACTS

DeVry Technical Institute
4141 Belmont Ave., Chicago 41, Ill., Dept. RN-2-N

Please give me a FREE Sample Lesson and your booklet, "Electronics and YOU."

Name Age

Please Print

Street Apt.

City Zone State

☐ Check here if subject to military training.

#1080

DeVry's Canadian Training Center is located at
580 Roselawn Avenue, Toronto 12, Ontario



AR-22



TR-2



TR-4

CDR ROTORS



TR 11 and 12



AR 1 and 2

5-star feature...




the best color TV picture

the growth of color TV means an even greater demand for CDR Rotors for pin-point accuracy of antenna direction.



a better picture on more stations

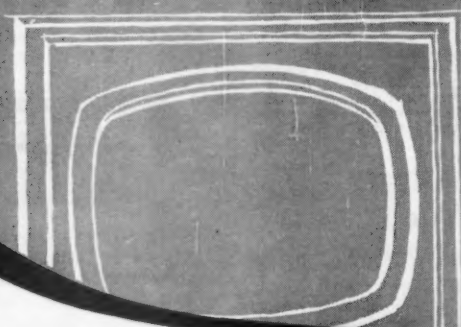CDR Rotors add to the pleasure of TV viewing because they line up the antenna perfectly with the transmitted TV signal giving a BETTER picture... and making it possible to bring in MORE stations.



tested and proven dependable

thousands and thousands of CDR Rotors have proven their dependability over years of unfailing performance in installations everywhere in the nation. Quality and engineering you know you can count on.



pre-sold to your customers

the greatest coverage and concentration of full minute spot announcements on leading TV stations is working for YOU... pre-selling your customers.



the complete line

a model for every need... for every application. CDR Rotors make it possible for you to give your customer exactly what is needed... the right CDR Rotor for the right job.



CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

**GREATEST
ADVANCE IN
SHOP-METHOD
HOME TRAINING**

EARN MORE MONEY... GET INTO

TELEVISION


ELECTRONICS-RADIO

Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE

At Home - In Spare Time

YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

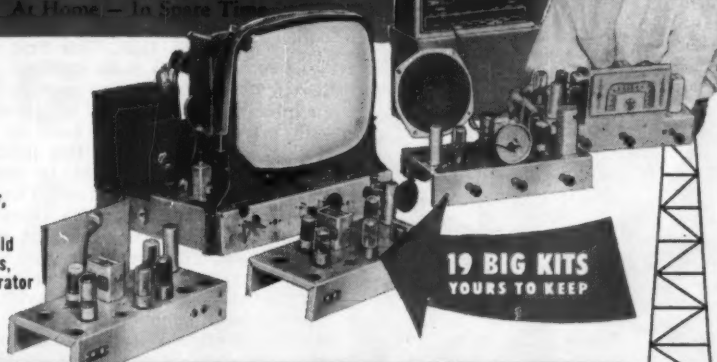- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester



**19 BIG KITS
YOURS TO KEEP**

YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

- | | |
|------------------------------------|--------------------------------|
| 1. TELEVISION, INCLUDING COLOR TV | 5. PREPARATION FOR FCC LICENSE |
| 2. RADIO, FM AND AM | 6. AUTOMATION |
| 3. INDUSTRIAL ELECTRONICS | 7. RADAR AND MICRO WAVES |
| 4. SOUND RECORDING AND HI FIDELITY | 8. COMMUNICATIONS |

YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY!

You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits - even prepare for FCC License without taking a special

course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!

EARN AS YOU LEARN. Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

YOU GET EVERYTHING YOU NEED - Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects - all the valuable equipment shown above

- many other materials and services
- consultation privilege with our qualified staff, and Graduate Employment Service. **EVERYTHING YOU NEED** for outstanding success in Electronics

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school—and part time job while you learn. Check box in coupon for full information.



MEMBER



FREE!

Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson—yours at no cost, no obligation. CLIP COUPON NOW... MAIL IT TODAY!

APPROVED FOR G.I. TRAINING

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.
187 N. LA SALLE ST., CHICAGO 1, ILL.
IN CANADA: 811 W. HASTINGS ST., VANCOUVER, B. C.

NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA


GET FAST SERVICE - MAIL NOW TO OFFICE NEAREST YOU!

NATIONAL SCHOOLS, DEPT. RH-27
4000 S. FIGUEROA ST. 187 N. LA SALLE ST.
LOS ANGELES 37, CALIF. OR CHICAGO 1, ILL.
Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

☐ Check if interested ONLY in Resident School training at Los Angeles.
VETERANS Give date of Discharge _____

Star Performer
at a Modest Price

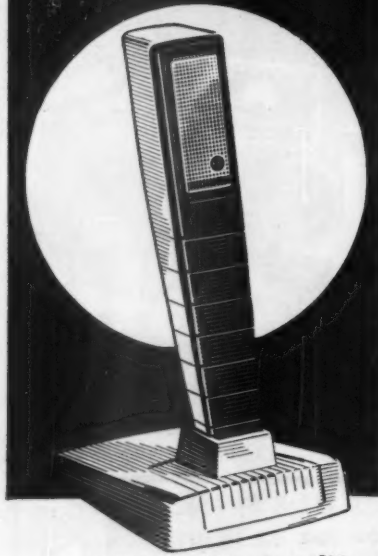

E-V Model 927 Microphone. $1\frac{1}{4}$ " wide x $1\frac{1}{2}$ " deep. $7\frac{1}{16}$ " long. Weight: 14 oz. with cable. Complete with desk stand and 5' cable, \$22.50 List.

Electro-Voice

Model 927 Crystal Microphone

No one—not even Electro-Voice—makes one microphone that does everything. Electro-Voice does make the closest thing to an all-purpose microphone on the market, the Model 927. For public address, call and paging systems, for dictating machines and home recorders, for amateur radio, for every general communications need.

Maximum versatility at a modest price. That's what you get in the E-V Model 927. Designed primarily for hand use, it comes complete with a heavy die-cast slip-in stand for desk use. Attractive, streamlined microphone case of sturdy die-cast metal and plastic in metalustre medium gray. It's omni-directional, has a 60 to 6,000 cps frequency response, can be used with any standard amplifier.

See your E-V Distributor or write for booklet N71, "A B C's of Microphones."

Electro-Voice®

ELECTRO-VOICE, INC. • BUCHANAN, MICHIGAN

Canada: E-V of Canada Ltd., 1008 Avenue Road, Toronto, Ontario, Export: 18 East 40th Street, New York 16, U. S. A. Cables: ARI-AB

For the RECORD.

RADIO—THIRTY YEARS AGO

THE first radio network was organized (NBC) and began broadcasting on November 15, 1926. This first network comprised 25 radio stations. Today NBC has grown to include 188 radio stations and 207 TV affiliates.

In retrospect we look back to the November, 1926 issue of this publication, then seven years old, to review the technology of the period: The use of vacuum tubes for radio reception was, at the time, replacing the crystal detector. The first cone-type loudspeakers (not dynamics) were reaching popularity and were available from several suppliers. Radio receivers had finally developed to the point where a single tuning dial could be ganged to an average of three variable condensers for tuning purposes.

Audio was receiving some attention, and a new transformer was offered at \$12 which, according to the "amplification curve," was somewhat flat between 500 and 4000 cycles. Response at that time was based on a musical scale. A feature article appeared in the November, 1926 issue titled, "Television en Route." It began with "The day of television is rapidly approaching; it will be with us very shortly." The article told how inventions by German scientists had removed the last difficulties in the field of "photo-telegraphy" and went on to describe the apparatus.

Another feature titled, "Radio Is Making Us 'Ear-Minded,'" served to teach the listener to enjoy programs by hearing and not to continually look at the loudspeaker as a subconscious aid to the distinguishing of different volume levels in music. The service industry (and it could hardly be called that) was not without its "grafters," and an article revealed case histories where unscrupulous mechanics had already taken advantage of a gullible public. At the time one of the favorite tricks was for the technician (if you'll pardon the expression) to shake his head dolefully and look at the customer as the ammeter indicator pointed only to "3." Batteries of all descriptions were used commonly for the operation of radio apparatus in 1926. They included $1\frac{1}{2}$ -volt dry cells, single cell wet and dry "A" batteries, 48-volt storage "B" batteries, and 45-volt dry cell "B" batteries. Battery chargers were a necessity in the average home.

New products announced in November, 1926, included a shielded 6-tube receiver, a double-range receiver, a new variable condenser designed to obtain the greatest possible separation of stations, a console receiver having

ample space to house battery eliminators at sufficient distance from the set to escape any hum, a variometer-tuned receiver connected to a single dial, a talking book (loudspeaker in the form of an open book), a 7-tube neutrodyne, several cone speakers and an electrolytic rectifier B unit.

The home builder was giving serious attention to the design of portable sets. The staff of this magazine designed such a unit which they called a "superhet travelling companion." It would work well on all local stations using a loop antenna and was capable of some DX with an outdoor aerial. In contrast to present-day transistorized portables, the one described required the use of an "A" battery comprised of six $4\frac{1}{2}$ -volt batteries connected in parallel, four $22\frac{1}{2}$ -volt "B" batteries wired in series, and three $4\frac{1}{2}$ -volt flashlight cells used for the "C" battery. A small horn-type loudspeaker was included. Dimensions were $6\frac{1}{4}$ " x $13\frac{1}{4}$ " x 20" and the "portable" weighed about 34 pounds.

Our November, 1926 issue also reported on the Third Annual Radio World's Fair which was held in New York City during September of that year. Most of the receivers on exhibit employed from six to ten tubes, were totally shielded, and used loop aerials as a "collective agency." The absence from view of coils, condensers, and tubes was reported as being very novel. Considerable attention was also paid to the audio end with an emphasis on quality. Transformer-coupled audio amplifiers with the output stage designed for a power tube were in prominence. The newest designs permitted the set to operate directly from the electric light mains.

The hi-fi fan of 1926 could buy a cone speaker with "free-edge design," and some of the latest types had driving rods off-center to eliminate resonance points and prevent the creation of harmonics. Some of these speakers took the shape of an oval and ranged in diameter from 18 to 36 inches.

And what about tubes: one could buy the UX-120 at \$2.50, the storage battery or a.c. UX-171 for \$6, the storage power tube UX-112 for \$6.50, or the new super-power UX-210 for \$9 (we used this latter type in one of our first ham rigs, but with base removed and inverted into a jar containing mineral oil for cooling).

Radio has indeed come a long way since the immortal Will Rogers dispensed his home-spun philosophy over the air waves in 1926 to the shouting of Elvis Presley over the radios of today. O. R.

RADIO & TELEVISION NEWS

ALLIED'S 1957

value-packed 356-page

CATALOG

free!

the only **COMPLETE** catalog
for everything in electronics

World's Most Complete Stocks

- Latest Hi-Fi Systems and Components
- Super-Value KNIGHT-KITS
- P.A. Systems & Accessories • Recorders & Supplies • TV Tubes, Antennas, Accessories
- Amateur Receivers, Transmitters, Station Gear • Test and Lab Instruments
- Specialized Industrial Electronic Equipment • Huge Listings of Parts, Tubes, Transistors, Tools and Books . . .

Get ALLIED's 1957 Catalog—it's *complete*, up-to-date—356 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get *every* buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices and guaranteed satisfaction . . .

send for the leading electronic supply guide




Our 36th year

ALLIED RADIO

World's Largest Electronic Supply House

February, 1957

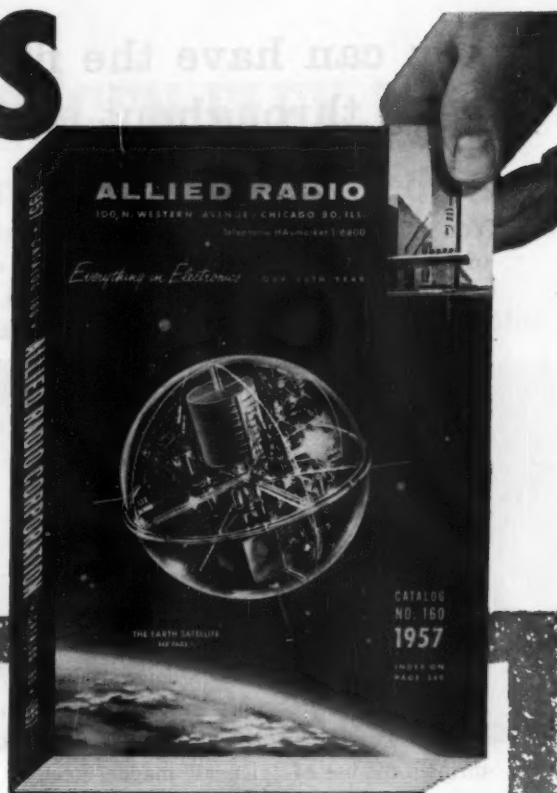

FEATURING

SUPER-VALUE knight-kits

The very finest electronic equipment in money-saving kit form—Test Instruments, Hi-Fi Kits, Ham Kits, Hobbyist Kits. Easiest to build and you **SAVE MORE!**

EVERYTHING IN HI-FI:

World's largest selection of quality Hi-Fi components and complete music systems. **MORE PEOPLE BUY THEIR HI-FI FROM ALLIED THAN ANYWHERE ELSE IN THE WORLD!**

EASY-PAY TERMS:

Only 10% down, up to 18 months to pay. Available on orders over \$45. Fast handling—no red tape.



FREE

ALLIED RADIO CORP., Dept. 1-B-7
100 N. Western Ave., Chicago 80, Ill.

☐ Send **FREE** 356-Page 1957 ALLIED Catalog

Name.....

Address.....


City..... Zone..... State.....

You can have the finest sound reproduction throughout all frequency ranges without distortion

You will hear a remarkable difference in the clarity of Norelco *Full Response Speakers. In a single speaker, twin-cones reproduce low frequencies, middle range, as well as the higher frequencies extending beyond the audible range—without distortion.

WHY ARE NORELCO FRS SPEAKERS SO EXCEPTIONAL?

They have incorporated a number of technical refinements which are evident the moment you listen. The air gap has been made long so that the coil is completely enclosed in an even magnetic field at all times. A copper ring has been fitted into the deep air gap to keep the voice coil impedance constant over the whole frequency range; this avoids incorrect matching. High flux densities are obtained through the use of "Ticonal" magnet steel.

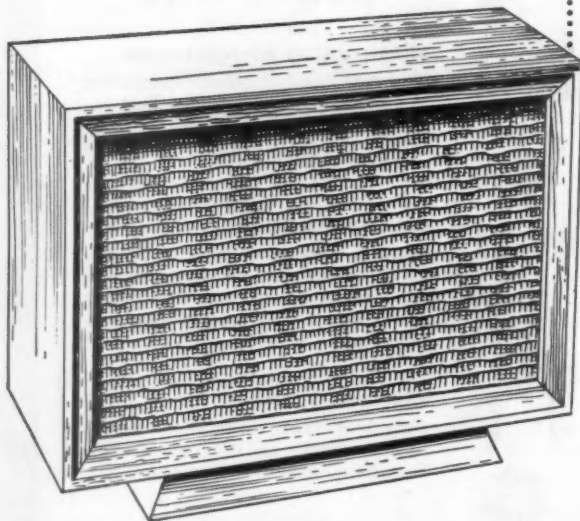

Norelco FRS Improved Bass Reflex Enclosures are available in three sizes; FRS Enclosures I, II and III. Priced from \$33.75 to \$119.95.



ADD TO...and improve any sound system with **Norelco®**

***FULL RESPONSE SPEAKERS**

Write today to Dept. G2 for brochures and prices of these unique speakers.

NORTH AMERICAN PHILIPS CO., INC., 100 E. 42nd Street, New York 17, N.Y.



Norelco F.R.S.

speakers are available
5", 8" or 12" sizes in standard impedances.

Priced from \$6.75 to \$59.98

Blue prints are available for the
do-it-yourself enclosure builder.

Norelco speaker-matched enclosures are scientifically designed acoustical boxes which enhance the exceptional tone qualities of FRS speakers; bringing out their true performance values.


Norelco FRS Speaker Enclosures are available in three sizes to match the characteristics of the speaker in use. Supplied in either mahogany or blond, these enclosures incorporate a removable base permitting the enclosures to be placed horizontally or vertically to suit any room arrangement or decor.



INTRODUCING BOGEN FLEX-PAK®

custom flexibility in packaged PA

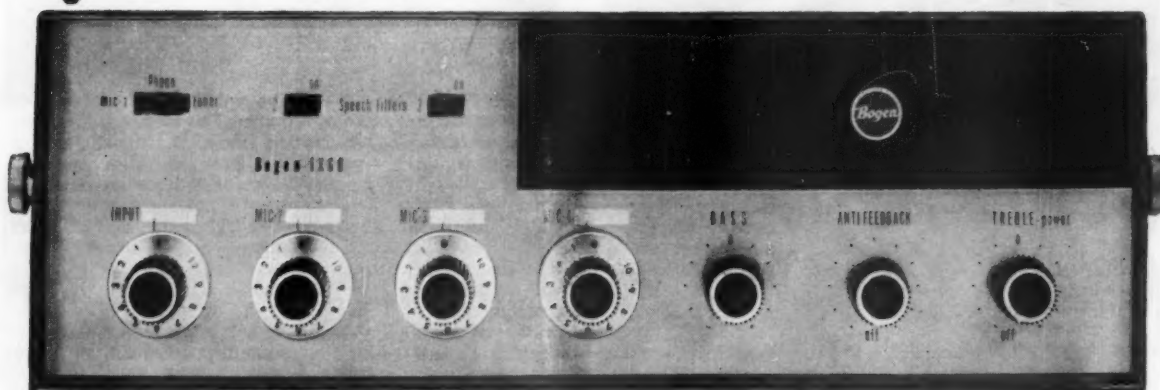
portable . . . or permanent . . . make more sales, more profits




HOW'S THIS FOR EASY SERVICE ... EASY INSTALLATION



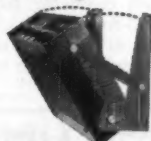Loosen 4 thumbscrews and the lid's off for easy access and fast servicing.



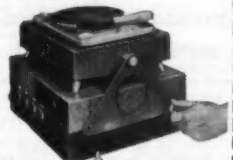Folds back when not in use in easy-sliding accessory wall-mount bracket.



4 Thumbscrews attach accessory record player mount. (Note: "cooling area" protects phono mechanism.)



Write-in on each gain control prevents embarrassing mistakes in volume settings. (Easy to erase markings.)

Meet Bogen's Flex-Pak public address line. Here's true portability. Here's easy servicing. And here's all the flexibility, performance and dependability you'll need to satisfy 90% of your commercial applications—without going to the additional effort and delay of expensive custom designs. You can offer Flex-Pak systems in every price range,

at practically every popular wattage. Get in touch with your Bogen representative or write for all Flex-Pak specifications and prices. NOTE: We also supply famous-make indoor and outdoor speakers, microphones and other accessories for all your Bogen public address system installations. Mail coupon now for the exciting details.

Two of 12 New Amplifiers In The Exciting Flex-Pak PA Line



Deluxe LX30 30-Watt Amplifier

4 Microphone Inputs (panel switch converts one microphone channel for phono or tuner), Built-In Remote Gain-Control Circuit, Exclusive Anti-Feedback Control, Speech Filters, Separate Bass and Treble Tone Controls
Size: H. 5 3/4", W. 16 1/4", D. 13", Wgt.: 25 lbs.



with
accessory
Manual Phono

Superb L330 30-Watt Amplifier

3 Microphone Inputs (panel switch converts one microphone channel for phono or tuner), Speech Filters, Separate Bass and Treble Tone Controls
Size: H. 5 3/4", W. 14 1/4", D. 13", Wgt.: 24 lbs.

Bogen
PUBLIC ADDRESS SYSTEMS
A UNITED STATES CORPORATION AFFILIATE

MAIL THIS COUPON TODAY FOR DESCRIPTIVE BROCHURES AND PRICES

Dept. MN, David Bogen Co., Inc., P. O. Box 500, Paramus, N. J.
Gentlemen: Please send me descriptive literature and price information on your BOGEN FLEX-PAK public address equipment.

NAME _____

FIRM _____

check one ☐ dealer ☐ jobber ☐ sound specialist

ADDRESS _____

CITY _____

ZONE _____

STATE _____

☐ Please send me 24-page, illustrated brochure, "What You Should Know About Sound Systems."

☐ Please send me your 56-page, illustrated book, "Understanding High Fidelity," by L. H. Bogen and L. Biancolli. (I enclose 25c.)

Profit-Making! PROTO Professional-Quality Pliers Job-Designed for Fast Turnover



NEW! Multiple-Groove Joint Utility Plier.
Wide range of openings—quickly changed for many jobs.
242—7½", 243—9½".



NEW! Mighty Midget Plier for Electronics. Perfectly balanced feel for working on small objects in tight places where others won't.
6 models, 4" to 4½".

NEW! "Snip-Grip" Plier. Red plastic inserts in cutting edges hold end of wire after cutting. Prevents electrical shorts, protects user from injury.



NEW! Electronics and Ignition Cutting Plier. Cutter is close to tip. Spring opens long narrow jaws.



Also NEW! Comfortable "Handeze" Plier Grips. Slip on easily, fit tight, are long wearing.



NEW! V-Notch Wire Stripper. Two V-notches cut through the insulation, slight side pressure strips it.
299—5½".

Sensational "Multi-Plier"!
Increases grip 10 times. 234—8".
"A chest of tools in one!"

Fast turnover because they are job-designed to do each job right! Because they're backed by broad national advertising. Because they come to you in many attractive counter, stand, and wall merchandisers that boost "impulse" buying! So... if you want to turn plier profits your way, send for catalog of entire line to

PROTO TOOLS

2205 Santa Fe Ave.
Los Angeles 54, Calif.
Eastern Warehouse & Factory, Jamestown, N.Y.
Canadian Factory, London, Ont.



Spot Radio News

★ Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS'
WASHINGTON EDITOR

THE RECENT DEVELOPMENT and widespread use of tropospheric scatter propagation, radio noise, modulation, and navigation techniques has prompted the Bureau of Standards to reorganize its radio-propagation engineering division in Boulder, Colorado, and divide the original two research sections into seven new units.

The new divisions will concentrate on data reduction instrumentation, modulation systems, navigation systems, radio noise, tropospheric measurements, radio-systems application engineering, and various tropospheric analysis.

Another new section at the Bureau will concern itself with sun-earth relationships. In a closely coordinated program engineers will study the sun and its effect on radio communication, and the use of solar and geophysical data to forecast short-wave radio communications conditions.

OVER-THE-HORIZON scatter propagation has also become the subject of an intensive study by the Air Research and Development Command; a program that, it is hoped, will provide answers to long-distance transmission problems on the ultra-high portion of the spectrum.

The probe will feature the use of two communications stations; a receiving station near Baltimore and a transmitting site 285 miles away in Verona, New York; there are no intervening repeater or booster stations along the 285-mile path. A few years ago transmission-reception over a 285-mile distance would have been considered impossible. The theory was then that line-of-sight distances of about 30 miles to the horizon was the maximum limit of signalling in the higher frequency bands.

In the scatter technique extremely large transmitting and receiving antennas are required. In addition, the transmitters must be high powered and extremely sensitive receivers must be employed. Signals radiated in a narrow, beam-like path are reflected or scattered from the troposphere and a portion of these scattered waves are received by another antenna beyond the horizon.

In the installation near Baltimore, a metal prefabricated building serves to house the receiving equipment, which is linked to a 28-foot diameter parabolic antenna on a 33-foot tower. At Verona, the antenna site, there is a 10,000-watt transmitter.

(Continued on page 16)

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL	CHANNEL	FREQUENCY	POWER*
Pennsylvania	Lancaster	WLAN-TV	21	512-518	17
Kentucky	Paducah	6	62-88	58.3
Maine	Augusta	10	192-198	316
Michigan	Port Huron	WHLS-TV	34	590-596	22.9
Texas	Bryan	KGTU-TV	3	60-66	60.3

New Call Letter Assignments

STATE	CITY	CALL	CHANNEL	FREQUENCY
Montana	Missoula	KMSO-TV (Formerly KGVO-TV)	13	210-216
New Jersey	Atlantic City	WHTO-TV (Formerly WFFG-TV)	46	662-668
Virginia	Arlington	WARL-TV	20	508-512
Wyoming	Riverton	WERE-TV	10	192-198

*ERP-(effective radiated power, kw.)

FREE...ANY 3

OF THESE SUPERB HIGH-FIDELITY

12" COLUMBIA RECORDS

If you join the Columbia  Record Club now—and agree to accept as few as 4 selections during the coming 12 months




The most exciting high-fidelity performances

 

 


ever offered to new members



of the Columbia  Record Club

 

 "Columbia", ,  Marcas Reg.

YES! You may have, FREE, ANY 3 of these best-selling 12" Columbia  records. We make this unique offer to introduce you to the money-saving program of the Columbia  Record Club... a program that selects for you each month the greatest works in every field of music—performed by the world's finest artists, brilliantly reproduced on Columbia  records.


HOW THE CLUB OPERATES: To enjoy the Club's benefits—mail the coupon, indicating which one of the four Club divisions best suits your musical tastes: Classical; Jazz; Listening and Dancing; Broadway, Movies, Television and Musical Comedies.

Each month you will receive free the Club Magazine which describes the current selections in all four divisions. You may accept or reject the monthly selection for your division... or you may take records from other Club divisions... thereby assuring you the widest possible choice of recorded entertainment. Or you may tell us to send you NO record in any month.

Your only obligation is to accept as few as 4 selections from the almost 100 that will be offered during the next 12 months. The records you want are mailed and billed to you at only \$3.98 (original cast Broadway Shows somewhat higher), plus a small mailing charge.


FREE BONUS RECORDS GIVEN REGULARLY: The 3 records sent to you now represent an "advance" of the Club's bonus system—given to you at once. After you have fulfilled your membership obligation by purchasing four records, you will receive an additional free Bonus record of your choice for every two additional Club selections you accept. Bonus records are superb 12" Columbia  records—the very best of the Columbia  catalog—just like those shown here.

Indicate on the coupon which 3 records you want free, and the division you prefer. Then mail the coupon at once. You must be delighted with membership or you may cancel it by returning the free records within 10 days.

COLUMBIA  RECORD CLUB
165 West 46th Street, New York 36, N. Y.

February, 1957

MAIL ENTIRE COUPON NOW!


COLUMBIA  RECORD CLUB,
Dept. 686, 165 West 46th St.,
New York 36, N. Y.

Please send me as my FREE gift the 3 records indicated here: (Select the records you want by checking the 3 boxes in the list at the right)

...and enroll me in the following Division of the Club:

(check one box only)

- ☐ Classical ☐ Listening and Dancing
☐ Broadway, Movies, Television and Musical Comedies ☐ Jazz

Each month you will send me the Columbia  Record Club Magazine which describes the records offered in all four Club divisions. I have the privilege of accepting the monthly selection in the division checked above, or any other selection described, or none at all. My only obligation is to accept a minimum of four records in the next 12 months at the regular list price plus a small mailing charge. After accepting 4 records, I will receive a free Bonus record for every two additional records I purchase. If not delighted with membership, I may cancel within 10 days by returning all records.

Name.....
(Please Print)

Address.....

City..... Zone..... State.....

CANADA: Prices slightly higher.
Address 11-13 Soho St., Toronto 2B

If you wish to have this membership credited to an established Columbia Records dealer, authorized to accept subscriptions, please fill in the dealer's name and address also.

CHECK THE 3 RECORDS YOU WANT:

- | | |
|---|--|
| <input type="checkbox"/> Tchaikovsky: Nutcracker Suite; The Sleeping Beauty Ballet. Philadelphia Orchestra, Ormandy, cond. | <input type="checkbox"/> Concert by the Sea. Erroll Garner—recorded in an actual performance at Carmel, Calif.—playing 11 numbers—Red Top, Where or When, etc. |
| <input type="checkbox"/> Day Dreams. Doris Day sings 13 popular songs—including Sometimes I'm Happy, You Go To My Head, etc. | <input type="checkbox"/> Levant Plays Gershwin 3 works—Rhapsody In Blue; Concerto in F; An American in Paris. |
| <input type="checkbox"/> King of Swing: Vol. I. Benny Goodman and Original Orch., Trio, Quartet, Rides High, Moon Glow—8 more. | <input type="checkbox"/> The Voice. Frank Sinatra in 12 songs that first made him famous—Love, Fools Rush In, etc. |
| <input type="checkbox"/> My Fair Lady. Percy Faith and his Orchestra play music from this hit show. | <input type="checkbox"/> Rimsky-Korsakov: Scheherazade. Philadelphia Orch., Ormandy, conductor. A superb performance of this exotic score. |
| <input type="checkbox"/> Brahms: Double Concerto: Variations on a Theme by Haydn; Tragic Overture. Stern, violin; Rose, 'cello; N. Y. Philharmonic, Walter, cond. | <input type="checkbox"/> Music of Jerome Kern. Andre Kostelanetz and his Orchestra play 20 Kern favorites. |
| <input type="checkbox"/> Songs from Walt Disney's Magic Kingdom 12 happy songs from famous Disney films. | <input type="checkbox"/> Jazz: Red Hot and Cool. Dave Brubeck Quartet in Love Walked In, The Duke—5 more. |


Dealer's Name.....

Dealer's Address.....

48-3

IT TAKES TWO:

RCA and YOU

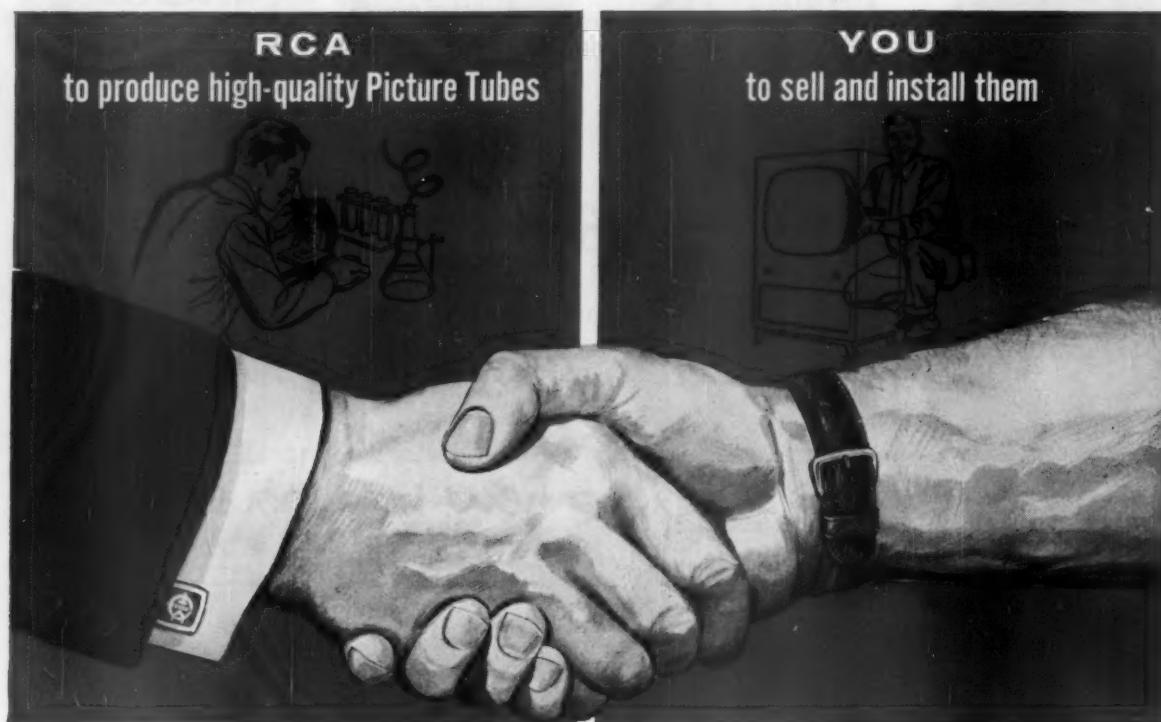

When the customer says, "Why?", "What?", "How Much?", don't just talk tubes, talk:

- QUALITY** Tell them how an RCA picture tube must pass well over 100 careful inspections before it's good enough for you—or your customer.
- ACCEPTANCE** Remind them that more people view TV shows on RCA picture tubes than on any other brand.
- BRAND NAME** Emphasize RCA—the name that's first in electronics.
- WARRANTY** The Warranty Card you give your customers says the tube is an RCA tube; it says it's factory-fresh; above all it says: "warranted for a year."

Today, your customers are well-informed TV viewers who demand the best in picture tube performance. These are the people who, week in and week out, read the RCA Silverama story in *Life*, *TV Guide*, the *Saturday Evening Post*. These are the people who see and hear the RCA Silverama quality story on NBC's network radio and TV shows. And these are the very customers who say "yes" to RCA. So, team-up with RCA. You'll know the difference, and your customers will see it—big and bright as life.

Silverama




PICTURE TUBES

RADIO CORPORATION OF AMERICA
Tube Division • Harrison, N. J.


No antennas ever made can match the performance and sales appeal of these outstanding Channel Master models.

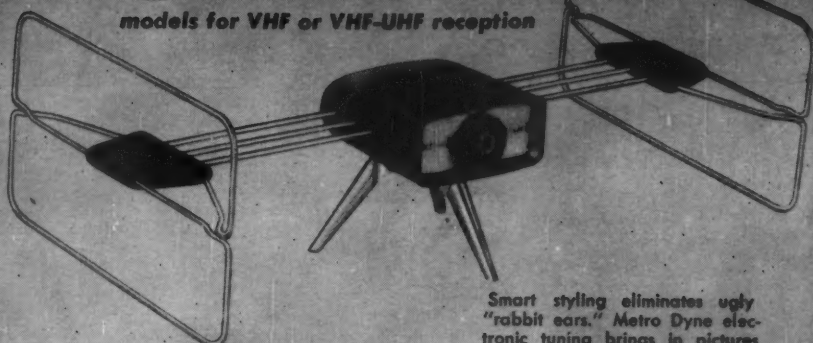"Showman" indoor antenna models for VHF or VHF-UHF reception



Smart styling eliminates ugly "rabbit ears." Metro Dyne electronic tuning brings in pictures sharp and clear.

T-W outdoor antenna

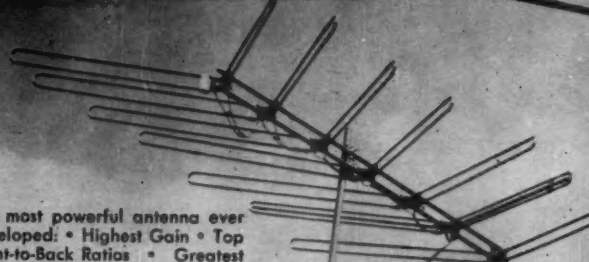

The most powerful antenna ever developed: • Highest Gain • Top Front-to-Back Ratios • Greatest Mechanical Strength.

MORE PROFITS for CHANNEL MASTER dealers

In every TV reception area Channel Master dealers are racking up new sales records with the most popular TV antennas on the market today. Superior products plus consistent consumer advertising is a double-barrelled profit combination you can't beat. When you feature the Channel Master line you always have that extra selling edge . . . that extra PLUS that means faster turnover . . . easier sales . . . bigger profits.

Isn't it time you called your Channel Master distributor?



Channel Master's massive national and local advertising program . . . establishes you as the local TV authority . . . is creating loads of new prospects right in your own selling area . . . and is opening millions of homes to antenna replacement.



H. H. Scott Model 310-B FM Tuner \$159.95
(Mahogany Case \$19.95)

Other H. H. Scott tuners from \$119.95. All prices slightly higher West of Rockies. All tuners meet FCC radiation specifications

**Exclusive wide band design ...
new silver sensitive front end ...**


Most Sensitive ... Selective FM Tuner Ever Made!

High Fidelity Magazine says:

"The 310 seems as close to perfection as is practical at this time"

One look at all the features ... one listen to the superlative sound ... and you'll agree!

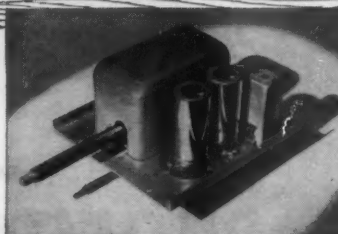Wide band circuit design, heavy silver plating in the RF section, and three stages of full limiting make possible noise-free reception of even the weakest stations. Three IF stages insure maximum selectivity with virtual elimination of adjacent and co-channel interference.



**Silver Sensitive Front End
Makes Distant Stations
Sound Close By!**

H. H. Scott never compromises on design. The front-end pictured above is a good example. Silver is one of the best conductors known, yet only H. H. Scott heavily silver-plates their cascade RF section for maximum gain and most reliable performance. This Scott exclusive assures a sensitivity of 2 microvolts throughout the entire FM Band.

Look at these many features and specifications that defy obsolescence:

- Sensitivity 2 microvolts on 300 ohm antenna terminals for 20 db of quieting (equivalent to 1 microvolt with matched 75 ohm antenna)
- Planetary drive tuning • Logging Scale
- Dynaflex Interstation Noise Suppressor cuts out FM roar between stations • Illuminated Signal Strength and tuning meter • Separate tape recorder and multiplex outputs • 2 1/2 db capture ratio permits virtually noise free reception of stations only slightly stronger than interference on the same channel • Easily panel mounted, matches all H. H. Scott amplifiers • Dimensions in mahogany case 13 1/2 x 5 x 9 1/2.



H. H. Scott, Inc.
385 Putnam Avenue, Cambridge, Mass.
Export Dept: Telesco International Corp.
270 Park Avenue, New York 17, N. Y.

Mail Now For New Catalog

Rush me your new catalog RTV-70 and complete technical specifications on the new H. H. Scott line for '57'.

NAME

ADDRESS

CITY STATE

(Continued from page 12)

AN IMPROVED WEATHER STATION, featuring a radiosonde, that is ejected from a plane to determine weather characteristics in inaccessible parts of the world has been developed by ARDC. The instrument, technically a weather-sensing radio transmitter, was designed by ARDC's Wright Air Development Center, and is said to be more accurate and adaptable than earlier types.

For several years, radiosondes have been used by the Air Weather Service to determine the weather characteristics over oceans and polar regions where permanent weather stations are not practical. The units, which are parachuted from airplanes, transmit a complete record of humidity, temperature, and air pressure until they hit the earth.

The improved model has been designed for use from altitudes up to 60,000 feet and at speeds up to *Mach .98* (*Mach 1* is the speed of sound) as compared to the 30,000-foot and *Mach .43* limits on the older model. In addition, the designers say that the new unit is 95 per-cent reliable as compared to a previous reliability of 80 per-cent.

The radiosonde consists of two dry-cell batteries, a radio transmitter, and a parachute assembly; it is only 21 1/2 inches long, 5 inches in diameter, and weighs 9 pounds.

Radiosondes can be dropped manually from large aircraft or by remote control from an eight-unit dispenser in smaller craft where space is scarce. But the sondes must be designed so that the delicate transmitter will not be harmed by the shock of the unit hitting the airstream or by the parachute opening.

Six seconds after leaving the plane, the radiosonde parachute pops out of its housing, stabilizing the unit and lowering it gently toward the earth. Simultaneously, a 1-foot antenna automatically snaps downward and a short arm extends perpendicular to the radiosonde.

On the arm are located relative humidity and temperature-sensing elements and inside the container is an air-pressure bellows. These three devices immediately begin to sense temperature, humidity, and pressure and transmit this data by radio back to the plane.

Inside the plane a receptor picks up the signals, then decodes and records them. This record is evaluated by a technician who, in turn, radios the findings to a central weather station.

About 25,000 radiosondes are dropped each year by seven weather squadrons flying daily in the northern hemisphere. Data collected in this way is transmitted through a world-wide weather network within four hours after it is collected. This enables advance weather predictions to be made; in the case of California, for example, two to three days in advance.

The weather squadrons fly over areas of a (Continued on page 96)

RADIO & TELEVISION NEWS

Electro-Voice

664 VARIABLE D* HIGH-FIDELITY CARDIOID DYNAMIC MICROPHONE



Outperforms Any Other P. A. Cardioid — Or Your Money Back!



It took an entirely new concept, Variable D, to do it, but here it is... a broadcast-quality microphone for every P. A. installation... every personal tape recorder... every radio amateur rig. The high-fidelity "664" is such a revolutionary improvement in the field that we can guarantee it to outperform any other P. A. cardioid... or your money back!

Uniform cardioid polar pattern gives high front-to-back discrimination. You get smooth, peak-free response at all frequencies from 40 to 15,000 cps, no boominess from close talking.

Exclusive, indestructible Acoustalloy Diaphragm—a single moving element—withstands high humidity, temperature extremes, corrosive effects of salt air, and severe mechanical shocks. With the E-V "664" you are sure of dependable, long-life operation indoors and outdoors.



Unidirectional, the E-V Variable D cardioid "664" provides highly directional sound selectivity, reduces pickup due to ambient noise and reverberation up to 50%. Proper microphone placement stops unwanted sounds, gives accurate, natural pick-up of voice and music. Highest sound level to feed-back ratio. The "664's" greater pick-up range doubles working distance over conventional microphones. *Pop-proof* filter minimizes wind and breath blasts.

*E-V Pat. Pend.

ASK A BROADCAST OR RECORDING ENGINEER ABOUT E-V MICROPHONES

Model 664. Variable D Super-Cardioid Dynamic Microphone. Uniform response at all frequencies from 40 to 15,000 cps. Output level, -55 db. 150 ohm and high impedance. Impedance changed by moving one connection in cable connector. Low impedance balanced to ground and phased. Acoustalloy diaphragm, shielded from dust and magnetic particles. Alnico V and Armco magnetic iron in non-welded circuit. Swivel permits aiming directly at sound source for most effective pick-up. Pressure cast case. $\frac{3}{4}$ "-27 thread. Satin chrome finish. 18 ft. cable with MC4M connector. On-Off switch. Size: $1\frac{1}{4}$ in. diam., $7\frac{3}{4}$ in. long, not including stud. Net wt: 1 lb. 10 oz. List Price \$82.50


Model 419. Desk Stand. Modern, sturdy design (extra). List Price \$10.00

Write for: A. B. C.'s of Microphones, Dept. N72.

FOR PERFORMANCE! FOR VALUE!
NO FINER CHOICE THAN

Electro-Voice®

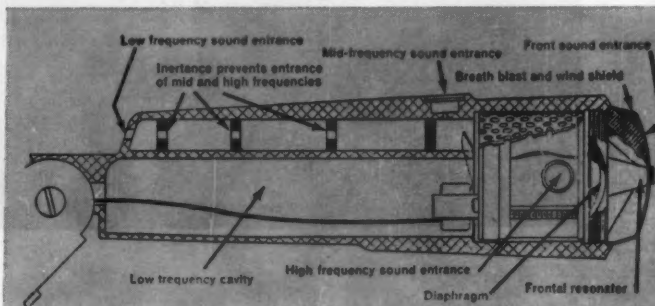ELECTRO-VOICE, INC., BUCHANAN, MICH.
Canada: E-V of Canada Ltd., 1908
Avenue Road, Toronto, Ontario
Exports: 13 East 40th Street,
New York 16, U.S.A. Cables: ARLAB



HOW MANY CAN YOU ANSWER "YES?"

1. Do you wish to extend your experience in electronics systems?

2. Would you like to instruct others in advanced fire control systems and laboratory techniques?

3. Would you like to handle a responsible position representing a leading electronics organization?

4. Do you believe that you can accurately relate your findings and studies in technical language?

5. Are you interested in such devices as analog computers, digital computers, power supplies, transmitters, receivers, and microwave antennas?


6. Do you enjoy working with people?

If you can answer "yes" to four of the above questions and have an Electrical Engineering or Physics degree, chances are that you can qualify for one of the several engineering positions in the Hughes Field Engineering department.

In addition to giving you well-rounded experience in electronic systems and controls, Hughes offers you training at full salary, moving and travel allowances, per diem expenses, and many other benefits. For further information write Mr. W. A. Barnes at the address below.

HUGHES

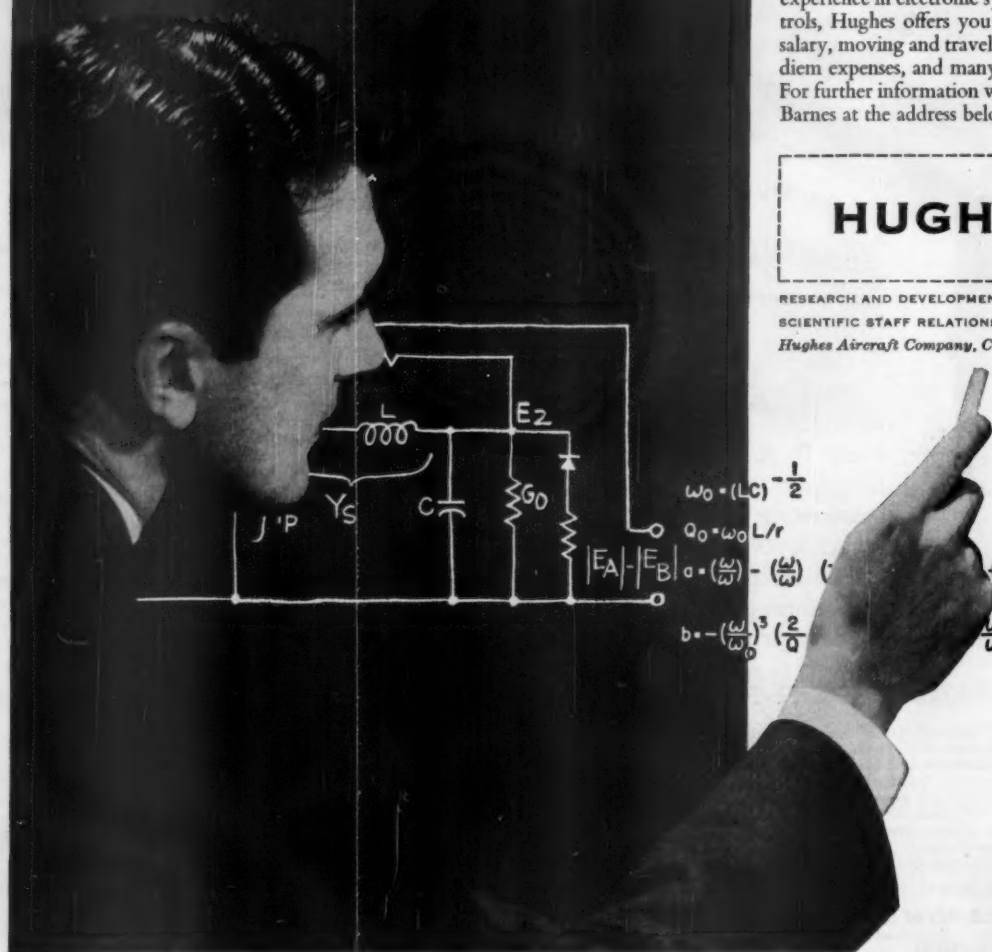RESEARCH AND DEVELOPMENT LABORATORIES
SCIENTIFIC STAFF RELATIONS
Hughes Aircraft Company, Culver City, Calif.




$$\omega_0 = (LC)^{-1/2}$$

$$Q_0 = \omega_0 L / r$$

$$a = \left(\frac{\omega}{\omega_0}\right) - \left(\frac{\omega_0}{\omega}\right) \left(1 + \frac{2}{Q_0}\right) + \left(1 + \frac{2}{Q_0}\right)$$
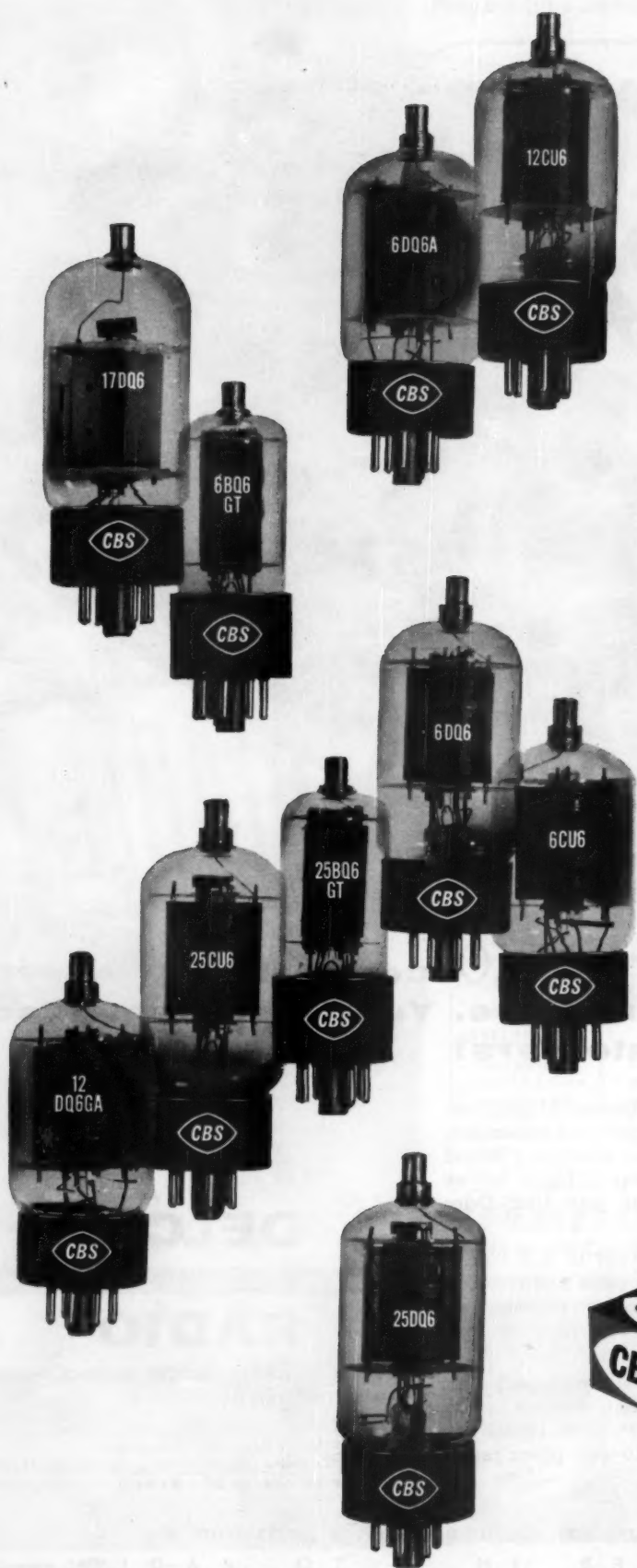
$$b = -\left(\frac{\omega}{\omega_0}\right)^3 \left(\frac{2}{Q_0}\right) - \frac{\omega_0}{\omega} \left(\frac{1}{Q_0^2} + \frac{3}{Q_0} + 2\right)$$



From the originator
of the 6BQ6GT • 6CU6 • 6DQ6

TIPS ON REPLACING HORIZONTAL AMPLIFIERS

No one tube satisfactorily replaces the 6BQ6GT, 6CU6, and 6DQ6 . . . or their heater-voltage variations. CBS knows because, foreseeing the need for each of these three families of horizontal amplifiers, CBS originated the 'BQ6, 'CU6, and 'DQ6. The latter two were designed: 1. With increasingly greater safety margins to combat high voltage and heat. 2. With improved sweep characteristics.

In general, replacement of each tube should be with the original type. But in some sets, larger, wider-angle picture tubes using higher voltages place overloads on the original horizontal amplifiers. Here replacement should be a step upwards at a time: 'CU6 for 'BQ6 . . . 'DQ6A for 'CU6. Following these rules will give reliable safety margins and neither too little nor too much sweep, especially important in receivers with no horizontal width control.

Another good rule is to replace them all with CBS tubes. The reason is logical. It's better to use CBS originals . . . because CBS has had more experience in making them better.



Reliable products
through Advanced-
Engineering

CBS-HYTRON, Danvers, Mass.
A Division of
Columbia Broadcasting System, Inc.



FROM DELCO RADIO come the speakers
with highest performance. You trust them...so
do your customers!

Engineering skills of Delco Radio and General Motors combine to offer a full line of speakers for home and auto radios, phonographs, TV, and Hi-Fi. National advertising behind the Delco Wonder Bar Radio develops a bigger service market for you! For fast service call your UMS-Delco Electronics Parts Distributor.

14 Standard Models: Designed and built to R.E.T.M.A. standards with heavily plated metal parts and Alnico-V magnets. Precision felted cones give uniform response over full operating frequency range. All are fully dustproof and dependable.

Dual-Purpose Hi-Fi Model 8007: A superior speaker for custom-built audio systems and for replacements in AM, FM, TV and phonograph sets. Size 8", 50 to 12,500 CPS frequency range; Alnico-V magnet; 10-watt power rating; 4.1 v.c. impedance; $1\frac{1}{4}$ " voice coil.

DELCO

RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA




A GENERAL MOTORS PRODUCT — A UNITED MOTORS LINE
 Distributed by Delco Electronic Parts Distributors

A complete line of original equipment service parts from the
 WORLD LEADER IN AUTO RADIO

RADIO & TELEVISION NEWS

Prepare for a Good Paying Job — Or Your Own Business

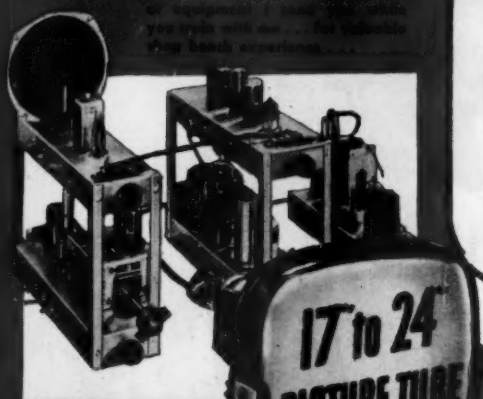Learn PRACTICAL RADIO-TV
with 25 BIG KITS




"I Will Train You at Home in RADIO-TELEVISION On Liberal No Obligation Plan!"

New Equipment! New Lessons! Enlarged
Course! The true facts are yours in my
big new catalog . . . YOURS FREE . . .

JUST MAIL COUPON!

I can train and prepare you in as little as
10 months to step into the big opportunity
Radio-Television service field. Train *without*
signing a binding contract . . . without oblig-
ating yourself to pay any regular monthly
amounts. You train entirely at home in spare
hours . . . you train as fast or as slowly as
you wish. You'll have your choice of **THREE SPRAYBERRY TRAINING
PLANS** . . . planned for both beginners as well as the more experienced
man. Get the true facts about the finest most modern Radio-Training avail-
able today . . . just mail the coupon for my big new 56 page fact-filled
catalog plus sample lesson—both FREE.

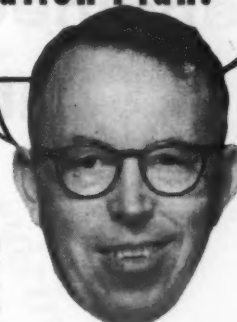

Frank L. Sprayberry
President, Sprayberry
Academy of Radio

Train the Practical Way—with Actual Radio-Television Equipment

My students do better because I train both the mind and the hands. Sprayberry
Training is offered in 25 individual training units, each includes a practice giving
kit of parts and equipment . . . all yours to keep. You will gain priceless practical
experience building the specially engineered Sprayberry Television Training Re-
ceiver, Two-Band Radio Set, Signal Generator, Audio Tester and the new Spray-
berry 18 range Multi-Tester, plus other test units. You will have a complete set
of Radio-TV test equipment to start your own shop. My lessons are regularly
revised and every important new development is covered. My students are com-
pletely trained Radio-Television Service Technicians.

NEWEST DEVELOPMENTS

Your training
covers U H F, Color
Television, F M,
Oscilloscope
Servicing, High
Fidelity Sound
and Transistors.

See for Yourself... Make Your Own Decision ... Mail Coupon Today!

The coupon below brings you my big new catalog plus
an actual sample Sprayberry Lesson. I invite you to read
the facts . . . to see that I actually illustrate every item
I include in my training. With the facts in your hands,
you will be able to decide. *No salesman will call on you.*
The coupon places you under no obligation. Mail it now,
today, and get ready for your place in Radio-Television.

SPRAYBERRY ACADEMY OF RADIO
111 North Canal Street, Dept. 25-H, Chicago 6, Illinois

Mail This Coupon For Free Facts and Sample Lesson


SPRAYBERRY ACADEMY OF RADIO
Dept. 25-H, 111 N. Canal St., Chicago 6, Ill.

Please rush all information on your ALL-NEW Radio-Te-
vision Training Plan. I understand this does not obligate me
and that no salesman will call upon me. Include New Cata-
log and Sample Lesson FREE.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

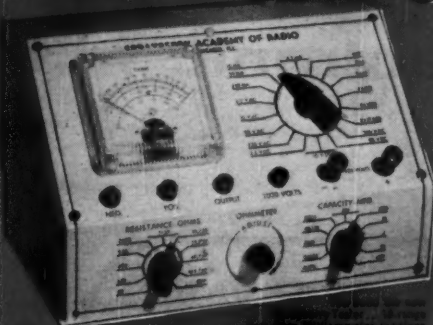

In addition to modern lesson training, I also give you
plenty of home practice on actual Radio-Television
equipment . . . you will build and use the units shown
here plus many more. All this equipment is yours to
keep . . . keep everything you need to set up your shop.



If it's worth
engineers'
time...



Mil. Spec.

Mil. Spec.



...it's worth
engineered
electronic wire



6-8

Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable

Col

COM

RTTA of
vision Te
up-to-the
maintena
pared —
uses the
teaching
at the t
ment an
an overa
analyzed
fast and



Technician
The Col
authorized
ested in
servicing.

4

Co
1 AP
2 FC
3 TH
4 GI
TE
5 PI
RE
6 PI
RE
7 DI
TE
8 TH
9 CO
10 CO
11 AD
12 CO
13 TR
14 SE

Ra

Licen

February

There's a 'pot of gold' waiting for you
at the end of this **COLOR TV Servicing** Rainbow!

Introducing **RTTA'S**

Color TV Technician Course

(For men with previous radio & TV training)

COMPLETE! DEPENDABLE!

RTTA offers you the most complete and practical Color Television Technician Correspondence Course. It includes the latest, up-to-the-minute data and procedures for the servicing and maintenance of all Color TV receivers and equipment. Be prepared — gain your share of those profits ahead! This course uses the same step-by-step approach found so successful in the teaching our other famous courses to thousands of men. Starting at the transmitter the lessons guide you through the development and transmission of the composite Color TV signal. With an overall view of how the receiver function each circuit is then analyzed in a simple, easy-to-follow manner that make learning fast and accurate.



Sylvania Now Sponsoring
RTTA's Color TV Technician Course

One of the nation's largest electronics manufacturers and marketers, Sylvania Electric Products Inc., in its continuing effort to cooperate with independent service dealers is now sponsoring the RTTA Color Television Technician Course.

The Color Television Technician Course is being made available to authorized Sylvania Dealers throughout the 48 states who are interested in expanding their knowledge and experience in Color TV servicing.

14 THOROUGH LESSONS!

Color Television Technician Course

- 1 AN INTRODUCTION TO COLOR
- 2 FORMATION OF THE COLOR SIGNALS
- 3 THE CHROMA SIGNALS
- 4 GENERAL OPERATION OF THE COLOR TELEVISION RECEIVER
- 5 PICTURE TUBES FOR COLOR TELEVISION RECEIVERS — PART I
- 6 PICTURE TUBES FOR COLOR TELEVISION RECEIVERS — PART II
- 7 DETAILED OPERATION OF THE COLOR TELEVISION RECEIVER
- 8 THE CHROMINANCE CHANNEL
- 9 COLOR TELEVISION CIRCUITS — PART I
- 10 COLOR TELEVISION CIRCUITS — PART II
- 11 ADJUSTING THE COLOR TV RECEIVER
- 12 COLOR TV TEST EQUIPMENT
- 13 TROUBLESHOOTING THE COLOR TV RECEIVER
- 14 SERVICING PROCEDURE



L. C. Lane, B.S., M.A.
President, Radio-Television
Training Association
Executive Director, Pierce
School of Radio & Television

Other RTTA Courses

covering all phases of Radio, FM and TV

Radio-FM-Television Technician Training

My Radio-FM-Television Technician Course is especially prepared for men with no previous experience or training. I have trained hundreds of men for successful careers in radio-television-electronics. Many of them had only a grammar school education and no previous experience whatsoever in the field.

Expert FM-TV Technician Training:

My FM-TV Technician Course lets you take full advantage of your previous experience — either civilian or Armed Forces. YOU CAN SAVE MONTHS OF TIME. Train at home with kits of parts, plus equipment to build TV RECEIVER. ALL FURNISHED AT NO EXTRA COST!

Practical TV Studio Technician Course

(For men with previous radio & TV training)

I train you at home for an exciting to pay job as the man behind the TV camera. Work "on location" at remote pick-ups! Available if you want it . . . one-week course of practical work on TV studio equipment at Pierce School of Radio & TV, our associate resident school in New York City.

SEND TODAY FOR YOUR ENROLLMENT

MAIL THIS COUPON TODAY!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
22 East 19th Street, New York 3, N. Y.

Dept. RT-28

Dear Mr. Lane: Without obligation, please RUSH me complete information on the course checked below.

(PLEASE PRINT PLAINLY)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I AM INTERESTED IN:

☐ Radio-FM-TV Technician Course

☐ FM-TV Technician Course

☐ TV Studio Technician Course

☐ Color TV

Technician Course

Radio-Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y.

Licensed by the State of New York • Approved for Veteran Training

Two Great Names
get together . . .

Plasti-Kote
and Argos

To bring Spray Paint to
The Electronics Industry



\$1.27


Dealer Net

16.4 oz.

Developed by electronic engineers
for electronic experts—with the
highest dielectric strength—800
volts mil.

The new Plasti-Kote X-11 acrylic
spray is the best ever developed
for coating terminals, rust proofing
antennas and other electronic uses.

Ask your Argos parts distributor now!

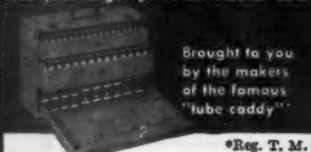

Reg. T. M.

Argos
PRODUCTS COMPANY

310 MAIN STREET • GENOA, ILLINOIS

Within the Industry

JOSEPH J. KEARNEY, formerly equipment and parts promotion manager, Tube Division, has been named manager, Distributor and Industrial Sales, of the newly created **RCA Components Division**.



In his new position, he will be responsible for establishing and administering sales programs for components, parts, and test equipment.

He joined the company in 1943 and has been with the War Contract Services Dept. and Tube Division. From 1951 to 1953, he acted as tube district manager for the company's East Central Region and in 1953 he was appointed manager, Battery Marketing.

CHARLES FENTON, president of the *Fenton Company* of New York and treasurer of the Institute of High Fidelity Manufacturers, passed away recently at the age of 51.

He had been active in Institute affairs since its inception and gave unstintingly of his time and talents to further the cause of the audio industry.

DAYSTROM, INCORPORATED announces that it has negotiated an agreement for the purchase of **FORD ENGINEERING CO. INC.**, Upland, Calif. Upon completion of the sale, the subsidiary will continue its operations and production at its two plants in Upland and will receive technical assistance from **DAYSTROM PACIFIC CORP.**, Santa Monica, Calif. . . . **INTERNATIONAL AUTOMATIC ELECTRIC CORPORATION** has changed its name to **AUTOMATIC ELECTRIC INTERNATIONAL INCORPORATED** . . . Approval of terms for a merger between **MIDWESTERN INSTRUMENTS, INC.**, Tulsa, Okla., and **MAGNECORD, INC.**, Chicago, Ill., has been announced. The merger plans, which have been approved by both boards of directors, will be submitted to stockholders of the two companies for immediate action. Present plans are for operation of the subsidiary as a division of the parent firm, with an integration of personnel of both organizations . . . **PHILCO CORPORATION** has purchased the **SIERRA ELECTRONIC CORPORATION** of San Carlos, Calif. It will be operated as a wholly owned division of the parent firm . . . **CORNELL-DUBILIER ELECTRIC CORPORATION** announced the acquisition of the substantial majority stock control in the **TOBE DEUTSCHMANN CORPORATION** of Norwood, Mass. The

policy is to continue manufacture of the line in its Norwood plant . . . Announcement has been made of the formation of **MADISON FIELDING CORPORATION**, 863 Madison Ave., Brooklyn, N. Y. The firm will manufacture equipment both in components and in finished units for the high-fidelity market . . . **HOWARD W. SAMS & CO., INC.** announces the formation of a new Industrial Service Department. This new department will serve manufacturers of electronic and electro-mechanical equipment as well as Government agencies who require the preparation of any type of instruction manual covering technical equipment . . . **GENERAL ELECTRIC COMPANY** announces the creation of a new operating division, the Communication Products Department, which will absorb functions previously handled by the company's Communication Equipment Section. Products of the new department will include mobile radio, microwave radio relay, radio traffic coordination units, power line carrier equipment, terminal equipment, and other communication systems.

WALTER E. PEEK, formerly sales manager of Electronic Mechanical Products, has been appointed general sales manager of *Centralab*, a division of *Globe Union Inc.*



His new assignment covers all products: variable resistors, wave switches, packaged electronic circuits, semiconductors, piezo ceramics, special ceramics, ceramic capacitors, and distributor and export sales.

Mr. Peek has been with the company since 1953. Prior to his employment with this organization, he was with such firms as *Arvin Industries*, *Colonial Radio Corp.*, *General Instrument Corp.*, *Electronic Labs.*, and *P. R. Mallory* in engineering, production, sales, and management.

RETMA has requested all of its member companies to submit answers to a questionnaire pertaining to industry practices aimed at alleviating the shortage of engineers, scientists, and other technical personnel.

The industry survey is being conducted in order to fulfill a Department of Defense request that the electronics industry study the problems of technician shortages in the Armed Services and propose means by which the situation might be improved. A comprehensive report will be compiled

RADIO & TELEVISION NEWS

Join the NEL-KAYE
RECORD CLUB
SAVE \$150 or more
on ALL L.P. RECORDS

... Any Label

... No Exception

plus **FREE** with your membership: **ANY** 10" or 12" Record of your choice.

If you are a true record collector, be it classical, pop, or jazz... this club was designed for you. As a member you can get ANY L.P. ever recorded at actual **DEALERS COST**, that's a saving of **38%** off the current list price. If you purchase as few as one record a week you will save over \$75 a year.

The Nel-Kaye Record Club has been established for many years. Each year thousands of members take advantage of its unprecedented 38% saving. The membership fee is only \$10 for 2 years (less than 2c a day) and entitles you to the following:

1 One 10" or 12" LP record absolutely **FREE**, **ANY** record—**ANY** label—the choice is entirely up to you. (the value of this **FREE** record alone is actually worth the greater part of your \$10. membership fee.)

2 During the 24 month period of your membership, you may purchase as many or as few records as you wish.

3 There are no restrictions of any kind. You may order any LP record—any label, major or minor—RCA, Decca, Columbia, Capital, Mercury, London, Westminster, Urania, Vox,

Hayden Society, etc., any LP listed in any record Catalog. No exceptions—in short, any LP ever recorded.

4 Each month you will receive, absolutely **FREE**, a new record catalog worth 25¢, listing every LP ever recorded.

5 All records are guaranteed factory-new and in perfect condition assuring the highest standards of Hi Fidelity recording. Exchanges on any defective records are made immediately without charge.

★ Foreign Memberships accepted. ★

Special Offers at Dealer's Cost

will be made from time to time to club members on all accessories such as diamond needles, tapes, record racks, Hi-Fi phonographs etc.

MONEY BACK GUARANTEE

Full membership fee (less cost of Free membership record) refunded within 60 days if not completely satisfied.

Make checks payable to
NEL-KAYE RECORDS, Inc. 1604 York Ave., New York 28, N. Y.

I am enclosing \$10 ☐ check or ☐ money order covering two year membership in the "Nel-Kaye Record Club of the Year." This does not obligate me in any way. I may order as many or as few records of my choice as I wish.

My Free L.P. record choice is.....

NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

Dept. R-2

JOIN TODAY
and save many,
many dollars
throughout
the year.

Note: There is a small postage
and handling charge on all orders.

from the industry findings and submitted for Defense Department examination.

The two-stage survey is designed to obtain, in general terms, a quantitative analysis of programs which are already in use in the electronics industry, and submit any workable or proven practices which have been the most helpful in meeting the challenge of manpower shortages.

At the same time, RETMA believes that the survey will provide, for the first time, a library of comprehensive information on this vital subject, and will provide guide lines to member firms for the adoption and expansion of programs in this area to thus enable manufacturers to meet and solve the problem of manpower shortages.

ALLEN B. Du MONT, JR. has been appointed assistant division manager of the Receiver Division of **Allen B. Du-Mont Laboratories, Inc.**



In his new position, he will supervise product development from a technical and styling standpoint for television receivers, high-fidelity phonographs and combinations, and clock, table, and portable radios. Other administrative duties will include plant and office layout, market and merchandising analysis, and leasehold improvements of wholly-owned subsidiaries.

He was formerly a divisional sales representative, assistant to the Tube Division manager, and has recently held posts in merchandising and administration with the Television Receiver Division.

F. D. EDES has been appointed assistant to the vice-president and general manager of **Raytheon Manufacturing Company's** Receiving and Cathode Ray Tube Operations. He will make his headquarters in Newton, Mass. . . .

ROBERT L. SHAW has been appointed general sales manager of the Radio and Television Division of **Sylvania Electric Products Inc.** . . . **Filtors, Inc.** has named **C. G. "SPEC" BARKER** sales manager of the company . . . **J. F. MAIER** has been made administrator, Tube Industry Sales, **RCA Tube Division** . . . **RICHARD W. WALKER** is now vice-president in charge of manufacturing at **Transitron, Inc.**, a subsidiary of **Van Norman Industries, Inc.** He has taken permanent residence in Manchester, N. H. . . . **University Loudspeakers, Inc.** has named **LAWRENCE J. EPSTEIN** director of Sales and Merchandising, and **CHARLES RAY** as Jobber Sales manager . . . The appointment of **HARLEY T. LITTERAL** as radio sales manager of the Radio and Television Division has been announced by **Sylvania Electric Products Inc.** . . . **GEORGE D. RICE** has been elected a vice-president in charge of manufacturing and a mem-

(Continued on page 112)

How to Pass



Let us send You
FREE

Tells where to take FCC examinations, approved way to prepare for FCC examinations, positive method of checking your knowledge before taking the examination.

the entire story on How to
PASS Your FCC Commercial
License Exams.

Get Your FCC License

WE GUARANTEE To Train You
Until You Receive
YOUR FCC LICENSE

If you fail to pass your Commercial License exams after completing our course, we guarantee to continue your training, without additional cost of any kind, until you successfully obtain your Commercial License.

Cleveland Institute Training Results in

success with commercial FCC examinations . . . easily
. . . and quickly.

every month our trainees get jobs like these:



Boyd Daugherty:

"I recently secured a position as Test Engineer with Melpar, Inc. A substantial salary increase was involved. My Cleveland Institute training played a major role in qualifying me for this position."
Boyd Daugherty
103 Goodwin Ct., Apt. C
Falls Church, Va.



Irving Laing:

"You cover topics that were not presented by the Navy at the E. I. School . . . Your course has helped greatly to get my 2nd class FCC ticket. I am now a radio and T.V. engineer at WTV's and WDR in Detroit, Michigan."
Irving L. Laing
15887 Robson
Detroit 27, Michigan

TOP GRADE EMPLOYERS LIKE THESE LOOK

BENDIX RADIO:

"We shall look forward to receiving completed applications from your students."

PHILCO:

"We have employed a great number of well qualified electronics personnel who were graduates of Cleveland Institute."

WESTINGHOUSE:

"We would appreciate your listing our current openings in your monthly Job Opportunities."

FCC Commercial Operator License Exams

An FCC License can be your
Guarantee of Success in Electronics

In a Minimum of Time

mail
coupon
Now!

here's proof...

Get all **3** FREE

Name and Address	License	Time
Walter Eggers, Pacific Grove	1st	12 weeks
Paul Reichert, West Salem, Ohio	2nd	10 weeks
Harold Phipps, La Porte, Indiana	1st	28 weeks
John H. Johnson, Boise City, Okla.	2nd	12 weeks
James Faint, Johnstown, Pa.	1st	26 weeks



Bob Thompson:

In a year and a half, he received his first class FCC License. He is continuing his training with Cleveland Institute. His goal is much higher than his present position with Eastern Airlines, so he is adding technical "know-how" to his practical experience.

Bob Thompson
2035 Ironwood Drive
Nashville 14, Tennessee

James Glen:

When Jim enrolled, he was a temporary employee of the City of Tacoma, Washington. In the space of 14 months, he completed the Master Course and received his first class license. He is now installing and maintaining mobile and microwave equipment.

James S. Glen, Jr.
2920 Knob Hill Road
Tacoma, Washington





TO CLEVELAND INSTITUTE

Aerjet-General
American Airlines
American Telephone &
Telegraph Co.
Bendix Radio
Braniff Airways
Burroughs Corp.
Capital Airlines
Continental Air Lines, Inc.
Convair
General Electric
Glenn L. Martin Co.

Goodyear Atomic Corp.
IBM
International Telephone
& Telegraph Co.
Mohawk Airlines
Motorola
North American Aviation,
Inc.
Northwest Airlines
Philco
RCA
Ryan Aeronautical Co.

*Plus many others

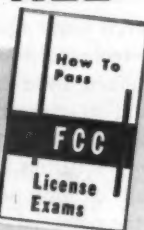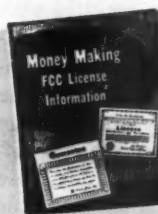

Accredited by National Home Study Council

Cleveland Institute of Radio Electronics

Desk RN-2, 4900 Euclid Ave., Cleveland 3, O.

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other _____ |

In what kind of work are you now engaged? _____

In what branch of Electronics are you interested? _____

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Special Tuition Rates to Members of Armed Forces

Do you need a Degree for success in Electronics?

Not necessarily," says Dick Brani, 33-year-old Field Engineering Instructor in Project Sage at IBM—Kings-ton, New York. "Oh, sure—I'm aware of my limitations to design electronic equipment even though I am qualified to maintain it. That's the biggest advantage of a formal degree. The point is . . . there are many responsible management positions opening all the time in IBM for men like myself . . . and comparable positions elsewhere would probably require an engineering degree."


Some seven years ago, IBM took the initiative with respect to technical training within its own organization. It realized, even then, that a great number of intelligent and otherwise capable men were falling by the wayside merely because they lacked 4 years of college engineering. Statistics indicated that because of financial difficulty or improper high-school preparation, close to 50% of the potential engineers in the country became lost in the educational shuffle. While some people with less foresight ignored the fact or bemoaned it, IBM did something about it. Consequently, fellows like Dick Brani can now enjoy more satisfying, more rewarding work than ever before.

Great Interest in Mathematics. While Dick was attending Boys' High in Brooklyn, his principal academic interest was mathematics. And, like many other young fellows of that era, Dick was realistic about his future.

He decided his best bet might be business accounting. When Dick graduated in 1940, he accepted a position with a New York banking firm. It was not until Dick entered the Army in 1943 that he had the opportunity to pursue a more advanced form of mathematics, an A.S.T.P. training program at Lehigh University. This all-too-brief experience convinced Dick that he should make his career in a field that was in some way related to electrical technology.

Postwar Education. Discharged with the rank of Staff Sergeant, Dick returned to Allentown, Pa., to marry a girl he had met while enrolled at Lehigh. During this period, he successfully supported his family and himself selling various lines of food. In the evening, however, Dick continued his study of radio, TV, and electronics at the Allentown Branch of the Temple Institute. In two years' time, he graduated and secured an F.C.C. license. His technical career was beginning to take shape.

IBM Looks Especially Good. Glancing through an issue of *Time Magazine* one evening, Dick happened to read an article about Thomas J. Watson, Jr., the president of IBM. The story emphasized Mr. Watson's great faith in the future of electronic computers . . . the wonderful promise it holds for the ambitious, intelligent young man. Some time later, Dick spotted a classified ad describing IBM's association with Project Sage. Phil-

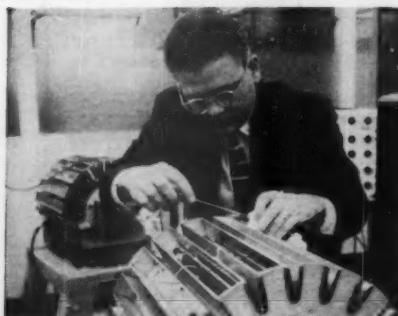

Brani trouble shooting Magnetic Drum Frame. Brani studies computer pluggable unit. Dick explains computer logic to a Systems Class.

RADIO & TELEVISION NEWS



33-year-old Dick Brani feels that technicians can grow into more responsible positions.

adelphia was one of the work locations available after training. That was all Dick Brani needed.

Asked to Become an Instructor. When Dick was three-quarters of the way through his nine month computer systems course, he was invited to remain at Kingston as an instructor. "It was like a bolt out of the blue," he recalls. "I knew I'd enjoy teaching, but I always thought it was out of the question. I accepted all right, and I can't tell you how much I've enjoyed helping these fellows and watching them grow within the organization. For instance, there's a fellow in my class right now whose education is limited to correspondence school. He's in the top third of his class, and has a real future with IBM—all because he has the native talent and is willing to work."

What Does Dick Brani Teach? "Actually, I teach three separate courses for technicians in field engineering. One is computer systems testing, which is for the more advanced student. This training lasts for 33 weeks—a long time, perhaps, but it's well worth it. Another is a program of 24 weeks' duration that deals with computer input-output units. Finally, I teach a course in computer units displays. This also lasts for 24 weeks. Each one of these courses is an education in itself." Experience has shown that IBM's educational programing is most successful. Men accepted receive their training

with no strings attached—no contracts. Upon graduation the road to success is wide open in *all* divisions of the corporation.

The World's Largest Electronic Computer. "This computer is really fantastic. It contains approximately 1,000,000 parts, and it's housed in a building 4 stories tall. Information is filtered in from Texas towers, picket ships, reconnaissance planes—even ground observers. Every object in the sky is analyzed. Then it checks each object against available traffic data and identifies it as either friendly or hostile. It can make suggestions, but it can't send a Nike missile against a 'baddie.' Only authorized personnel can make that decision."

What About Dick's Future? "Well, right now, I'm doing work that most technicians couldn't touch with a ten-foot pole. I know of few companies where technicians are actually doing engineering work. I guess it's a matter of approach. Both kinds of companies will get the job done, but IBM prefers to think in terms of the man, encouraging him to grow into more responsibility. You might say that IBM gets more out of the man, and in the final analysis, it seems a lot more efficient from the corporation's and employee's viewpoint. Personnel policy at all levels—management, engineering, or technical—is the same. The future is wide open."

Just recently, Dick bought a home in Saugerties, near Kingston, where his wife Betty and their three children, David, 9, Sharon, 7, and Paul, 3, enjoy a pleasant, contented life together. Occasionally, in the summertime, Dick plays softball with his co-workers. But his family is—and always will be—his predominant interest.

What About You? Opportunities in the Project Sage program of long-range national importance are still growing. If IBM considers your experience equivalent to an E.E., M.E. or Physics degree, you'll receive 8 months' training, valued at many thousands of dollars as a Computer Systems Engineer. If you have 2 years' technical schooling or the equivalent experience, you'll receive 6 months' training as a Computer Units Field Engineer, with opportunity to assume full engineering responsibility. *Assignment in area of your choice.* Every channel of advancement in the entire company is open. All the customary benefits and more. **WRITE to:** Nelson O. Heyer, Dept XXX, IBM, Kingston, New York. You'll receive a prompt reply.



At the Maintenance Console.
February, 1957




At home Dick plays with one of his three children.

Customer Engineers: opportunities are also available, locally, for servicing IBM machines, after training with pay. Consult your nearest IBM office.

IBM

**MILITARY
PRODUCTS**

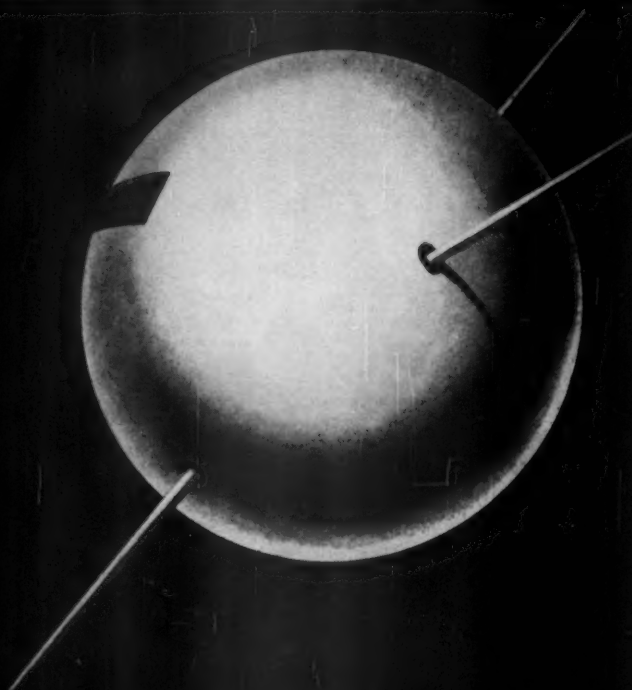DATA PROCESSING
ELECTRIC TYPEWRITERS
TIME EQUIPMENT
MILITARY PRODUCTS



A NEW FRONTIER FOR TECHNICIANS

RCA offers an opportunity for you to apply your technical skill to its Missile Test Project at Patrick Air Force Base, Florida—"Launching Site of the Satellite."

Here at the world's longest missile testing range, extending from Florida far across the South Atlantic, you can enjoy improved status with the recognized leader in Electronics. Unprecedented growth opportunities are offered in various phases of data acquisition, transmission and processing, including Radar—Communications—Optics—Computers—Timing—Telemetry.

At RCA's Missile Test Project you will enjoy technical advancement

combined with famous Florida living. Your family will appreciate the ideal climate—allowing year 'round outdoor activities—and pleasant social surroundings.

Immediate assignments are available in Florida, the Bahama Islands, and aboard tracking ships in the South Atlantic. Attractive home leave policy and salary differential make the Bahama Islands and tracking ship assignments especially attractive for single men.

Let the Missile Test Project become *your* symbol of the future. Join in our assault on the frontier of space!

For complete information about this new and challenging field, write to:

Personnel Manager, Dept. N-16B
RCA Service Company, Inc.
Missile Test Project
P.O. Box 1226
Melbourne, Florida



RADIO CORPORATION of AMERICA



Terrific TV traffic-builder!

remote CONTROL INSTANT TUNER for TV!

changes channels
from your
easy chair!



DON WILSON—RADIO AND TV'S GREATEST SALESMAN WILL BRING CUSTOMERS IN DROVES!

Don Wilson, one of America's long-time favorite radio and TV announcers, will lend his strong support to help you sell I-T Remote Control Instant Tuners on television. So place your order now for a big stock of I-T's and capitalize on this big advertising campaign.



Goes On Practically Any Set!


The I-T Remote Control Instant Tuner is engineered to go on practically any set—new or old. Your market is wide open!

No Installation Problems!

Customers can install I-T themselves in less than 3 minutes! It's easy—no tools needed—no electrical connections. And, there's no service problem!

HERE'S HOW SELLS!

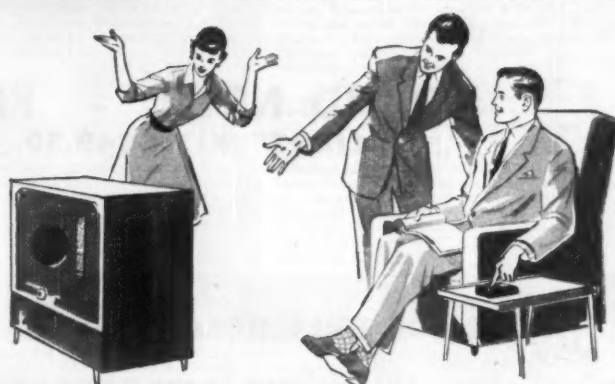I-T sells like hot cakes! All you have to do is demonstrate it—and you'll sell I-T's by the bushel! Almost every TV set owner is a red hot prospect. IN ADDITION—I-T is the perfect gift for every occasion—wedding, housewarming! You name it—and you'll sell I-T!



I-T IS SOLD AND FULLY GUARANTEED BY

THE ALLIANCE MANUFACTURING CO., INC., ALLIANCE, OHIO

(Division of Consolidated Electronic Industries Corp.)

In Canada—Alliance Motors, Schell Ave., Toronto, Ontario

WRITE, WIRE, OR CALL NOW FOR INFORMATION ON HOW YOU
CAN ORDER and PROFIT with I-T Remote Control INSTANT TUNER!



WE TRADE HIGHER!

SKEPTICAL? WE'LL PROVE IT! WRITE TODAY!



BRAND NEW! - FROM JOHNSON
"VALIANT" KIT \$349.50 - WIRED \$439.50

WRITE FOR FULL DETAILS ABOUT OUR TIME PAYMENT PLAN

All prices f. o. b. St. Louis • Phone Chestnut 1-1125

Walter Ashe
RADIO CO.

P. O. BOX 4444 • PLAZA STATION
ST. LOUIS 1, MO.

WALTER ASHE RADIO COMPANY

OUR 35TH YEAR

☐ Rush "Surprise" Trade-In Offer on my.....
 for.....
 (show make and model of new equipment desired) RN-2-57
☐ Send NEW 1957 Walter Ashe catalog.
 Name.....
 Address.....
 City..... Zone..... State.....

RADIO & TELEVISION NEWS




NEW DYNAMIC CONDUCTANCE TUBE and TRANSISTOR TESTER #666

KIT \$69.95
WIRED \$109.95

COMPLETE with steel cover and handle.

SPEED, ease, unexcelled accuracy & thoroughness. Tests all rectifying tubes (8 pic tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel. of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges motor sensitivity (1% shunts & 5% pot). 10 SEX-position lever switches: free-point connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply.

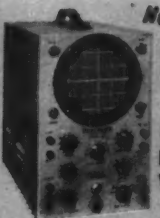

NEW COLOR and Monochrome DC to 5 MC LAB & TV 5" OSCILLOSCOPE #460

KIT \$79.95
WIRED \$129.50

• Features DC Amplifier!

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input 2.5 mcps; direct-coupled & push-pull throat; 8-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions; auto. sync. ampl. & lim. FLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equip. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. 2-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.



NEW TV-FM SWEEP GENERATOR & MARKER #368 KIT \$69.95 WIRED \$119.95

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional tuning accuracy: edge-lit hairlines, 330° scale. Sweep Osc. Range 3-216 mc in 8 fund. bands. Variable Marker Range 2-75 mc in 8 fund. bands; 60-225 mc on harmonic band. Xtal-controlled Marker Osc., 4.5 mc atal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: 50-ohm term. output, 'scope horiz., 'scope vertical with isolation probe.

7 NEW BEST BUYS by

The specs are the proof...



NEW HIGH FIDELITY PREAMPLIFIER

#HF61A KIT \$24.95, WIRED \$37.95

With Power Supply: #HF61 KIT \$29.95, WIRED \$44.95

Will not add distortion or detract from the wide-band or transient response of the finest power amplifiers at any control settings. High quality feedback circuitry throughout plus the most complete control & switching facilities. Heavy-gauge solid brushed brass panel, concentric controls, one-piece-brown enamel steel cabinet for lasting attractive appearance. Feedback-type, sharp cut-off (18 db/octave) scratch & rumble filters. Low-distortion feedback equalization: 5 most common recording curves for LPs & 78s including RIAA. Low-distortion feedback tone controls: provide large boost or cut in bass or treble with mid-freqs & volume unaffected. Centralized printed-circuit Series "Compucontrol" loudness control with concentric level control. 4 hi-level switched inputs (tuner, tv, tape, aux.). & 3 low-level inputs (separate front panel low-level input selector permits concurrent use of changer & turntable). Proper pick-up loading & attenuation provided for all quality cartridges. Hum bal. control: DC superimposed on filament supply. 4 convenience outlets. Extremely flat wideband freq. resp.: ± 1 db 3-100,000 cps; ± 0.5 db 12-50,000 cps. Extremely sensitive. Negligible hum, noise, harmonic or IM distortion. Size: 4-7/8" x 12-5/16" x 4-7/8". 8 lbs.



60-WATT Ultra-Linear

HIGH FIDELITY POWER AMPLIFIER #HF60
with ACRO TO-330 OUTPUT TRANSFORMER
KIT \$72.95, WIRED \$99.95

Superlative performance, obtained through using the world's finest components & circuitry, at an incredibly low price. Circuit comprises EF86 low-noise voltage amplifier direct-coupled to 6SN7GTB cathode-coupled phase inverter driving a pair of Ultra-Linear connected push-pull EL34 output tubes operated with fixed bias. Rated power output: 60 w (130 w peak). IM Distortion (60 & 6000 cps at 4:1): less than 1% at 60 w; less than 0.5% at 50 w. Harmonic Distortion: less than 0.5% at any freq. between 20 cps & 20 kc within 1 db of 60 w. Sine-wave Freq. Resp.: at 1 w: ± 0.1 db 5 cps to 90 kc; at 60 w: ± 0.1 db 16 cps to 90 kc. Square Wave Resp.: excellent from 20 cps to 25 kc; 3 usec rise-time. Sensitivity: 0.35 v for 60 w. Damping Factor: 17. Inverse Feedback: 21 db. ACRO TO-330 Output Transformer (fully potted). GZ34 extra-rugged rectifier (indirectly-heated cathode eliminates high starting voltage on electrolytics & delays B+ until amplifier tubes warm up). Input level control. Panel mount fuse holder. Both bias and bias-balance adjustments. Std octal socket provided for pre-amplifier power take-off & remote on-off switching. Size: 7" x 14" x 8". 30 lbs. Matching cover available.



NEW

COMPLETE with Preamplifier, Equalizer
& Control Section
20-WATT Ultra-Linear Williamson-Type
HIGH FIDELITY AMPLIFIER #HF-20
KIT \$49.95, WIRED \$79.95

A low-cost, complete-facility amplifier of the highest quality that sets a new standard of performance at the price, kit or wired. Rated Power Output: 20 w (34 w peak). IM Distortion (60 & 6000 cps at 4:1) at rated power: 1.5%. Max. Harmonic Distortion between 20 & 20,000 cps at 1 db under rated power: approx. 1%. Mid-band Harmonic Distortion at rated power: 0.5%. Power Response (20 w): ± 0.5 db 20-20,000 cps; ± 1.5 db 10-40,000 cps. Freq. Resp. (34 w): ± 0.5 db 15-35,000 cps; ± 1.5 db 7-50,000 cps. 5 feedback equalizations for LPs & 78s. Low-distortion feedback tone controls: large boosts or cuts in bass or treble with mid-freqs & volume unaffected. Loudness control & separate level set control on front panel. Low Z output to tape recorder. 4 hi-level switched inputs: tuner, tv, tape, aux.; 2 low-level inputs for proper loading with all cartridges. Hum bal. control. DC superimposed on filament supply. Extremely fine output transformer: interleaved windings, tight coupling, careful balancing, grain-oriented steel. 8 1/4" x 15" x 10". 24 lbs. Matching cover available.

NEW COMPLETE with FACTORY-BUILT CABINET— 2-WAY HI-FI SPEAKER SYSTEM #HFS1 \$39.95

See the "BEST BUYS" NOW IN
STOCK at your nearest distributor.
Fill out coupon for FREE CATALOG.

Prices 5% higher on West Coast.



Genuine 2-way book-shelf size speaker system. Jensen heavy duty 8" woofer (6.6 oz. magnet) & matching Jensen compression-driver exponential horn tweeter with level control. Smooth clean bass & crisp extended highs free of coloration or artificial brilliance. Factory-built tuned bass reflex birch hardwood cabinet (not a kit) constructed to high quality standards. Neutral acoustical grille cloth framed by a smooth-sanded solid birch molding. Freq. Resp. measured 2 ft. away on principal axis in anechoic chamber with 1 watt input - Woofer: ± 4 db 80-1800 cps; Tweeter: ± 2 db 2800-10,000 cps; Crossover Region: 1800-2800 cps, shift in level over this region depends on tweeter level control setting. Power-handling capacity: 25 watts. Size: 23" x 11" x 9". 19 lbs. Wiring Time: 15 min.

84 Wilhens Street, Brooklyn 11, N. Y.



Turn page for other EICO ad.

the specs prove
who's best!
for COLOR & Monochrome
TV servicing

NEW!



#324

**RF SIGNAL GENERATOR
KIT \$26.95 WIRED \$39.95**

150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble-shooting of TV, FM, AM sets; marker gen.; 400 cps audio testing; lab. work. 6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to $\pm 1.5\%$; 0:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial, plexiglass windows, edge-lit hairlines. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. amplifier; only 3.0 v needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. 8" x 10" x 4 3/4". 10 lbs.

NEW!

**PEAK-10-PEAK
VTVM #232
& UNI-PROBE
(pat. pend.)
KIT \$29.95
WIRED \$49.95**



Half-turn of probe-clip selects DC or AC-Ohms.


Uni-Probe — exclusive with EICO — only 1 probe performs all functions! Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4 1/4" meter, can't burn-out circuit. 7 non-skip ranges on every function. 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms. Uniform 3 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 mega. 12AU7, 6AL5, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. 8 1/4" x 5" x 5". 7 lbs.

Turn page for other EICO ad



**FREE 1957
EICO CATALOG!**

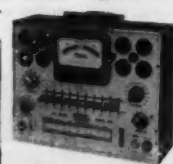Tells you how to SAVE 50% on
your test equipment costs!




Pix Tube Test Adapter

**TUBE TESTER
#825
KIT \$34.95
Wired \$49.95**
• tests 600 mil series string type tubes
• illuminated roll-chart

.....\$4.50

**SINE & SQUARE WAVE AUDIO
GENERATOR #377**

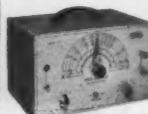**KIT \$31.95
Wired \$49.95**
Ranges: sine, 20-200,000 cps; square, 60-50,000 cps. Resp. ± 1.5 db 60-150,000 cps. Accuracy $\pm 2\%$.



**5" PUSH-PULL OSCILLOSCOPE #425
KIT \$44.95
Wired \$79.95**
**7" PUSH-PULL OSCILLOSCOPE #470
KIT \$79.95
Wired \$129.90**




**VACUUM TUBE VOLTMETER #221
KIT \$25.95
Wired \$39.95**
**DELUXE VTVM : 214 (7 1/2" METER)
KIT \$34.95
Wired \$54.95**



**RF SIGNAL GENERATOR #320
KIT \$19.95
Wired \$29.95**
150 kc-34 mc, calibrated harmonics to 102 mc. Pure or mod. RF, & Colpitts osc. 400 cps sine outputs.



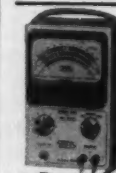
**NEW! REDI-TESTER #540
KIT \$12.95
Wired \$15.95**
Multi-range ac/dc voltmeter, ammeter, ohmmeter, leakage checker for home & auto repairs.



**#844 FLYBACK TRANSFORMER & YOKE TESTER
KIT \$23.95
Wired \$34.95**
• fast check all flybacks & yokes in or out of set.
• spots even 1 shorted turn!



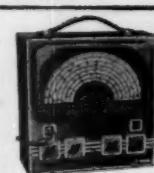**TV/FM SWEEP GENERATOR #380
5MC-4.5MC CRYSTAL\$3.95 ea.**




**1% accuracy on all 7 ranges. Range 75 kc-150 mc. Volt reg.
KIT \$39.95
Wired \$59.95**
DELUXE RF SIGNAL GENERATOR #315




6V & 12V BATTERY ELIMINATOR & CHARGER #1090



DELUXE MULTI-SIGNAL TRACER #147

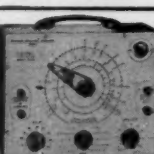

R-C BRIDGE & R-C-L COMPARATOR #950B

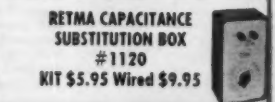

**RETMA CAPACITANCE SUBSTITUTION BOX #1120
KIT \$5.95 Wired \$9.95**



**RETMA RESISTANCE SUBSTITUTION BOX #1100
KIT \$5.95
Wired \$9.95**

**20,000 Ohms/Volt MULTIMETER #565
KIT \$24.95
Wired \$29.95**

**1000 Ohms/Volt MULTIMETER #536
KIT \$12.90
Wired \$14.90**

**VTVM PROBES
Peak-to-Peak\$4.95 \$6.95
RF\$3.75 \$4.95
High Voltage Probe-1\$6.95
High Voltage Probe-2\$4.95**

**SCOPE PROBES
Demodulator\$3.75 \$5.75
Direct\$2.75 \$3.95
Low Capacity\$3.75 \$5.75**

For FREE 1957 catalog, mail coupon NOW!

EICO®

84 Withers St. • Brooklyn 11, N. Y.

Prices 5% higher on West coast and subject to change without notice.

EICO, 84 Withers Street
Brooklyn 11, New York

Send FREE 1957 Catalog and name of neighborhood EICO jobber.

Name.....
Home Address.....
City.....Zone.....State.....
Occupation.....

Over a Decade of Know-How & Value Leadership in Kits & Instruments — Over 1 Million Sold to Date!



Authors Hankinson and Fallgren tune up the tiny transistorized transmitter with a grid-dip meter prior to going on the air.

Transistorized Amateur Transmitter

45,000 Miles-per-Watt

By

GUS FALLGREN, W10GU & AL HANKINSON, W1OSF

Research Technicians, Missile Systems Div., Raytheon Manufacturing Company

YES, that's what we said! On .08 watt (6 volts at 13 ma.) to a Raytheon 2N113/CK761 transistor doubler stage, we worked OZ7BO in Denmark, about 3600 miles away. And, as simple math will show, 3600 miles \div .08 watt = 45,000 miles per watt!

It all started one lunch hour last September when the three of us—Gus (W10GU), Hank (W1OSF), and Dick Wright (W1UBC), a senior at Worcester Polytechnic who had a summer job with us at Raytheon—were kidding about low power. Dick said, "Let's go on 20 c.w. with transistors and work all continents." We laughed at this, all of us being medium-power DX hounds. But we talked it over through lunch as a joke project, and brought it up again that evening when the three of us met again at Gus's home.

None of us was a transistor expert so we called up a fellow ham who is a transistor applications engineer. He thought that Raytheon 2N113/CK761's, readily available at parts suppliers, should do the trick. We obtained them a few days later, and that evening a breadboard rig crudely haywired together was ready for preliminary tests.

Since Gus has the only three-element wide-spaced beam on 20, there was no argument about where the rig would be fired up. With a "by guess and by gosh" measurement, we tapped the coax lead from Gus's beam directly onto the final tank and plugged the key into the jack.

The first note, clear and steady, blasted forth from the receiver—not

one of those chirpy notes that infest the 20-meter band but a note of pure d.c.


Feeling like characters in a science fiction thriller, we carefully scanned the band for a 599 plus 40-db-over signal. After a couple of false starts we decided to use Gus's big rig for the initial contact and then switch over to the small rig.

First call went out to WØVZB in Kansas City, Missouri. He came back to the big rig and then agreed to listen for the small rig. Out went the call—all 80 milliwatts flooding the airwaves. "Break" went W10GU and a 559 re-

*Bored with your big rig?
Want a new and exciting
experience? Build this
tiny .08 watt transmitter
for your DX-ing. It is
transistorized and compact!*

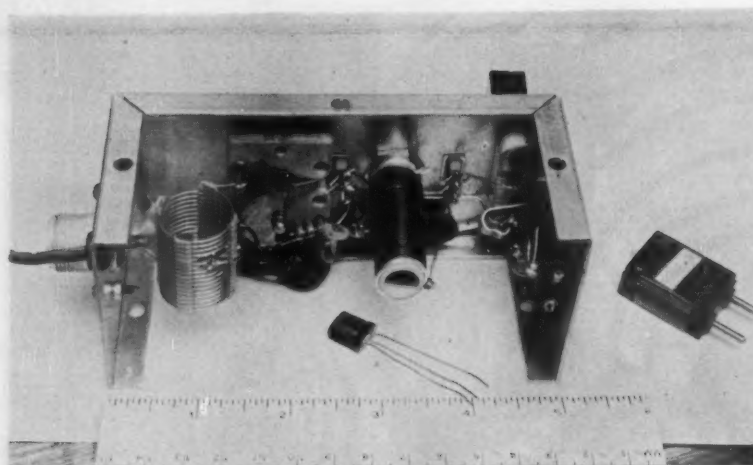Gus Fallgren keys the transmitter whose power source is the battery shown.





Under-chassis view of transistorized transmitter. Note the simplicity of the construction. Output tank circuit is at left, oscillator tank just right of center.

port came back. This was too much! Like horse players, we decided to try "just one more." Again it worked, the QSO this time being with a K4 in Virginia. That did it—we were ready for the big venture. As far as we knew, no one had ever worked outside the continental U.S.A., but we were going to try.

Our call went out to a KV4 in the Virgin Islands but QRM was hashing up the band. Suddenly, KP4ZW in Puerto Rico broke in to tell us he was copying the small rig. He was the first DX contact. In the days that followed, Gus manned the rig morning and evening before and after work, and the following QSO's resulted: T12PZ, Costa Rica, report 439; OZ7BO, Denmark, 339; and G3AAM, England, 349.

At this point the big rig was out of a job—QSO's were coming in fast and easy with the transistor rig alone. All it took was plenty of listening and


making sure the frequency was clear except for the intended victim, who had to be someone calling CQ DX with a 599-plus-plus-plus signal.

Of course, plenty of credit goes to the beam which selected those nice fat signals. However, some contacts were made using an 80-meter doublet with tuned feeders, so the city cave-dweller need not despair.

Comments of operators worked cover the whole band from surprise to outright disbelief—from "wow!" to "ridiculous!" No one has failed to mention the sweet-sounding note. Signal strength reports have ranged from 239 to 579 at W8OCT. The score sheet for the first two weeks shows nine states, five countries (including the first transatlantic jump on record at the ARRL), and many duplicate contacts. Requests for schematics and construction data come in every day.

Meanwhile, with the able assistance

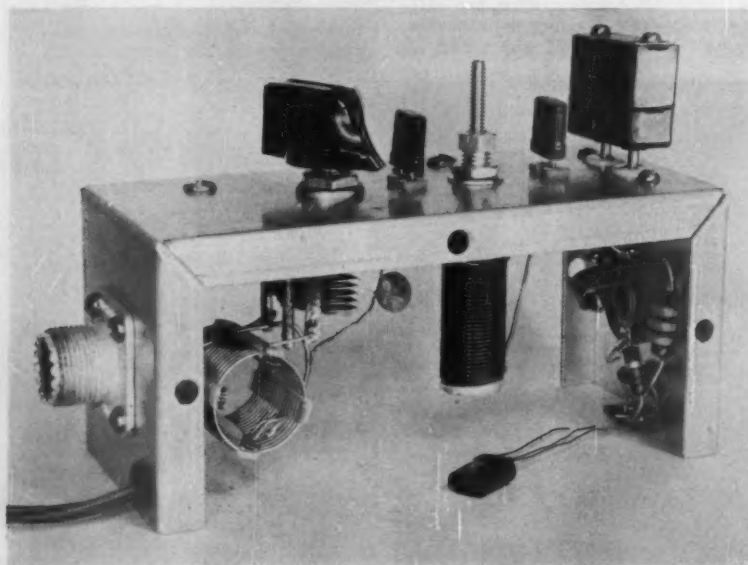The complete transmitter is built into a case measuring 5" x 2 1/4" x 2 1/4". Parts are identified in the text but the layout is non-critical and can be changed.



of our friend the transistor applications engineer, we have been catching up on transistor theory and can now explain why the 2N113/CK761 transistors perform so well in our rig. These transistors are of the fusion-alloy germanium type. They were introduced by Raytheon over a year ago and have been widely used in portable receivers and medium-speed computers.

Three important factors in the design of high-frequency transistors are low collector capacitance, a high α cut-off frequency, and a low value for a parameter called "extrinsic base resistance."

Collector capacitance is simply the capacitance of the collector junction; it is ordinarily kept low by keeping the area of the collector junction as small as possible. In the 2N113/CK761, this value is about 12 μ fd. at 6 volts.

α cut-off frequency is defined as the frequency at which the current gain of the transistor has fallen to .7 of its very-low-frequency value. However, this is not necessarily the maximum usable frequency. The 2N113/CK761 has an average α cut-off frequency of about 10 mc., yet it operates successfully as a doubler final in our transmitter at 14 mc.

It is true that α cut-off frequency does affect efficiency, and that an α cut-off value four or five times our operating frequency of 14 mc. would theoretically give our rig increased efficiency. However, transistors with very high α cut-off frequencies are so much more expensive than the 2N113/CK761 that the improvement in efficiency is not worth the greater cost. Furthermore, an increase in α cut-off frequency in abrupt junction types like the 2N113/CK761 results in a reduction in the maximum voltage that can be applied. It may well be that more useful power can be obtained at 14 mc. from a unit like the 2N113/CK761 than from one having a higher α cut-off but a lower permissible power input.

Extrinsic base resistance, the third factor, is the series resistance of the semiconductor body between the point where the external connection is made to the transistor and the point inside the body where transistor action really occurs. It is called "extrinsic" because in a sense it is not a true (intrinsic) transistor characteristic. This series resistance causes a reduction in the input signal. It is only about 75 ohms in a 2N113/CK761 but may run as high as several hundred ohms in an audio-type transistor.

Although the output power has not been measured, the efficiency is probably not greater than 25%; hence 60 mw. is being dissipated within the transistor and 20 mw. is delivered as useful power.

The amount of power that a junction transistor can handle is mainly determined by the temperature rise of the junction and the maximum safe temperature. In the 2N113/CK761, the temperature rise in free air is specified as about .6° C per milliwatt and

the
App
we
our
room
may
is
spe
T
of
tran
stra
sini
rise
inci
by
tur
for
lim
2N1
tem
the
circ
N
skip
orig
nea
usin
cuit
T
ard
case
show
crys
the
men
tran
stag
tank
con
brou
the
com
are
criti
fit t
F
tran
main
H
the
sche
oscil
out,
indi
the
tran
T
a re
foll
simp
or y
milli
cator
indio
very
tran
whic
51 o
He
empl
1.
the
coil
step
tran
easil
2.
the
Febr

the maximum temperature as 85° C. Applying these specifications to our rig, we get a temperature rise of 36° C for our 80 mw. input. Adding this to a room temperature of 28° C we get a maximum temperature of 64° C, which is well within the 85° C maximum specified.

There is additional latitude because of the intermittent nature of a c.w. transmission. Also, it is possible to strap down the transistors to a heat sink so as to lower the temperature rise to about .4° C per milliwatt, thus increasing the permissible dissipation by 50% for a given ambient temperature. However, there is another reason for approaching maximum temperature limits with caution. Although the 2N113/CK761's will stand junction temperatures of 85° C without damage, they will not necessarily operate in a circuit at this temperature.

Now for construction details. We'll skip the breadboard stage, for our original rig has been refined into a neater and more efficient transmitter using the same transistors and circuitry.

The entire unit is built in a standard 5" x 2 1/4" x 2 1/4" ICA "Flexi-mount" case. Bottom photo on facing page shows, right to left, the key jack, the crystal socket, a transistor socket for the oscillator section, the slug adjustment for the oscillator coil, another transistor socket for the doubler-final stage, the tuning knob for the output tank capacitor, and the antenna coax connector. The battery leads are brought out below the coax fitting in the lower left-hand corner. No further comments on component placement are needed, as nothing seems to be critical; you can adapt the layout to fit the components available.

For matching the antenna to the transmitter, we use 52-ohm coax—mainly because we had some on hand.

However, you will do well to wind the oscillator coil as indicated on the schematic. Don't attempt to build the oscillator separately and then check it out, as you may run into trouble from individual transistor variations. Build the entire transmitter, plug in the transistors, and you are ready to tune.

Tuning is a little different than with a regular tube transmitter, but if you follow directions you should find it simple. You will need a grid-dip meter or your receiver's "S" meter, a 0-25 milliammeter, and the simple r.f. indicator shown on the schematic. The r.f. indicator is easily constructed and is very handy for working with transistor transmitters. R_s is a carbon resistor which matches the line impedance—51 ohms for a 52-ohm coax, etc.

Here is the tuning procedure to be employed:

1. Using either the grid-dip meter or the "S" meter, adjust the slug-tuned coil L_1 for maximum 7-mc. output. This step should give you no trouble, as transistor oscillators seem to oscillate easily.

2. With the milliammeter inserted in the final stage collector lead, adjust

link L_s for maximum current (12 to 15 ma.).

3. Again using either the grid-dip meter or the "S" meter, adjust the final tuning capacitor for maximum 14-mc. output.

4. You are now ready to select the tap for the collector. Using the grid-dip meter as an absorption wavemeter tuned to 14 mc. record the meter reading, then change the tap and hunt for a point where the output is maximum. Simple but effective! The best tap will be quite far down on the tank coil because of the low collector impedance.


5. Using the r.f. indicator, move up and down the final coil until the point of maximum output is found, and connect the antenna tap at this point.

Now that you have a working rig, any variations are up to you. One that we tried and discarded only for the sake of simplicity was the use of a 1-megohm potentiometer in place of R_1 and R_2 . With a pot in this location, you will have control over your drive and also your keying characteristics. We had no keying trouble whatsoever so we eliminated the pot.

Another possible refinement is to include a closed-circuit jack in the "high voltage" lead to the final. Then all you have to do to go on 20-meter phone is plug in a carbon mike of the F1 variety. We haven't given this any serious study but have worked locally on phone with excellent modulation reports.

As a final note, we are the cautious type so we limited our "high voltage" supply to 6 volts instead of operating the transistors at the maximum collector voltage permitted by the specifications.


Take it from us, if you're tired of

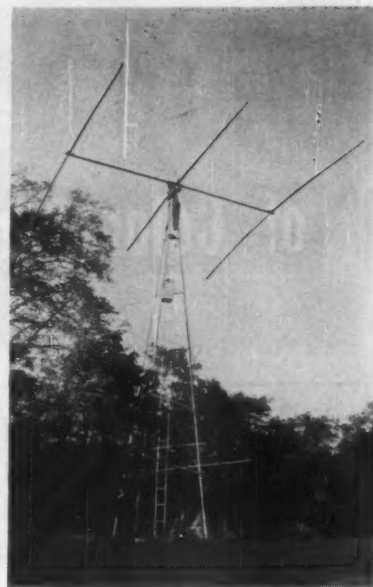

The 20-meter, 3-element, wide-spaced rotary beam that was connected to the little rig for its record-breaking DX.

traffic handling and rag chewing at length, if you would like to work on the new frontiers of the radio art, build your own transistorized rig and get a load of thrills. We know, because we have worked all sorts of DX on regular rigs in our time. Gus has 140 countries confirmed, Dick has 101, and Hank has years of maritime mobile QSO's, yet the first DX on transistors topped all the thrills of the past. All except one—the day we received our ham tickets and made our first solid QSO's! —50—

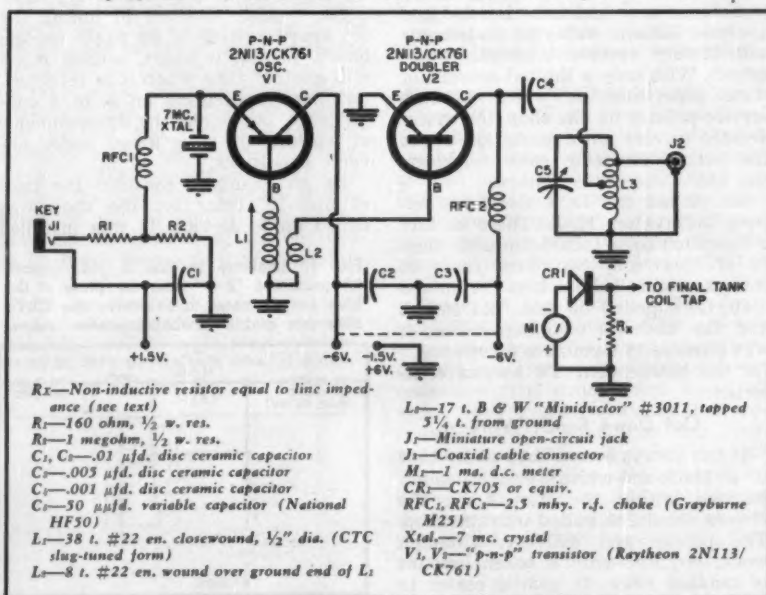Complete schematic diagram of the transistorized transmitter. Note that the oscillator and doubler transistor collector voltages can be tied together, as shown by the dotted line, after the initial tune up with the milliammeter has been completed. The circuit for determining the correct output tap and for tuning up the little transmitter is shown in the lower right-hand corner.



The Strategy of Color Servicing

The line between home and shop service shifts, but skilled technicians will take the changes in stride.

A YEAR ago two service technicians were working side by side at the bench. Neither had seen a color set up until then.

"Do you think you'll have any trouble with color sets?" one asked.

"Maybe so," the other answered, "but get it on the bench in front of me, and I'll fix it!"

He was right. Since then, this pair has tackled quite a few color repair jobs. They weren't always easy, but there wasn't one set that didn't eventually get repaired.


While black-and-white experience is invaluable, a slightly modified viewpoint is needed for handling color work. Ideas of when to pull a chassis have had to be changed. Policies on quoting estimates and delivery dates must be revised. Some new delivery techniques have had to be learned and a closer liaison with the distributor and factory service branches established. With only a limited amount of color experience on which to base service policies for the shop, the writer decided to visit an organization where the art of servicing color television has had a chance to mature.

He picked the RCA Service Company in Trenton, N. J. There he met a top-notch color technician with plenty of ideas and two busy years of color servicing behind him. From the material supplied by this "old timer" and the author's own experience, it was possible to formulate a "strategy" for the independent TV service technician.

Cut Down Bench Work

It has always been a shop policy that if a black-and-white receiver didn't respond within the first hour, the chassis should be pulled into the shop. The pickup and delivery, although work, required only a token amount of manual labor. It proved easier to

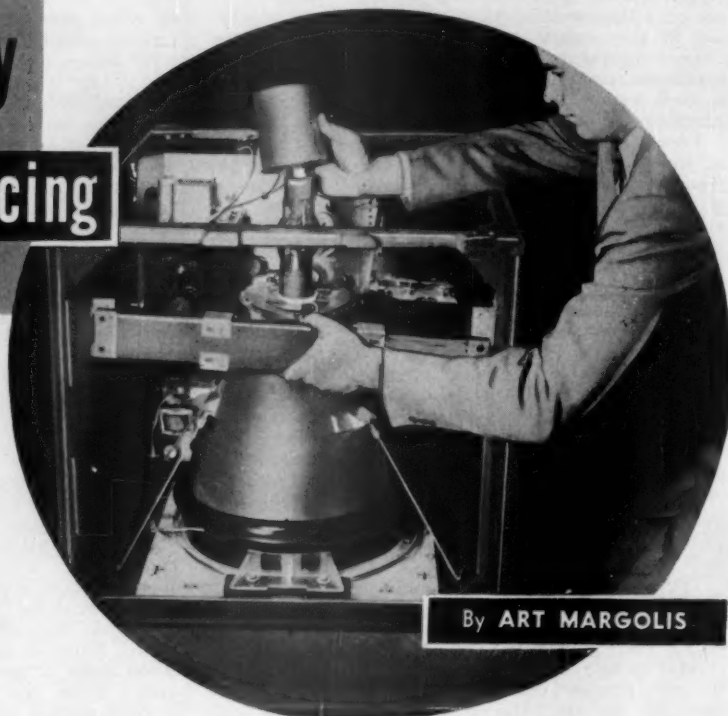Dismantling and transporting a color set for shop work and bringing it back take much time and skill. Repair in the home when possible.



By ART MARGOLIS

solve tough repair jobs in the quiet, well-equipped security of the test bench rather than in the helter-skelter, customer-over-your-shoulder, test-equipmentless private home.

Unfortunately, this situation has been somewhat changed by the advent of color. Ironically, when working on the basically harder-to-fix color set, it is wise to ignore the "first hour" principle and go further. In fact, the rule should be to work on the set until absolutely stuck. Then, of course, the set must be pulled into the shop.

The trouble involved in taking the set apart, setting it up again on the bench, pulling it apart, setting it up still another time when it is returned, and finally executing an A to Z convergence, outweighs the inconvenience of working on your knees under adverse conditions.

As an example, consider the case of one 12" color set the shop was called on to service. It was installed

in an exclusive apartment house and the tenant lived on the ninth floor. The freight elevator was at the rear of the building and a sign near the front door advised that "Tradespeople must use freight elevator for pickup and delivery."


The set was turned on. A beautiful bright blue was in evidence with other colors unavailable. The color tube was checked but the picture remained blue. The chassis was pulled out on the floor but a series of resistance checks revealed nothing as to the possible cause of the trouble. Normally, at this point, our policy would have been to pull a black-and-white chassis, but the thought of the work involved in this particular pickup and delivery caused a momentary pause.

The checking was continued and it wasn't long until some "B+" was discovered on the blue gun grid. The .1 μ fd. capacitor in the grid leg, shown in Fig. 1, had changed value. Once out of the circuit, the capacitor measured about 800,000 ohms. It evidently shorted down even further when the set was on. A new capacitor brought back all three colors.

On another complaint, the picture was all green. The appropriate tubes were checked first and when that didn't help, the chassis was pulled out on the floor.

Voltages were checked in the 12BH7 G-Y demodulator and found to be correct except at the plate. Instead of having the usual +37 volts, there were about 200. A pair of 56,000-ohm "B+" dropping resistors in series with the plate (Fig. 2) had shorted down

Fig. 1. Leakage in this .1 μ fd. capacitor permitted "B+" from the plate of the blue output stage to overdrive the CRT's blue gun grid, overwhelming other colors.

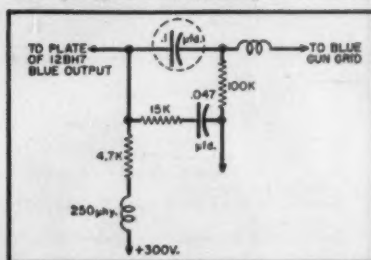

in value. A new pair of resistors restored performance.

A 21" set was reported as having no color. The black-and-white picture was fine but on the colorcasts there wasn't a hint of hue. Checking voltages in this set revealed only one discrepancy. The "B+" was on the grid of the color killer instead of the normal -1 volt. The .01 μ fd. capacitor (Fig. 3) in the grid circuit had a dead short. A routine capacitor replacement licked this problem.

Don't Give Estimates

No technician can fix every set in the home and there are a goodly number of receivers which must be pulled into the shop. While in monochrome servicing past experience can be relied upon in estimating the cost and delivery date, in color such experience is lacking until a few "toughies" like the one to be described have been encountered.

The picture on this particular set had some color tones but they were weak. In addition, the 920-kc. beat (the difference between the intercarrier sound and the color oscillator) was extremely strong. The circuitry from the burst keyer through the video amplifiers to the color CRT was checked for several hours before it was decided that this chassis had to be pulled.

On the bench the technician sweated this one out with an assist from the whole staff. The time spent on this "dog" wasn't even calculated. Only by a tedious process of trial and error was the defect finally uncovered. For lack of anything else to do, it was decided to touch up all the solder joints with an iron. When the color take-off can was reached where it joined a 10,000-ohm resistor, the trouble ceased. A tight rosin joint at the point shown in Fig. 4 had been causing all the trouble.

Another hard one involved a 21" set on which the color picture was perfect when the set was first turned on. Then during the show, color sync would deteriorate intermittently. This showed up as a rainbow wave rolling vertically through the picture. The longer the set remained on, the greater the sync loss. A check of tubes was wasted effort, so the chassis was pulled. A static check-out of all components in the reactance circuit and the 3.58 mc. oscillator stage read good. A tedious substitute-and-wait process was begun. Then the 3.58 mc. crystal was changed.

The symptom now altered. The picture started a continuous sync roll instead of rolling intermittently. With re-alignment of the oscillator, the sync condition cleared up. The old crystal (Fig. 5) was good, however, its natural resonant frequency was slightly off the required oscillation. So, while the color sync signal held the oscillator somewhat in place, it didn't hold firmly enough, causing the instability.

All technicians will have to go through a similar "trial by fire" but the tough ones are the "experience

makers." They may actually cost the shop money but, in the long run, it will be money well spent. To cut down on these inevitable losses, use discretion in naming prices and delivery to customers. Instead of quoting an approximate price and delivery, tell the customer that he will be kept posted on progress. Fortunately, most color TV set owners go along with this approach.

Know Your Convergence

Probably the most-often-heard complaint regarding color TV is the three-gun picture tube. Overcoming the convergence bugaboo is the key to color TV servicing success. It is the one major hardship that sets color service work apart from other troubleshooting and repair jobs. If the A to Z setup is thoroughly mastered, convergence procedures can be handled by a top technician in about half an hour. This same trained man should be able to install a new color CRT, which includes a convergence job, in about an hour.

While such timing should be considered exceptional, it is a good target for the newcomer to shoot for. After some practice though, the newcomer should average about an hour on a convergence. That means the delivery of a color chassis will require normal monochrome time plus about sixty minutes. This is not too bad and most customers will not balk at the charge.

In factory service branches, a color CRT assembly is set up in the shop, thus it is only necessary to pull the chassis instead of the entire set. No doubt, this same technique can be adopted by the independents as soon as the volume of color servicing business warrants. One drawback, as far as the independent is concerned, is that rather than specializing in one brand, all makes and models will be handled, which complicates things.

Ask for Help!

If the technician encounters difficulty in servicing a color set, he should not hesitate to get in touch with the distributor or factory branch and ask for help. All of the manufacturers are anxious to get color "off the ground" and to this end they are spending plenty of money on lectures and literature for the independent technician.

Since the public's acceptance of color television will depend on the service they get on their sets, if the technician needs help—it's available. Here

Fig. 2. Defective "B+" dropping resistors passed too much voltage to the plate of the G-Y demodulator. Its overconduction resulted in a picture that was all green.

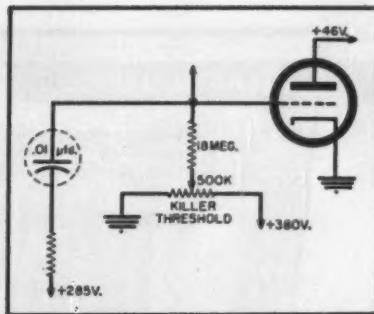
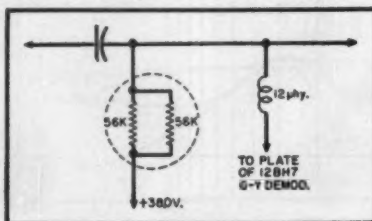


Fig. 3. Routine part replacement licked failure to produce color pictures caused by a constantly activated color killer.

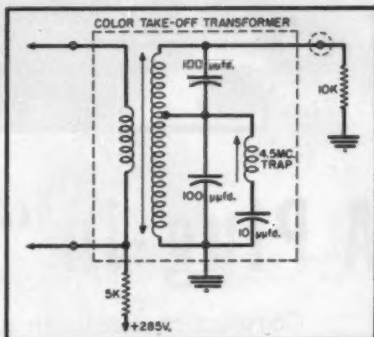


Fig. 4. The symptom, partial color loss, was unfamiliar. The defect responsible, a cold solder joint, was an old story.

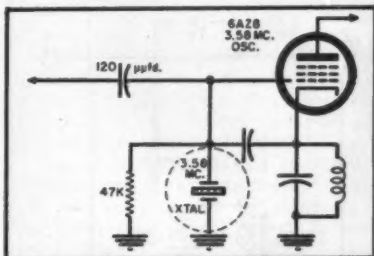


Fig. 5. Poor color sync—a rainbow rolling through the picture—resulted when a control crystal's resonance had shifted.


is a good case to illustrate the point.

One 21" color set was encountered that had no red in the picture. A seasick-looking blue-green picture showed on the screen. Turning up the red grid and screen pot provided no action. It proved to be open and after the pot was changed, the red returned and the picture lost its pallor. About a month later there was a callback on the same set. The "seasick" look had returned. The pot was again open but before installing a new one the manufacturer's distributor was contacted. The counterman knew all about this trouble since he had received a special memo on this from the factory as this had proved to be an "epidemic" condition. He advised increasing the ohmage and wattage on the pot and changing the other two screen pots at the same time. This eliminated the problem.

(Continued on page 152)

By ALLAN M. FERRES

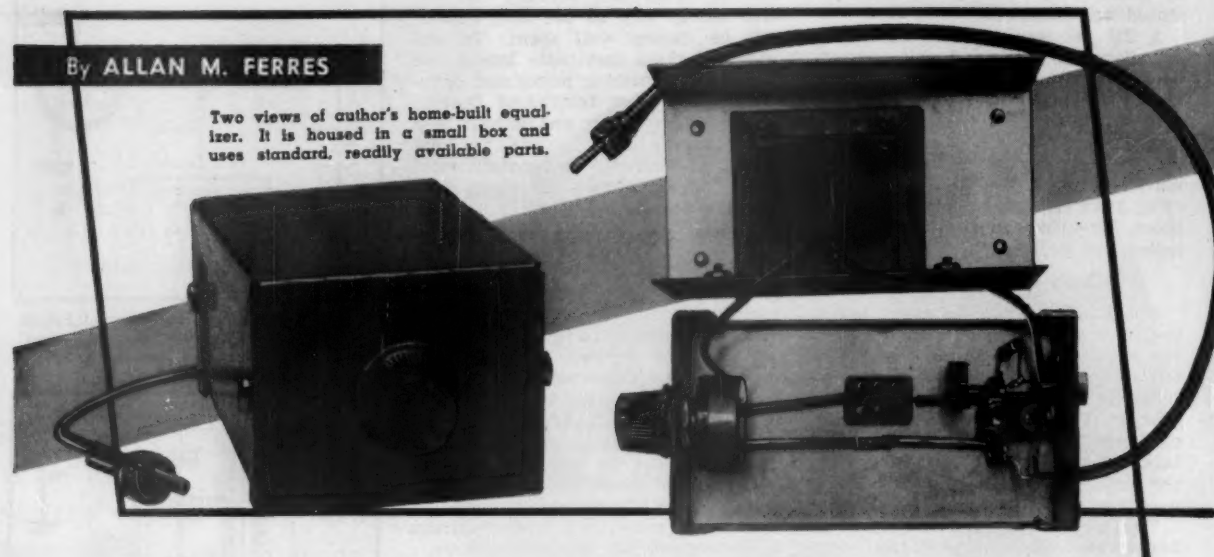Two views of author's home-built equalizer. It is housed in a small box and uses standard, readily available parts.



A Plug-in "Presence" Equalizer ★

Construction details on a simple and compact unit designed to boost mid-frequencies in hi-fi setup.

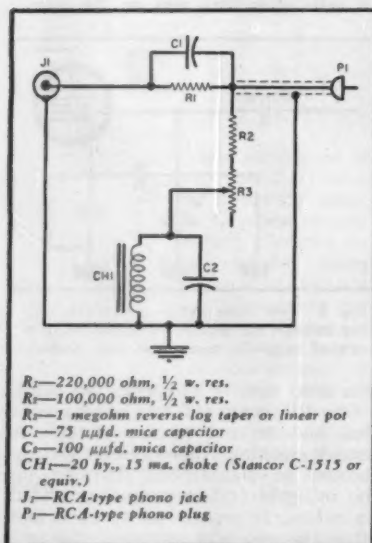


Fig. 1. Schematic of the equalizer unit.


THE mid-range, or "presence," equalizer is an interesting addition to any home high-fidelity installation. It furnishes a boost of up to 6 db at 3000 cycles without affecting the response at the extreme ends of the frequency range. This type of equalization is often used in film and disc recording to emphasize solo voices and instruments. When used on speech reproduction, the articulation factor, or "understandability," is increased without producing the annoyance of excessive sibilance.

In a home reproducing system the presence equalizer will not produce as marked an effect as the bass or treble controls, but it will tend to highlight most solo instruments and for this reason it is a worthwhile attachment.

The presence equalizer described here is a simple device which can be attached to the existing equipment between the equalizing preamp and the power amplifier.

The circuit is simple and uses only a few standard, readily available parts.

Fig. 2. Frequency response curve of equalizer when input resistor of the power amplifier is about 500,000 ohms. See discussion in text.

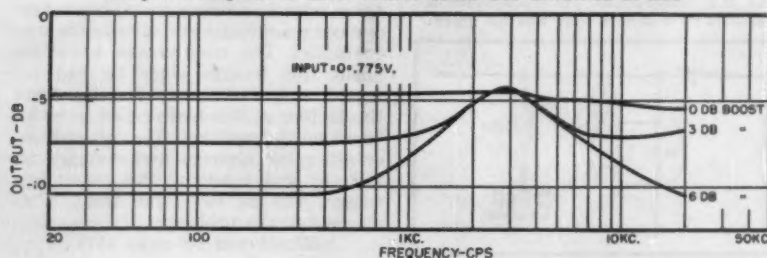

As can be seen in the schematic, Fig. 1, the equalizer is basically a voltage divider, the series leg consisting of R_1 , shunted by C_1 , and the shunt leg, made up of a parallel tuned circuit, CH_1 - C_2 , in series with R_2 and R_3 . As CH_1 - C_2 is resonant at 3000 cycles, the impedance of the shunt leg is highest at this frequency and the loss in the voltage divider is minimum, furnishing the mid-range boost. The amount of the boost is controlled by the total value of R_2 and R_3 in series. The boost is 6 db when R_3 is set at minimum resistance and zero when set at maximum. C_1 is used to compensate for high-frequency losses caused by stray and cable capacities in the divider circuit.

The frequency response curves of Fig. 2 are obtained when the input resistor of the power amplifier is about 500,000 ohms, the usual value. If the input resistor is less than 470,000 ohms, it should be changed to this value. If the resistor is 1.0 megohm, a 1.0 megohm resistor can be connected across the output cable of the equalizer and no wiring change will be necessary in the power amplifier.

The length of the shielded leads to the preamp and the main amplifier should be kept as short as possible to reduce the chance of hum pickup and uncompensated high-frequency loss.

The construction of the presence equalizer can be seen in the photographs. CH_1 is mounted on the bottom section of the case and wired into the circuit with its flexible leads. The pot should be wired so that minimum resistance is obtained when the control shaft is in the full clockwise position. The winding-to-core capacitance of the Stancor C-1515 choke used in this equalizer causes the circuit to resonate (Continued on page 184)

ELECTRONIC AGITATOR

For Color Film Processing

By ARTHUR ROSS, JR.

Details on a compact and simple unit for the darkroom. Standard non-critical parts are employed.

COLOR film processing calls for close attention to details. The three most important factors are: time, temperature, and agitation. Time and temperature are fairly easy to control. Correct agitation is time consuming and is generally taken care of by imprecise methods, i.e., a few shakes of the tank or reel every couple of minutes. Good mechanical agitation is necessary if accurate and consistent results are to be obtained.

The agitation should duplicate the manufacturer's instructions. In the case of *Ektachrome* film, the manufacturer recommends that the film be removed from the solutions and drained for five seconds; once each minute. Other color processes and black-and-white processing require different time cycles. With this flexibility in mind, the agitator described here has been made adjustable for any immersion period from 0-10 minutes and for a 5-30 second drain period. The agitator will operate reliably and continuously and free the processor from the inconvenience of hand agitation.

Construction is simple and inexpensive. The outside case, a 4" x 5" x 6"

steel utility box, and the inside, 4" x 5" x 1/4" plywood chassis, are faced by two 5" x 6" x 1/4" plywood panels. The builder may find it more convenient to construct the entire unit of plywood.

In the illustrated model, small strips of plywood, glued to the edges of the inner chassis, give sufficient thickness to accept 1/4" No. 6 wood screws which hold the outside panels to the chassis. The outside panels are then fastened to the metal box with 1/2" No. 8 wood screws or with sheet metal screws.

All the electronic circuit components are readily available at local ra-

dio parts dealers. The motor is available from W. W. Granger, Inc., 118 S. Oakley Blvd., Chicago 12, Illinois.


The timer consists of a simple a.c.-operated thyatron, which controls the motor through a relay. The circuit has coarse and fine timing controls operated from the front panel.

The timer cycle begins to operate when L_1 and L_2 are connected to the 117 volt a.c. line and the filament of the 2050 tube is energized through transformer T_1 . Rectification occurs in the grid-cathode circuit and a charge of the indicated polarity will


(Continued on page 138)

Over-all view of the home-built agitator. It is clamped to a shelf in darkroom so that controls are accessible at eye level.

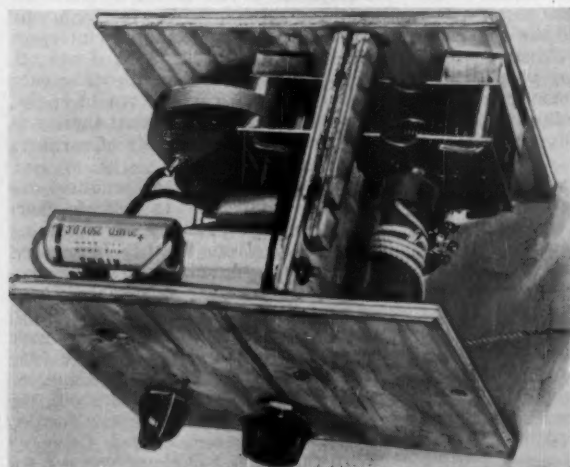Top view of the agitator showing the correct placement of the 8 r.p.m. motor. A more elaborate housing can be employed.



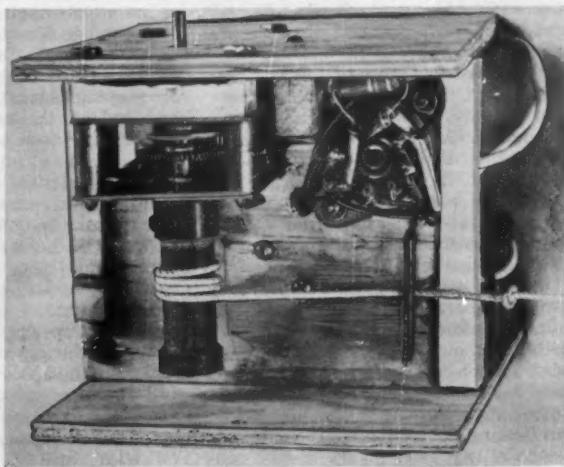Side view of home-built unit showing the operating principle of the string guide and motor drum. Top of unit is to the left.



CHOOSING a loudspeaker system for your home is a highly subjective process. Some manufacturers have tried to reduce it to a science based on response curves, distortion analysis, etc., but they have never been able to eliminate a fundamental fact: *tastes differ*.

Catering to these tastes has been a major part of the author's work for over 15 years, first at the microphone controls of various broadcasting stations and more recently as a seller of high-fidelity equipment for the home.

As a hi-fi salesman, I see all types and must be prepared to suit them. Too many people, it seems to me, are afraid to trust their own taste and are looking for an objective standard to tell them which is the "best" loudspeaker. They are sometimes shocked when I tell them there is no "best"—the best loudspeaker is simply the one they like the best.

What is the "best" symphony? Or, for that matter, which is "best," a symphony, a string quartet, or an opera?

At this point, someone is sure to jump up and say, "But you're not comparing like objects. There may be room for a difference of opinion as to music types, but the best speaker is obviously the one that reproduces the music, whatever its type, most exactly like the original."

So that leads us to still another question: What, exactly, is the "original"? It is the sound heard at a particular point in the room (studio, auditorium, concert hall) in which the original performance took place. Is this what everyone wants to hear? Definitely not! Is it the "best" sound? That is where taste enters and science must bow out.

If you are one of those fortunate enough to be able to attend live symphonic performances regularly, where do you like to sit—in the orchestra? In the balcony? Up close? Far back? On the left hand side of the house or the right?

Wherever you choose to sit, you hear something different from what you hear in any other seat in the house. Orchestra and balcony seats differ widely in sound. So do left and right sides, or front and rear of orchestra. Yet where is the set of scientific standards which can tell you the "best" seat? It's all a matter of personal taste.

Myself, I like to sit in Box E or F of the San Francisco Opera House, where I get the blare of the brass full in my face, plus all the "liveness" of the vastness of the hall—the sounds bouncing back from wall to wall and blending together.

On the other hand, I encounter many people who like to sit downstairs, up close, where they can more easily pick out the individual instruments. Such a seat, on the few occasions I have occupied one, makes the music sound intolerably "dead" to me and lacking in brilliance. It completely spoils my enjoyment. Yet it en-



It all depends on where you want to "sit in the concert hall." Let your own preferences decide which is the best loudspeaker for your listening.

hances others'. This is where the element of personal taste comes in.

Perhaps you never noticed it before, but loudspeakers can "place" you in the auditorium. Irrespective of the record (or broadcast performance), some speakers will put you "down front, up close," others "orchestra, rear," and still others in the balcony, or, yes, my beloved Box E.

This effect is due to a combination of speaker qualities and recording acoustics. Modern orchestral recordings are almost invariably recorded with fairly "live" acoustics. This was not always the case.

Originally, in the early days of acoustic recording, it was necessary to use small, "dead" rooms as studios and to crowd the performing artists as close as possible to the inverse megaphone which applied the sound power of the music directly to the diaphragm which carried the cutting needle. There was no room for the subtleties of varying acoustic characteristics—and, indeed, the recording mechanism would have been totally insensitive to them.


When electrical disc cutting revolutionized the recording process, there was no corresponding change in studio design. Old habits prevailed, and studios, though they grew bigger to accommodate large groups, remained dead in sound.

The Europeans preceded us in discovering the more natural quality of live studio acoustics. In the early thirties they produced some superb (for the times) recordings, while American companies continued in their old ways.

American broadcasting practice originally followed American recording practice as far as studio acoustic design went. But the broadcasters began to experiment much sooner with live acoustics. CBS, early in the thirties, was a pioneer in the development of "live end—dead end studios," in which orchestra and singers were placed at the end of a room treated to give "liveness," while the microphone was placed in the other end, treated for "deadness." This gave a certain blending to the sounds before they reached the microphone.

It was during this period that broadcasters began to experiment with what we at the microphone controls termed "audio perspective"—the *apparent* relationships of singer or orchestra to microphone as interpreted by the loudspeaker. Of course, we had only our control room speakers to interpret through, and I think most, if not all, of us failed to realize the difference that different speakers would make, not to mention the fact that there was not then the great variety of speakers available today!

The broadcaster made practical use of audio perspective to indicate characters in plays approaching or leaving or speaking from another room; and to "place" orchestra and solo instruments in relation to each other. Close-up mike technique gave intimacy; placing performers farther away gave added liveness and a feeling of "big time." With the former technique, we control engineers could make you, the listener, feel the program was for you alone. Remember Morton Downey? With the latter technique, you got the

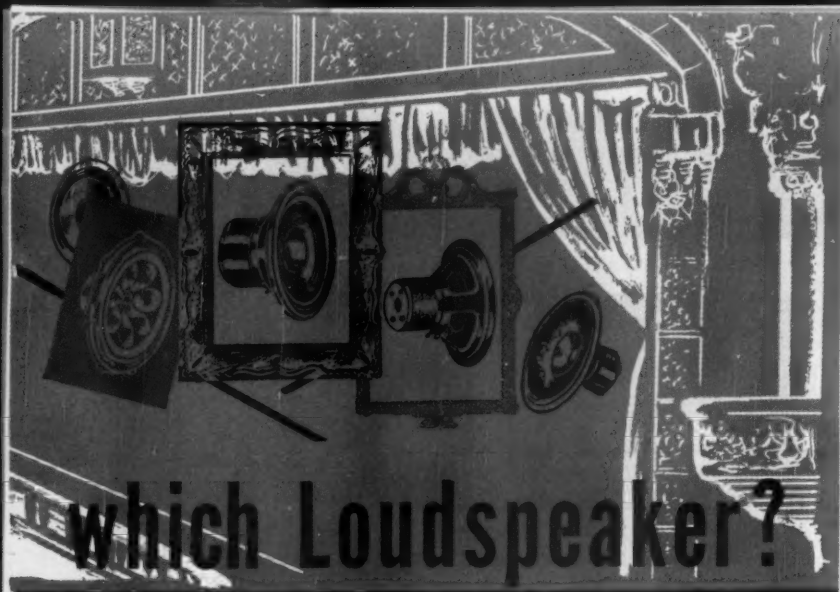

By PHIL BERNHEIM

feeling that you were privileged to sit in the audience with many others, in a vast theater, watching the vaudeville antics of Bob Hope or hearing a Jolson or Cantor.

To bring the same feeling to orchestral recording—to place you in the hall with the symphony, rather than to bring the symphony into your home—modern recording technique utilizes the liveness of studios, theaters, and symphony auditoriums. The liveness comes, of course, from reverberation—sound bouncing around the studio walls before it hits the microphone to re-inforce, some milliseconds later, the sound reaching the microphone directly from the instruments.

The amount of reverberation on the record is fixed. But if, in spite of that, the amount reaching your ears can be controlled and varied, some interesting effects can be secured—effects that might be called “seat placement.” Oddly enough, your loudspeaker does just this.

Reverberation can, and does, take in all frequencies, but at different rates. That is, in a given auditorium there may be more reverberation of low frequencies than of high, or *vice versa*. When there is pronounced reverberation of low frequencies there is “boominess,” noticeable in many halls and auditoriums. When there is pronounced reverberation of high frequencies, there is “liveness,” or even, if carried too far, echo.

Single channel, or “monaural,” hearing tends to enhance, psychologically, the reverberant effects of a room. A microphone placed at a given point in a room, picking up and transmitting sounds through an amplifier and speaker to a listener in another room, will make the sound seem more “live” to the listener than it would were the listener himself, with both ears functioning, at the same point as the microphone.

To make a recording sound “natural,” then, requires very careful microphone placement so as not to exaggerate the reverberation of the recording studio or concert hall.

As a matter of practical concert hall and recording studio design, low-frequency reverberation is held down to prevent unpleasant boominess, but high-frequency reverberation is engineered in—up to a point—to enhance the pleasing “liveness.” Only—how much liveness is pleasing? That is what is arguable. I like a lot; Box E gives it to me. The “down front, up close” boys like comparatively little; the direct sound they get effectively drowns out most of the weaker reverberation.

If we are to control our recorded “seat” in the auditorium, the problem becomes largely one of controlling high-frequency reverberation effects. Actually, “control” with a given speaker is difficult, but different speakers, because of the unavoidably different ways in which they respond to the audio spectrum, seem to put us in different areas of the auditorium.

To be specific, for example, the *Jim Lansing* D-130 and D-131 put you “down close and up front.” It is significant that more musicians and conductors, in my experience, choose *Lansing* speakers than any other. They are used to hearing music while sitting in the midst of the orchestra, where reverberation is practically non-existent. They say that these speakers enable them to pick out the individual instruments better than any other.

A few months ago I attended a symphony concert and had to sit in the orchestra section, about mid-house and to the right. Next morning I set out to find the speaker in our rather extensive stock which most nearly reproduced the character of the sound I had heard the night before. It was *Electro-Voice's* SP-15.

My own favorite speaker system—the nearest thing to Box E I've found yet—is the combination of *Altec's* 802-C driver and 811B horn with any good woofer such as *Altec's* 803-A or *Stephens' 103-LX*.

Some other speakers and speaker systems are not so specific in their “seating” because of differing balances between the high and low ends of the audio spectrum. The *Jensen H-520* is very near to a good box seat, but the bass end is a little heavy for what one would hear up there.

For another “middle of the ground floor” seat, try the *University Master* 3-way system—but, again, for ideal balance something should be done to tame down the woofer in relation to the other two units.

One of the standing jokes in the industry is about the two hi-fi addicts who go to a live symphony concert. As they come out, one turns to the other and says, “But where was the bass?”

This is inspired by the current trend toward seeking heavier and heavier bass (having already been through the phase of higher and shriller highs) without regard to the naturalness of the balance.

A good case can be made for not attempting natural balance at all in a hi-fi system. The argument runs that, since completely natural reproduction is impossible anyway, why not just go hog-wild on any kind of electronic exaggeration—either in recording or in reproduction—that is pleasing to the listener.

That is a very valid argument, as far as I am concerned, as long as you recognize what you are doing and do not confuse it with naturalness—and as long as you do not insist that yours is the “best” way of doing it. Other people may certainly have different tastes.

If, on the other hand, you are seeking to come as close as possible to concert hall listening—or, at least, its emotional equivalent—then here is a new approach to the search for an ideal speaker system: where do you like to sit, and which speaker puts you there?

Viewed in this light, the choice of a speaker is indeed subjective rather than scientific, and there is no reason at all why the hi-fi fan, whether experienced or neophyte, should not trust his own taste, without seeking the false security of a scientific standard of what is “best.”


I have not mentioned speaker enclosures up to now, since enclosures affect only the bass end—or, at least, good enclosures do; bad ones may cause mid-range cancellation, as some of the bass-reinforcing ones do. The “placement effect” of a speaker, on the other hand, comes principally from its high and middle response, and the balance between them.

Since the object of listening to music is to enjoy it, choose the speaker system that gives you the most enjoyment, and let those who disagree go buy their own!

A Portable Thyatron Tester

By
W. PHILBROOK

Fig. 1. The Aleetric thyatron tester.

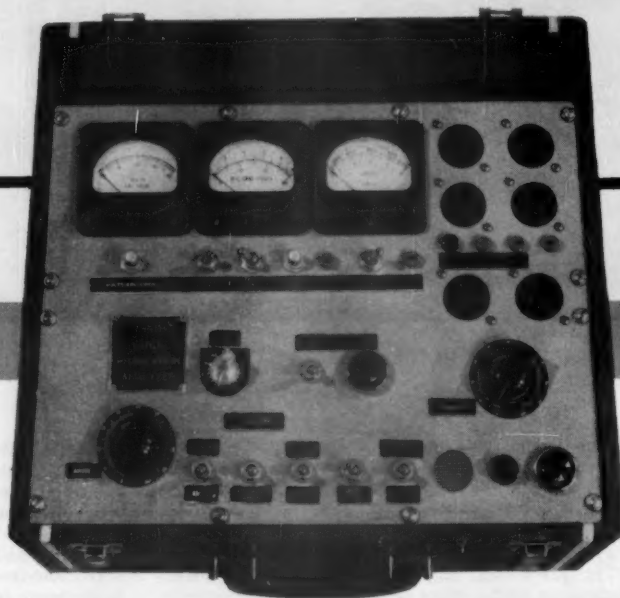

A commercially available instrument uses several unique circuits to test specialized tube types.

THERE are receiving tube checkers of almost every conceivable variety on the market but there has been no portable, easily usable tester for thyatron tubes. Why this condition has existed is difficult to say because, with the volume of industrial electronic equipment in current use, there should be an excellent sales potential for such a device. Now a tester has been developed which not only permits the rapid and accurate checking of a thyatron tube's characteristics, but does so with a number of unique circuits. Before we examine these circuits, it may be desirable to review the basic operation of a thyatron tube.

Thyatrions are gas-filled tubes in which the flow of current is either at zero or at the saturation value. The grid voltage, usually negative, keeps them cut off until such time as it is desired to trigger them. At that time, the grid voltage is made relatively positive and electrons are thus permitted to flow from the cathode to the plate.

Once this movement starts, even in a minute degree, the molecules of gas enclosed in the tube tend to become positively ionized. This condition of positive ionization neutralizes the holding or controlling voltage on the grid. This action completely opens the dam, so to speak, to the electrons being emitted by the cathode and permits current to surge freely through the tube to the plate. Once this flow has started, the grid loses all control over the rate of flow and—as long as the plate voltage is kept above a cer-

tain critical minimum—all electrons leaving the cathode travel to the plate.

This, roughly, is how a thyatron tube operates. And to determine the operating condition of such a tube obviously requires a special type of tester. Let us therefore note the various thyatron features which are important and see how the tester shown in Fig. 1, made by the *Aleetric Mfg. Co.* of Kenosha, Wis., accomplishes its testing function.

One of the first things to observe is that most thyatrions operate with alternating voltage on the plate (or anode). This is done so that the grid may resume control of the tube after it has been fired or triggered. There is no point in having a tube in the circuit over which no control at all is possible, and the simplest way to achieve this control is to apply a.c. to the plate. When the plate voltage goes negative, conduction ceases, the ionized gas de-ionizes, and the control grid is able to prevent the flow of electrons from cathode to plate. The tube is now ready for the next triggering pulse.

Hence, if you examine the schematic diagram of this tester, Fig. 2, you will see that a.c. voltage is brought to the plate from one of two points: either the variable-voltage transformer, T_1 , or the step-up transformer, T_2 . Voltages from 0 to 200 volts are obtainable from T_1 , while 0 to 3000 volts (peak) can be obtained from the secondary of T_2 . The purpose of the low a.c. voltage is to check thyatrions at their rated currents—in this case, either 1, 2.5, or 6 amperes. By using a low voltage and

proportionately low-valued resistors in the plate circuit, the wattage requirement and, with it, the heat dissipation can be kept within reasonable bounds. When checking 2.5 and 6 ampere tubes, even under these conditions, it is still necessary to place the plate load resistors in a separate box. If a higher plate voltage were used, the load resistances would be correspondingly higher and the wattage requirements would raise the cost of these units excessively. Hence, low plate voltages are used for certain tests where maximum rated anode currents are desired.

On the other hand, when a thyatron tube is being checked for its grid-plate characteristics, we can use a high plate voltage and employ high-valued load resistances in the plate circuit to keep the current down. In this test, it is simply a question of establishing "trigger points" or critical grid voltages, not to determine what the peak plate current is. More on this test presently.

The path of the a.c. voltage from T_1 to the plate of the thyatron tube to be checked can be readily followed from Fig. 2. The start can be made at T_1 . From the center tap, point B , the line leads to switch S_2 , which for the purpose of this test is turned to the a.c. position. From S_2 , the path goes to point C , then through S_{1-1} , which is now closed, to point D , then E , and finally through R_1 to the plate of the thyatron.

The other side of the circuit is completed from point A through S_{1-2} , which

is now closed, to F and from here to the center tap of the filament transformer, T_5 .

Arc-Drop Test

Now, as a measure of tube reliability, a direct measurement is not made of the tube's peak plate current. Rather we measure the voltage drop across the tube when the latter is conducting at full current. This voltage is known as the *arc drop* and its value is sought because an increase in the arc-drop voltage is the most outstanding indication of the end of life of a thyatron tube. However, a single arc-drop reading in itself will not indicate the life factor; rather what is needed is a series of readings over a period of time to anticipate the end. See Fig. 3. The technique could, in a way, be compared to the predicting of weather conditions by taking comparative readings on a barometer.

It is suggested that a reading be taken after about every 400 hours of operation. As the arc-drop value begins to rise, a shorter interval should be observed—say every 200 hours as the tube approaches the end of its useful life.

To be most effective, the arc-drop reading permits the end of life to be predicted so that the tube can be removed from operation before costly work stoppage occurs. A reasonable amount of arc-drop may well establish the limits at which such tubes should be removed to prevent emergency shut-downs.

Once a tube is placed in operation, its arc-drop voltage will vary throughout its life. Typical variations are shown in Fig. 3. With tube "C" the rate of increase of the arc drop accelerates, but the curve is easily recognized. As a result, the tube can be replaced before this reading reaches its published limit. The steady linear rise with tube "B" is also easily recognized. As happens with some tubes, the limit is reached early with tube "A" but this condition is only temporary. The arc-drop voltage reduces below the limit again. However, the upward rise is soon resumed, so the tube should be changed the first time the limit is reached.

When measuring the arc-drop voltage, simply placing an a.c. voltmeter across the tube would produce an erroneous indication. This is because on one half-cycle, when the tube is conducting, we would be measuring the true arc-drop value; however, on the other half-cycle, when the tube is non-conducting, the meter would be subject to the full applied a.c. voltage. The average of these two readings would be much higher than the true arc-drop value.

In the *Alectric* tester, this difficulty is overcome by inserting the current coil of a wattmeter in series with the plate of the tube to be checked, while the voltage coil of the meter is placed across the tube, from plate to cathode. Since tube current flows only during one half-cycle, the wattmeter will be

affected only during this period. During the subsequent negative half-cycle, no plate current flows, the current coil is inactive, and the meter is not actuated. Furthermore, the plate circuit resistance is so chosen that only 1 ampere flows through the current coil. This permits the meter scale to be calibrated directly in volts representing the arc-drop voltage. Additional switches (S_2 and S_1) and load resistors (R_{17} and R_{18}) permit tubes with plate currents up to 6 amperes to be checked. (Although 6 amperes is the maximum current available, tubes through the 16-ampere rating are tested at the 6-ampere level.)

Critical Anode Voltage

Another characteristic of a thyatron is its critical anode starting voltage. This test is made at a specified control-grid voltage, usually on the order of 4 volts positive on the grid. The anode voltage, which is d.c. now, is slowly increased from zero until the firing point of the tube is reached. This value can be compared to that given by the manufacturer. Most of the time, the tube-data sheet will list the anode starting voltage for an average tube of a given type and also for the tube within the type with the highest starting voltage.

The d.c. voltage required for this test is obtained from selenium rectifier SR_1 , resistor R_1 , and filter capacitor C_1 . For the test, S_2 is placed in the d.c. position and the d.c. voltage developed across C_1 is fed, via S_{1-4} , to the anode of the thyatron tube to be tested. (S_{1-4} is closed for this test.) The voltmeter is placed in the position indicated by the dotted lines from the

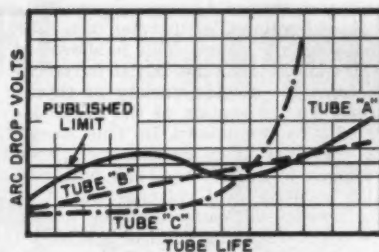


Fig. 3. The arc-drop voltage of a thyatron increases generally with the age of the tube, but may vary during life. It is an indication of tube condition.


anode of the tube, through R_{17} and R_{18} . Readings are taken on the low 100-volt scale, since the anode starting voltage seldom exceeds 50 or 60 volts when the control grid is 4 volts positive.

The necessary positive grid voltage for the thyatron is obtained from the network consisting of T_1 , the two selenium rectifiers connected across T_1 , R_{28} , C_6 , R_{25} and R_{24} . The control grid is directly connected to the center tap of R_{21} . The center arm of R_{28} goes to the filament of the thyatron via a center tap on filament transformer T_5 . When the movable arm of R_{28} is exactly at its center position, there will be no difference of potential between the grid and filament. Turning the arm of R_{28} in one direction produces a negative grid potential; rotating the arm in the opposite direction produces a positive grid voltage. This arrangement is simple and quite effective.

Critical Grid Voltage

To understand the purpose of the

Fig. 2. Complete schematic for the *Alectric* specialized thyatron tester.

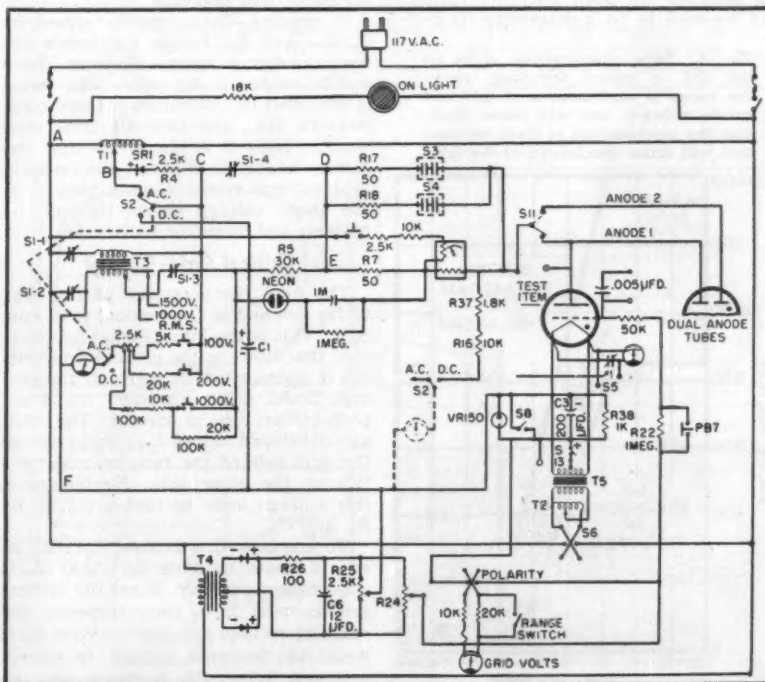

next test, that of determining the critical grid voltage, let us refer to a tube characteristic chart. This is shown in Fig. 4 for a C3J tube, but it is typical in form for a wide variety of thyratrons. In the section of the graph labeled "No Breakdown In This Area," no combination of certain a.c. anode voltages on the left-hand side with certain negative grid voltages shown at the bottom will cause the tube to fire. To reach the firing point of a tube, we must move into the shaded area. Some tubes may have to be driven deeper into this area (meaning either higher plate voltages or less negative grid voltages) before they are triggered, but they should fire before they reach the extreme right-hand edge of the shaded section. If this does not occur, some defect or variation from normal is indicated and the tube should be replaced.

Beyond the shaded area and to the right of it, the control grid is generally so positive that almost any positive anode voltage will trigger the tube. Operation in this area is not sought because control of the tube is either difficult, variable, or impossible.

To test a thyatron tube for its critical grid voltage, high-valued a.c. anode voltages are required. These are obtained from the secondary of transformer T_s , where voltages having r.m.s. values to 1500 volts are available. In carrying out this test, S_{1-2} and S_{1-3} are closed, while S_{1-4} and S_{1-5} are open. Switch S_2 is in the a.c. position. The voltage developed across the secondary winding of T_s reaches the plate of the test thyatron via R_p and R_f . R_p is purposely made high in value so that the anode current will be kept below 40 ma. This is done because there is no desire to check the ability of the tube to produce its peak current; rather, all we wish to do is determine its crit-

ical grid voltage at a certain anode voltage. By keeping the current low, it is possible to use a low-wattage, inexpensive resistor for R_p . We obtain the same value for the critical grid voltage whether a large or a small current flows after the tube has been triggered.

Now to the test itself. It could be carried out by fixing the anode voltage at some value and then slowly reducing the negative grid voltage—making it more positive—until the tube fires. This would be done by slowly rotating R_g until the neon light in the plate circuit flickered on.

However, the same characteristic can be determined automatically because of the presence of C_g and R_m . Initially, R_m is set until it is 4 volts positive with respect to the filament. The a.c. anode voltage is then slowly increased until the tube fires. When this happens, the surge of current through the circuit charges C_g , counteracting the initial +4 volts on the grid. During the next positive half-cycle of a.c. anode voltage, the tube firing point is governed by the combined voltage from R_m and C_g . This combination, after a few cycles, attains an equilibrium level which is the critical grid voltage for that value of applied anode voltage.

If we now change the anode voltage, by adjusting T_s , then the total grid-to-filament voltage will re-establish itself at another equilibrium value which will represent the critical grid voltage for that anode voltage. For example, if the anode voltage is raised, the voltage across C_g will increase, effectively making the grid-to-filament potential more negative than it was before. Conversely, if the anode voltage is lowered, the average voltage developed across C_g will decrease.

In essence, the network formed by C_g , R_m , and R_g swings the tube's operating point a minute distance above and below the firing point. The range is governed by the values of these components (i.e., the over-all time constant). Here it is chosen so that the meter needle recording the critical grid voltage remains quite steady as the anode voltage passes through its positive and negative half-cycles.

Critical Grid Current

The final characteristic of the tube to be checked is the critical grid current. This is the infinitesimal grid current that flows as the critical grid voltage is approached. It starts at the grid and flows down through R_m when push-button PB_1 is opened. The voltage developed across R_m is negative on the grid side of the resistor and positive on the other side. Furthermore, this voltage adds to that provided by R_g and C_g .

To see how this critical current itself is measured, note first that R_m is a 1-megohm resistor. Since the critical grid current is in microamperes, the value of voltage developed across R_m is equal to the grid current in microamperes. When PB_1 is closed, and the

system is set up so that the critical grid voltage is indicated automatically, then the value of the total grid voltage is revealed by the grid voltmeter. This meter is connected between the bottom of R_m (and hence is not affected by any voltage that may develop across R_g) and the center tap of the filament transformer. If, now, PB_1 is opened, the critical grid current will flow through R_m and develop several volts here. This will alter the total grid-to-filament potential and drive the grid more negative. To bring the over-all voltage back to the critical grid value point, the voltage across C_g will decrease by an amount equal to that brought into the circuit by R_m .

This change in C_g voltage will be reflected in the grid voltmeter reading since the latter, remember, measures both C_g voltage and that developed by R_m . Thus, the change in reading on the grid voltmeter when PB_1 is depressed represents the critical grid current in microamperes.


This covers the operation of the tester in general and the tests it performs. Some odds and ends still remain, such as the VR-150 which is placed in parallel with C_g . This tube serves to protect C_g when switch S_1 is first opened and C_g is being charged initially. Voltage surges of a thousand volts or more frequently occur at this time. These would destroy C_g unless the latter had a sufficiently high breakdown voltage value. Since C_g possesses a high capacitance, using a unit with a high surge rating would be extremely costly. The difficulty is solved much more economically by having the VR-150 tube as protection.

In the anode voltmeter circuit at the left, four ranges are obtained using only three push-buttons. With all buttons open, the voltmeter is on its 2000-volt range. For the 1000-volt range, the button so marked is depressed. The same is true for the 100- and 200-volt ranges; that is, the desired range is brought in by depressing the associated button. The circuit is so set up that, when either the 1000- or 2000-volt ranges are in use, depressing the 100- or 200-volt buttons accidentally will have no effect on the meter.

This tester will also check phanotron tubes. These are tubes which are essentially thyratrons without a control grid. Hence, the tests are considerably simplified for them. Tests usually include arc-drop voltage, anode starting voltage, and an interelement short-circuit check.

The prime purpose of any tube tester or analyzer is to permit a decision to be made on the condition of the tube. It is not a practical matter to construct a tester like the conventional radio-tube tester where a meter reads "good" or "bad." In a thyatron, there are many factors other than the tube's ability to conduct a given quantity of current that determine its acceptance. That is why all of the foregoing tests are provided for and all should be performed if a true picture of condition is to be achieved. —50—

Fig. 4. Tube characteristic chart for the C3J, a typical thyatron, shows the range of combinations of grid and anode voltages that will cause firing, also the combinations of these voltages that will cause breakdown of the tube.

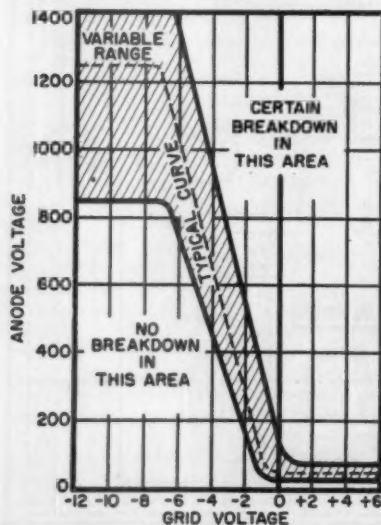


Portable 90-Degree Test CRT

By
JOHN T. JANS
Senior Applications Engineer
Sylvania Electric Products Inc.

Rectangular CRT test unit matches 90-degree sets to permit work on width and linearity problems.

Fig. 1. Where more convenient, the 8XP4 CRT used in the complete substitute test unit can be slid out of its box for use with the yoke assembly of the receiver.

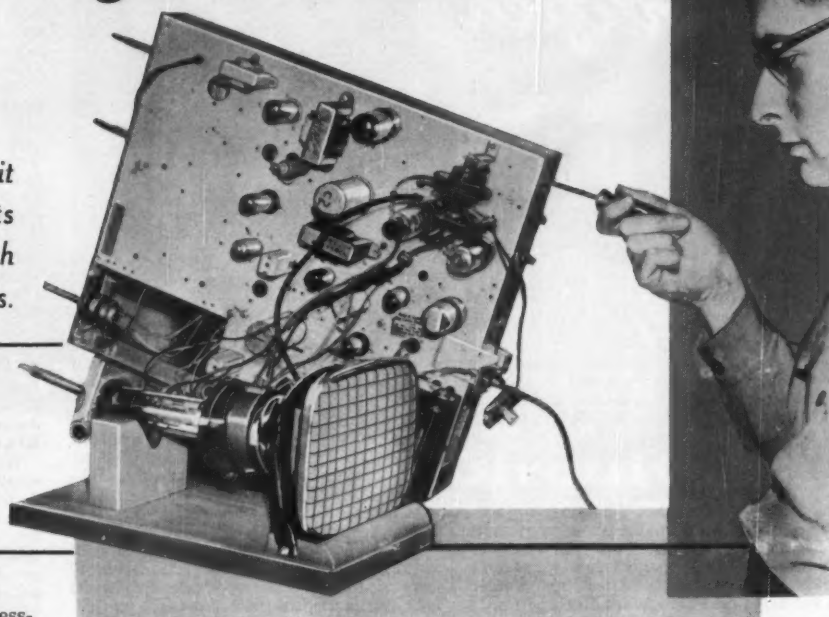

IN THE wake of last year's successful introduction of the 5AXP4 substitution CRT, the Sylvania 8XP4 has recently made its appearance as a companion tube to provide conveniences, with some types of TV receivers, that the earlier tube does not. As was the case with its predecessor, it is a boon in situations where the service technician would otherwise be faced with such possibilities as dismantling an entire receiver or taking that receiver, cabinet and all, into the shop; especially in those cases where the picture tube is cabinet-mounted, separate from the chassis.

With the 8XP4 the service technician can provide a universal substitute for the picture-tube assembly to operate under the most stringent conditions. The 8XP4 is a 90-degree, rectangular, self-focus, non-ion-trap tube of small, handy 8-in. diagonal size. Therefore, a 90-degree receiver with narrow scan would show up narrow on the 8XP4. It would not overscan, as might be done if the tube were designed for use in 55- or 70-degree deflection circuits.

With this tube and a 90-degree yoke such as or similar to the Merit MDF 91, the service technician can build a substitute unit for the picture-tube assembly which will prove useful on almost every make TV receiver. Most 90-degree receivers have yokes with about the same impedance (12 millihenrys and 30 ohms in the horizontal winding, and 40 millihenrys and 50 ohms in the vertical) so this yoke will match satisfactorily nearly all makes of receivers using 90-degree picture tubes. Note the absence of a balancing capacitor in the horizontal windings of the yoke, as shown in Fig. 2. With the yoke in question, this should

introduce no distortion of the picture or raster.


A large number of 70-degree receivers and many 55-degree receivers will also match this same yoke. However, on the latter types, the scan power supplied to the yoke will be low enough so the check tube will not scan fully. All that need be done is outline the limits of a picture from a 70-degree and a 55-degree receiver in good

operating condition on the face of the 8XP4 tube for use as a reference. This can be done with ordinary marking crayon. Then if a receiver using a 55-degree tube scans a picture large enough to fill the 55-degree outline, the receiver is scanning correctly.

Many receivers require a high-voltage filter capacitor to scan correctly. This capacitor is often supplied by the

(Continued on page 142)

Fig. 2. Dimensions, construction, and mounting details for the housing of the 8XP4 are shown immediately below. Alligator clips connect the matching yoke, discussed in text, to the receiver. Completed unit is shown at lower right.

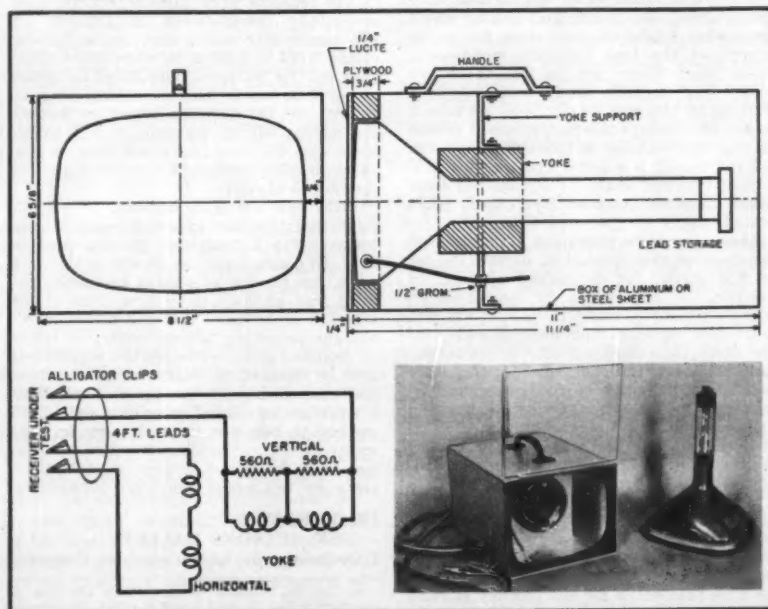

Certified RECORD REVIEW

By BERT WHYTE

WITH all the talk lately of stereophonic tape, one could rightfully assume that stereophonic sound *via* disc is a pretty dead issue. Emory Cook, pioneer in the stereo disc field has been virtually unheard from in this department for some time, and the general consensus seems to be that stereo on disc is impractical.

Well, friends, this may be how things appear on the surface but I have recently discovered that stereo on disc is very, very much alive! Yessir, there are more than a few engineers who are convinced that stereo on a disc is not only practical but that it offers advantages over tape. While I still personally feel that tape is the ideal stereo medium, the advocates have a few points on which they score heavily. One is ease of handling, to be sure, until someone comes up with a good inexpensive workable tape cartridge or magazine load affair, tape is more cumbersome. Another point is ease of duplication . . . the stereo discs can be pressed the same as any other discs. A very potent factor is price . . . the champions of the disc say that stereo discs can be sold as cheaply as present LP's. I have no doubt that all these problems with tape will or are being solved, but it will take time and that's what some people are counting on to exploit the discs.

Now lest someone say . . . "Bert must be goofy, cause there aren't any stereo discs", let me give you the word! It is true that the *double-track Cook* stereo disc is gradually disappearing, but I am not talking about those when I refer to stereo discs, but to the advent of the long heralded *monogroove* stereo disc! There are no less than four (count 'em) separate groups now feverishly working on this type of disc, who are known to me, and perhaps there are others. I cannot divulge their identity at this time, but I can tell you that it is a better than fair bet that at least two will be able to demonstrate these stereo discs at the next New York Hi-Fi Show!

Most seem to be taking the same technical approach or variations of it, namely the use of FM carrier for the second channel. In practice, the discs would be compatible on today's regular 1 mil pickups . . . if you don't have the extra equipment necessary for the stereo, the record will play in the normal fashion. The special equipment for the stereo playback would not be too extensive . . . naturally as with tape, one must have an extra amplifier and speaker for the second channel. Beyond that there is the pickup which is likely to be a pretty complex affair, and the FM carrier demodulator.

As far as I can learn the FM carrier may operate as high as 35 or 40 thousand cycles and the pickup requirements will be very demanding of extremely high lateral compliance and the stylus diameter will have to be no more than half a mil and possibly as small as three tenths of a mil in order to trace

these frequencies! As any knowledgeable audiophile is aware, there are only about two, possibly three, present day cartridges which meet the requirements of compliance and extended frequency response and only one pickup which is commercially available with a half-mil stylus. However it is generally felt that when confronted with this problem, the makers of the top quality cartridges will be able to meet the stringent specifications.

The demodulator is more or less straight electronics and presents no particular problems. As to the engraving of these frequencies on a disc in the first place, there are reportedly at least two cutters capable of response beyond 40,000 cycles. Admittedly, the fabrication of the pickup and the styli and the pressing of the record as well will be the big hurdle and it goes without saying that these discs will have to be played on a turntable with special arm, at least until someone comes up with a super-charger capable of tracking at very low stylus forces.

The stereo disc will not come easily . . . indeed some factor may turn up as it has in the past to torpedo the whole idea. Many years ago the great English record combine EMI patented a method of simultaneous "hill and dale" (vertical) and lateral recording, and *Western Electric* in this country fooled around with the same thing, but nothing has ever come of it. Much more recently it was reported that *London Records* had successfully demonstrated, in London, an FM carrier type stereo disc, but so far the official word is mum as to when and if these discs will be marketed. One thing is certain . . . if these stereo discs ever reach commercial fruition, the economic impact on the record market will be fantastic. It will, in essence, give disc recording a new lease on life, although oddly enough, I feel that tape will continue to expand.

Right now I'm from Missouri. . . I still think that tape has advantages over disc as far as stereo is concerned that are hard to deny. Of course I may be all wet on this next point, but in view of present knowledge the thing that intrigues me is how, even at the very low stylus force that will be employed, will the incredibly delicate tracery of 35 or 40 thousand cycles withstand the friction and wear of repeated playings without vanishing and thus destroy the second channel? This is a fascinating subject to be sure and I'll do my best to keep you up to date on developments. In the meanwhile, enough of my yak, and on to the new recordings of which there are many this month which are outstanding.

GLAZUNOV THE SEASONS BALLET L'Orchestre de la Societe des Concerts

The opinions expressed in this column are those of the reviewer and do not necessarily reflect the views or opinions of the editors or the publishers of this magazine.

du Conservatoire de Paris conducted by Albert Wolff. London LL1504. RIAA curve. Price \$3.98.

The only other recording of this charming work is the Desormiere reading on a *Capitol* disc, and this new *London* makes for an interesting comparison. Wolff does not espouse as lyrical approach to the score as does Desormiere, choosing instead to emphasize the rhythmic aspects. If he has not the delicacy some people might prefer, this is not a cardinal sin and he brings a great deal more fire and spirit to the work especially in the rousing and familiar finale, "Autumn". As usual with this conductor, *London* affords him magnificent sound. With the smooth, yet incisive strings, the mellow French woodwind . . . the splendid orchestral balance and an appropriately spacious acoustic frame, this is clearly superior to the earlier *Capitol* disc. Try this as a breather from the usual ballet repertoire.

BEETHOVEN SYMPHONY #6 ("PASTORALE") Berlin Philharmonic Orchestra conducted by Andre Cluytens. Angel 35350. RIAA curve. Price \$4.98.

What special qualities can this 19th "Pastorale" offer, over all the competing versions? A fair question certainly in these days of seemingly endless duplication. One cannot say this is a definitive version . . . yet it has qualities which will endear it to a great many people. Cluytens has not previously been noted for his affinity with Beethoven, but as heard here, he gives considerable evidence that he would not be over his depth with some of the other Beethoven symphonies. Cluytens essays tempi which are a mite on the slow side, but he doesn't drag his feet. His approach is essentially lyrical, but he does not subvert the rhythmic qualities in maintaining this mood. His view of the famous "Storm" is robust and vigorous, and we should not decry either Cluytens or indeed any other conductor if he cannot equal the intensity of the tempest stirred up by Toscanini.

Over-all, a pleasing performance, but to me the real value of this disc is the truly miraculous precision and polish of the Berlin Philharmonic. With the smoothly sumptuous sound afforded by *Angel*, the strings, especially first violins and cello, are an ear-filling delight. Woodwind and brass are on the same elevated plane and their balance in ensemble is just plain marvelous. The evidence of one's ears would seem to bear out the critical acclaim afforded the Berlin orchestra on their recent American tour. Summing up . . . one of the most satisfactory "6th's" in the catalogue, certainly one of the best sounding and worth owning if for no other reason than the virtuosity of the performers.

KACHATURIAN CONCERTO FOR PIANO AND ORCHESTRA

Leonard Pennario, pianist, with Concert Arts Symphony Orchestra conducted by Felix Slatkin. Capitol P8349. RIAA curve. Price \$3.98.

The sixth version of this work to appear, it has negative and positive values about equally distributed. Pennario easily copes with the technical demands of the work, and while his performance is competent, it lacks the sparkle and zip of the late William Kapell's reading . . . something which is needed to sustain interest in this rather overblown work. Slatkin conducts a good and knowing accompaniment to Pennario and the orchestra plays with considerable skill. As far as sound is concerned this is the prime virtue of this disc, being easily the most "hi-fi" of all the versions. Piano is sharp and clean, (Continued on page 162)

Realistic

High Fidelity

Audio Output Tubes

and Circuits

H. A. HARTLEY
Audio Consultant

IN PART 9 of this series I said that, ideally, the power required to drive horn-loaded, acoustic phase-inverter, and infinite baffle or closed box speakers should be 3, 6, and 11 watts respectively, but that practical considerations required these output powers to be raised to 7, 15, and 25 watts, if an adequate margin of safety was desired. Tubes age, lose their properties, or even may be grossly mismatched. The characteristics given by the makers assume a pure resistive load, and in any case are "average" values. It is not a practical proposition to design absolutely for ideal conditions when the components used are not perfect.

Before discussing the sorts of tubes that will give undistorted outputs of from 7 to 25 watts, I should like to make a "heretical" observation. We all know that negative feedback greatly improves an amplifier, both as to damping factor and distortion, and so feedback, used wisely or otherwise, is written into the constitution. Associated with this is usually a specification of fantastically low intermodulation distortion for the output the tubes are supposed to give, according to the tube manuals. These claims may be quite right, and I will agree that they can be proved right, but it calls for pretty good engineering, and tubes right on the top of their form. Now comes my heresy, for speaking as an engineer I ask "is this pretty good engineering absolutely necessary?" The reply can be that as a matter of satisfaction to the engineer it is necessary, and if a manufacturer has to produce the maximum results at the minimum cost it is also necessary and that is why he hires engineers to do the design work. But quite a lot of people like to build their own amplifiers, and I should like to emphasize that the semi-technical amateur is

really up against it when he tries to get the maximum possible from a given output stage.

It is much easier to design roughly for twice or three times the output you would normally require, use just a little feedback (to avoid any possibility of low-frequency instability) and keep the volume down, for your roughly designed amplifier will sound pretty bad if going all out. Put it this

EDITOR'S NOTE: This article concludes the present series "Realistic High Fidelity" by H. A. Hartley. From the many letters we have received on this series it is evident that our readers found it informative and interesting to learn of the opinions of one noted audio authority. We thank Mr. Hartley for his wholehearted cooperation during the preparation of these articles and for his many long and interesting letters of explanation concerning some of the points made. We hope that we will be publishing future articles by Mr. Hartley dealing with subjects in which our readers are most interested.

way—design for a 50-watt amplifier and call it a 25 and don't try and get more from it. Under these conditions it would have to be a fairly bad amplifier to sound other than good at ordinary room level.

Later on in this part I shall give the circuit of a 20-watt output stage of an amplifier I made and sold for some years. I don't make it any more, for I have enough to do with speakers alone, but that amplifier was produced in 1948 in response to an insistent demand for something better than usual. It was most carefully designed, and its 20 watts fed into one of my ordinary 215 speakers were enough to fill lecture theaters with an audience of 200. But . . . it was designed for home

use, and I suppose in the average home its peak output was on the order of 5 watts. Then it sounded very good indeed, and I am told even today that it sounds cleaner than many highly respected amplifiers incorporating all the latest developments. There is nothing mystically wonderful in the design; it is just working well within its possible maximum output, even when the output tubes are getting tired after many years' use.

This, however, is by the way, and no fit subject for engineers and would-be engineers. Let us seriously consider the selection of tubes for output powers of 7 to 25 watts. Seven watts can be obtained from a single tube, but the advantages of push-pull operation are so manifold that it is invariably used in high-fidelity amplifiers.

Selection of Tubes

The first decision is, therefore, that two tubes will be used in class A or AB push-pull, but there is no general agreement as to which tubes should be used, or how they should be used. It is an easy matter to skim through the data sheets in the tube manuals and note that some particular pair of tubes gives x watts at $y\%$ distortion, but to depend on this is rather like visiting a foreign country with no knowledge of the language beyond what you will find in a phrase-book. That will enable you to get around in a limited sort of way, but you won't get the utmost pleasure from your vacation abroad. So, if you want the best amplifier, you must learn a little of the language of electronics. Only then can you judge critically the various

circuits in the textbooks and magazines and the amplifiers shown to you in the dealer's store.

Some of what follows has formed the basis of many articles and textbooks over the past 30 years. I am sorry to have to put it in, for diagrams of tube characteristics have been repeated *ad nauseum*, but you must know how to get the right answer. I have cut out all the padding and got down to the skeleton; but the skeleton may have more bones than you thought. I think the comparative tables will enable you to determine the best tubes for your particular requirements without having to refer to other texts, and as some tubes are better than others, you should know wherein they are better.

The tubes considered are of two main types, those with plate plus screen dissipation of 12 or 25 watts. Note the distinction between plate dissipation and output power; dissipation indicates the power consumed (d.c.) within the tube itself to produce audio power (a.c.) to drive the speaker. The ratio between the audio output power and the total d.c. input power, including the power dissipated within the tube, is the efficiency of the stage. This is rarely greater than 30-50%, so two tubes each of 12 watts dissipation are usually needed for 10 to 12 output watts and two 25-watt tubes for powers up to 25 watts. Higher efficiencies can be obtained by special techniques, which will be described in some detail later in this article.

Most people seem to want greater outputs than 10 watts, so my treatment of characteristics curves will be restricted to 25 watt tubes, but the

same basic principles apply to the smaller ones.

As to tubes that are available, it is a surprising thing that very few are available. In the old days British manufacturers had a wide range of triodes ranging from 12 to 250 watts plate dissipation, and some of them were very good, consistent, and reliable. Most of these have disappeared since the advent of the beam power tetrode. In the U. S. the 2A3 (now available in standard octal base as the 6B4G) is hardly ever used, and it is a sardonic commentary on audio usage that whereas the beam tube was developed to give greater stage efficiency, it is now *mis-used* by being triode connected to overcome the disadvantages of beam tubes, real or alleged, simply because the beam power tube has supplanted the triode. This development is not only illogical, it is also technically unsound, for the highly competent designers of tubes know how to design tubes for a specific purpose. The beam power tube is designed to be used as a beam power tube, a triode as a triode.

One real advance in output tube design is found in the Dutch *Philips-Mullard* EL34 and the American *Tung-Sol* 6550 pentodes. These are intended for "distributed load" or "Ultra-Linear" operation, but I am quite sure it won't be very long before some writer comes out with an amplifier design using these very same pentodes as triodes.

In Table 1 I have displayed side-by-side the characteristics of the more popular tubes. The parameters of single tubes are given so that you may assess the basic attributes of each type, while the power output and dis-

tortion of push-pull pairs gives you the data you require for various plate supply voltages. The table shows some interesting facts.

The KT66 made its appearance in the U. S. as a result of publicity given to the Williamson amplifier circuit. This circuit did not have any novel features, and the elaborate balancing controls included only contributed to getting the maximum undistorted output from an output stage of somewhat limited capabilities. There are other, and simpler, ways of getting the desired results. I have had my own opinion of the circuit—lack of stability—confirmed by many competent engineers, but it "caught on" because at the time it was described it seemed to behave better than many contemporary American amplifiers. In the process the tube specified by the author came to be endowed with special properties, but reference to the table (which has been compiled from the data issued by the manufacturers) shows that the 6L6 is a rather good match. It should be remembered that the 6L6 was not designed to work on plate voltages as high as 400, so its power output is somewhat limited; but the 807 has the same characteristics and can be used safely up to 600 volts. If you must build a Williamson amplifier then the tube to use is an 807. As an amplifier manufacturer in Britain before World War II I had experimented with precursors of the Williamson circuit and decided then the tube for me was the 807. In regular production, however, I used 6L6's as pentodes, for even 20 years ago it was well known by engineers that feedback over several stages was liable to introduce very-low-frequency instability through phase-shift. High performance amplifiers were best arrived at by using as few stages as possible, and this implied the utilization of the beam power pentodes. Feedback took care of the high output impedance.

Another suitable tube that should be mentioned at this point is the 5881. This can be considered to be a single-ended 6L6 with about 20 per-cent more plate dissipation. Plate voltages as high as 400 volts may be employed.

Table 1 also shows that as compared with the 6L6 or the KT66 the new power pentodes are a great step forward, either as pentodes or triodes. The transconductance is about twice as good as the prewar beam tubes, which means higher efficiency as an input voltage—power output converter. It also means greater power output for a given plate voltage. It would be unfair to say that the EL34 is better or worse than the 6550, for everything depends on the way it is used. The EL34 usage is described by the *Mullard Co.* as of the "distributed load" or "Ultra-Linear" type. To get the best out of these newer tubes involves special techniques, which will shortly be described.

The power output figures of Table 1 are without negative feedback. As I

Table 1. Data on 19-35 watt tubes, used singly (A) and in push-pull pair (B). For triode operation, screen grids are tied to plates through 100-ohm resistors.

Connected as:	6L6		KT66		EL34		6550	
	Pentode	Triode	Pentode	Triode	Pentode	Triode	Pentode	Triode
Plate volts.....	250	250	250	250 400	250	375	250
Screen grid volts.....	250	250	250	250
Cathode bias res. (ohms).....	170	490	160	315 600	120	370
Peak a.f. grid volts.....	14	20	15	19 38	13.5	18.9	14
Transconductance (μ mhos).....	6000	4700	6300 5500	11,000	8000	11,000
Load res. (ohms).....	2500	6000	2200	2750 4500	2000	3000	1500
Plate res. (ohms).....	22,500	1700	22,500	1450	15,000	12,000
Distortion (%).....	10	6	9	6 7	10	8	7
Power output (w.).....	6.5	1.3	7.25	2.2 5.8	10	6	12.5
(A)								
Connected as:	6L6		KT66		EL34		6550	
	Tetrode	Triode	Tetrode	Triode	Pentode	"Ultra-Linear"	Pentode (self-bias)	"Ultra-Linear"
Plate volts.....	270 360 400	250 350 250 400	375 430 430 400 430	400 430 450	450
Screen grid volts.....	270 270	250 275	375 425 425	300 275 450
Peak a.f. volts (grid to grid).....	28 41 90	36 70 40 80	59.5 45 77.5 58 64	53 46 96	92
Load res. (ohms, plate-to-plate).....	5000 9000 3000	4000 8000 2500 4000	3400 6600 6600 5000 10,000	4500 3500 3300 4000
Distortion (%).....	2 4 3	4 6 2 3.5	5 .8 1.3 3 <1	4 3 2.5 2.5
Power output (w.).....	18.5 24.5 15	17 30 4.5 14.5	35 20 37 16 14	41 55 70 28
(B)								

pointed out in Part 9, feedback cannot increase the power output of a tube but it can reduce the distortion. The figures in Table 1 for distortion can be reduced with feedback, but you cannot get more power output. If you use feedback, you will find that up to the figure given in the table, the power output for a pair of tubes contains less distortion with feedback, but the moment you go past that figure, the distortion with feedback will be greater than without. It is a characteristic of negative feedback that up to the optimum point of power output the gain in quality is substantial, but the moment you cross the threshold the results are terrible. The overload point is reached very suddenly.

If you fancy KT66's in push-pull triode operation you can't get more than 14½ watts at the maximum rated plate voltage advised for the tube. You can get more with 807's as triodes because the tube will just about stand 600 volts as a triode. Or you can use 6550's. But if you really want substantially higher powers than those shown in Table 1, then you must use four tubes in push-pull parallel. If you don't want to do that, then you must give up the idea of having a triode amplifier.

Output tubes with 12 watts plate dissipation are detailed in Table 2. The 6V6 you all know, and a pair is used in almost every 10-watt amplifier on the market. The KT61 is quoted because it is used in an imported British amplifier, although the tube was never designed for hi-fi amplifiers. Its very high transconductance is explained by its intended use immediately after the detector diode of a mass-produced radio set. It gives reasonable power output of a quality associated with such equipment. It does this very successfully, but is surpassed by the Mullard EL84, as can be seen at once by looking at the data for push-pull pairs. What Table 2 does show is that the triode addict is very badly served, for he cannot get more than 6 watts from a pair of any of them. The only 12-watt solution I know is the 25-year-old British PX4 triode, for which there is no American equivalent, but the tube is fitted with a British 4-pin base, has a 4-volt filament, and so calls for non-standard tube sockets and power transformers. A pair gives 13.5 watts with 2.5% distortion.

The two tables list nearly every output tube that can interest us (I did not include the 5881, a tube which I like, for its characteristics are similar, if a little better, than the 6L6). But we must also face the fact that these figures are for average tubes with a resistive load. In practice, the inductive load of a speaker system will result in less output for a given distortion or the same output for more distortion, although the discrepancy will not be as great with triodes as with tetrodes. But for a clearer idea of what really goes on inside a tube recourse must

Connected as:	6V6	KT61		EL84	
	Pentode	Pentode	Triode	Pentode	Triode
Plate volts.....	250	250	250	250	250
Screen volts.....	250	250	250
Peak a.f. grid volts.....	12.5	4.3	5.5	6	8.3
Transconductance (μmhos).....	4100	10,500	9800	11,300
Load resistance (ohms).....	5000	6000	5000	5200	3500
Distortion (%).....	8	8	5	10	9
Power output (watts).....	4.5	4.3	7	5.7	1.9
(A)					
Plate volts.....	285	275	350	300	300
Screen volts.....	285	275	300
Peak a.f. volts (grid-to-grid).....	38	16	23	28	28
Load resistance (ohms).....	8000	10,000	6000	8000	10,000
Distortion (%).....	3.5	6.5	2	4	2.5
Power output (watts).....	14	11.5	6	17	5.2
(B)					

Table 2. Comparative data pertaining to beam power pentodes with plate dissipations of 12 watts. Part (A) is for a single tube, part (B) is for a push-pull pair.

usually be made to the tube's characteristic curves as published in many tube manuals.

Characteristic Curves

I have no wish to use up a lot of space on this matter, for the material has been printed over and over again, but a few notes will not come amiss. Fig. 38 shows the plate volts—plate current curves of a 6L6 connected as a triode, the sort of curves you see in the tube manuals. To these I have added a 25-watt dissipation curve to indicate the limit of the tube's handling capacity. The load line XOY has a gradient representing 2500 ohms, and to prove this I have extended it dotted to cut the voltage and current axes; you will notice it cuts the horizontal axis at 500 volts and the vertical at 200 ma., and 500 volts/0.2 amp = 2500 ohms.

If the distance OX, representing a signal swing from -15 to 0 volts on the grid, equals the distance OY, which represents a signal swing from

-15 to -30 volts, there will be no second harmonic distortion. If these two distances are not equal, there will be. If the ratio of OX to OY is 11 to 9, the distortion will be 5%, which is usually reckoned a suitable figure for second harmonic distortion (but 5% of third harmonic would sound very bad indeed, our ears being what they

(Continued on page 168)

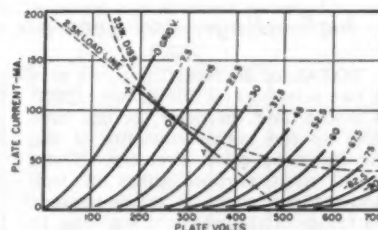


Fig. 38. Plate characteristics of the 6L6 connected as a triode. A 2500-ohm load line has been added to the curves along with a line denoting the maximum plate dissipation power of 25 watts.

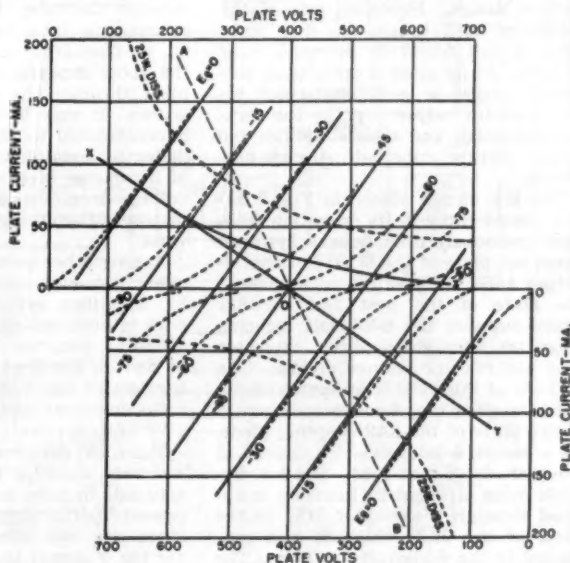


Fig. 39. Composite characteristics of a pair of 6L6's in class A push-pull. The point "O" is the operating point, through which passes the basic composite characteristic labeled "45 volts" and marked as a solid line. Other composite characteristics are shown as solid lines. The load line XOY represents a load of 3000 ohms as recommended in Table 1. For the meaning of the load line AOB, representing a 10,000-ohm load, see text.

Sylvania

Color TV

Circuits

By
WALTER H. BUCHSBAUM
 Television Consultant
 RADIO & TELEVISION NEWS

An unusual chassis layout, a new way of developing high voltage, and generous design margins are noted.

A TOTAL of 28 receiving tubes plus two selenium rectifiers, two crystal diodes, and the color picture tube make up the active elements of the new *Sylvania* color circuitry. There are 12 multi-purpose tubes of well known types such as triode-pentode and triode dual-diode combinations. In general, the tube complement and circuitry of the *Sylvania* color models are similar to the recently described *Hoffman* and *Emerson* receivers, as well as several others based on the 1956 *RCA* 28-tube design. However, one of the generally used tubes, the h.v. regulator, is not found in *Sylvania* color TV sets. In its place a completely different system is used, one which requires no h.v. adjustment by the service technician and thus simplifies the actual picture tube adjustment procedure.

The h.v. circuit shown in Fig. 2 differs considerably in its operation from most previously used flyback systems. From the plate of the 6CB5 horizontal-output tube, the positive pulse goes to the plate of the first 3A2 rectifier which supplies the 6-kilovolt focusing potential through a filter capacitor (C_5) and resistor voltage divider. The cathode of this tube is at approximately 6 kilovolts d.c. and connected directly to the plate of the 3A2 coupling diode. As a result, 6 kilovolts also appear at the cathode of that tube. The h.v. flyback pulse of about 20 kilovolts is applied through a capacitor (C_1) to the plate of the 3A3, which is also connected to the 6-kilovolt d.c. point. The


result of this arrangement is that the 3A3 rectifies the 20-kilovolt pulses in addition to passing the 6-kilovolt d.c., thereby providing a 26- or 25-kilovolt potential for the anode of the color picture tube.

The box marked "corona regulator" in Fig. 2 represents a glass-and-metal enclosed discharge tube of special design. Its operation is similar to that of a gas-type voltage regulator in that, when voltage impressed upon it increases, more current is passed through the tube. In the case of the corona-type tube the amount of corona, or discharge of electrons through the tube, depends on the voltage applied through the series-limiting resistors. It may be said that the tube is constructed to depend on controlled dielectric breakdown under the stress of increasing high voltage, so that the voltage drop over the breakdown path disposes of anything over the regulated value.

Among other technical features, *Sylvania* receivers use a 4-stage 41-mc. i.f. amplifier section in conjunction with intercarrier sound and a separate sound i.f. detector. The sound section, as seen in the block diagram of Fig. 3, consists of one limiter-driver, the 6T8 ratio detector—audio amplifier, and a 6W6 output tube.

From a designer's point of view, *Sylvania* color sets are well on the safe side in gain, bandwidth, and component performance. For example, there are two 6CL6 video amplifiers for the Y signal and the first of these

Fig. 1. Note unusual mounting for tuner subchassis (upper left), with on-off and volume control (lower right), and shorting bar to ground out h.v. automatically (to right of h.v. rectifier) in this rear view of the three-sided chassis.

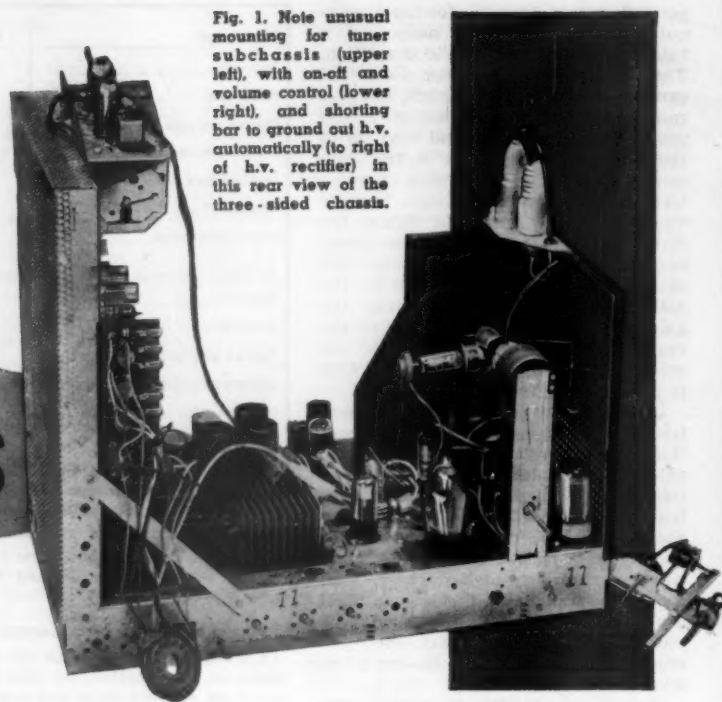

stages also amplifies the color sub-carrier. This latter signal is then passed through still another amplifier for bandpass limiting before being applied to the demodulator driver amplifier. Demodulation is accomplished with the widely used high-level triode circuit described in detail in the March 1955 issue of *RADIO & TELEVISION NEWS*. To insure sufficient amplitude of the blue color difference signal, a separate stage of B-Y matrix amplification is provided.

The chassis arrangement consists of an L-shaped structure which surrounds the picture tube. While no printed circuitry is used in the first production runs, the entire chassis consists of three major subassemblies and a total of 8 plugs and jacks including a set of pin-jacks which connect the picture and screen grids of the color picture tube with the main chassis. All these assemblies can be of great help to the service technician in troubleshooting, especially since these points as well as some test points are clearly marked in the circuit diagram.

Unlike most other color sets, the *Sylvania* models do not provide controls under a sub-panel which both the viewer and the technician can adjust. In addition to channel selection and fine tuning there are only the "on-off," volume, tone, contrast and brightness controls available for monochrome adjustment. Used for color reception only, the hue and the color or chroma gain controls are at the front. All other adjustments are accessible either from the rear or top of the chassis. This arrangement has some advantages and some drawbacks.

The advantages include the fact that customer misadjustment of such tricky

control
 bias, p
 less li
 to avo
 ondary
 the se
 the fe
 the dr
 are so
 and w
 adjust
 color-l
 by the
 tions.
 recept
 with
 owner
 these
 A fu
 of a m
 second
 we mi
 never
 ing re
 most
 wholly
 descri
 to bec
 of his
 weird
 Fig.
 Sylva
 is use
 table
 three

Y

A.



A Field-Strength Meter that Tests Tuners

By **ROBERT G. MIDDLETON**
Chief Field Engineer, Simpson Electric Co.

This extra-duty piece of test equipment is useful on the bench as well as in signal-strength tests.



Fig. 1. Field-strength meter operates on u.h.f. as well as v.h.f., provides substitution test for suspected tuner, and will also recharge 6-volt battery.

Fig. 2. Rear chassis view shows output connection for front-end testing on the turned-up apron (right) behind tuner.

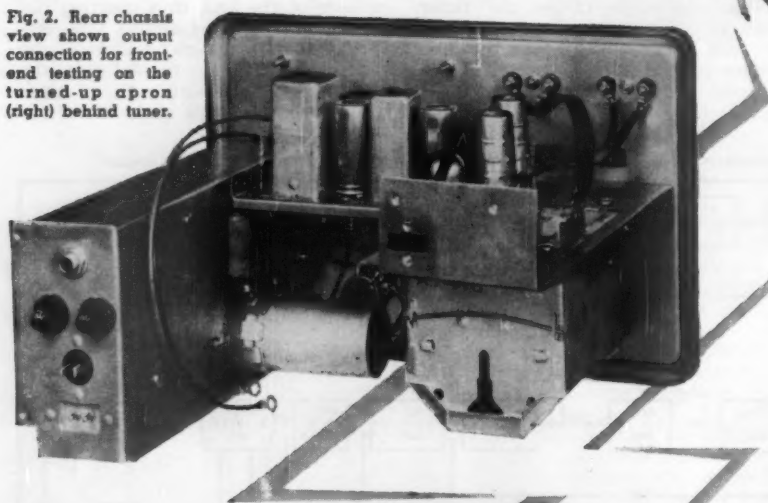


Fig. 3. Access door at rear of cabinet is for removal and insertion of battery; connectors are available through door.



THE ever-popular field-strength meter has been elaborated in function by *Simpson Electric Co.* so that tests of front-end performance can be made with it. Accordingly, field-strength meters are now useful at the bench, as well as in the field. Front ends can be tested for both u.h.f. and v.h.f. performance, as will be explained.

The external appearance of the versatile field-strength meter is shown in Fig. 1, from which it is seen that terminals are provided for either u.h.f. or v.h.f. input. The meter has a full-scale sensitivity of 50 microvolts, although the full sensitivity need be utilized only in the far-fringe areas. The dual tuning control is arranged for convenient and rapid adjustment on both u.h.f. and v.h.f. functions.

Note the battery-test position on the function switch, which provides direct indication on the meter scale of battery condition. The internal 6-volt storage battery can be recharged from the 117-volt power line by means of a built-in trickle charger, or can be recharged from the cigarette lighter on the dashboard of the service truck. The instrument also operates from a 117-volt power line, if desired. When the service truck is garaged, the car battery can be recharged over-night from the trickle charger of the instrument.

Fig. 2 shows the chassis construction of the field-strength meter. A *Standard Coil TE Series XT41C* tuner is utilized for high gain and low-noise performance on both u.h.f. and v.h.f. channels. The phone plug provides an audio outlet for monitoring of the sound signal with a headset, and the dual-prong outlet permits the internal battery (not shown) to be recharged from the generator in the service truck, or facilitates recharging of the car battery from the instrument. The standard 117-volt receptacle permits

The output connection for front-end testing is seen on the turn-up apron at the right-hand side of the chassis in Fig. 2. This receptacle accommodates a 300-ohm output lead for connection to the antenna-input terminals of a receiver on the bench. The manner in which this novel test is made will be discussed shortly. A rear view of the instrument is shown in Fig. 3, which shows the access door to the internal storage battery and the various connectors. Two fuses are accessible from the rear of the case, for convenience in the event that replacement should be required. The test cables can be stored inside the instrument, when the access door is opened.

Test Signal from Instrument

The signal for bench tests of receiver front ends is obtained from the cathode circuit of the first i.f. stage in the field-strength meter, as seen in Fig. 4. This is a 47-ohm low-impedance source, which provides almost the same signal level as is present at the mixer-output terminal of the tuner in the instrument. Being a low-imped-

ance signal source, the video voltage from the instrument can be applied at any desired point in the receiver under test, without appreciable loading of the field-strength meter.

The tuner output provides the video signal at a picture-carrier frequency of 45.75 mc. Accordingly tuner tests of receivers must be made at this frequency, and the test signal is not usable for receivers with a 23-mc i.f. However, most present-day TV receivers utilize the 45.75-mc. i.f., including all color-TV sets on the market.

To make a test of tuner response in a TV receiver, the 300-ohm output cable is plugged into the receptacle on the rear of the field-strength meter. The alligator clips at the other end of the 300-ohm cable are connected to the grid of the first i.f. tube in the receiver, and to receiver ground, usually the chassis, the black clip going to ground. However, if desired, the alligator clips can be connected between cathode and ground of the first i.f. tube in the receiver, since the signal is provided at low impedance.

Either a u.h.f. or a v.h.f. antenna lead-in is connected to the field-strength meter via the front-panel terminals, and the instrument is adjusted for maximum indication on the desired

channel. The meter indicates the signal strength in microvolts, and the incoming picture is reproduced on the screen of the receiver picture tube. (Of course, the i.f. and video circuits of the receiver must be operative.)

The contrast of the picture is noted on the screen of the picture tube, and then the lead-in is transferred to the receiver input terminals, with the field-strength meter disconnected from the receiver. As much or slightly more contrast should now be observed on the picture-tube screen. *If a weak picture or no picture is obtained, the front end is undoubtedly defective.*

It will be apparent that the foregoing test serves to answer the question: "Is it the front end, or is the trouble originating in the i.f. or video amplifier?" In case of i.f. or video-amplifier (or picture-tube) trouble, the picture will be weak or absent when the receiver is driven from the field-strength meter.

Technicians in u.h.f. areas will recognize the great value of being able to check out u.h.f. tuners for operation and adequate sensitivity. Tuner repair stations will also find the novel test procedure useful for determining whether or not a repaired tuner has been restored to proper condition. —30—

Fig. 4. Schematic of the Simpson field-strength meter shows low-impedance take-off at cathode of the 1st i.f. Signal taken from this point can be fed to a TV receiver's i.f. strip as a test substitute for the set's own front-end signal.

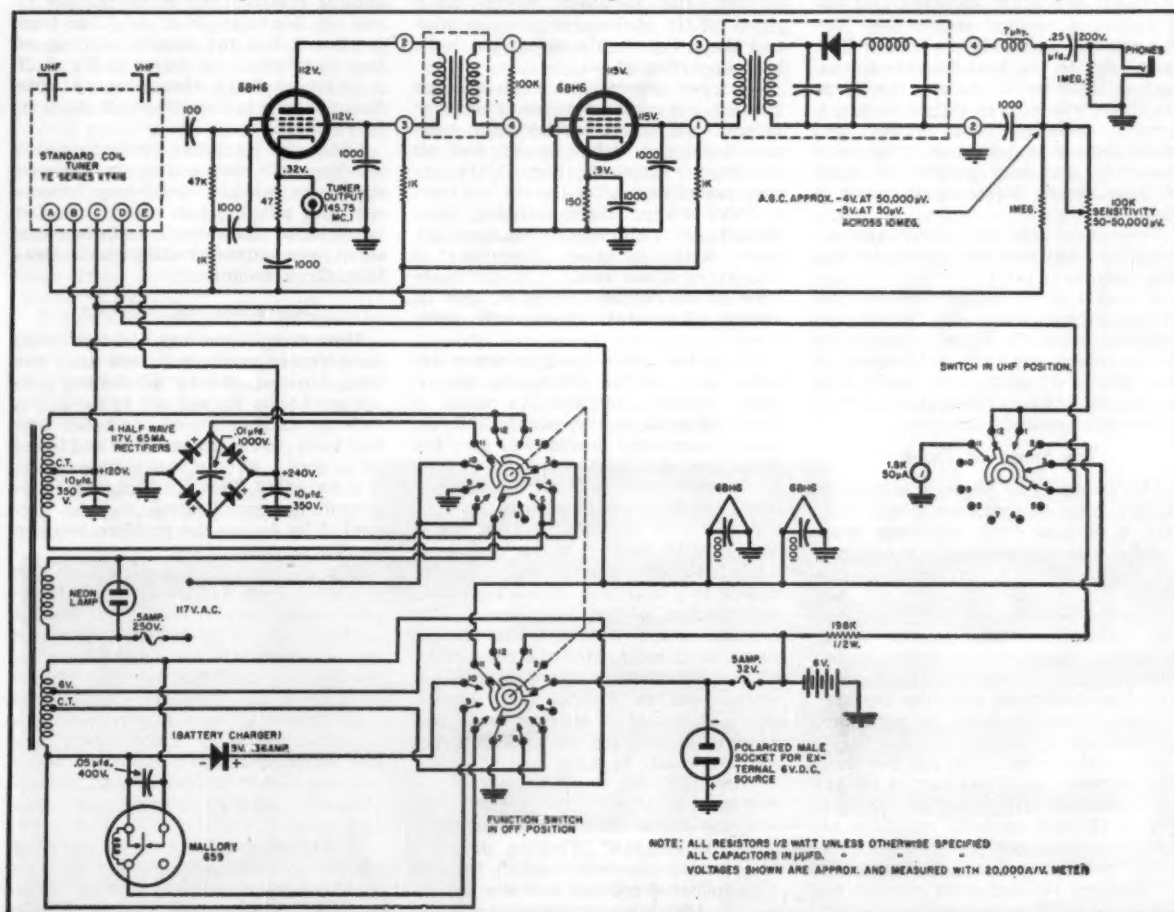




Fig. 1. Feeling selenium rectifiers for excessive heat after a few minutes of operation will often yield a quick clue as to the causes of inadequate "B-plus."



Fig. 2. A cold wirewound resistor may provide a shortcut to an open circuit.


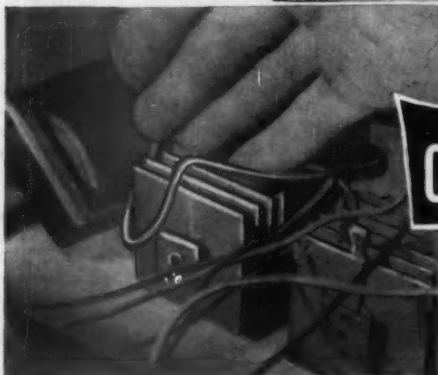


Fig. 3. With the h.v. rectifier out of its socket, the flyback transformer should run cold—unless it is defective.

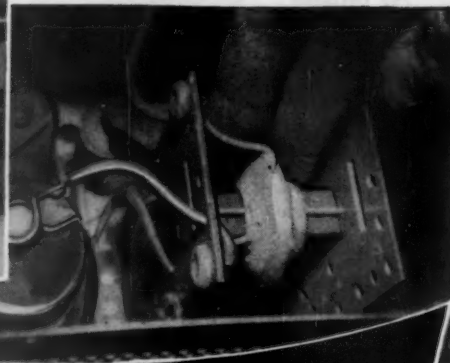

Common-Sense Troubleshooting

By CHARLES GARRETT

Direct methods "not in the book" sometimes produce quicker results than purely theoretical techniques.

THERE are many talented and experienced service technicians, but some of them do not use their knowledge to the best possible advantage in their work. Among the latter are those who adhere rigidly to a systematic technique for service and parts replacement that is often very elaborate, and may involve all types of instruments before a diagnosis is made.

These first-rate men eventually accomplish what they set out to do—but they can be notoriously slow. To get the most out of his ability, the so-called theory man can benefit by adopting, when the situation warrants it, the direct-approach techniques of the "practical" man. This would tend to complement his systematic approach rather than exclude it.

The Sense of Touch

The presence or absence of heat in certain types of components will often give a clue to their condition more rapidly than the set-up for a test can. Selenium rectifiers, for instance, normally run warm—although not hot, unless the receiver has been in operation for two or three hours. Where operating symptoms (narrow raster, poor focus, etc.) indicate the possibility of an inefficient selenium rectifier, a quick, direct check can be performed as follows:

Allow the receiver to run for three or four minutes. Then turn it off and feel the rectifiers' plates, as shown in Fig. 1. If one or both rectifiers are hot, it or they are faulty; no further proof is needed once the technician familiarizes himself with normal and abnormal rectifier heat. If a short had

existed, the rectifiers would have given off an obvious, unpleasant odor and the set probably would not have been operating at all.

An open wirewound, high-wattage resistor is a common cause of receiver failure. So, before methodically voltage-checking a defective set, feel all wirewound resistors (Fig. 2) for the presence of heat after the set has been on for two or three minutes, then turned off. All these resistors get warm with operation. Therefore, if one stays stone cold, it is certainly open or the circuit it feeds is open. A simple ohmmeter check will show which is so.

If, on the other hand, a power resistor gets red hot after only two or three minutes operation, a short is likely to exist in the circuit it feeds. Again, ohmmeter checks will give the technician the final proof. Of course, for safety's sake, turn off the receiver when touching power resistors.

A defective horizontal-output transformer with shorted turns, ordinarily difficult to prove good or bad, often responds to a heat test. If the high voltage winding of the transformer (the rim or outside winding) has shorted turns, as is most often the case in defective horizontal outputs, it will get warm, even hot. Shorted turns act the same as would a shorted secondary winding in drawing excessive current and eventually heating.

With the 1B3 or 1X2 high-voltage rectifier removed, the high-voltage winding draws no current; therefore, it should run cool. That is, unless it is defective. So before going through a complicated process with the flyback tester, try this: Remove the high-

voltage rectifier and allow the set to run for five minutes or so. Then turn it off and feel the outside winding of the transformer, as shown in Fig. 3. If it has heated up, there can be little doubt that it is defective and needs to be replaced.

Often the insulating coating on this winding will soften and, in extreme cases, the winding itself may become soft and pliable when enough shorted turns exist. This simple test alone can often save hours of testing and frustration for a technician.

Elimination and Isolation

How many times has a defect in an intermittent receiver or one that has been unresponsive to all testing procedure finally turned out to be only a tube or combination of two tubes that had been previously checked and found to be good? Even if this happens once, it is too often. This discouraging, time-consuming complication can be prevented by facing the problem head-on in this manner:

When routine testing procedure fails to pinpoint the defect, temporarily replace every tube in the set. If the set comes to life or its defective operation ceases, re-install the original tubes, one by one, until the defective one or ones show up. Temporary mass tube replacement is especially recommended when servicing radios where only five or six tubes are involved. Many puzzling cases involving hum, distortion, and fade-outs can be cured quickly this way.

A lighted yet inoperative radio, or the sound section of a TV set showing similar symptoms, can be slow to diagnose if the technician is not certain

in which amplifier, i.f. or a.f., the trouble lies. To be able either to eliminate or to accuse definitely the audio-amplifier section as being at fault is a worthwhile step.

Here is a simple yet accurate check for audio-amplifier activity. Turn the set on and the volume control up to full. Then touch a finger to the center terminal on the volume control. A loud hum will issue from the speaker if the audio stages are normal. This hum may vary from faint to strong, depending on the polarity of the line plug, especially on a.c.-d.c. receivers. Portable radios will not hum on battery, so operate these on a.c. while testing. Practice this procedure on normally operating audio sections until the average hum level is recognized.

The i.f. section of a TV set can be eliminated as containing a defect, or a defective i.f. stage pinpointed, in this manner. Set a modulated AM signal generator to the middle of the i.f. passband, usually 24 or 42 mc., and at maximum output. Then inject this signal into the detector stage at point 1 in Fig. 4. Turn the contrast control to full. Faint horizontal bars should appear on the screen at this point, if the generator output is a tenth of a volt or more and the detector and video amplifier stages are functioning properly.

Then move the generator from plate to grid, plate to grid, through successively numbered points, working back towards the converter. The bars should increase in intensity from plate to grid all the way back to the converter plate, if the i.f. strip is normal. However, if the bars decrease or disappear at any one plate or grid, the defect has been localized to the stage associated with that plate or grid. The change in intensity of the bars as the generator lead is moved progressively back from detector to front end is shown in Fig. 5.

A similar technique can be used on the 455-kc. i.f. system of the conventional radio. Set the generator on maximum modulated output at the radio's i.f. and again work back from the detector diode plates to the converter

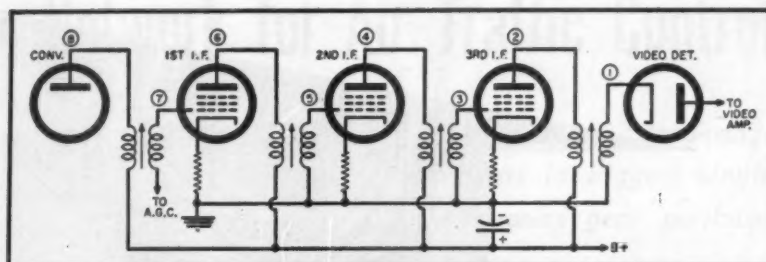


Fig. 4. This 3-stage I.F. plus video detector circuit shows how signal injection can be used, with the picture tube of the TV receiver acting as an indicator, to localize a video-circuit defect to one stage in the video chain. An amplitude-modulated output from a signal generator, adjusted to the i.f. of the receiver under test, is fed first to the input side of the video detector, shown as point 1 above. If vertical-bar output is not noted on the raster, the defect probably lies in the output side of the detector or in the video amplifier stage. If the bars appear on the picture tube, the injected signal is successively moved back, point by point, in the sequence numbered. Intensity of the bars should increase as the signal is moved back another stage, as the photographs of Fig. 5 show. If this increase in amplitude fails to take place, a defective stage is probably responsible. If this stage-by-stage increase in gain is apparent up to the converter plate, trouble is probably in the tuner or antenna circuit. A similar technique may be employed in tracing the circuits of AM radios, except that an audible tone is evident instead of bars.

grid. The signal may be barely audible at the detector but should increase to strong at the i.f. tube grid, then to very loud at the converter grid, if the i.f. is tuned and functioning properly.

Push-pull audio output stages can be given a quick, rough check for distortion or unequal output simply by removing one tube, replacing it, then removing the other tube, while noting the volume level and clarity of each single remaining tube. Volume and tone should be about equal with either tube in the circuit, although less than with both tubes functioning. But in abnormal operation, distortion may clear up when one tube is removed. Or on the other hand, the set may drop drastically in volume if one half of the push-pull circuit is out of order.

If distortion clears up with one tube removed, the distortion originated in or was fed to the speaker through the removed tube. If it drops in volume though, and some distortion results, the remaining tube or circuitry or its signal source is defective. (This check is of no value if one push-pull tube receives its signal from the output of

the other as is done in some older radios.)

Another direct elimination-and-isolation method is useful for the measurement of socket voltages. A voltage discrepancy that is not readily obvious with a tube in its socket may be exposed by removal of the tube. For instance, leaky coupling capacitors may not measurably affect grid voltages due to the counteracting cathode bias and developed negative grid bias. But, with the tube removed, these counteracting voltages disappear, thus allowing a leaky coupler to expose itself by placing thirty or forty, or more, volts positive in the grid circuit.

A circuit in which a leaking coupling capacitor might be concealed by operating action is the multivibrator shown in Fig. 6. The cathode and grid voltages developed during oscillation—the eventual result of action in both triode sections—can easily conspire to mask the fact that capacitor C_1 is leaking. With the tube removed, circuit action ceases. If the static voltage measured at pin 7 is now at all


Fig. 5A. Signal injected at test point 1 in Fig. 4 will look like this, low in level, with little contrast between light and dark areas.



Fig. 5B. Signal injected at test point 5, grid of 2nd I.F., shows greater gain, contrast.



Fig. 5C. Injected at the converter plate, test point 8, the AM i.f. signal shows deepest contrast, evidence of greatest gain in normal operation.

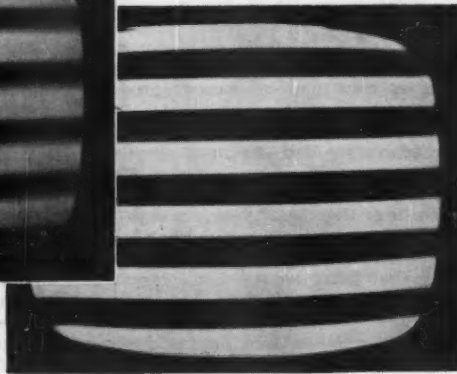



Service

Diversification

By
**WILLIAM
LEONARD**

Handling a wider variety of products helps some service businesses survive; mergers help others.

THE AVERAGE TV service dealer, alternately buoyed by the fall business booms that start with the football season and dejected by the ever-recurrent slumps that are wafted in with the breezes of spring, hopes longingly for some kind of a system that would stabilize his business. Uninformed about and unusually uninterested in the workings of the economic forces that govern his entire life, he is inclined to favor licensing or some other type of activity control as a cure for all of the ills of his business.

The spectacular public acceptance of TV as an indispensable part of our way of life and the multi-million dollar service market it spawned, have led to many uneconomical practices in the entire TV field. Our economic system will tolerate inefficiencies as long as consumption exceeds production, but when production starts to run far ahead of sales, the pressure for economies and improved efficiency grips all levels of an industry in a steadily tightening vise.

During the past year, many TV receiver manufacturers either sold out or abandoned production. Along with that there has been a steady attrition in the number of TV set distributors. More recently the vise started to clamp hard on the service shops that specialize in TV service.

An interesting sidelight on the relative stability of TV service as a business as compared with other widely used electronic products, is reflected in the history of the auto-radio service shops that either stayed away from TV service or got into it and then dropped it.

The shops that stuck with auto-radio service and promoted the new auto electronic accessory products as they were developed have prospered, while their brothers in TV continued to ride the roller coaster of boom and bust.

The advantage of auto-radio service as a business is that it does permit diversification of effort within its own field. As an example, alert auto-radio service dealers found the 110-volt auto battery inverters of interest both to business executives and to many TV set owners. For the former, they provide an opportunity to dictate memos, notes and observations on a tape recorder during the formerly "lost" time used up in driving. Many TV set owners have had the inverters installed in their cars to enable them to use their portable TV's on picnics and for the facility they provide to use regular motorized tools at any place the car is driven.

Many TV service dealers have now reached the conclusion that their businesses are anchored to a foundation of quicksand that is getting more

treacherous every month. While they do not intend to abandon TV service completely, they plan to expand their field of activity either through mergers with other shops or by the addition of other allied services and departments.

An excellent example of service diversification is the establishment in Port Chester, N. Y., operated by William J. Bova and George Catalona. Functioning under the name of *Like-New Appliance & TV Service, Inc.*, the Bova-Catalona team has built a business that handles anything in the home that runs by electricity with the exception of sealed-unit refrigerating devices.

The partners feel that one of the most valuable advantages they have gained from their plan of activity diversification has been its stabilizing effect on the firm's labor needs. Although some types of service fluctuate seasonally, there is never an over-all slack period. While the summer would normally be a slow season for shops that do not handle domestic refrigerators, their organization is kept busy by servicing commercial air conditioning and installing and servicing room air conditioners.

"The biggest advantage of being diversified," said Mr. Bova, "is its value in promoting business. Home owners like to deal with one firm that can service anything in the house. Diversification helps us run our business more efficiently, too, by stabilizing our labor needs and by permitting us to do a large volume of business in a limited area.

"To begin with," continued Mr. Bova, "a customer who phones us for service or who brings in an appliance has probably heard of us from her friends because of the volume of service work we do. We may have repaired different types of appliances for her friends, but every recommendation is effective because we can handle any type of service she may need. That helps to put us in touch with many new customers.

"The fact that we fix everything builds confidence in itself. The customer knows that we will do a careful, fairly priced job on her washer, for instance, because we want to be called later to repair her ironer or electric range."


The firm has been able to get an adequate volume of business from an area within ten miles of the shop. This results in a considerable reduction in travel time and car operating costs for the technicians.

Business Mergers

A recent development in the southwest may prove to serve as the survival pattern for many television service shops. Motivated by the conviction that independent electronic service shops must provide more complete and dependable service to survive, five San Antonio, Texas, service dealers recently merged their businesses to form a \$100,000 service company operating.

(Continued on page 196)

Radar Network for Air Traffic Control

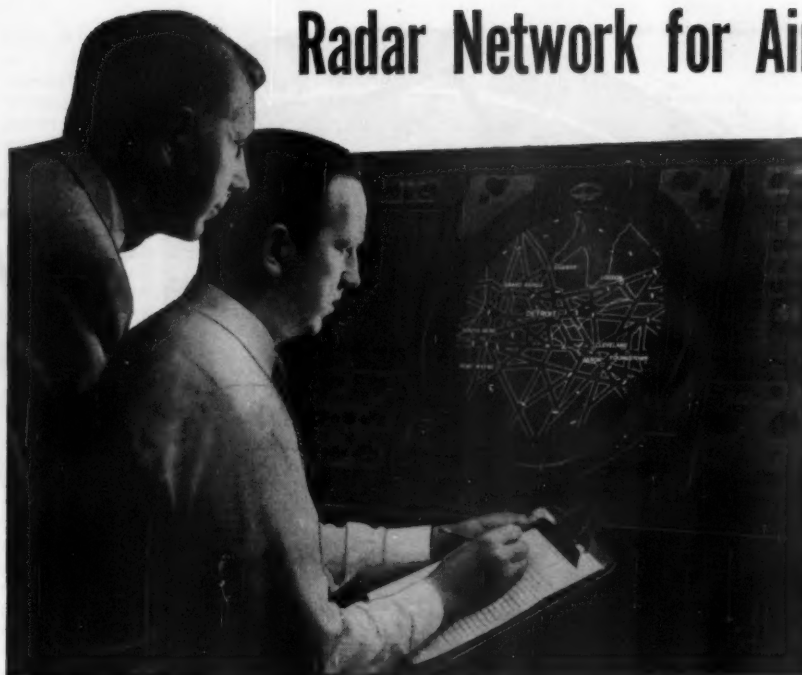

CAA orders 23 long-range radars in biggest single electronics gear purchase.

Radar operators scan skies on long-range radar. Shown on the scope are air lanes connecting cities. Planes appear as light spots. Electronically projected map overlay enables the operator to pinpoint plane's position.

Giant 40-foot search antenna to be used with the new radars. This antenna will be equally effective for jet operation at 35,000 feet and higher or for low-altitude slower aircraft.



A MAJOR step in a sweeping plan for improvement of the nation's air traffic control system was taken recently, with announcement by the Civil Aeronautics Administration of an order for 23 long-range radars, biggest single purchase of electronic equipment in the agency's history.

The radars are the heart of a CAA plan announced last April by Secretary of Commerce Sinclair Weeks. The plan is designed to handle a fourfold increase in U. S. air traffic with minimum delay and maximum safety. The new radars will help CAA controllers accomplish this by scanning the skies for all aircraft up to 200 miles away, depending on size and altitude.

Raytheon Manufacturing Co. of Waltham, Mass., will design and build the equipment, which will cost approximately \$9,000,000. Deliveries will begin this summer.

The 23 radars will be part of an expanding coast-to-coast traffic control network of more than 70 civil and military radar installations. The network will give controllers a picture of aircraft from 15,000 to 70,000 feet in virtually all the U. S. airspace, and of aircraft at lower altitudes on densely traveled routes. Thus, radar will serve to track the civil and military jets which move at 600 miles an hour or more in the higher altitudes, and the conventional aircraft traffic using the lower altitudes.


Each radar uses a large 40-foot antenna, and effectively covers more than 125,000 square miles of area. A single set will be able to feed up to 15 different monitor screens simultaneously, so that each controller on duty in a CAA center can have a picture of traffic movement. At present, with the exception of the radar-equipped New York and Washington

centers, CAA controllers depend on position reports radioed in by pilots en route. CAA also has radar for surveillance around 34 airports, which will continue to serve traffic within a range up to 30 miles.

The new equipment employs either linear or circular polarization of the radar signal so as to minimize the effect of rain or other bad weather interference. Another feature is an improved moving target indication arrangement that removes radar echoes from fixed objects, thereby allowing signals from moving aircraft to show up clearly.

Chances of breakdown are reduced because of the use of dual controls and functioning parts, allowing uninterrupted operations.

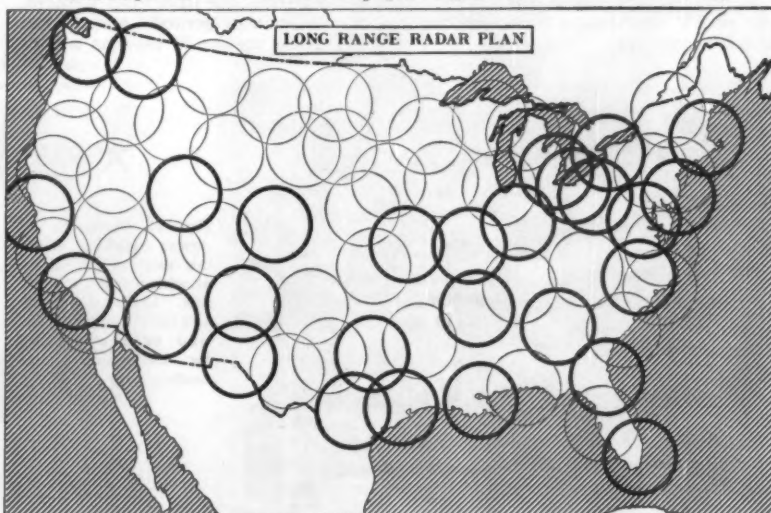New radars are to be installed at 23 of the 28 heavily circled areas shown below. Remaining 5 areas will use military gear. Light circles show future coverage.



A Compact 6 Watt Power Amplifier

By E. TAYLOR HORTON

This simple miniature audio amplifier is small enough to be tucked out of sight. Two 2" by 4" by 5" chassis used.



Fig. 1. Over-all view of miniature audio amplifier. Separate power supply is used.

WHEN space and cost limitations of an audio system dictate the use of a small speaker and enclosure, these same limitations also dictate the use of a small, low-cost amplifier. As long as the amplifier distortion can be kept to a negligible amount at normal listening level, the maximum power capabilities of the amplifier are unimportant for non-critical use. This unit was designed to produce a practical compromise among the often conflicting factors of size, cost, frequency response, distortion, and simplicity.

The amplifier is small enough to be tucked away out of sight in a bookcase or TV cabinet, and yet has enough power output to adequately drive a small, good-quality speaker. It is well suited for use with an external speaker to improve the audio quality of a radio or TV set or as a tape recorder playback amplifier.

The amplifier is built on a 2" x 4" x 5" chassis and is only 4½" high over-all. The power supply is mounted on a separate chassis to make it easier to install in cramped quarters. Its chassis also measures 2" x 4" x 5" and stands 5" high. Both chassis were made from a 3" x 4" x 5" aluminum case, with one inch cut off the 3" side. A series of ventilating holes were drilled in the bottom section of both chassis and ½" rubber feet mounted on each corner. As the bottom sections are not needed for shielding, but are used only to improve the appearance of the equipment, they may be eliminated if desired.

The schematic diagram of the two units is shown in Fig. 3. The amplifier uses only three tubes and a minimum of other parts. The first tube, a 6AN8, is a combination pentode and triode. The pentode section is used as a con-

ventional voltage amplifier direct-coupled to the triode section which is connected as a split-load phase inverter. The power output stage uses two 6CM6's in push-pull with screen feedback being provided from taps on the output transformer. The 10,000-ohm terminals of the transformer are connected to the plates and the 4000-ohm taps connect to the screens. This type of operation permits the tubes to be biased so as to draw a total cathode current of only 44 ma. while delivering six watts output at 1.6% distortion. The gain of the stage is greater than with triode operation and the distortion is less than if the tubes were used as pentodes. This low current drain allows the use of a small power transformer with the resulting saving in size and cost. Additional voltage feedback is provided from the voice coil winding of the output transformer to the cathode of the first stage. The power supply uses a 5Y3 in the usual full-wave rectifier circuit followed by a two-section RC filter.

The amplifier is very easy to assemble and makes a good "first project" for the novice builder. By using the parts specified, hole drilling on the chassis is kept to a minimum. The parts layout of the amplifier can be seen in Figs. 1 and 2. The underside of the chassis is not particularly crowded and a smaller chassis could be used if necessary. When wiring the amplifier it is advisable to keep the input and output sections well separated, and to run the a.c. heater leads as far from the input jack and pin 8 of the 6AN8 as possible.

All grounds can be made directly to the chassis at any convenient point. Near the 6AN8 socket, a 2-point tie

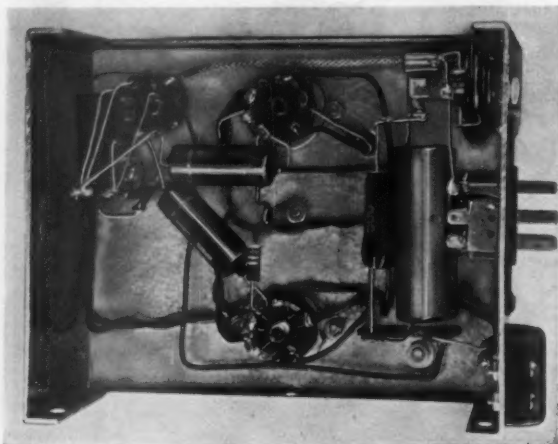


Fig. 2. Underside of power amplifier showing extreme simplicity of wiring and construction. Input jack, 6-contact power plug, and terminal strip for loudspeaker connection are at right.

strip is mounted above the chassis by a $\frac{1}{2}$ " brass spacer. One tie point is connected to ground and the other to terminal 2 of the Cinch-Jones male power plug. Resistors R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 are connected between their respective socket pins and to the two tie points, as indicated. In order to maintain a good balance in the phase inverter, R_3 and R_4 should be closely matched in value. These resistors can either be purchased as a matched pair or several resistors can be checked with an ohmmeter and two, whose value is as close as possible to the required 47,000 ohms, selected.

If R_1 is used, it is mounted directly on the input jack which is wired to pin 8 of the 6AN8 by a short length of shielded wire. C_1 is placed against the back drop of the chassis and connected between pin 7 and a soldering lug placed under the $\frac{1}{2}$ " brass spacer. The interstage coupling capacitors, C_2 and C_3 , are connected between the socket pins of the 6AN8 and the 6CM6's. R_7 and R_8 connect between the grid pins of the 6CM6's and a soldering lug fastened to the chassis between the two tube sockets. Another 2-point tie strip is mounted near the output terminal block. One tie point is connected to pin 9 of the 6AN8, and R_{10} , the feedback resistor, is connected between this point and the 8-ohm terminal of the output block. The other tie point is connected to pin 7 of both 6CM6's, and R_9 and C_4 are wired between this point and another soldering lug mounted on the chassis near the input jack.

The output transformer is mounted directly on the chassis, as shown, and three $\frac{1}{4}$ " holes are drilled through the chassis to pass the leads from the transformer terminals to the tubes and to the output terminal block.

When wiring the amplifier it is very important that the connections to the

Fig. 6. View of power supply required for miniature, high quality audio power amplifier. Power transformer, rectifier tube, electrolytic capacitor, output socket, and switch can be seen.

Fig. 5. Underside of separate power supply is shown below. Two filter resistors and protective fuse are clearly visible.

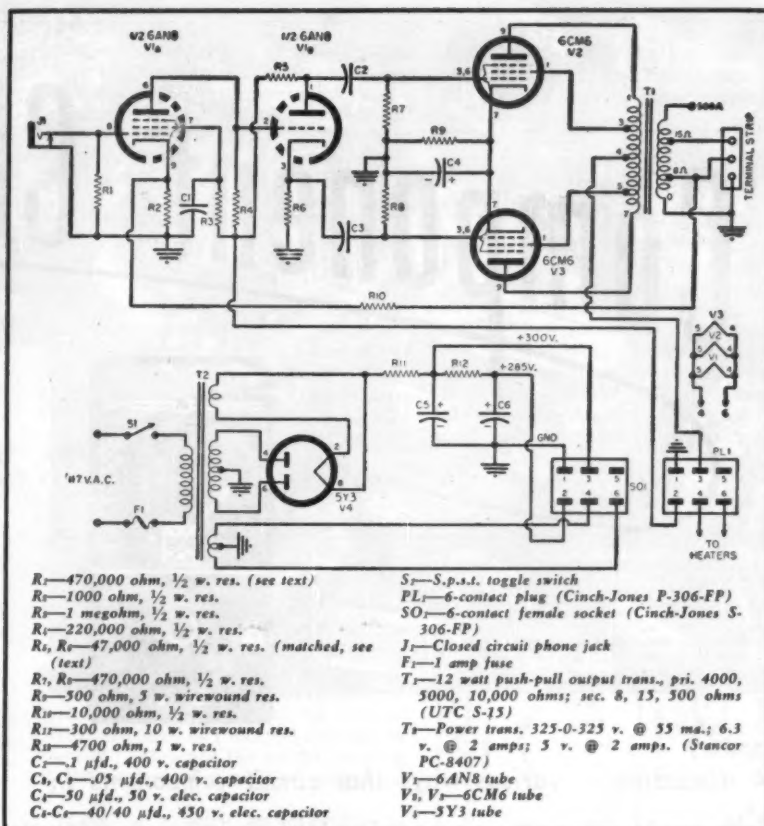
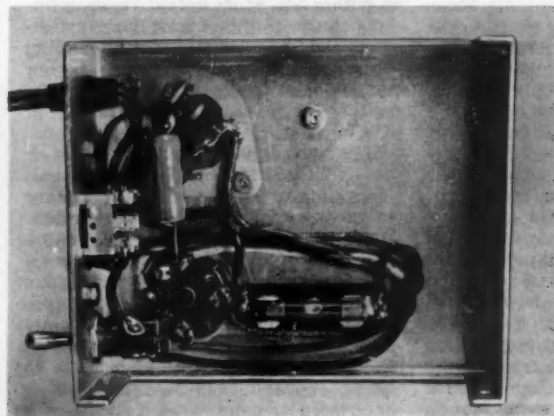


Fig. 3. Complete schematic diagram of audio amplifier and separate power supply.


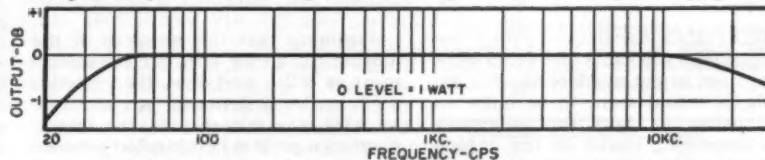


Fig. 4. Over-all frequency response of power amplifier. Zero level is at 1 watt.

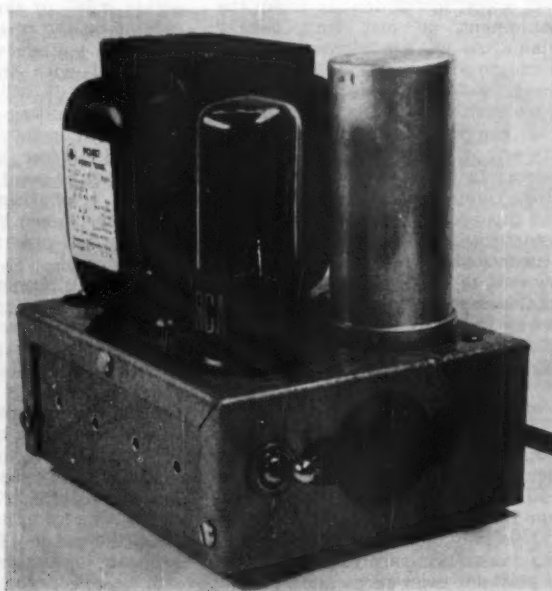



A discussion of various ways that circuit components in radio and audio equipment can be checked without trouble.

SOMETIMES the simpler things one encounters in radio and audio work are apt to get overlooked. For example, it would seem to be quite an easy matter to check the inductance of a smoothing choke or the capacitance of an electrolytic capacitor, with the correct polarizing current or voltage. However, when one looks around to find a test instrument to make the measurement, it just isn't readily available, so we are virtually forced into the routine of taking things for granted.

If we wish to check as to whether a certain component is functioning correctly or not, the only available method seems to be by substitution, using another component of the same type. Often this proves to be somewhat unsatisfactory, because the results can be inconclusive. We really need to know how to check the various fundamental components used in radio: resistance, inductance, and capacitance, to varying degrees of accuracy, according to their purpose.

Resistance Values

The simplest method of resistance checking is by means of a simple ohmmeter, either an instrument built specifically for this purpose or an ohmmeter range on a volt-ohm-milliammeter. Accuracy of this method of measuring resistance rarely exceeds 10% and may not even be as good as this.

Assuming that the accuracy of the moving coil meter used for the instrument is $\pm 2\%$ and that the resistors used in the instrument are accurate to $\pm 1\%$, the accuracy of the instrument as a perfect comparator between the internal and external resistances cannot be better than $\pm 1\%$. And the accuracy of comparison is only to within $\pm 2\%$ of the full-scale current reading on the scale. If the scale reading, on a voltage or current scale, is compared with the reading on the ohms scale, it will be found that an error representing 2% of full scale in voltage or current reading may amount to an 8% error in resistance value. This is at the point of maximum accuracy of comparison, between the external resistance being measured and the internal resistance of the instrument.


Thus it is seen that the best accuracy obtainable using an instrument with a $\pm 2\%$ movement and $\pm 1\%$ internal resistance gives a guaranteed accuracy at center scale reading of 9%. At readings between one-third and 3 times the resistance value, which is the range one might expect to use before switching to the next scale, the accuracy can reasonably be expected to stay within 10%. With an instrument using lower accuracy components than those used for illustration, the accuracy of the final reading in ohms will be considerably poorer than 10%.

From this it will be evident that an ohmmeter can only be used to make a rough check as to whether a resistance is within the preferred value range for which it is color coded—if it is of a $\pm 10\%$ or higher tolerance rating. To check that the resistance is within $\pm 10\%$ of its rated value, the result is a little doubtful and it is certainly impossible to rely on an ohmmeter reading to check to a tolerance of $\pm 5\%$ or closer.

Although the ohmmeter readings cannot be trusted for checking to close tolerances, it is possible to use an ohmmeter to check for reasonably good matching between pairs of resistors, if this happens to be the requirement rather than close precision in actual value.

As an example, in many push-pull amplifiers the resistors responsible for controlling the gain in the two halves of the push-pull arrangement must be closely matched to ensure balance. Production values may be specified to 5% or even closer tolerances, to avoid the necessity of having to select matched pairs, but the essential feature is that the value of the two corresponding resistors shall be within a close tolerance of one another. It will not necessarily matter if both of them are, say, 10% or 15% from their nominal rating, as long as they are within 5% of each other. This the ohmmeter is reasonably capable of checking, because it is quite possible to read an ohmmeter scale to within 5%. Since the question as to whether the reading is within 5% of its actual value is unimportant in this particular application, the significance of the reading does not matter as much as whether the two resistors which should be matched give readings within 5% of one another.

For some applications, however, such as calibrated attenuators or instruments for use in radio it is necessary to check resistor values to closer limits such as 5%, 2%, or even 1%, as the case may require. In these circumstances it is important that the value shall really be within the specified percentage of its rated value. The only method of making a measurement that is satisfactory for this purpose is to use a Wheatstone type bridge, using calibrated elements whose accuracy is

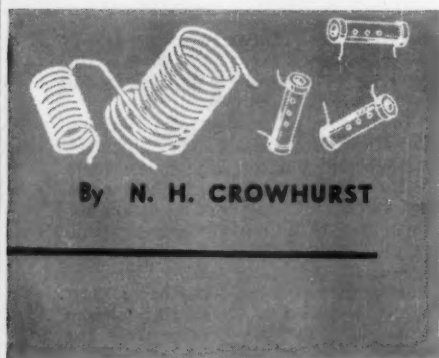

better than the required component accuracy.

For most radio purposes the *Leeds & Northrup* bridge used for telephone line work is quite accurate enough. In using a bridge there are two things that control the accuracy of the reading obtained: (1) the accuracy of the resistance elements of the bridge itself, and careful attention to see that contact resistance does not contribute an appreciable fraction under any circumstances; and (2) the sensitivity of the null detector.

This second cause of inaccurate results can be checked by unbalancing the bridge by a known percentage to see that an adequate off-balance reading is obtained. Suppose, for example, the value required is 120,000 ohms, $\pm 5\%$. Having balanced the bridge and obtained a null at, say, 120,000 ohms, the resistance in the calibrated arm should be altered by 5%, which represents a change of 6000 ohms.

If clicking in 6000 ohms additional in the calibrated arm shows appreciable deflection, then the reading may be regarded as accurate; but if the addition of 6000 ohms does not produce noticeable deflection from balance on the null detector, the result is not reliable. To improve its reliability one can either use a larger battery voltage or source of supply to the bridge, or else get a more sensitive null indicator.

Before leaving this discussion of resistance values it should perhaps be emphasized that it is not wise to put absolute trust in the color coding on a resistor. Occasionally even the best resistor will be found incorrectly color coded. If the error happens to be in the third color of the code, then the discrepancy in resistance value will be a matter of shifting the decimal point which can be quite serious. Also with some sets of coding colors the difference between some of the colors is somewhat difficult to determine, especially after the component has aged. For example, orange and brown can get to look quite alike.

Usually the first and second colors in the code can be identified by the combination used, from the recognized preferred value range. If the first color is blue, representing 6, the second color will most likely be either red, representing 2, or gray, representing

8, because 62 and 68 are the preferred values in the 60 to 70 range. But there is no such ready clue as to the likely color of the third band: it could just as easily be brown or orange. Thus a resistor in which this color looks at all doubtful could be either 620 ohms or 62,000 ohms, which is a considerable difference!

This is where an ohmmeter check can easily determine which of the two values is correct.

Inductance

Turning now to various kinds of inductance: the measurement of components not intended for the passage of d.c. and without iron cores is a fairly simple matter, with the aid of a conventional inductance bridge. Using such a bridge, employing either the Hay or Maxwell configuration (see Fig. 1), the inductance can be measured at a frequency suitable for the purpose, with a method quite similar to the operation of a bridge for measuring resistance.

The principal difference is that two kinds of adjustment are usually necessary to achieve null, because of the necessity for balancing the bridge in both amplitude and phase. This enables the bridge to give a reading of both inductance value and "Q" or loss factor. Bridges of this type are clearly marked to indicate the correct setting of the controls for making each kind of measurement.

There is usually no difficulty in achieving a null with the air-core type of coil, but if the inductance employs any kind of core, the null may not be quite as definitive, because of the distortion of the injected test signal caused by the core. Also, if the generator signal itself has any appreciable harmonic content, a Hay bridge will never give a balance at both fundamental and harmonics at the same setting. On the other hand, with an inductance where the only loss is due to its resistance, such as occurs in an air-core coil, the Maxwell bridge will give a fairly satisfactory balance for both fundamental and the lower harmonic frequencies at the same setting.

When measuring an inductor that employs any kind of core to increase the permeability, the magnetizing current is liable to distort so the inductor itself will generate some harmonics not present in the input from the generator. When the bridge is balanced to the fundamental generator input, there will be a residual harmonic present at the null point, generated by the inductor itself.

This is a good reason for using earphones if the generator frequency is in the audio range. Otherwise an oscilloscope with amplifier may be used as a null detector. It is then possible, listening to the tone or looking at the trace, to determine when the fundamental is balanced and the residue consists of harmonics.

But the conventional type of bridge is only suitable for measuring inductances where there is no polarizing

current. The usual variety of smoothing filter choke has to provide a specified inductance when polarizing current is flowing and the inductance in the absence of such polarizing current will be considerably higher than the rated inductance of the choke with polarizing current. Unfortunately there is no simple fixed relationship between these two values.

If the choke has been designed to provide its maximum inductance at the polarizing current for which it is designed, the air gap will be adjusted so that, at this value of polarizing current, either reduction or increase of the air gap would result in a reduction of inductance value. However, in the absence of polarizing current, increasing the air gap will *always* reduce inductance value, while reducing the air gap will *always* increase inductance value.

From this simple fact it is evident that measuring an inductance with no polarizing current flowing is no criterion of its performance with polarizing current. It can, of course, provide a check that the inductance is not

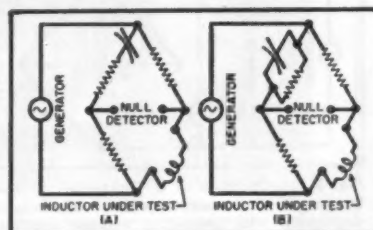


Fig. 1. Bridge configurations for measuring inductance. (A) the "Hay" bridge, (B) the "Maxwell" bridge. Relative advantages of each type are discussed in the article.


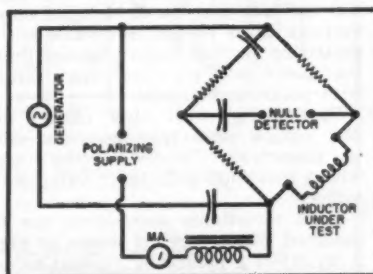


Fig. 2. Modification of the "Hay" bridge to enable it to measure inductance with polarizing current flowing. Care is necessary not to exceed the dissipation rating of the various bridge elements. See text.

Fig. 3. A simple inductance checker circuit for determining inductance with the polarizing current flowing in the component.

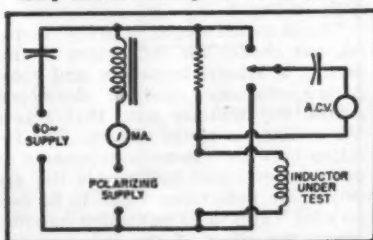

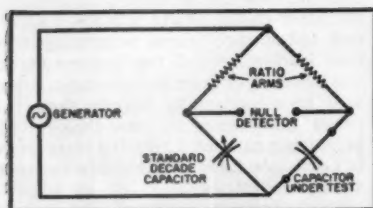


Fig. 4. The "Drysdales" bridge which is used for measuring capacitance. Refer to text.

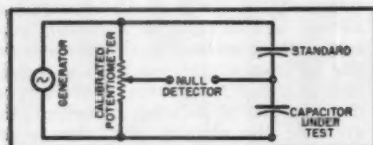


Fig. 5. A simple bridge for capacitor checking that forms the basis of a number of commercial units on the market. The null detector is usually a "magic eye" tube.

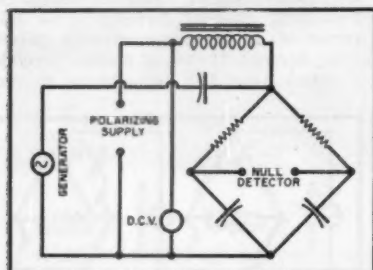


Fig. 6. Modification of a "Drysdales" bridge to permit the measurement of electrolytic capacitors with polarizing voltage applied.

completely missing, due to short-circuited turns, in which case the inductance might not even be adequate without polarizing current flowing. But the fact that the inductance may measure twice its required value with polarizing current is no evidence that the choke will give its rated value with polarizing current.

Fortunately, with filter chokes of this nature close tolerances are not too important. Usually a compliance with a minimum inductance value will suffice.

It is sometimes possible to use a modified Hay bridge, as shown at Fig. 2, to inject a polarizing current so as to measure the inductance with the polarizing current flowing. But this can be a dangerous procedure, because the polarizing current may exceed the wattage rating of some of the internal components of the bridge and cause permanent injury to it. It is, therefore, better to devise a simple checking arrangement, as shown schematically in Fig. 3.

This does not employ a bridge method, but checks the inductance by injecting a known frequency and comparing the a.c. voltage developed across the inductor with that across the resistor in series with it. The relation between the a.c. components of voltage developed will enable the approximate inductance value to be calculated. This does not take into account the effect of the inductor dis-

torting the waveform of the a.c. signal component, which invariably occurs in this type of inductor and is, in fact, another reason why any attempt to produce a precise figure of inductance will be somewhat meaningless. A rough check of this nature is quite adequate for the purpose.

If 60 cycles is the supply frequency for the a.c. component, dividing the calculated impedance of the inductor by 377 will give the inductance value. For example, suppose the series resistor used is 100 ohms (carefully checked in value), and the a.c. voltages measured across the resistor and inductor are 2 and 30 volts, respectively: then the impedance of the inductor at 60 cycles is 1500 ohms, representing approximately 4 henrys.

Capacitance

For measuring all except electrolytic capacitors there are two methods, which correspond in relative accuracy with the ohmmeter and bridge methods used for measuring resistance.

The Drysdales bridge (see Fig. 4) is a modified Wheatstone bridge, in which resistance arms are used in the ratio positions, while a calibrated decade capacitor is substituted for the calibrated resistance in the variable standard arm. This type of instrument can give capacitance results comparable to those obtained with the Wheatstone or Leeds & Northrup bridge for resistance, but its use involves careful adjustment of a number of controls until a null is achieved.

The alternative method of capacitance measurement also uses a bridge, but one in which the null is much more quickly achieved. In this bridge (see Fig. 5) a standard capacitor is used in one arm, the unknown capacitor in another arm, and a single potentiometer-type resistance for the other two arms. This resistance is calibrated on the basis of the ratio between the unknown and standard capacitors necessary to achieve null.

With this type of bridge the unknown capacitor is connected across the terminals of the bridge and the one dial turned until null is indicated. The capacitance value is then read off the dial. The accuracy of this type of instrument is usually comparable to that of an ohmmeter, depending upon the accuracy with which the potentiometer type resistance has been calibrated.

Neither of these methods is really satisfactory for the measurement of

electrolytics. This can better be understood by discussing a little further the behavior of electrolytic capacitors under different conditions.

In the first place, electrolytic capacitors freshly formed ready for use, have a dielectric film on the active plate of the correct thickness for the working voltage. Under this condition the capacitor should have its rated capacitance.

But if the capacitor is operated consistently at a lower polarizing voltage, the thickness of the formed film will gradually deteriorate with the result that the effective capacitance will increase somewhat. This is not necessarily detrimental to the performance of the capacitor, provided it is not subsequently required for service at its nominal working voltage.

In much the same way electrolytic capacitors kept in storage also show a deterioration in the dielectric film resulting in an increase in effective capacitance. This means if a six-month-old capacitor is taken from the shelf and measured on a regular capacitance bridge, without applying the necessary polarizing, it will probably show a value considerably in excess of its nominal value. However, it will not be satisfactory for operation until the electrolytic film has been formed up to the requisite thickness for its working voltage.


This will have to be done with the aid of a limiting resistor connected in series with the capacitor to limit the polarizing current while the film is forming. Only when the film has formed up so the voltage appearing across the capacitor is at its working value without excessive leakage current can its capacitance be measured to give a reliable indication of its operating condition.

Also, if the capacitor is to be installed in a piece of equipment for operation at its nominal working voltage, it is vital that this reforming of the capacitor be performed before installation, so the capacitor does not take an abnormally high leakage current when the power is switched on and possibly destroy itself before it has had a chance to become correctly reformed.

The correct measurement of electrolytic capacitors with polarizing voltage applied can be undertaken with either type of bridge, modified to a certain extent, as shown in the schematics of Figs. 6 and 7. If the actual capacitance value of an electrolytic capacitor is not vital, which often is the case, then all that is necessary in installing a new one is to ensure that it is correctly formed to its working voltage before connecting it in. This may be done with the aid of the circuit shown in Fig. 8, which consists of a high resistance feeding the capacitor with a voltmeter across it to indicate when working voltage has been reached. The resistor limits the leakage current through the capacitor to well within the maximum leakage

(Continued on page 185)

Fig. 7. Modification of the simple bridge of Fig. 5 to enable polarizing voltage to be applied to the electrolytic capacitors.

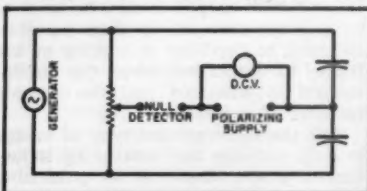


A Simplified Automatic Tone Compensator


By

ED. C. MILLER

Tech. Dir., Inland Broadcast Co.

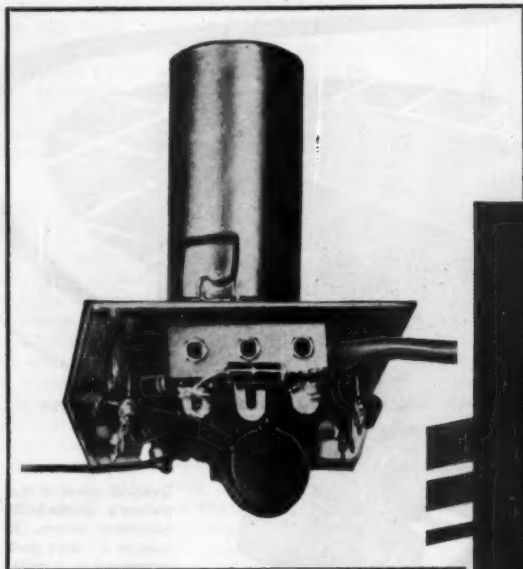

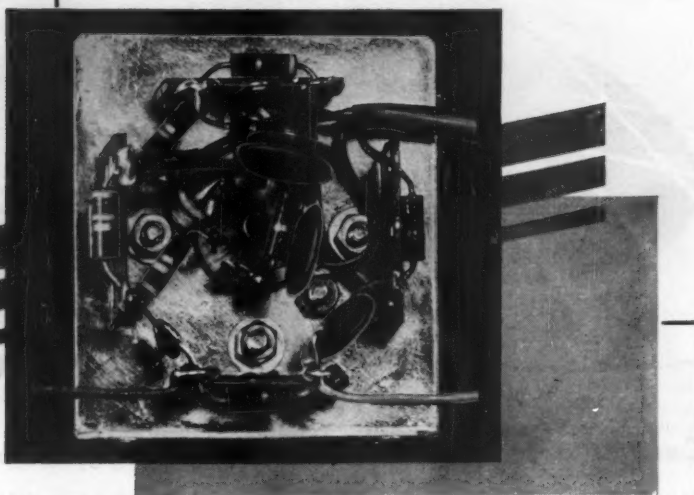Two views of the automatic tone compensator. It is built on a small sub-chassis which can be put into amplifier chassis.



Details on a one-tube device which automatically boosts bass response at low audio levels. It is easy to build.

SINCE the appearance of the author's previous article on "The Auto-Tone" (RADIO & TELEVISION NEWS, April, 1954, page 54), many letters have been received asking for information on a less critical and more easily built device to provide automatic bass boost at low volume levels. This article covers such a circuit, reduced to its simplest practical form.


The unit shown in the photographs and schematically in Fig. 1 differs from the previous automatic tone control in many ways besides being of much simpler construction. Most significant, probably, is that because the control tube uses bias increasing in a negative direction with the application of signal, the control capacitor is in series with the plate impedance of the control tube, rather than in parallel. Fig. 2 is the equivalent circuit, with R_1 inserted in place of the plate resistance of the control tube. If capacitor C in Fig. 2 is selected so that its reactance is large in relation to R_1 at some frequency under consideration, changing the value of R_1 will have little or no effect on the output. But if the reactance of C is small in relation to R_1 , and R_1 is at all times less than R_2 , then changing the value of R_1 will have a marked effect on the

output at that frequency. As the reactance of a capacitor increases with a decrease in frequency, maximum control will take place at the higher frequencies.

In effect, what we have is a volume expander that for a given range of input levels provides more expansion at the higher frequencies than at the bass frequencies. By proper selection of component values, a satisfactory expansion rate can be had that will be the same rate at all frequencies above about 500 cycles, with as much as a 2 or 3 to 1 reduction in rate at 50 cycles.

At first it may seem improper to use volume expansion as a type of control. Actually, it is one of two choices: 1. linear reproduction of the middle and high range of audio, with compression of the bass frequencies at higher volume levels; or 2. linear reproduction of a particular bass frequency with expansion of the middle and high frequencies. The use of the latter method adds about 15 db to the dynamic range of recording, if it is used with commercial pressings, and a similar amount of dynamic range increase in radio reception also (to a somewhat lesser extent, due to the sharp knee

(Continued on page 160)

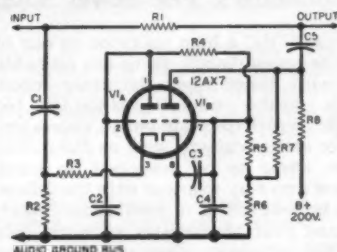

R_1 —2.2 megohm, $\frac{1}{2}$ w. res.
 R_2 , R_3 —470,000 ohm, $\frac{1}{2}$ w. res.
 R_4 , R_5 —1 megohm, $\frac{1}{2}$ w. res.
 R_6 , R_7 —4.7 megohm, $\frac{1}{2}$ w. res.
 R_8 —15,000 ohm, $\frac{1}{2}$ w. res.
 C_1 —500 μ fd., 400 v. capacitor
 C_2 , C_3 , C_4 —0.02 μ fd., 400 v. capacitor
 C_5 —0.005 μ fd., 400 v. capacitor
 V_1 —12AX7 tube

Fig. 1. Complete schematic of the automatic tone compensator. Parts are standard.


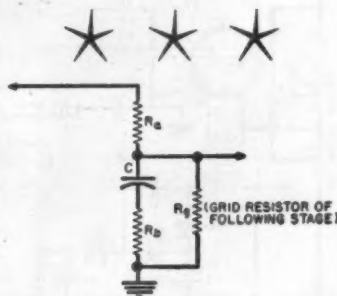


Fig. 2. Equivalent circuit to that of Fig. 1.

Miniature Scope for the Hamshack

By ROB WAGNER, W6WGD

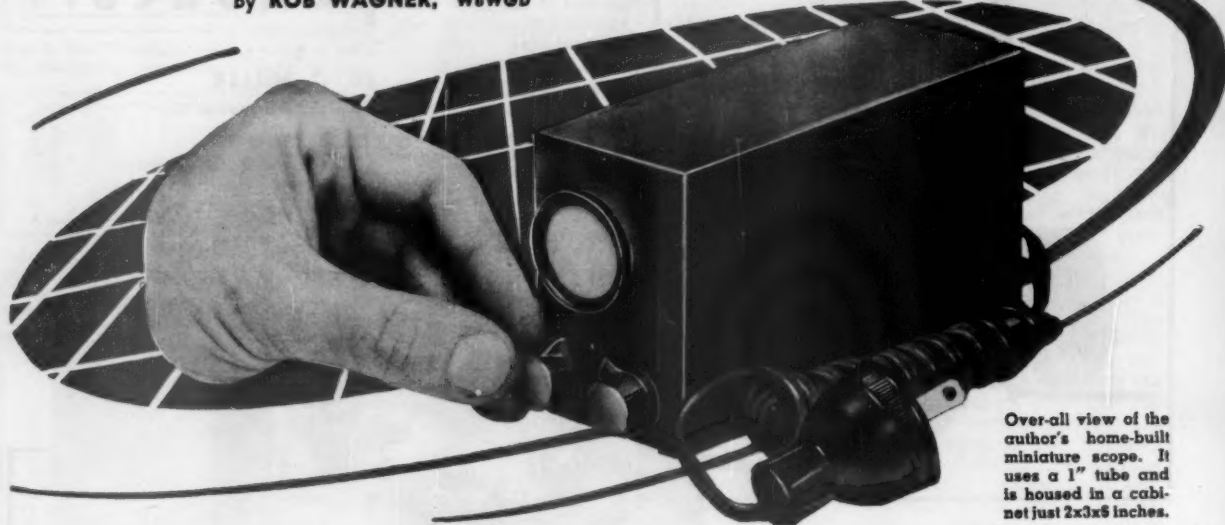

Over-all view of the author's home-built miniature scope. It uses a 1" tube and is housed in a cabinet just 2x3x5 inches.

Construction details on compact unit for checking AM phone transmitters. The power supply is included on same chassis.

IF YOU'RE a ham operator on one of the phone bands, there are probably many times when the other fellow tells you the modulation is too low, too high, or perhaps plain lousy! Unless you have an instrument such as the miniature scope to be described on hand, there's no way to argue with the fellow. To be assured of a good audio report, adjust your transmitter with the help of this simple oscilloscope, which uses a minimum of parts and the one-inch 913 tube, or any of the other small scope tubes presently available. Then

it will be constantly apparent that the rig is correctly adjusted, not only for satisfactory amplitude, but with respect to proper operation of the transmitter itself.

Electronic Description

Fig. 1 is the schematic diagram of the instrument. Simple, isn't it? By limiting the scope's function to trapezoidal (triangular) presentation, a minimum of parts is required.

The one-inch 913 makes miniaturized construction possible, although the

two-inch 902 or 2AP1A tubes are electrically interchangeable with the 913.


The 913 plugs into a standard octal socket. The 6.3 volts a.c. come from T_1 , a small 0.6 ampere transformer, obtained from your junk box or supply house. Because oscilloscopes require extremely small current at relatively high voltage, there's no necessity for a power transformer in this circuit. The circuit utilizes a voltage tripler power supply operating directly from the 117-volt a.c. line. It delivers about 325 volts d.c., allowing an adequately bright screen presentation.

SR_1 , SR_2 , and SR_3 are small selenium rectifiers visible in Figs. 2 and 3. In the author's model, IRC #U15HM miniature rectifiers are employed; their ratings are 360 volts peak at 1.5 milliamperes. These units are more difficult to obtain than their slightly larger counterparts specified in the parts list.

Capacitors C_1 , C_2 , and C_3 , in conjunction with the rectifiers, form the high-voltage, low-current internal supply.

Note that the positive voltage output grounds to the chassis, because the scope cathode operates at negative potential with respect to the other elements. These, the control anode and focusing anode, are controlled with less negative amounts of potential derived from the voltage divider, R_1 , R_2 , and R_3 .

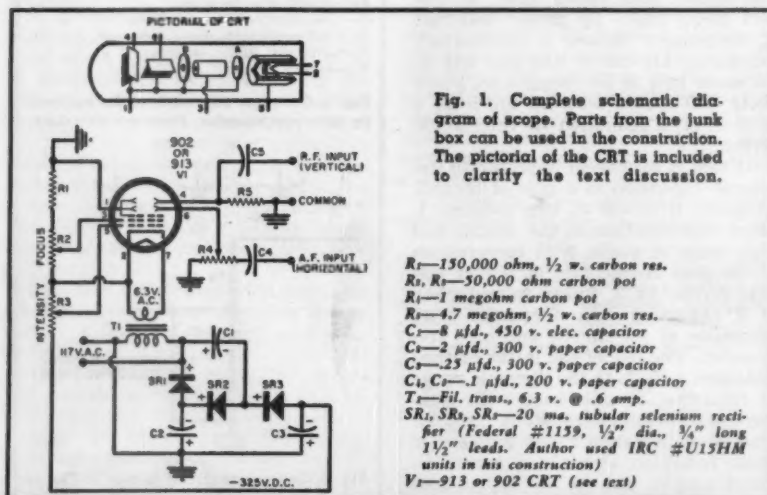R_1 , a 150,000-ohm, $\frac{1}{2}$ -watt resistor, forms the divider's fixed element. The 50,000-ohm potentiometer, R_2 , serves as the focus control, and spot intensity is varied by the second 50,000-ohm pot, R_3 . Very little current flows through the voltage divider allowing R_1 and R_3



to be midget carbon pots, the surplus items visible in Fig. 3.

R_1 is a 1-megohm carbon pot used to vary the amount of external audio voltage applied to the horizontal deflection plate. The blocking capacitor, C_1 , isolates the modulator's high voltage d.c., and C_2 prevents the r.f. pick-up link from being a d.c. closed circuit. R_2 maintains the vertical deflecting plate at the same d.c. potential as its grounded partner. R_3 serves the same purpose for the horizontal plate, in addition to its function as a "Horizontal Gain" control.

Theory of Operation

If you're not familiar with the oscilloscope's function, the following paragraphs may help toward an understanding of how the tube operates in this basic circuit.

Refer to Fig. 1, where the tube schematic is shown in pictorial form. In the smaller CR tubes, the cathode is internally connected to one side of the heater (2). When heated by the filament, the cathode emits electrons, which pass through a small hole at the center of control electrode (5). By varying R_4 , the bias on (5) can be made more negative than the cathode, thus controlling the number of electrons which pass through and, consequently, the intensity of the electron beam.

Shown as (A), the #1 accelerator anode operates at high positive voltage with respect to the negatively charged cathode electrode. (A) pulls the beam forward and through, giving it a push toward the tube's front.

The electron stream then passes through the focusing anode (3), which functions by a process of electron optics too complicated to discuss here. For all practical purposes, the procedure may be considered analogous to optical light focusing.

Accelerator anode #2 (B) operates similarly to (A), giving the pinpointed electron beam another shove toward the screen. The beam now passes between the deflecting anodes and strikes a fluorescent coating on the rear of the glass screen. The coating glows visibly when electrons strike it.

The electron beam may be either attracted or repelled by an electric field. When a.c. is applied to the horizontal deflecting plate (6), the first half-cycle being positive pulls the spot to the right, and the second negative half-cycle pushes it back to the left. Alternating voltage on the vertical deflecting plate (4) moves the spot up and down in the same manner.

The r.f. voltage applied to (4) oscillates between plus and minus at millions of cycles per second, thus the spot's motion is invisible, and a straight line (Fig. 5J) appears. The same is true of an audio frequency fed to (6), except as follows:

When r.f. and audio voltages are applied simultaneously from a plate-modulated transmitter as shown in Fig. 4, the spot moves very rapidly in complex directions, and a solid fluores-

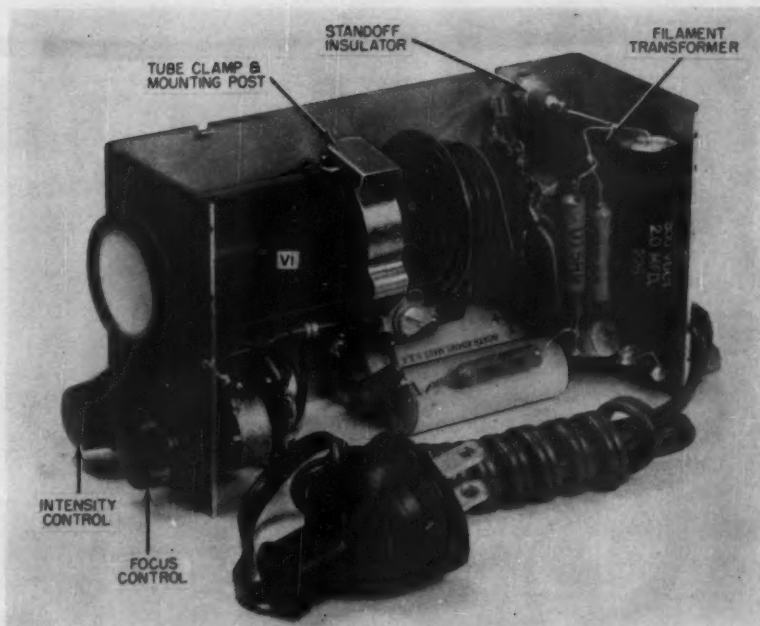


Fig. 2. Internal view of scope. Three units at right-hand edge and bottom center are tubular selenium rectifiers. Small stacked units may also be employed here.

cent pattern appears on the screen. These patterns and their causes are discussed in the Applications section following Construction Details.

Construction Details

The scope, complete with power supply, is built within a two-section box chassis measuring 2 x 3 x 6 inches. Fig. 2, the box with cover removed, shows details of assembly. A hole large enough to allow insertion of the 913 through the front panel supports the tube at its front end. A standard octal socket plugs onto the tube's prongs,


and is not mounted at the rear, because the tube must be rotated until its horizontal and vertical axes occur at the proper angles. The socket wiring hangs loosely to allow this positioning.

A tube base clamp snaps around the tube's metal body, and mounts on a stud secured to the box's base. When the snap is loosened, the tube may be rotated to the correct viewing angle, then locked into position by the clamp.

The filament transformer mounts directly behind the tube socket on the chassis' rear wall, as seen in Fig. 2.

(Continued on page 186)

Fig. 3. Bottom view of instrument. The horizontal amplitude control, potentiometer R_1 , is screwdriver-adjusted through a hole between focus and intensity controls.

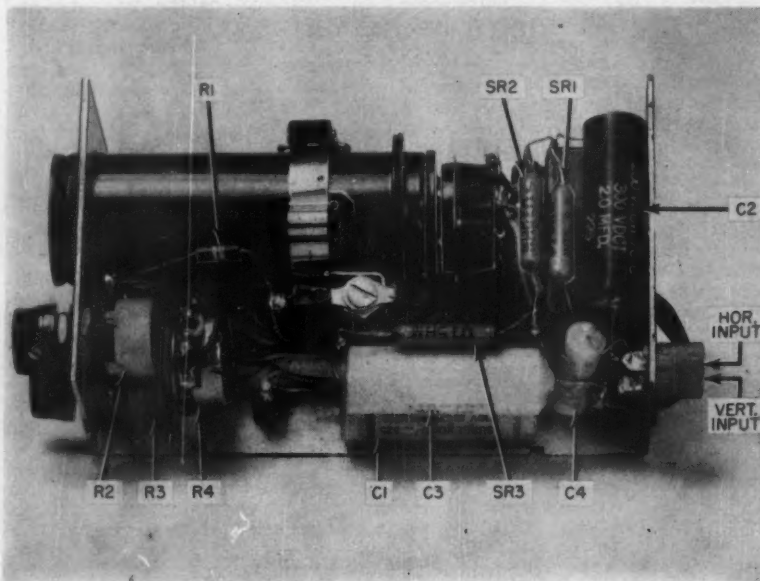

Behind the Giant Brains

By FRANK LEARY

Typical of the 700 series of scientific and commercial computing systems now being produced by International Business Machines is the IBM 701, which was also the first of the series. Primarily a scientific computer (the commercial members of the family are the 702 and 705), the 701 is extremely fast in computing speed, but limited in flexibility, since it depends primarily on punched cards for input.

Part 2. Advantages and characteristics of electronic computers, along with a general survey of the field and some predictions of the future effects on us all.

LAST month we discussed the development of the computer and its basic functions. Now we proceed with the advantages and a survey of the field.

The reason computers are valuable, and increasingly more valuable, in our time, has nothing to do with their innate ability, which is extremely limited. It has to do with their speed, which is fantastic, and their relative reliability.

A man figuring out his own pay, for example, might spend five minutes or more multiplying rates by times, computing and subtracting deductions, and finally arriving at his salary figure. A desk calculator permits him to reduce this to about two minutes. A punched-card calculator could make the same computations in a few seconds. An electronic computer like "Univac" could do the same work in less than a tenth of a second.

The man may tire of doing this work in an hour; certainly by the end of a day most men would be bored beyond distraction. Industry has discovered that most people cannot perform such repetitive work for more than three or four hours at a stretch without a sharp rise in the incidence of error. Machines, whether mechanical or electronic, never tire, never need to break for coffee or lunch, and never get bored; but after a few thousand opera-

tions, mechanical parts begin to wear. Electronic tubes can be slammed from cut-off to saturation millions of times a second (as they are in many electronic computers), and still operate for months without fatigue; new developments in electronics indicate even higher orders of efficiency. Solid-state circuitry, such as the transistor and Sperry Rand's still-newer "Ferractor," seem capable of almost limitless operation without fatigue. So, just as a mechanical device is better than a human being for repetitive tasks, an electronic device is usually better than a mechanical one; it lasts relatively longer at a high operating efficiency.

Programming a Computer

The first requirement for any job that is to be done by a computer is that it be capable of precise description. Or, as Dr. John Mauchly, co-inventor of ENIAC and "Univac," once remarked, "any activity that can be precisely described can be done by a machine. You're already well on your way to designing the machine in formulating the description." If anyone could analyze and define the complex operation we know as thinking, for example, the engineers could develop a machine to do it for us. Until that time, the name "thinking machine," or the concept of machines that think, merely wastes time.

Putting a job on a computer first requires a complete analysis of the job, and an exact definition of its scope. Then every step that a human being performs in doing the job, every decision he makes, every value he weighs, must be translated into terms that the computer can recognize, steps that the computer can recognize, steps it can perform, or values it can weigh. A complete listing of the step-by-step instructions, recognizable to the computer's blind and dumb hardware, must be drawn up. Then the computer can do the job.

This operation, consisting of the analysis of the problem and the synthesis of the instruction routine, is known as programming. As is perfectly clear, the computer's decisions are really the programmer's decisions; its criteria for evaluation are given to it by the programmer.

Drawing up such a program can be a costly and time-consuming job. That is why advanced programmers concentrate some of their efforts on a technique called automatic coding, which gives the computer a library of simple, frequently used, chunks of programs, and makes it collaborate in the formulation of its own program of instructions.

It is also the reason why "repeatability" is one of the major criteria for determining which jobs will be done by a computer. The cost of making the program can be amortized if the job is to be repeated over and over again. A company payroll, for example, which must be computed every week or two, is a far more likely candidate for mechanized or electronic treatment than is the design of the earth satel-

lite; but many of the myriad computations incident to the satellite design are being done by computers simply because of time a computer can save.

The Field Today

There are still some companies—but their numbers are decreasing—who are reluctant to submit their paperwork problems to electronic treatment, some because they do not trust the machines, others because they are not convinced of the economies of electronics. That computers are economical when the job is big enough is now an established fact. Evidence of the economies of electronic data-processing has been available ever since the first "Univac" was bought by the Census Bureau more than five years ago. The evidence is growing daily. And the acceptability of electronic record-keeping has even been tested—and accepted—in the courts.

The manufacture of electronic computers and computing systems has become a major industry, and a hotly competitive one, too. Led by *Remington Rand's* "Univac," which, started in 1949, was the first production-designed business computer on the market; and by *International Business Machines*, which has concentrated millions of dollars in the design and production of its 700 series of computing systems, the industry has grown in very few years to become a giant. Some fifty companies are now manufacturing complete electronic computer systems or major systems components such as high-speed magnetic-tape units, magnetic-drum storage systems, instrumentation and data-presentation systems, and so forth. Business machine manufacturers, such as *Underwood*, *Burroughs*, *National Cash Register*, and *Royal-McBee*, and electronics manufacturers, such as *RCA*, *Philco*, *Raytheon*, and *General Electric*, have all contributed to the progress. And no one can overlook the contributions made by the *Bell Telephone Laboratories* in basic research and logical design of information-handling systems.

Business and industry are gradually accepting the machines. Not considering the countless analogue computers in use all over the world, and in Army, Navy, and Air Force fire-control and missiles-control equipment, the big digital computers alone—million-dollar systems all—form an impressive roster: *Remington Rand's* fifty-odd "Univacs"; *International Business Machines Corporation's* seventy-odd 701's, 702's, 704's, and 705's; *Burroughs Corporation's* two UDEC's and a scattered shot of university, research center, and one-time industrial designs. And within not too long we can expect to see *RCA's* "Bizmac"; the "Datamatic 1000," being built by the joint efforts of *Minneapolis-Honeywell* and *Raytheon*; and *Remington Rand's* much-heralded LARC, which was "commissioned" by the *Livermore (Calif.) Atomic Research facility*.

This besides the increasing flow of small systems, such as *Burroughs' E101*, *National Cash's* CRC series, *Un-*



The Burroughs-built UDEC (Unutilized Digital Electronic Computer), shown in the Wayne University's Computation Laboratory in Detroit. This computer, also basically a scientific computer, is much used by the automotive industry for engineering problems.

derwood's "Elecom" 50, *Remington Rand's* "Univac" 60 and 120, *IBM's* CPC, 607, and 604; and the medium-sized systems, such as the "Univac" File-Computer, the "Elecom" 125, *IBM's* 650, *Burroughs' "Datatron,"* and many more. These compact and efficient machines are bringing the advantages of electronic data-processing to the small and medium-sized business. The market is ripe for the computers, and more companies enter the field daily.

And Tomorrow

Communications is also becoming an increasingly important consideration,

and *Western Union* and *AT&T*, on the one hand, and the computer makers on the other have cooperated on a number of plans to facilitate the transmission of data from place to place. These plans range from the conversion of data to telecommunications code and regular transmission over ordinary telegraph wire, to the direct transmission of the very-high-speed computer codes over special coaxial lines.

Naturally, all the activity has strained the creative facilities of the small nucleus of scientists and engineers who first launched the computer

(Continued on page 114)

New markets for computing systems are being tapped by the medium-sized general-purpose computer, typified by *Underwood's* Elecom File Processor. The Elecom system reduces the contents of 1600 conventional file drawers to less than three cubic feet of space; savings in space such as this, added to time saving, plus the different kinds and configurations of management information which computers provide, have given impetus to the furor of interest in electronic computing.



Subminiature Construction Techniques for the Home Builder



Fig. 1. A representative selection of the subminiature components that are now available at parts jobbers. Parts illustrated are fully described in the article.

By LOUIS E. GARNER, JR.

The availability of these tiny parts makes it possible for hobbyists with limited space to build electronic equipment.

FOR some time, the average home builder or electronics experimenter has followed a rather general path as he acquired greater skill and ability in his hobby. Starting with simple one- and two-tube receivers or amplifiers, the builder would work into more and more complex (and larger) equipment, eventually building such items as ten- to fifteen-tube communication receivers, complex test equipment, hi-fi audio amplifiers, and television receivers. Almost every hobbyist has, at one time or another, reached the point where "what to build next?" becomes an important problem.

Today, however, with the increasing availability of miniature and subminiature components, an entirely new construction field has opened for the experimenter— assembling subminiature equipment. Nor is this field restricted only to the experimenter; hams will find that the construction of subminiature receivers and transmitters offers a real challenge to their skill, hi-fi "bugs" can apply subminiature

construction techniques to the assembly of compact preamplifiers, and technicians will find that subminiature test equipment reduces the weight and space requirements of equipment that must be "toted" to a customer's home.

In addition to the advantages just outlined, assembling subminiature equipment is the ideal solution to the problem of the experimenter who lives in an apartment and has limited space at his disposal. The equivalent of a "shop full" of tools may be carried in a large briefcase. Enough components to assemble several receivers and amplifiers may be easily stored in a cigar box and a coffee or end table offers ample working area for most projects.

Subminiature Components

Recently subminiature components have become widely available at local radio-electronic wholesale supply houses. Previously, such parts were so difficult to obtain that the would-be builder soon gave up in disgust. Today most of these components may be pur-

chased across the counter as stock items. A few still have to be obtained on special order, but delivery time is now reckoned in days rather than in weeks and months.

A sample selection of components that were purchased at a local radio wholesaler is shown in Fig. 1. The 6" rule in the photo illustrates the sizes of the components shown.

Across the back is shown (from left to right) Burgess No. 7 and type Z penlite cells and Mallory RM-12 (RM-1200) and RM-4000 mercury cells. These cells are generally used as "A" batteries in subminiature equipment. Also shown is a Burgess U10, 15-volt hearing aid battery and a Burgess U20, 30-volt hearing aid battery. Batteries of this type are used as "B" supplies.

On the left side is shown (from top to bottom), a Centralab PC-201 3-stage printed circuit audio amplifier, two types of "subminiature" tubes with their corresponding sockets (a Sylvania type 1E8 and a Raytheon type CK512), a printed circuit "Couplate," a standard 1/2-watt carbon resistor, and a miniature volume control (Centralab type B16-224). The miniature volume controls are available in a number of resistance values and both with and without switches.

On the right side of the photograph is shown a small iron-core audio transformer, a miniature ceramic coil form, a miniature tuning capacitor, a miniature "metallized" paper capacitor (size shown is .25 μ fd., 200 volts), a miniature tubular paper unit, and a disc ceramic capacitor. The small iron-core audio transformers are available from a number of manufacturers, although the UTC SO (Sub-Ouncer) and SSO (Sub-Sub-Ouncer) series are the ones most often carried in stock by local suppliers.

Millen manufactures the miniature ceramic coil form shown and can supply these forms with either adjustable iron cores or brass slugs as stock items. The tuning capacitor shown is also a stock item and is manufactured by the E. F. Johnson Co. A type 20M11 is shown (2.6-19.7 μ fd.).

Large-capacity, small-size metalized paper capacitors are made by a number of manufacturers and stocked by most suppliers. A *Pyramid* type MT capacitor is shown in the photograph as representative.

In addition to the above the photo shows a miniature two-conductor jack (*Walsco* type 791) and a midget ear-set (*Telex* No. A4680). Again, both of these are stock items.

In addition to the items shown, there are a number of other miniature and subminiature components available that might appeal to the specialized builder. Such items include miniature sensitive relays hardly bigger than a standard miniature tube (such relays are manufactured by *Potter & Brumfield*). However, the items shown in the photograph are those most likely to be encountered as "stock" items at local distributors.

Tools

The builder of subminiature equipment will find it worthwhile to obtain tools that fit in best with his hobby. A typical assortment of tools is shown in Fig. 2.

The collection shown includes a *Casco* power tool with an assortment of accessories, including drills, brushes, slitting saws, etc. A set of *Moody* jeweler's screwdrivers is shown in the background. On the right is a set of jeweler's type pliers manufactured by *Kraeuter* and purchased by the author at a local radio wholesalers. Included are "dikes," "long-noses," and other useful pliers.

In the foreground are shown an *Ungar* pencil iron with small tip, a magnifying glass, a small triangular file, a small rat-tail file, a pair of tweezers, and a penlite.

Another useful tool, not shown in the photograph, is a small bench or hand vise. If a vise is not available, a small C-clamp may sometimes be used instead.

Materials

Some of the materials used in the assembly of subminiature equipment are illustrated in Fig. 3. Included are service cement, Bakelite cement, *Scotch* tape, *Scotch* electrical tape, rubber cement, a small aluminum box (*Bud* "Minibox"), a small plastic box, sheets of Bakelite and plastic, plastic tubing and rods, aluminum foil (used for shielding), small wire and spaghetti tubing, and small size machine screws and nuts (the "large" screws are size 4-40, the smaller ones size 2-56).

Not all the material shown may be available at local radio supply houses, and it may be necessary to go to a plastics "hobby" shop to obtain a supply of plastic sheets, rods, and tubing. Aluminum foil may be obtained at many drug stores and at most supermarkets. Rubber cement can be obtained at dime stores or stationery stores. Small machine screws and nuts may generally be purchased at hardware stores. The prospective builder



Fig. 2. Some of the tools that the builder of subminiature gear will find useful. Shown are power tool, jeweler's screwdrivers and pliers, soldering pencil, etc.

will find it convenient to purchase corresponding taps and dies at the same time.

In addition to the material shown, the builder will find it worthwhile to check through the small parts assortments offered in packages by most radio parts wholesalers. Assortments of small brackets, springs, and similar components often prove handy when assembling equipment.

Small diameter wire is likely to prove a little difficult to obtain in some cases, for many radio wholesalers do not stock wire smaller than #20 or #22 gauge, and these sizes are considered as "bus bars" in some types of subminiature construction work. However, it is often possible to "manufacture" small sized wire by removing individual strands from large size stranded wire and using small diameter plastic spaghetti tubing as insulation.

Although the basic methods used when designing subminiature electronic equipment are the same as those used when designing conventional sized equipment, there are certain special considerations that must be kept in mind.

First, since most subminiature equipment is self-powered, using small


batteries, it is necessary that the current drains be kept to a minimum to insure long battery life. Tubes or transistors should be selected so that optimum performance at minimum battery drain is obtained. As few parts as are necessary to accomplish the builder's minimum requirements should be used.

An example is in the design of audio amplifiers. While most conventional audio amplifiers are designed to have considerably more than the average gain needed, so that gain controls are left near "zero" in most work, it is not unusual to find a subminiature audio amplifier with the gain control usually adjusted almost to "full gain" as a normal operating condition.

This requirement makes it imperative to avoid the use of power amplifiers unless absolutely necessary, and here only to drive an earphone. While it is possible to build a subminiature amplifier with sufficient output power to operate a loudspeaker, this may result in the production of signal distortion.

The compact construction necessary in subminiature equipment requires small coils with, usually, high distributed capacities to ground. These factors lead to low "Q" circuits. Because

Fig. 3. "Accessory" items used in assembling small equipment. Service cement, Bakelite cement, *Scotch* tapes, aluminum and plastic boxes, foil, tubing, etc. are shown.

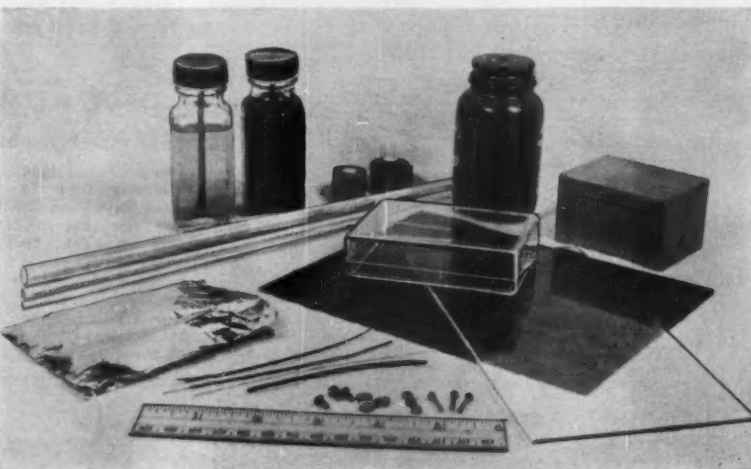

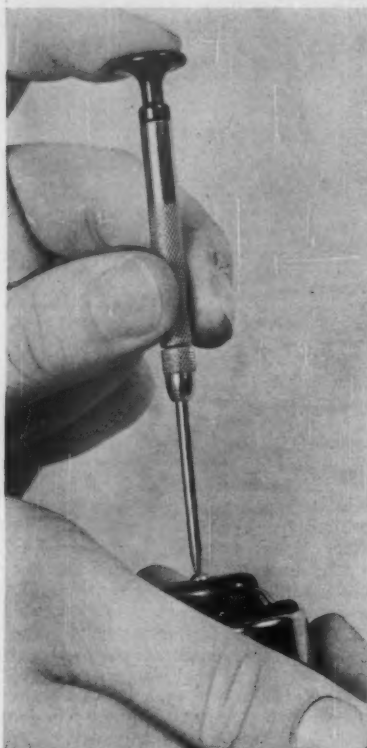


Fig. 4. One technique for working with subminiature parts. A jeweler's screwdriver should be used on small machine screws.

of this, r.f. circuits selected for subminiature assembly must be capable of operating satisfactorily with low "Q" coils. With subminiature-type tubes, "B" voltages as low as 15 volts may often be used, while a "high B" voltage is 45 volts. This makes it necessary to select circuits which can operate with very low "B" voltages, and sometimes makes an additional stage necessary to obtain sufficient over-all gain.

The builder of subminiature equipment will also find that "high fidelity" is actually difficult to achieve except in resistance-coupled stages due to the small amount of iron used in the miniature audio transformers.

Better results with subminiature

r.f. circuits will be obtained if the builder chooses parts designed specifically for the type of work contemplated. Check through the characteristics carefully before picking a particular component.

Wiring Techniques

A small "pencil" type soldering iron with a $\frac{1}{8}$ " tip will be found satisfactory for most subminiature wiring. The iron should be kept well tinned.

Most connections are made by pre-tinning the components to be wired and using simple "lap" joints, applying the iron only as long as is necessary to flow the solder. Care should be taken not to overheat subminiature components.

Some builders prefer to clamp the soldering iron in a small vise and to hold the subminiature assembly or components to the iron tip, as illustrated in Fig. 5. Note that this technique is just the opposite to that employed in wiring conventional sized equipment. If this method is used, be careful when clamping the iron in the vise. Use enough pressure to hold the iron securely, but remember that too much pressure may damage the iron.

Point-to-point wiring is generally used in subminiature construction in order to reduce over-all space requirements.

Tubes are sometimes wired directly into the circuit while, at other times, the special subminiature sockets are employed. The choice of which to use is a matter of individual preference.

Construction Practices

The builder contemplating subminiature construction should spend a little time becoming familiar with the tools used (Fig. 2). Somewhat greater skill and patience is required when working with subminiature components than is necessary when working with "full-sized" equipment.

Special care is required when working with small machine screws and the use of a "jeweler's" screwdriver is almost mandatory. One technique for using such a screwdriver is illustrated in Fig. 4 (the author is left-handed). Note that this technique makes it virtually impossible to apply very much twisting force to the screw-

driver handle, thus avoiding any tendency to bend the screwdriver blade or to "strip" the threads of the small screws used.

It is customary to mount many parts (even including small iron core transformers and complete printed circuit amplifiers) simply by cementing them in place, using either *Duco* cement or regular radio service cement.

When it is desired to keep a plastic surface free from scratches during construction work and layout, plain white paper may be cemented to the surface using rubber cement. All layout may be made directly on the paper, using a lead pencil. Once the construction is completed, the paper may be "peeled" off, with excess rubber cement removed simply by rubbing it with a finger.

Subminiature equipment is more often assembled in plastic cases than in metal because of the greater ease of mounting parts (using cement) and of avoiding wiring shorts. Where shielding is necessary, two techniques may be employed; one is to mount the plastic cased assembly inside a larger metal case, the other is to cement aluminum foil to the plastic case as a close fitting shield. "Heavy" grade aluminum foil should be used.

When working with plastics, an ordinary scratch awl makes an admirable "center punch" for small holes. Hand pressure is generally all that is needed to make a good sharp impression in most plastic materials to guide the drill.

It is generally not practical to "punch" large holes in plastic. Rather, a large drill or a series of small holes around the circumference of the large hole may be used instead, with the final "sizing" obtained with a file or pocket knife. Still another technique (generally used by the author) is to lay out the desired hole and then to use one of the "carving" bits of the electric power tool set to cut out the plastic.

Conclusion

Subminiature construction offers interesting possibilities to the electronics experimenter, ham, or home builder. Very little space and no "heavy" equipment is required.

As far as cost is concerned, the builder will find that individual items are generally somewhat more expensive than their counterparts in conventional sized equipment; however, the total cost of components for a finished piece of equipment is likely to be no higher than its full-sized "equivalent." This is due primarily to the use of batteries in place of expensive a.c.-operated power supplies and filter circuits.

Construction projects are numerous, being limited primarily by the ingenuity and interest of the builder. Typical projects are hearing aids, small pre-amplifiers, "vest-pocket" broadcast receivers, miniature transceivers, and transmitters (for licensed hams), vibration pickups and amplifiers, etc.



Fig. 5. Pencil type soldering iron is ideal for subminiature electronic construction work. To avoid damage to components, iron can be clamped in a vise—with part brought to the tip instead of usual technique.

ROHN

Give what the buyer
WANTS

**HOT
DIPPED
GALVANIZED**

**UNEQUALLED
DESIGN!**

**LIFETIME
OF
DEPENDABLE
PERFORMANCE**

These 3 BIG sales features are ROHN Exclusives... features that have been proved positively. Sell—recommend—install ROHN... the world's largest manufacturer of this type of tower... you have the BEST by far!

ROHN Manufacturing Co.

116 Limestone, Bellevue Peoria, Illinois Ph: 4-9156

MAIL THIS COUPON FOR FREE LITERATURE

Rohn Manufacturing Company
116 Limestone, Bellevue
Peoria, Illinois


Gentlemen: Please rush me complete details on
the full line of Rohn Towers and Accessories.

Firm _____

Name _____ Title _____

Address _____

City _____ State _____

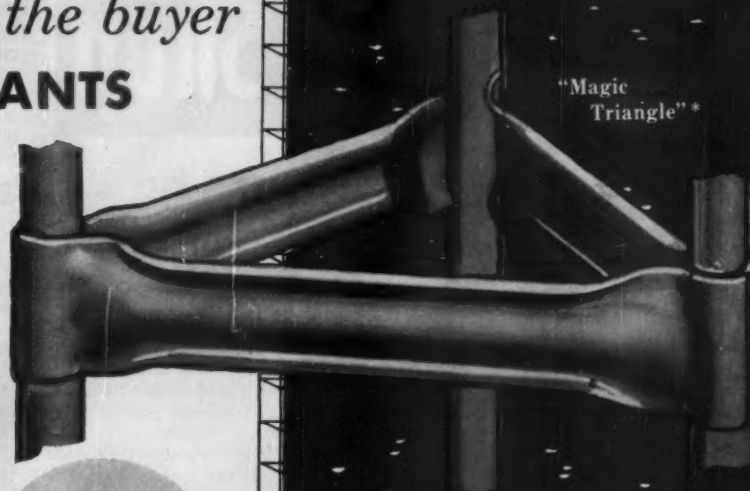

"Magic
Triangle"*



By JOHN T. FRYE

SAFETY LECTURE

WHISTLING "Blue Suede Shoes" softly to himself, Barney was working away at a rather battered three-way portable receiver while Mac, his employer, watched him. At some time or other the loop on the hinged back lid of the set had been discarded and replaced with a ferrite-core type antenna fastened inside the lid. The short length of solid enameled wire serving to give increased pickup to the loop came out through the crack between the lid and the case and stuck straight up, waving around as the set was moved. Barney, intent on getting a knob loose, bent over the set and then jerked his head back and rubbed his forehead where it had been pricked by the sharp end of the wire. As he started to return to his effort to loosen the stuck knob, Mac's hand fell heavily on his shoulder and pulled him back from the set.

"Does danger have to club you over the head before you recognize it?" Mac asked gruffly. "Next time that wire may pierce an eye."

Mac fashioned the end of the wire into a small loop and then taped it flat against the inside of the lid. "There now," he said, "that wire will not destroy the sight of a technician or anyone else handling the receiver. I hate to keep harping on the subject, but I want you to be more alert to danger in your work. Now that my eyes are beginning to slip a little, I can really appreciate how precious good eyesight is, and I don't ever want to see you taking any chances of injuring your eyes again."

"I'm usually pretty careful," Barney defended himself.

"'Pretty careful' is not good enough," Mac declared flatly. "I've seen you doing something again lately that I've warned you about time and again: holding a hot iron on a solder joint while you pull the wires soldered to that joint toward you. When the wires come loose, they often flip hot solder right into your face. I've seen you rubbing a spot where a little blob of molten solder hit your face more

than once. Can't you imagine what will happen if a bit of that hot solder strikes an eye?"

"Okay, I'll remember," Barney promised. "From now on I'll push instead of pull on those wires. Have you noticed my doing anything else wrong, I'm foolish enough to ask?"

"Plenty! But I've already taken care of one threat. I saw you using the scratch-awl the other day to pry loose wires you were unsoldering. Ignoring the dubious wisdom of misusing the scratch-awl in this fashion, I noticed that you had the right-angle point down inside the set while the needle-sharp straight point was directed right at your face. I stuck corks on both points, and I had better never catch you employing that tool without a cork on the point you are not actually using."

"Okay," Barney said with an impish grin, "I'll be sure you don't catch me when I'm doing it."

"Another thing not to let me catch you doing is being careless with that contact cleaner," Mac went on. "I'm not sure, but I have a strong suspicion that the stuff contains some carbon tetrachloride. If so, that makes it dangerous to the eyes. Don't go slopping and flipping it around carelessly. Remember your eyes."

"Aye, aye, Sir!" Barney punned.

"And don't forget," Mac continued relentlessly, "that you can hurt your irreplaceable eyes without punching them out or flipping harmful chemicals into them. It may take longer, but the end result will be the same. I've equipped our bench with the best lighting I know of, but you can still misuse it. For example, that flexible bench light is intended to throw the light exactly where you want it so that you can see into dark spots in the chassis not illuminated by the overhead lights. But every now and then I notice you allowing the flexible lamp to shine directly into your eyes simply because you are too lazy to reach up and turn it away."

"You could have said I was too intent on my work instead of saying I

was too lazy," Barney remarked bitterly. "Do I do things that endanger other parts of my anatomy besides my eyes?"

"Only about every square inch of it," Mac said promptly. "A prize example was when I saw you holding your hand behind a panel you were drilling the other day. I gathered you were trusting your reaction time being quick enough to stop the drill the instant it went through the panel. Well, it wasn't; and that gash across the side of your index finger proves it."

"Another thing I have seen you do quite often is to try and use a large bit with a cut-down shank in our quarter-inch hand drill for making a large hole in a panel or chassis. All at once the bit catches and twists the drill right out of your hand or starts the thing you are trying to drill going around like a fan blade. It is mighty easy to get a nasty cut, break a finger, or even break a wrist that way. That is a job for the drill press and not for the hand drill; and when you are using the press, make sure the material being drilled is clamped securely so it cannot budge when the rotating tool takes a heavy cut."

"I always think I'll be able to hold the darned drill," Barney muttered.

"Another thing I don't like are the number of soldering iron burns you have on your hands most of the time," Mac said as he reached over and spread Barney's hands out in front of him. Sure enough, the youth had three red welts on the fingers of his left hand. "There's no call for that," Mac said firmly. "You should be able to keep your fingers out of the way of the solder gun tip. Hold what you are soldering with pliers or tweezers; then if the tip slips off, you will not be branded with one of those 'carelessness' brands."

"Just remember a burn is always a good place for infection to enter the body, not to mention the painful annoyance it represents. Another dandy way to get burn marks on your arms is to reach back into a chassis for a tube and let your arm rest lovingly on a red-hot rectifier or output tube. It only takes a second to roll down your sleeve or to lay a newspaper over the hot tubes, but the burn you may get if you fail to take these precautions will be hurting you for several days."

"You keep on," Barney warned, "and you're going to have me scared to touch a radio or TV set."

"A little fear, plus a good imagination as to what *could* happen, is the best insurance against being hurt. A fine example is when you see a technician wearing a heavy glove or using a tube puller to wrestle hard-to-get-out tubes from their sockets. Every time I see a fellow pulling and tugging at one of these with his bare hands, I cringe inside. I keep remembering very vividly the time I saw a loctal tube break in the hand of a friend of mine and very nearly sever his thumb."

(Continued on page 197)



(Left to right) Dr. John Bardeen*, Dr. William Shockley* and Dr. Walter H. Brattain, shown at Bell Telephone Laboratories in 1948 with apparatus used in the early investigations which led to the invention of the transistor.

Bell Telephone Laboratories Salutes Three New Nobel Prize Winners

Drs. John Bardeen, Walter H. Brattain and William Shockley
are honored for accomplishments at the Laboratories

The 1956 Nobel Prize in Physics has been awarded to the three inventors of the transistor, for "investigations on semiconductors and the discovery of the transistor effect."

They made their revolutionary contribution to electronics while working at Bell Telephone Laboratories in Murray Hill, N. J. Discovery of the transistor was announced in 1948. Bell Laboratories is proud to have been able to provide the environment for this great achievement.

This is the second Nobel Prize awarded to Bell Telephone Laboratories scientists. In 1937 Dr. C. J. Davisson shared a Nobel Prize for his discovery of electron diffraction.

Such achievements reflect honor on all the scientists and engineers who work at Bell Telephone Laboratories. These men, doing research and development in a wide variety of fields, are contributing every day to the improvement of communications in America.

*Dr. Bardeen is now with the University of Illinois, and Dr. Shockley is with the Shockley Semiconductor Laboratory of Beckman Instruments, Inc., Calif.



Bell Telephone Laboratories

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT

Low-Cost Power Transistors

FOR EXPERIMENTERS AND RADIO AMATEURS

Now you can build a variety of economical transistorized amplifiers capable of real power output . . . 10 watts in Class B push-pull. The CBS 2N255 and 2N256 feature high power coupled with high current amplification and their construction permits high heat dissipation. These alloy-junction germanium transistors are also designed for six-volt (2N255) and twelve-volt (2N256) battery operation . . . ideal for mobile use.



It's easy to put these transistors to work. CBS Power Transistor Applications, PA-16, gives complete data . . . operating notes . . . and six simplified power transistor circuits. Pick up this free booklet . . . and get your low-cost 2N255 and 2N256 transistors at your CBS Tube distributor's — today.

*Reliable products through
Advanced-Engineering*



semiconductors

CBS-HYTRON

Semiconductor Operations, Lowell, Mass.

A Division of

Columbia Broadcasting System, Inc.

78

Sylvania Color TV (Continued from page 55)

right of Fig. 1, just beside the plastic h.v. connector.

Fig. 6 shows the underside of the main chassis, housing the power and deflection circuits, with the h.v. and horizontal sweep circuits occupying the left portion.

Installation

The chassis and picture tube are ordinarily shipped inside the cabinet and, once uncrated, the set is ready to play. Connection to a good antenna is made through the conventional 300-ohm terminals at the rear of the set. After the power cord is plugged into the 117-volt power line, the "off-on" lever at the upper left of the screen is actuated. Volume, tone, brightness, and contrast controls operate just as in any ordinary monochrome set. To change channels, push the upper right lever to the right. For fine tuning, use the rim-type control next to the channel lever. The actual channel number is then visible in the upper center window.

Adjustment for color reception is done in two steps. The first step involves adjustment for good monochrome reception. Accordingly, the "Color" control is turned to the extreme left until it clicks off and adjustments are made for proper brightness, contrast, and fine tuning. Then the color control is turned on and adjusted for proper saturation while the "Hue" control is manipulated to make sure that colors, especially flesh tones, are correct.

If this procedure does not result in a good color picture, or if any of the controls do not seem to function, more skill is required. If it appears that a control knob turns without stop, the mechanical linkage to the actual control is probably missing. Sometimes re-alignment of the chassis in the cabinet can cure this type of defect. Should poor purity, convergence, color sync loss, or any of the other possible misadjustments or defects be observed,

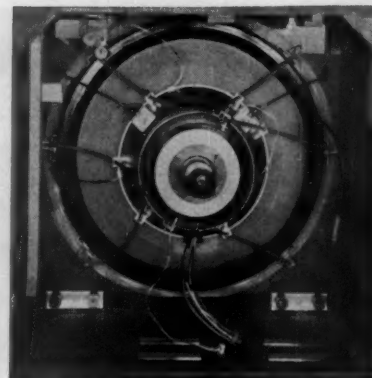


Fig. 4. Control shafts from the chassis mate with the knobs at the CRT corners.

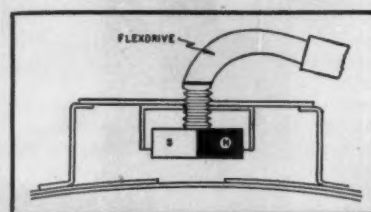



Fig. 5. Field neutralizing magnets are adjustable by flexible extension shafts. These shafts are also visible in Fig. 4.

the full set-up and alignment procedure may be needed. A detailed step-by-step convergence and purity adjustment of the Sylvania color sets is included in the service data.

In troubleshooting these receivers, good use can be made of the many special test points provided on the chassis and clearly shown in the circuit diagram together with the voltages and waveshapes which should be expected. The various connectors and plugs used in the Sylvania sets also speed up servicing because they facilitate isolating certain sections, and many voltages and signals can be checked at those connectors.

The technician who has some experience with other color receivers and who possesses the basic understanding of color circuitry will not find it difficult to service Sylvania models. —50—

Fig. 6. Underside of the main chassis. Horizontal sweep and h.v. circuits are to the left. Other deflection circuits are also on this chassis, as well as the power supply. Remaining circuits appear on vertical section of the L-shaped chassis.

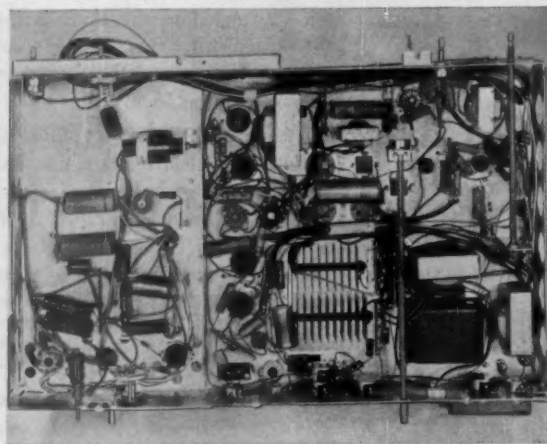

RADIO & TELEVISION NEWS



For Electronic Knowledge and Skill Quickly, Easily...at Low Cost

READ RIDER BOOKS

New Book Covering the Growing 'Intercom' Field HOW TO INSTALL & SERVICE INTERCOMMUNICATION SYSTEMS by Jack Darr

The growth of the intercom as a modern tool of business presents an important service and installation opportunity. This book covers completely installation and maintenance of commercial intercommunication equipment. Basic amplifiers, special speakers, switching arrangements, a-c and a-c/d-c systems, wireless systems, cabling networks, all-call systems, paging systems, remote and master systems, one and 2-way intercom systems, installation for home and industrial use, outdoor wiring, and system requirements for particular applications are discussed. Complete servicing techniques and tools and equipment needed for troubleshooting are covered. Illustrations of test setups are included. Design and installation techniques also covered. Intercom terminology defined.

Soft Cover, 182 pp., 5½ x 8½", illus.
#189.....Only \$3.00

TRANSISTOR ENGINEERING REFERENCE HANDBOOK by H. E. Marrows

Covering transistor performance characteristics, operating specifications, manufacturing processes, applications, testing, sources etc. Related components—electrical characteristics, physical dimensions, sources, etc. The most complete handbook for use in engineering, scientific research and manufacturing of transistor devices. Authoritative—informative—up-to-the-minute.

Cloth Bound, 288 pp., 9 x 12", illus.
#193.....Only \$9.95

INTRODUCTION TO PRINTED CIRCUITS by Robert L. Swiggett

Gives complete coverage to the various manufacturing processes, practical applications and the servicing techniques peculiar to printed circuits.

Soft Cover, 112 pages, 5½ x 8½", illus.
#185.....Only \$2.70

PICTORIAL MICROWAVE DICTIONARY

by Victor J. Young & Meredith W. Jones

This pictorial dictionary, written by two acknowledged experts in the microwave field, presents with rigorous accuracy the microwave language.

Derivation, explanation, definition, and illustration are combined in such fashion as to give the reader complete coverage of the microwave activity. Organisation of the dictionary makes it easy to use...and very understandable.

Soft Cover, 5½ x 8½", illus.
#188.....Only \$2.95

BASICS OF PHOTOTUBES & PHOTOCELLS by David Mark

This book is devoted to the explanation of the principles and practices surrounding phototubes and photocells, with the utmost in visual presentation to make the subject most understandable. It is tantamount to a "picture course"...yet it is authoritative and modern.

Soft Cover, 186 pp., 5½ x 8½", illus.
#184.....Only \$2.90

PICTURE BOOK OF TV TROUBLES, Vol. 7 (Sound Circuits & L-V Power Supplies) by Rider Lab. Staff

Volume 7 of this famous and extremely popular series shows the effects of faults in the Sound and L-V Power Supply circuits by examples of incorrect waveforms at specific test points. The component at fault is identified.

Soft Cover, 64 pp., 5½ x 8½", illus.
#168-7.....Only \$1.50

REPAIRING TELEVISION RECEIVERS by Cyrus Glickstein

The most modern completely practical book, written by an expert with long experience in television receiver repair. Devoted to troubleshooting and repair techniques which are modern, yet down-to-earth. Covers the use of simple as well as elaborate test equipment of all kinds. Profusely illustrated.

Soft Cover, 212 pp., 5½ x 8½", illus.
#191.....Only \$4.40

SERVICING TV AFC SYSTEMS

by John Russell, Jr.

This book discusses the trouble, location, and repair of the major types of AFC circuits used today...as well as some of the less common AFC systems the technicians may encounter. Waveforms, components, common faults, and their diagnosis are presented in a manner that affords the reader a thorough understanding of AFC circuits. Supplemented by more than 75 illustrations.

Soft Cover, 128 pp., 5½ x 8½", illus.
#192.....Only \$2.70

TV TUBE LOCATION & TROUBLE GUIDE (RCA) by Rider Lab. Staff

This book shows the tube locations for all RCA TV receivers produced between 1947 and 1956. It lists the tube complement, key voltages, and common troubles correlated with the tubes that may be responsible for them. Complete chassis and model index.

Soft Cover, 66 pp., 5½ x 8½", illus.
#194.....Only \$1.25

BASIC SERIES

by Van Valkenburgh,
Nooger & Neville, Inc.

Basic Electricity.

#169, soft cover, 5 vols., 624 pp. per set \$10.00

#169H, cloth bound in single binding...\$11.50

Basic Electronics.

#170, soft cover, 5 vols., 550 pp. per set \$10.00

#170H, cloth bound in single binding...\$11.50

Basic Synchros and Servomechanisms.

#180, soft cover, 2 vols., 270 pp. per set \$5.50

#180H, cloth bound in single binding...\$6.95

Hi-Fi Loudspeakers & Enclosures

by Abraham D. Cohen.

#176, MARCO cover, 360 pp.....\$4.60

#176H, cloth bound.....\$5.50

How to Service Tape Recorders

by C. A. Tuthill.

#167, soft cover, 160 pp.....\$2.90

How to Troubleshoot a TV Receiver

by J. Richard Johnson

#152, soft cover, 128 pp.....\$1.80

Handbook of 630-Type TV Receivers

by Miller & Bierman.

#174, soft cover, 200 pp.....\$3.50

Basic Vacuum Tubes & Their Uses

by Rider & Jacobowitz.

#171, soft cover, 208 pp.....\$3.00

#171H, cloth bound.....\$4.50

Understanding Vectors & Phase

by Rider and Uslan.

#103, soft cover, 160 pp.....\$.99

How to Use Meter, by John F. Rider.

#144, soft cover, 144 pp.....\$2.40

Fundamentals of Transistors

by Leonard Krugman.

#160, soft cover, 144 pp.....\$2.70

Introduction to Color TV (2nd Edition)

by Kaufman & Thomas.

#136 soft cover, 160 pp.....\$2.70

How to Select and Use Your Tape Recorder

by David Mark.

#179, soft cover, 148 pp.....\$2.95

Obtaining & Interpreting Test Scope Traces

by John F. Rider.

#146, soft cover, 190 pp.....\$2.40

Television - How it Works (2nd Edition)

by J. Richard Johnson.

#101, leather finish MARCO, 352 pp.....\$4.60

#101-H, cloth bound.....\$5.50

PICTURE BOOK OF TV TROUBLES

by Rider Lab. Staff

Vol. 1: Horizontal AFC-Oscillator Circuits

#168, 80 pp.....Only \$1.35

Vol. 2: Vertical Sweep-Deflection Circuits

#168-2, 96 pp.....Only \$1.80

Vol. 3: Video I-F & Video Amplifier Circuits

#168-3, 96 pp.....Only \$1.80

Vol. 4: Automatic Gain Control Circuits

#168-4, 96 pp.....Only \$1.80

Vol. 5: Horizontal Output & H-V Circuits

#168-5, 108 pp.....Only \$1.80

Vol. 6: Horizontal & Vertical Sync Circuits

#168-6, 120 pp.....Only \$1.80

Buy these and many other RIDER BOOKS at your electronics parts jobber, book store or department store book department. Look for this Rider Bookseller. If your jobber, book store, or department store does not sell the Rider books you want, write direct. ORDER TODAY! Add state and city sales tax where applicable. Canadian prices approximately 5% higher.



AND...

ALL WHO WANT THE **BEST** IN TV SERVICE INFORMATION

RCA
PHILCO
ADMIRAL
EMERSON
SYLVANIA
HOFFMAN

ON
GE
CROSLEY
MOTOROLA
ZENITH
WESTINGHOUSE
PACKARD-BELL

(other manufacturers later on)

...ASK YOUR JOBBER ABOUT
RIDER'S NEW
S D O

("single diagram only")

ONLY **50¢** PER CHASSIS!

JOHN F. RIDER PUBLISHER, INC.

116 West 14th Street, New York 11, N. Y.

In Canada:

Charles W. Pointon, Ltd.

6 Alinga Ave., Toronto, Ontario

In Canada all prices approximately 5% higher



MODEL O-11

Shpg. Wt.
21 lbs.

\$69⁵⁰

New

- * An improved model of what was already an outstanding instrument.
- * Performance is unmatched in this price range.
- * Incorporates the extra features required for color TV servicing.

Extra!

A FULL YEAR TO PAY

SEND FOR DETAILS OF HEATH
TIME-PAYMENT PLAN.

**5
BIG
REASONS
WHY**



**HEATH
COMPANY**

A SUBSIDIARY OF DAYSTROM, INC.

BENTON HARBOR 15, MICH.

HEATHKIT ETCHED CIRCUIT, PUSH-PULL

5" Oscilloscope Kit

COLOR TV

The previous Heathkit oscilloscope (Model O-10) which was already a most remarkable instrument, has been improved even further with the release of the Heathkit Model O-11. It incorporates all the outstanding features of the preceding model, *plus* improved vertical linearity, better sync stability, especially at low frequencies, and much-improved over-all stability of operation, including less vertical bounce with changes in level. These improvements in the Model O-11 circuit make it even more ideally suited for color TV servicing, and for critical observations in the electronic laboratory. Vertical response extends from 2 CPS to 5 MC without extra switching. Response only down 2.2' DB at 3.58 MC. The 11-tube circuit features a 5UP1 cathode-ray tube. Sync circuit functions effectively from 20 CPS to better than 500 kc in five steps. Modern etched circuit boards employed in the oscilloscope circuit cut assembly time almost in half, permit a level of circuit stability never before achieved in an oscilloscope of this type, and insure against errors in assembly. Both vertical and horizontal output amplifiers are push-pull. Built-in peak-to-peak calibrating source — step-attenuated input — plastic molded capacitors and top-quality parts throughout — pre-formed and cabled wiring harness — and numerous other "extra" features. A professional instrument for the serveshop or laboratory. Compare its specifications with those of scopes selling in much higher price brackets. You can't beat it!

1 FEWER DOLLARS BRING MORE REAL QUALITY.

- Factory-to-you sales eliminate extra profit margin.
- "Build-it-yourself" eliminates labor charge.
- Heath purchasing power cuts component costs.

2 PERSONAL SERVICE ASSURES CUSTOMER SATISFACTION.

- You deal directly with the manufacturer.
- We are interested in you before and after sale.

Heathkits®

ARE YOUR BEST BUY...

3 PROVEN DESIGNS MEAN RELIABLE PERFORMANCE.

- Research and development efforts concentrated on kits only.
- All kits guaranteed to meet advertised specifications.

4 EVERY KIT BACKED BY WORLD-WIDE REPUTATION.

- The world's largest manufacturer of electronic equipment in kit form.
- Producer of more than a million electronic kits for the home workshop and industry.


5 EASY TIME-PAYMENT PLAN TO FIT YOUR BUDGET.

GREATEST SELECTION . . .

Whether your particular special interest is in servicing, ham-radio, high-fidelity, or just experimenting—there are Heathkits to fill your needs. You can equip an entire service shop or lab, buy a complete ham station or high-fidelity system, or set up a really deluxe home workshop, by choosing from the more than 70 different "do-it-yourself" electronic kits by Heath. Just glance through the kits displayed in this ad, and you will get some idea of the tremendous array of low-priced, high-quality electronic equipment available.

New HEATHKIT ETCHED CIRCUIT 5" Oscilloscope Kit

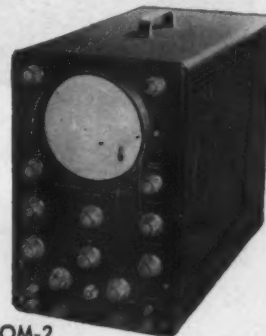- * Brand new model with improved performance specifications.
- * Full 5" scope for service work at a remarkably low price.
- * Attractively styled front panel in charcoal gray with sharp white lettering.
- * Easy to build from step-by-step instructions and large pictorials. Not necessary to read schematic.



MODEL OM-2

\$42⁵⁰

Shpg. Wt.
21 lbs.

This new and improved oscilloscope retains all the outstanding features of the preceding model, but provides wider vertical frequency response, extended sweep-generator coverage, and increased stability. A new tube complement and improvements in the circuit make these new features possible. Vertical frequency response is essentially flat to over 1 mc, and down only 1½ DB at 500 kc. The sweep generator multivibrator functions reliably from 30 to 200,000 CPS, almost twice the coverage provided by the previous model. Deflection amplifiers are push-pull, and modern etched circuits are employed in critical parts of the design. A 5BP1 cathode-ray tube is used. The scope features external or internal sweep and sync, one volt peak-to-peak reference voltage, 3-position step-attenuated input, adjustable spot-shape control, and many other "extras" not expected at this price level. A calibrated grid screen is also provided for the face of the CRT, allowing more precise observation of wave shapes displayed. The new Model OM-2 is designed for general application wherever a reliable instrument with good response characteristics may be required. Complete step-by-step instructions and large pictorial diagrams assure easy assembly.

HEATHKIT LOW CAPACITY PROBE KIT

Oscilloscope investigation of high frequency, high impedance, or broad bandwidth circuits encountered in television requires the use of a low-capacity probe to prevent loss of gain, circuit loading, or waveform distortion. The Heathkit low-capacity probe may be used with your oscilloscope to eliminate these effects. It features a variable capacitor, to provide correct instrument impedance match. Also, the ratio of attenuation can be varied.

No. 342

\$3⁵⁰

Shpg. Wt. 1 lb.

HEATHKIT ELECTRONIC SWITCH KIT

This handy device allows simultaneous oscilloscope observation of two signals by producing both signals, alternately, at its output. It features an all-electronic switching circuit, with no moving parts. Four switching rates are selected by a panel switch. Provides actual gain for input signals, and has a frequency response of ± 1 DB from 0 to 100 kc. Sync output provided to control and stabilize scope sweep. Will function at signal levels as low as 0.1 volt. This modern device finds many applications in the laboratory and service shop. It employs an entirely new circuit, and yet is priced lower than its predecessor.

MODEL S-3

\$21⁹⁵

Shpg. Wt. 8 lbs.

HEATHKIT SCOPE DEMODULATOR PROBE KIT

Extend the usefulness of your oscilloscope by employing this probe. Makes it possible to observe modulation of RF or IF carriers found in TV and radio receivers. Functions much like an AM detector to pass only modulation of signal, and not the signal itself. Among other uses, it will be helpful in alignment work, as a signal tracer, and for determining relative gain. Applied voltage limits are 30 volts (RMS) and 500 volts DC. It uses an etched circuit board to simplify assembly.

NO. 337-C

\$3⁵⁰

Shpg. Wt. 1 lb.

HEATHKIT VOLTAGE CALIBRATOR KIT

This entirely new voltage calibrator produces near-perfect square wave signals of known amplitude. Precision 1% attenuator resistors assure accurate output amplitude, and multivibrator circuit guarantees good, sharp square waves, as distinguished from clipped sine waves. Output frequency is approximately 1000 CPS. Fixed outputs selected by panel switch are: .03, 0.1, 0.3, 1.0, 3.0, 10, 30, and 100 volts peak-to-peak. Allows measurement of unknown signal amplitudes by comparing to known peak-to-peak output of VC-3 on an oscilloscope. Will also double as a square wave generator at 1000 cycles for determining gain, frequency response, or phase-shift characteristics of audio amplifiers. Equally valuable in the laboratory or in radio and TV service shops.

MODEL VC-3

\$12⁵⁰

Shpg. Wt. 4 lbs.

HEATHKIT ETCHED CIRCUIT VACUUM TUBE



MODEL
V-7A

\$24.50

Shpg. Wt.
7 lbs.

- * Easy to build — a pleasure to use.
- * 1% precision resistors employed for high accuracy.
- * Etched circuit board cuts assembly time in half.

Voltmeter Kit

The fact that this instrument is the world's largest-selling VTVM says a great deal about its accuracy, reliability, and overall quality. The V-7A is equally popular in the laboratory or service shop, and represents an unbelievable test equipment bargain, without a corresponding sacrifice in quality. Its appearance reflects the performance of which it is capable. A large 4½" panel meter is used for indication, with clear, sharp calibrations for all ranges. Front panel controls consist of a rotary function switch and a rotary range selector switch, zero-adjust, and ohms-adjust controls. Precision 1% resistors are used in the voltage divider circuits and etched circuits are employed for most of the circuitry. This makes the kit much easier to build, eliminates the possibility of wiring errors, and assures duplication of laboratory instrument performance. This multi-function VTVM will measure AC voltage (rms), AC voltage (peak-to-peak), DC voltage, and resistance. There are 7 AC (rms) and DC voltage ranges of 0-1.5, 5, 15, 50, 150, 500, and 1500. In addition, there are 7 peak-to-peak AC ranges of 0-4, 14, 40, 140, 400, 1400, and 4000. 7 ohmmeter ranges provide multiplying factors of X1, X10, X100, X1000, X10K, X100K, and X1 megohm. Center-scale resistance readings are 10, 100, 1000, 10K, 100K ohms, 1 megohm, and 10 megohms. A DB scale is also provided. The precision and quality of the components used in this VTVM cannot be duplicated at this price through any other source. Model V-7A is the kind of instrument you will be proud to own and use.

HEATHKIT Etched Circuit RF PROBE KIT

This RF probe extends the frequency response of any 11-megohm VTVM so that it will measure RF up to 250 megacycles within ± 10%. Employs printed circuits for increased stability and ease of assembly. Ideal for extending service and laboratory applications of your Heathkit VTVM. No. 309-C

\$3.50

Shpg. Wt. 1 lb.

ETCHED CIRCUIT PEAK-TO-PEAK PROBE KIT

Use this peak-to-peak probe with your 11-megohm VTVM to measure peak-to-peak voltages directly on the DC scales of the instrument. Will measure p-to-p voltages in the frequency range of 5 kc to 5 mc. Employs etched circuit boards for increased circuit stability and simplified construction. Extend the usefulness of your VTVM. NOTE: Not required for the Heathkit V-7A VTVM. No. 338-C

\$5.50


Shpg. Wt. 2 lbs.

HEATHKIT 20,000 OHMS/VOLT VOM KIT

Sensitivity of this instrument is 20,000 ohms-per-volt DC and 5,000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500, and 5000 volts for both AC and DC. Also measures current in the ranges of 0-150 microamperes, 15 ma, 150 ma, 500 ma, and 15 a. Resistance ranges provide multipliers of X1, X100, and X10,000, resulting in center scale readings of 15, 15,000, and 150,000 ohms. DB ranges cover from -10 db to +65 db. Housed in attractive black bakelite case with plastic carrying handle, this fine instrument provides a total of 25 meter ranges on its two-color scale. It employs a sensitive 50 microampere, 4½" meter and features all 1% precision multiplier resistors. Requires no external power, and is, therefore, valuable in portable applications where no AC power is available. MODEL MM-1

\$29.50

Shpg. Wt. 6 lbs.

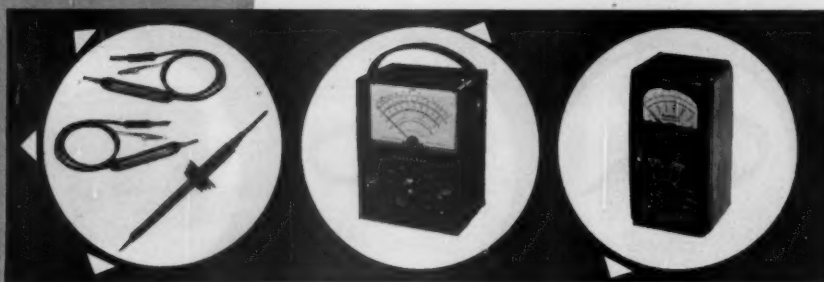

HEATHKIT 30,000 VOLT DC HIGH VOLTAGE PROBE KIT

This probe provides a multiplication factor of 100 on the DC ranges of the Heathkit 11-megohm VTVM. Precision multiplier resistor mounted inside the two-color plastic probe body. Plenty of insulation for completely safe operation, even at highest TV potentials. Designed especially for TV service work. No. 336

\$4.50

Shpg. Wt. 2 lbs.

HEATHKIT HANDITESTER KIT

The Model M-1 measures AC or DC voltage at 0-10, 30, 300, 1000, and 5000 volts. Direct current ranges are 0-10 ma, and 0-100 ma. Ohmmeter ranges are 0-3000 (30 ohm center scale) and 0-300,000 ohms (3,000 ohms center scale). Uses a 400 microampere meter for sensitivity of 1000 ohms-per-volt. A very popular test device for the home experimenter, electricians, and appliance repairmen, and for use as an "extra" instrument in the service shop. Its small size and rugged construction make it perfect for any portable application. Easily slips into your tool box, glove compartment, coat pocket, or desk drawer. Top quality, precision components employed throughout. MODEL M-1

\$14.50

Shpg. Wt. 3 lbs.



HEATH COMPANY
A Subsidiary of Daystrom, Inc.
BENTON HARBOR 15, MICH.

CONTROLLED QUALITY...

Incoming parts inspection, and inspection of material coming off of our own production line assures you of the finest "build-it-yourself" kit that money can buy. Each kit contains all the components you need for assembly—and you can have confidence in the quality of the parts themselves. In addition to this inspection procedure, an extensive proof-building program for each new kit guarantees easy-to-follow instructions and reliable performance.

This brand new AC vacuum tube voltmeter emphasizes stability, broad frequency response, and sensitivity. It is designed especially for audio measurements, and low-level AC measurements in power supply filters, etc. Employs a cascode amplifier circuit with cathode-follower isolation between the input and the amplifier, and between the output stage and the preceding stages. An extremely stable circuit with high input impedance (1 megohm at 1000 CPS). Response of the AV-3 is essentially flat from 10 CPS to 200 kc, and is usable for tests even beyond these frequency limits. Increased damping in the meter circuit stabilizes the meter for low frequency tests. Nylon insulating bushings at the input terminals reduce leakage, and permit the use of the 5-way Heath binding post.

The extremely wide voltage range covered by the AV-3 makes it especially valuable not only in high-fidelity and service work, but also in experimental laboratories. AC (RMS) voltage ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 V. Decibel ranges cover -52 DB to +52 DB. An entirely new circuit as compared to the previous model. Employs 1% precision multiplier resistors for maximum accuracy. Handles AC measurements from a low value of one millivolt to a maximum of 300 volts.

HEATHKIT NEW AUDIO VACUUM TUBE

Voltmeter Kit

- * Brand new circuit for extended frequency response and added stability.
- * Ten accurate ranges from 0-.01 to 0-300 volts.
- * Modern, functional panel styling. "On-off" switch at both extreme ends of range switch.



MODEL AV-3

\$29⁹⁵

Shpg. Wt.
5 Lbs.

HEATHKIT AUDIO WATTMETER KIT

This instrument measures audio power directly at 4, 8, 16, or 600 ohms. Load resistors are built in. Covers 0-5 MW, 50 MW, 500 MW, 5 W, and 50 W full scale. Provides 5 switch-selected DB ranges covering from -10 DB to +30 DB. Large 4½" 200 microampere meter and precision multiplier resistors insure accuracy. Frequency response is ± 1 DB from 10 CPS to 250 kc. Functions from AC power line. Use in the audio laboratory or in home workshop.

MODEL AW-1

\$29⁵⁰

Shpg. Wt. 6 Lbs.


HEATHKIT AUDIO ANALYZER KIT

This multi-function instrument combines an AC VTVM, an audio wattmeter, and an intermodulation analyzer into one case, with combined input and output terminals and built-in high and low frequency oscillators. The VTVM ranges are .01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 volts (RMS). Wattmeter ranges are .15 MW, 1.5 MW, 15 MW, 150 MW, 1.5 W, 15 W, 150 W. IM scales are 1%, 3%, 10%, 30%, and 100%. Provides internal load resistors of 4, 8, 16, or 600 ohms. A valuable instrument for the engineer or serious audiophile.

MODEL AA-1

\$49⁹⁵

Shpg. Wt. 13 Lbs.

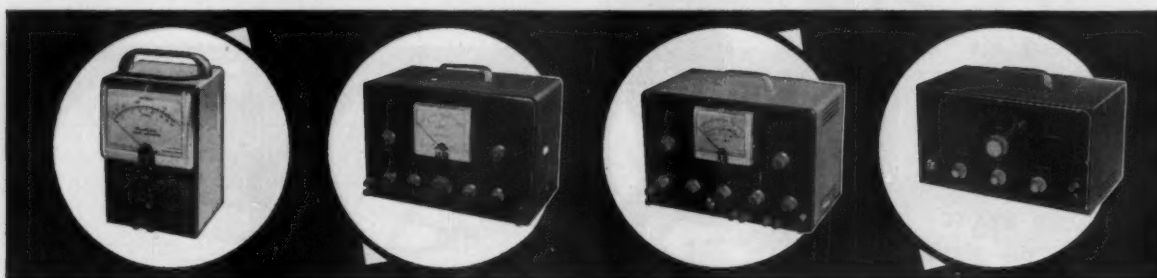

HEATHKIT HARMONIC DISTORTION METER KIT

The HD-1 is equally valuable for the audio engineer or the serious audiophile. Used with a low-distortion audio signal generator, this instrument will measure the harmonic content of various amplifiers under a variety of conditions. Functions between 20 and 20,000 CPS, and reads distortion directly on the panel meter in ranges of 0-1, 3, 10, 30, and 100 percent full scale. Built-in VTVM for initial reference settings and final distortion readings has voltage ranges of 0-1, 3, 10, and 30 volts. 1% precision resistors employed for maximum accuracy. Features voltage regulation and other "extras". Meter calibrated in volts (RMS), percent distortion, and DB.

MODEL HD-1

\$49⁵⁰

Shpg. Wt. 13 Lbs.

HEATHKIT AUDIO OSCILLATOR KIT

Producing both sine waves and square waves, the Model AO-1 covers a frequency range of 20 to 20,000 CPS in three ranges. An extra feature is thermistor regulation of output for flat response through the entire frequency range. AF output is provided at low impedance, and with low distortion. Produces good sine waves, and good, clean square waves with a rise time of only two micro-seconds for checking square wave response of audio amplifiers, etc. Designed especially for the serviceman and high-fidelity enthusiast. A real dollar value in test equipment.

MODEL AO-1

\$24⁵⁰

Shpg. Wt. 10 Lbs.

HEATHKIT



MODEL
AG-9

\$34⁵⁰

Shpg. Wt.
8 Lbs.

- * Less than 0.1% distortion — ideal for hi fi work.
- * Large 4½" meter indicates output.
- * Step-type tuning for maximum convenience.

Audio Generator Kit

This particular audio generator is "made to order" for high fidelity applications. It provides quick and accurate selection of low-distortion signals throughout the audio range. Three rotary selector switches on the front panel allow selection of two significant figures and a multiplier for determining audio frequency. In addition, it incorporates a step-type output attenuator and a continuously variable attenuator. Output is indicated on a large 4½" panel meter calibrated in volts and in db. Attenuator system operates in steps of 10 db, corresponding with the meter calibration. Output ranges are 0-.003, .01, .03, .1, .3, 1, 3, and 10 volts rms. A "load" switch provides for the use of a built-in 600 ohm load or an external load of higher impedance when required. Output and frequency indicators accurate to within ± 5%. Distortion is less than .1 of 1% between 20 cps and 20,000 cps. Total range is 10 cps to 100 kc. New engineering details combine to provide the user with an unusually high degree of operating efficiency. Oscillator frequency selected entirely by the switch method means that accurate resetability is provided. Comparable to units costing many dollars more, and ideal for use in critical high fidelity applications. Shop and compare, and you will appreciate the genuine value of this professional instrument.

HEATHKIT RESISTANCE SUBSTITUTION BOX KIT

The RS-1 contains 36 10% 1-watt resistors ranging from 15 ohms to 10 megohms in standard RETMA values. All values are switch-selected for use in determining desirable resistance values in experimental circuits. Many applications in radio and TV service work.

MODEL RS-1
\$5⁵⁰

Shpg. Wt. 2 Lbs.

HEATHKIT CONDENSER SUBSTITUTION BOX KIT

This kit contains 18 RETMA standard condenser values that can be selected by a rotary switch. Values range from 0.00001 mfd to 0.22 mfd. All capacitors rated at 400 volts or higher. Capacitors are either silver-mica, or plastic molded.

MODEL CS-1
\$5⁵⁰

Shpg. Wt. 2 Lbs.

HEATHKIT AUDIO GENERATOR KIT

The Model AG-8 is a low cost, high performance unit for use in service shop, or home workshop. It covers the frequency range of 20 cps to 1 mc in five ranges. Output is 600 ohms, and overall distortion will be less than .4 of 1% from 100 cps through the audible range. Output is available up to 10 volts, under no load conditions, and output remains constant within ± 1 db from 20 cps to 400 kc. A five-step attenuator provides control of the output. Precision resistors are employed in the frequency determining network.

MODEL AG-8
\$29⁵⁰

Shpg. Wt. 11 Lbs.

HEATHKIT DECADE CONDENSER KIT

Precision, 1% silver-mica capacitors are employed in the Model DC-1 in such a way that a selection of precision capacitor values is provided ranging from 100 mmf (.0001 mfd) to 0.11 mfd (110,000 mmf) in 100 mmf steps. Extremely valuable in all types of design and development work. Switches are ceramic wafer types.

MODEL DC-1
\$16⁵⁰

Shpg. Wt. 3 Lbs.



HEATHKIT DECADE RESISTANCE KIT

The Model DR-1 incorporates twenty 1% precision resistors arranged around five rugged switches so that various combinations of switch positions will provide a total range of 1 ohm to 99,999 ohms in 1-ohm steps. Switches are labeled "units," "tens," "hundreds," "thousands," and "ten thousands." Use it for ohm-meter calibration in bridge circuits as test values in multiplier circuits, etc.

MODEL DR-1
\$19⁵⁰

Shpg. Wt. 4 Lbs.

HEATHKIT VARIABLE VOLTAGE REGULATED POWER SUPPLY KIT

This power supply is regulated for stability, and the amount of DC output available from the power supply can be controlled manually from zero to 500 volts. Will provide regulated output at 450 volts up to 10 ma, or up to 130 ma at 200 volts output. In addition to furnishing B-plus, the power supply provides 6 volts AC at 4 amperes for filaments. Both the B-plus output and the filament output are isolated from ground. Ideal power supply for use in experimental work in the laboratory, the home workshop, or the ham shack. Large 4½" panel meter indicates output voltage or current.

MODEL PS-3
\$35⁵⁰

Shpg. Wt. 17 Lbs.



HEATH COMPANY
A Subsidiary of Daystrom, Inc.
BENTON HARBOR 15, MICH.

BONUS PERFORMANCE . . .

If a single word had to be selected to describe Heath Company advertising policy, it would be "conservative." By this we mean that the performance specifications and features are not exaggerated, and that the descriptions are accurate. We specify performance on the conservative side so you can be sure of equaling or exceeding our specifications. In almost every instance our kits will do more than we claim. Extra care in construction, and calibration against an accurate standard can extend performance well beyond advertised levels.

Here is an RF signal generator for alignment applications in the service shop or the home workshop. Thousands of these units are in use in service shops all over the country. Produces RF signals from 160 kc to 110 mc on fundamentals on five bands. Also covers from 110 mc to 220 mc on calibrated harmonics. RF output is in excess of 100,000 microvolts at low impedance. Output is controllable with a step-type and a continuously variable attenuator. Front panel controls provide selection of either unmodulated RF output or RF modulated at 400 cps. In addition, two to three volts of audio at approximately 400 cps are available at the output terminals for testing AF circuits. Employs a 12AU7 and a 6C4 tube. Built-in power supply uses a selenium rectifier.

One of the most outstanding features about the Model SG-8 is the fact that it can be built in just a few hours, even by one not thoroughly experienced in electronics work. Complete step-by-step instructions combined with large pictorial diagrams assure successful assembly. Pre-aligned coils make calibration from an external source unnecessary.

HEATHKIT

Signal Generator Kit

- * No calibration required with pre-aligned coils.
- * Modulated or unmodulated RF output.
- * 110 mc to 220 mc frequency coverage.



MODEL
SG-8

\$19⁵⁰ Shpg. Wt. 8 lbs.

HEATHKIT LABORATORY GENERATOR KIT

This laboratory RF signal generator covers from 100 kc to 30 mc on fundamentals in five bands. The output signal may be pure RF, or may be modulated at 400 cycles from 0 to 50%. Provision for external modulation has been made. RF output available up to 100,000 microvolts. Output controlled by a fixed step and a variable attenuator. Output impedance is 50 ohms. Panel meter reads RF output or percentage of modulation. Incorporates voltage regulated B+ supply, double shielding of oscillator circuits, copper plated chassis, and other "extras."

MODEL LG-1

\$48⁹⁵

Shpg. Wt. 16 lbs.


HEATHKIT TV ALIGNMENT GENERATOR KIT

This improved sweep generator model provides essential stability and flexibility for work on FM, monochrome TV, or color TV sets. Covers 3.6 mc to 220 mc in four bands. Provides usable output even on harmonics. Sweep deviation from 0-42 mc, depending on base frequency. All-electronic sweep circuit eliminates unwieldy mechanical arrangements. Includes built-in crystal marker generator providing output at 4.5 mc and multiples thereof, and variable marker covering 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking.

MODEL TS-4A

\$49⁵⁰

Shpg. Wt. 16 lbs.

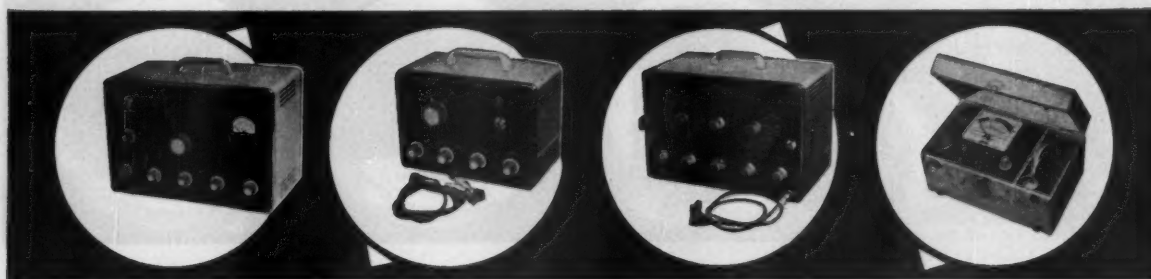

HEATHKIT LINEARITY PATTERN GENERATOR KIT

This instrument supplies information for white dots, cross-hatch pattern, horizontal bar pattern, or vertical bar pattern. It feeds video and sync signals to the set under test, with completely controlled gain, and unusual stability. Covering channels 2 to 13, the LP-2 will produce 5 to 6 vertical bars and 4 to 5 horizontal bars. The dot pattern presentation is a *must* for the setting of color convergence controls in the color TV set. Panel provision made for external sync if desired. Use for adjustment of vertical and horizontal linearity, picture size, aspect ratio, and focus. Power supply is regulated for added stability. Essential in the up-to-date TV service shop.

MODEL LP-2

\$22⁵⁰

Shpg. Wt. 7 lbs.

HEATHKIT CATHODE RAY TUBE CHECKER KIT

This instrument checks cathode emission, beam current, shorted elements, and leakage between elements in electro-magnetic picture tube types. It eliminates all doubt for the TV serviceman, and even more important, for the customer. Features its own self-contained power supply, transformer operated to furnish normal test voltages for the CRT. Employs spring-loaded switches for maximum operator protection. Large 4½" meter indicates CRT condition on "good-bad" scale. Luggage-type portable case ideal for home service calls. Special "shadowgraph" test permits projection of light spot on screen. Also gives relative check of picture tube screen coating.

MODEL CC-1

\$22⁵⁰

Shpg. Wt. 10 lbs.


HEATHKIT

MODEL
TC-2**\$29⁵⁰**Shpg. Wt.
12 lbs.

- * Attractive counter-style cabinet.
- * Wiring-harness simplifies assembly.
- * Large 4½" meter with two-color "good-bad" scale.
- * Separate tube element switches prevent obsolescence.

HEATHKIT PORTABLE
TUBE CHECKER KIT

This portable tube checker is identical, electrically, with the Model TC-2. However, it is housed in an attractive and practical carrying case, finished in proxylin impregnated material. The cover is detachable, and the hardware is brass plated. This rugged unit is ideal for home service calls or any portable application.

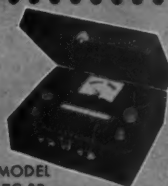MODEL
TC-2P**\$34⁵⁰**Shpg. Wt.
15 lbs.HEATHKIT
DIRECT READING
CAPACITY METER KIT

Operation of this instrument is simplicity itself. One has only to connect a capacitor to the terminals, select the proper range, and read the capacity value directly on the large 4½" meter calibrated in mmf and mfd. Ranges are 0 to 100 mmf, 1,000 mmf, 0.01 mfd, and 0.1 mfd full scale. Precision calibrating capacitors supplied. Not susceptible to hand capacity effects. Residual capacity less than 1 mmf. Especially valuable in production line checking, or in quality control.



HEATH COMPANY
A Subsidiary of Daystrom, Inc.
BENTON HARBOR 15, MICH.

MODEL CM-1

\$29⁵⁰Shpg. Wt.
7 lbs.

Tube Checker Kit

This fine piece of test gear checks tubes for quality, emission, shorted elements, open elements, and filament continuity. Will test all tube types normally encountered in radio and TV service work. Sockets provided for 4, 5, 6, and 7-pin large, rectangular, and miniature types, octal and loctal types, the Hytron 9-pin miniatures, and pilot lamps. Condition of tubes indicated on a large 4½" meter with multi-color "good-bad" scale. An illuminated roll chart is built right in, providing test data for various tube types. This tester provides switch selection of 14 different filament voltage values from 0.75 volts to 117 volts. Individual switches control each tube element. Close tolerance resistors employed in critical test circuits for maximum accuracy. A professional instrument both in appearance and performance.

The Model TC-2 is very simple to build, even for a beginner. It employs a color-coded cable harness for neat, professional under-chassis wiring. Comes with attractive counter style cabinet, and portable cabinet is available separately. At this price, even the part-time serviceman can afford his own tube checker for maximum efficiency in service work.

HEATHKIT TV PICTURE TUBE
TEST ADAPTER

Designed especially for use with the Model TC-2 tube checker. Use it to test TV picture tubes for emission, shorts, etc. Consists of 12-pin TV tube socket, 4 ft. cable, octal connector, and necessary technical data. Not a kit.



MODEL 355

\$4⁵⁰Shpg. Wt.
1 lb.


HEATHKIT VISUAL-AURAL SIGNAL TRACER KIT

Although designed primarily for radio receiver work, this valuable instrument finds extensive application in FM and TV servicing as well. Features a high-gain channel with demodulator probe, and a low-gain channel with audio probe. Will trace signals in all sections of a radio receiver and in many sections of a FM set or TV receiver. Uses built-in speaker and electron beam eye tube for indication. Also features built-in wattmeter and a noise locator circuit. Provision for patching speaker and/or output transformer into external set.

MODEL T-3

\$23⁵⁰

Shpg. Wt. 9 lbs.

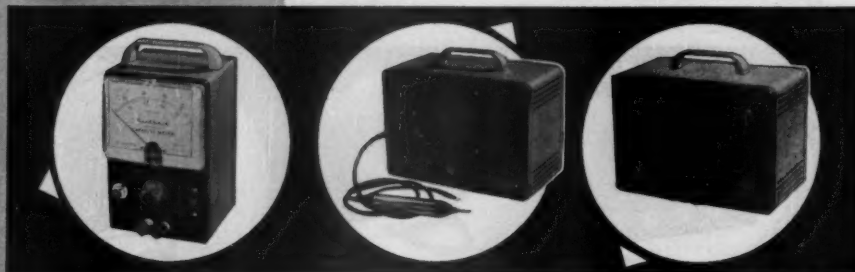

HEATHKIT CONDENSER CHECKER KIT

The Model C-3 consists of an AC powered bridge for both capacitive and resistive measurements. Bridge balance is indicated on electron beam eye tube, and capacity or resistance value is indicated on front panel calibrations. Measures capacity in four ranges from .00001 mfd to .005 mfd, .001 mfd to .5 mfd, .1 mfd to 50 mfd, and 20 mfd to 1000 mfd. Measures resistance in two ranges, from 100 ohms to 50,000 ohms, and from 10,000 ohms to 5 megohms. Selection of five different polarizing voltages for checking capacitors, from 25 volts DC to 450 volts DC. Checks paper, mica, ceramic, and electrolytic capacitors. Indicates power factor of electrolytic condensers.

MODEL C-3

\$19⁵⁰

Shpg. Wt. 7 lbs.

PIONEER DESIGN . . .

New and unique approaches to instrument and equipment designs are a Heath Company tradition. We concentrate all our development efforts on kit projects, since this is our prime activity—and not just a sideline. This logically results in more efficient, more reliable circuit designs—and you benefit from this constant engineering progress. Buying from the undisputed leader in the electronic kit field assures you of completely modern equipment, with outstanding advanced design features.

HEATHKIT

Impedance Bridge Kit

- * ½% precision resistors and silver-mica capacitors.
- * Battery-type tubes, no warm-up required.
- * Built-in phase shift generator and amplifier.

The Model IB-2 is a completely self-contained unit. It has a built-in power supply, a built-in 1000 cycle generator, and a built-in vacuum tube detector. Provision has been made on the panel for connection to an external detector, an external signal generator, or an external power supply. A 100-0-100 micro-ampere meter on the front panel provides for null indications. Measures resistance from 0.1 ohm to 10 megohms, capacitance from 10 mmf to 100 mfd, inductance from 10 mh to 100 h, dissipation factor (D) from 0.002 to 1, and storage factor (Q) from 0.1 to 1000. ½ of 1% decade resistors employed for maximum accuracy. Typical accuracy figures are: resistance, ±3T; capacitance ±3%; inductance, ±10%; dissipation factor, ±20%; storage factor, ±20%. Employs a Wheatstone bridge, a Capacity Comparison bridge, a Maxwell bridge, and a Hay bridge. Special two-section CRL dial provides maximum convenience in operation. Use the Model IB-2 for determining values of unmarked components, checking production or design samples, etc. A real professional instrument.



MODEL
IB-2

\$59⁵⁰ Shpg. Wt.
12 lbs.

HEATHKIT "Q" METER KIT

The Q Meter permits measurement of inductance from 1 microhenry to 10 millihenries, "Q" on a scale calibrated up to 250 full scale, with multiplying factors of 1 or 2, and capacitance from 40 mmf to 450 mmf, ±3 mmf. Built-in variable oscillator permits testing components from 150 kc to 18 mc. Large 4½" panel-mounted meter is features. Very handy for checking peaking coils, chokes, etc. Use to determine values of unknown condensers, both variable and fixed. Compile data for coil winding purposes, or measure RF resistance. Distributed capacity, and Q of coils.

MODEL QM-1

\$44⁵⁰

Shpg. Wt. 14 lbs.

HEATHKIT ISOLATION TRANSFORMER KIT

This device isolates equipment under test from the power line. It is rated at 100 volt-amperes continuously, or 200 volt-amperes intermittently. AC-DC sets may be plugged directly into the IT-1 without the chassis becoming "hot." Additionally, since the IT-1 is fused, it is ideal for use as a buffer between the power line and a questionable receiver, or a new piece of equipment. Protects main fuses. Features voltage control, allowing control of the output from 90 volts to 130 volts. Panel meter monitors output voltage. A very handy device at an extremely low price.

MODEL IT-1

\$16⁵⁰

Shpg. Wt. 9 lbs.



HEATHKIT 6-12 VOLT BATTERY ELIMINATOR KIT

This completely modern battery eliminator will supply DC output in two ranges for both 6-volt and 12-volt automobile radios. The output is variable for each range, so that operating voltage can be raised or lowered to determine how the receiver functions under adverse conditions. Range is 0-8 volts DC or 0-16 volts DC. Will supply up to 15 amperes on the 6-volt range, or up to 7 amperes on the 12-volt range. Two 10,000 microfarad output filter capacitors insure smooth DC output. Two separate panel meters indicate output voltage or output current. Makes it possible to test automobile radios inside at the workbench. Will also double as a battery charger.

MODEL BE-4

\$31⁵⁰

Shpg. Wt. 17 lbs.

HEATHKIT 6-VOLT VIBRATOR TESTER KIT

This instrument functions very much like a tube checker, to test auto radio vibrators. Vibrator condition is indicated on a simple "good-bad" scale. Tests for proper starting and overall quality of operation, of both interrupter and self-rectifier types of 6-volt vibrators. The model VT-1 is designed to operate from any battery eliminator capable of delivering continuously variable output from 4 to 6 volts DC at 4 amperes or more. It is an ideal companion unit for the Heathkit Model BE-4 battery eliminator. The construction book for the VT-1 contains vibrator test chart for popular 6-volt vibrator types. A real time saver!

MODEL VT-1

\$14⁵⁰

Shpg. Wt. 6 lbs.

HEATHKIT DX-100 PHONE AND CW



MODEL
DX-100

Shpg. Wt.
107 Lbs.

\$189⁵⁰

Shipped motor freight unless
otherwise specified.
\$50.00 deposit required
on c.o.d. orders.

- * Phone or CW on 160, 80, 40, 20, 15, 11 and 10 meters.
- * Built-in VFO, modulator, and power supplies.
- * High quality components used throughout for reliable performance.
- * Features 5-point TVI suppression.

HEATHKIT COMMUNICATIONS TYPE

ALL BAND RECEIVER KIT

This receiver covers 550 kc to 30 mc in four bands, and is ideal for the short-wave listener or beginning amateur. It provides good sensitivity and selectivity, combined with good image rejection. Amateur bands clearly marked on illuminated dial scale. Employs transformer type power supply—electrical bandspread—antenna trimmer—separate RF and AF gain controls—noise limiter—headphone jack—and automatic gain control. Has built-in BFO for CW reception.

CABINET: Fabric covered cabinet with aluminum panel as shown. Part 91-15A. Shipping weight 5 lbs. \$4.95

MODEL AR-3
\$29⁹⁵

INCLUDING NEW
EXCISE TAX
(Less Cabinet)
Shpg. Wt. 12 Lbs.



EASY ON THE BUDGET!

You can buy Heathkits on an easy time-payment plan that provides a full year to pay. Write for complete details and special order blank.



HEATH COMPANY

A Subsidiary of Daystrom, Inc.
BENTON HARBOR 15, MICH.

Transmitter Kit

The Heathkit DX-100 transmitter is in a class by itself in that it offers features far beyond those normally received at this price level. It takes very little listening on the bands to discover how many of these transmitters are in operation today. A truly amazing piece of amateur gear. The DX-100 features a built-in VFO and a built-in modulator. It is TVI suppressed, and uses pi network interstage coupling and output coupling. Will match antenna impedances from approximately 50 to 600 ohms. Extensive shielding is employed, and all incoming and outgoing circuits are filtered. The cabinet features interlocking seams for simplified assembly and minimum RF radiation outside of the cabinet. Provides a clean strong signal on either phone or CW, with RF output in excess of 100 watts on phone, and 120 watts on CW. Completely bandswitching from 160 through 10 meters. A pair of 1625 tubes are used in push-pull for the modulator, and the final consists of a pair of 6146 tubes in parallel. The VFO dial and meter face are illuminated, and all front panel controls are located for maximum convenience. Panel meter reads driver plate I, final grid I, final plate I, final plate voltage, and modulator current. The chassis is constructed of heavy #16 gauge copper-plated steel. Other high-quality components include potted transformers, ceramic switch and variable capacitor insulation, silver-plated or solid-silver switch terminals, etc. All coils are pre-wound, and the main wiring cable is pre-harnessed. The kit can be built by a beginner from the comprehensive step-by-step instructions supplied. It is a proven, trouble-free rig, that will insure many hours of "on-the-air" enjoyment in your ham shack.

HEATHKIT VFO KIT

You can go VFO for less than you might expect. Here is a variable frequency oscillator that covers 160, 80, 40, 20, 15, 11, and 10 meters with three basic oscillator frequencies, that sells for less than \$20. Provides better than 10 volt average RF output on fundamentals. Plenty of drive for most modern transmitters. Requires a power source of only 250 VDC at 15 to 20 ma. and 6.3 VAC at 0.45A. Incorporates a regulator tube for stability. Illuminated frequency dial reads frequency directly on the band being employed. Temperature-compensated capacitors offset coil heating.

MODEL VF-1

\$19⁵⁰

Shpg. Wt. 7 Lbs.



NEW HEATHKIT CW TRANSMITTER KIT

The brand new Heathkit Model DX-20 Transmitter is one of the most efficient little rigs available today. Featuring an entirely new circuit, it is ideal for the novice, and even for the advanced-class CW operator. A 6DQ6A final amplifier provides plate power input of 50 watts. A 6CL6 oscillator is employed, and a 5U4GB rectifier. The transmitter features one-knob bandswitching to cover 80, 40, 20, 15, 11 and 10 meters. It is designed for crystal excitation, but may be excited by an external VFO. A pi network output circuit matches antenna impedances between 50 and 1000 ohms. Front panel controls are functionally located for your convenience. If you appreciate a good signal on the CW bands, this is the transmitter for you!

MODEL DX-20

\$35⁹⁵

Shpg. Wt. 18 Lbs.

DOLLAR-SAVING ECONOMY . . .

There would be no particular achievement in selling inexpensive merchandise at a low price—although it is being done every day. However, there is something to crow about when, through tremendous purchasing power and factory-to-you distribution, Heath Company can offer top-quality equipment, using name-brand components, at such low prices. This is real economy, as opposed to the so-called "bargains". Needless to say, there is a big difference.

HEATHKIT PHONE AND CW

Transmitter Kit

- * 6146 final amplifier for full 65-watt plate power input.
- * Phone and CW operation on 80, 40, 20, 15, 11, and 10 meters. Pi network output coupling.
- * Switch selection of three crystals — provision for external VFO excitation.



MODEL DX-35

\$56⁹⁵

Shpg. Wt.
24 lbs.

The DX-35 features a 6146 final amplifier to provide 65 watts plate power input on CW, with controlled carrier modulation peaks up to 50 watts on phone. In addition, it is a most attractive transmitter. Modulator and power supplies are built-in, and the rig covers 80, 40, 20, 15, 11, and 10 meters with a single band-change switch. Pi network output coupling provided for matching various antenna impedances. A 12BY7 buffer stage provided ahead of the final amplifier for plenty of drive on all bands. 12BY7 oscillator and 12AU7 modulator. Provision for switch selection of three different crystals. Crystals reached through access door at rear. Front panel controls marked "off—CW—stand-by—phone", "final tuning", "antenna coupling", "drive level control", and "band change switch". Panel meter indicates final grid current or final plate current. A perfect low-power transmitter both for the novice, and for the more experienced operator. A remarkable power package for the price. Incidentally, the price includes tubes, and all other components necessary for assembly. As with all Heathkits, comprehensive instruction manual assures successful assembly.

HEATHKIT ANTENNA IMPEDANCE METER KIT

This instrument employs a 100 microampere panel meter and covers the impedance range of 0-600 ohms for RF tests. Functions up to 150 mc. Used in conjunction with signal source, such as the Heathkit Model GD-1B grid dip meter, the Model AM-1 will determine antenna resistance and resonance, match transmission lines for minimum standing wave ratio, determine receiver input impedance, etc. Will also double as a phone monitor. A very valuable device for many uses in the ham shack.

MODEL AM-1

\$14⁵⁰

Shpg. Wt. 2 lbs.





HEATHKIT "Q" MULTIPLIER KIT

The QF-1 functions with any receiver with an IF frequency between 450 and 460 kc that is not AC-DC type. Operates from the receiver power supply, requiring only 6.3 VAC at 300 ma. and 150 to 250 VDC at 2 ma. Simple to connect with cable and plugs supplied. Provides additional selectivity for separating two signals, or will reject one signal and eliminate heterodyne. A big help on crowded bands. Provides an effective Q of approximately 4,000 for sharp "peak" or "null". Tunes to any signal within the IF bandpass of the receiver, without changing main receiver tuning dial.

MODEL QF-1

\$9⁹⁵

Shpg. Wt. 3 lbs.

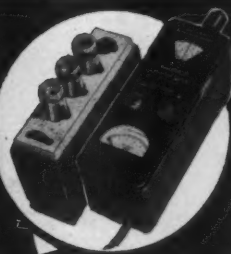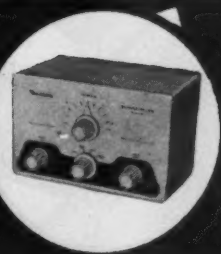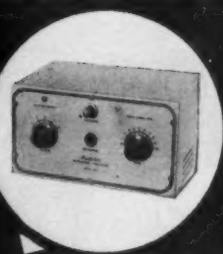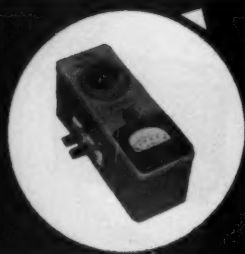

HEATHKIT ANTENNA COUPLER KIT

This device is designed to match the Model AT-1 transmitter to a long-wire antenna. In addition to impedance matching, this unit incorporates an L-type filter which attenuates signals above 36 megacycles, thereby reducing TVI. Designed for 52 ohm coaxial input. Handles power up to 75 watts, 10 through 80 meters. Uses a tapped inductor and variable capacitor. Neon RF indicator on front panel. Copper-plated chassis—high quality components throughout—simple to build. Eliminates waste of valuable communications power due to improper matching. A "natural" for all AT-1 transmitter owners.

MODEL AC-1

\$14⁵⁰

Shpg. Wt. 4 lbs.

HEATHKIT GRID DIP METER KIT

The grid dip meter was originally designed for the ham shack. However, its use has been extended into the service shop and laboratory. Continuous frequency coverage from 2 mc to 250 mc with pre-wound coils. 500 microampere panel meter employed for indication. Use for locating parasitics, neutralizing, determining RF circuit resonant frequencies, etc. Coils are included with kit, as is a coil rack. Front panel controls include sensitivity control for meter, and phone jack for listening to zero-beat. Will also double as an absorption-type wavemeter.

MODEL GD-1B

\$19⁹⁵

Shpg. Wt. 4 lbs.

HEATHKIT BROADCAST BAND



MODEL BR-2

(Less Cabinet)

Shpg. Wt. 10 lbs.

\$18⁹⁵

INCLUDING NEW
EXCISE TAX*

ATTENTION BEGINNERS...

This kit is an ideal "first project" if you have never built a Heathkit before. A good chance to "learn by doing."

- * Miniature tubes and high-gain IF transformer.
- * 5½-inch PM speaker.
- * Rod-type built-in antenna.
- * Provision for phono jack.
- * Good sensitivity and selectivity.
- * Transformer-operated power supply.

Receiver Kit

You need no previous experience in electronics to build this table-model radio. The Model BR-2 receiver covers 550 kc to 1620 kc and features good sensitivity and selectivity over the entire band. A 5½" PM speaker is employed, along with high gain miniature tubes and a new rod-type built-in antenna. Provision has been made in the design of this receiver for its use as a phonograph amplifier. The phono jack is located on the back chassis apron. A transformer operated power supply is featured for safety of operation, as opposed to the usual AC-DC supply commonly found in "economy radio kits." Don't let the low Heathkit price deceive you. This is the kind of set you will want to show off to your family and friends after you have finished building it.

Construction of this radio kit is very simple. Giant size pictorial diagrams and detailed step-by-step instructions assure your success. The construction manual also includes an explanation of basic receiver circuit theory so you can "learn by doing" as the receiver is built. The manual even provides information on resistor and capacitor color codes, soldering techniques, use of tools, etc. If you have ever had the urge to build your own radio receiver, the outstanding features of this popular Heathkit deserve your attention.

CABINET: Proxylin impregnated fabric covered plywood cabinet available for the BR-2 receiver as shown. Complete with aluminum panel, reinforced speaker grill, and protective rubber feet. Shipping weight 5 lbs., part No. 91-9A.....\$4.95*

HEATHKIT PROFESSIONAL RADIATION COUNTER KIT

This sensitive and reliable instrument has already found extensive application in prospecting, and also in medical and industrial laboratories. It offers outstanding performance at a reasonable price. Front-panel meter indicates radiation level, and oral indication produced by panel-mounted speaker. Meter ranges are 0-100, 600, 6,000 and 60,000 counts per minute, and 0-.02, .1, 1 and 10 milliroentgens per hour. The probe, with expansion cord, employs type 6306 bismuth counter tube, sensitive to both beta and gamma radiation. It is simple to build, even for a beginner.

MODEL RC-1

\$79⁹⁵

Shpg. Wt. 8 lbs.



- * Amazing new circuit for high efficiency.

- * Compact, portable and rugged.

- * Stable circuit requires only one 67½ volt "B" battery and two 1½ volt "A" batteries.



HEATH COMPANY

A Subsidiary of Daystrom, Inc.

BENTON HARBOR 15, MICH.


HEATHKIT CRYSTAL RECEIVER KIT

The crystal radio of Dad's day is back again, but with big improvements! The Model CR-1 employs a sealed germanium diode, eliminating the critical "cat's whisker" adjustment. It is housed in a compact plastic box, and features two Hi-Q tank circuits, employing ferrite core coils and variable air tuning capacitors. The CR-1 covers the standard broadcast band from 540 kc to 1600 kc, and no external power is required for operation. Could prove valuable for emergency signal reception. This easy-to-build kit is a real "learn by doing" experience for the beginner, and makes an interesting project for all ages.

MODEL CR-1

\$7⁹⁵

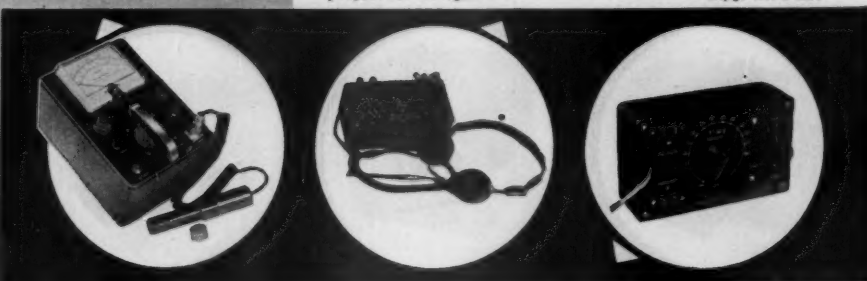INCLUDING NEW
EXCISE TAX*
Shpg. Wt. 3 lbs.



HEATHKIT ENLARGER TIMER KIT

The Model ET-1 is an easy-to-build device for use by amateur or professional photographers in controlling the timing cycle of an enlarger. It covers the range of 0 to 1 minute with a continuously variable, clearly calibrated scale. The timing period is pre-set, and the timing cycle is initiated by depressing the spring-return switch to the "print" position. Front panel provision is made for plugging in the enlarger and a safelight. The safelight is automatically turned "on" when the enlarger is "off". Handles up to 350 watts. The timing cycle is controlled electronically for maximum accuracy and reliability. Very simple to build in only one evening, even by a beginner.

MODEL ET-1

\$11⁵⁰

Shpg. Wt. 3 lbs.

COMPREHENSIVE INSTRUCTIONS . . .

The step-by-step assembly instructions provided with each Heathkit are the finest available anywhere. Each manual begins at the beginning, and assumes no previous training or experience on the part of the kit builder. This means that our kits can be built successfully by anyone who can follow instructions. As a matter of fact, new manuals are tested by having the kit built by someone in our office who has had no previous experience in electronics. This is your guarantee of complete and thorough instruction material.

Literally thousands of these preamplifiers are in use today, because the kit meets or exceeds specifications for the most rigorous high-fidelity applications, and will do justice to the finest available program sources. Provides a total of 5 inputs, each with individual level controls (three high-level and two low-level). Frequency response is within 1 DB from 25 CPS to 30,000 CPS, or within 1½ DB from 15 CPS to 35,000 CPS. Hum and noise are extremely low, with special balance control for absolute minimum hum level. Tone control provides 18 DB boost and 12 DB cut at 50 CPS, and 15 DB boost and 20 DB cut at 15,000 CPS. Cabinet measures only 12-9/16" W. x 3¾" H. x 4¾" D, and it is finished in beautiful satin-gold enamel. 4-position turnover and 4 position roll-off controls provide "LP," "RIAA," "AES," and "early 78" equalization, and 8, 12, 16, and 1 flat position for roll-off. Derives operating power from the main amplifier, requiring only 6.3 VAC at 1 ampere and 300 VDC at 10 MA. Easy to construct from step-by-step instructions and pictorial diagrams provided.

HEATHKIT HIGH FIDELITY

Preamplifier Kit

- * 5 switch-selected inputs, each with its own level control.
- * Equalization for LP, RIAA, AES, and Early 78's.
- * Separate bass and treble tone controls, and special hum control.
- * Clean, modern lines and satin-gold enamel finish.



MODEL (With Cabinet)
WA-P2 Shpg. Wt. 7 Lbs.

\$19⁷⁵

HEATHKIT HIGH FIDELITY FM TUNER KIT

- * Illuminated slide-rule dial covers 88 to 108 MC.
- * Modern circuit emphasizes sensitivity and stability.
- * Housed in attractive satin-gold cabinet to match WA-P2 and BC-1.

This amazing new FM tuner can provide you with real high-fidelity performance at an unbelievably low price level. Covering 88 to 108 MC, the modern circuit features a stabilized, temperature-compensated, oscillator, A.G.C., broadbanded

IF circuits, and better than 10 UV sensitivity for 20 DB of quieting. A high gain, cascaded, RF amplifier is used ahead of the mixer to increase overall gain and reduce oscillator leakage. It employs a ratio detector for high efficiency without sacrifice in high-fidelity performance. IF and ratio transformers are pre-aligned, as is the front end tuning unit. This means the kit can be constructed by a beginner, without elaborate test and alignment equipment. The FM-3A is designed to match the WA-P2 preamplifier and the BC-1 AM MODEL FM-3A tuner. An illuminated slide-rule dial is employed for frequency indication. Step-by-step instructions and large pictorial diagrams assure success.

\$25⁹⁵

INCLUDING NEW
EXCISE TAX
(With Cabinet)
Shpg. Wt. 7 Lbs.



HEATHKIT BROADCAST AM TUNER KIT

This AM tuner has been designed especially for high-fidelity applications. It incorporates a low-distortion detector, a broadband IF, and other features essential to usefulness in high-fidelity. Special voltage-doubler detector employs crystal diodes for low distortion. Sensitivity and selectivity are excellent. Audio response is ± 1 DB from 20 CPS to 2 kc, with 5 DB of pre-emphasis at 10 kc to compensate for station roll-off. Covers the standard broadcast band from 550 to 1600 kc. Incorporates a 10 kc whistle-filter and provides a 6 DB signal-to-noise ratio at 2.5 UV. RF and IF coils are pre-aligned, and power supply is built-in. Incorporates AVC, two outputs, and two antenna inputs.

MODEL BC-1

\$25⁹⁵

INCLUDING NEW
EXCISE TAX
(With Cabinet)
Shpg. Wt. 8 Lbs.

HEATHKIT ELECTRONIC CROSS-OVER KIT

This unusual device functions to separate low frequencies and high frequencies so that they may be fed to separate amplifiers and to separate speakers. This eliminates the need for conventional cross-over circuits, since the Model XO-1 does the complete job electronically. Cross-over frequencies of 100, 200, 400, 700, 1,200, 2,000 and 3,500 CPS are selectable with front panel controls on the XO-1, and a separate level control is provided for each channel. Minimizes intermodulation distortion problems. Handles unlimited power, since frequency division is accomplished ahead of the power stage. Attenuation is 12 DB per octave, with sharp "knee" at cut-off frequency.

MODEL XO-1

\$18⁹⁵

Shpg. Wt. 6 Lbs.

HEATHKIT ADVANCED-DESIGN



MODEL
W-5M
Shpg. Wt. 31 lbs.
Express Only

\$59.75

MODEL W-5

Consists of Model W-5M plus Model WA-P2 pre-amplifier.

Shpg. Wt. 38 lbs.
Express only.... \$79.50

- * Full 25 watt output with KT-66 output tubes.
- * All connectors brought out to front chassis apron.
- * Protective cover over all above-chassis components.

HEATHKIT DUAL-CHASSIS—WILLIAMSON TYPE HIGH FIDELITY AMPLIFIER KIT

This 20-watt high-fidelity amplifier employs the famous Acro-sound Model TO-300 "ultra-linear" output transformer and uses 5881 output tubes. The power supply is built on a separate chassis, and the two chassis are inter-connected with a power cable. This provides additional flexibility in mounting. Frequency response is ± 1 DB from 6 CPS to 150 kc at 1 watt. Harmonic distortion is only 1% at 21 watts, and 1M distortion is only 1.3% at 20 watts. (60 and 3,000 CPS). Output impedance is 4, 8, or 16 ohms. Hum and noise are 88 DB below 20 watts. A very popular high-fidelity unit employing top-quality components throughout.

MODEL W-3M: Shpg. Wt. 29 lbs. Express only..... \$49.75

MODEL W-3: Consists of Model W-3M plus Model WA-P2 pre-amplifier. Shpg. Wt. 37 lbs. Express only..... \$69.50

HEATHKIT 7-WATT AMPLIFIER KIT

This amplifier is more limited in power than other Heathkit models, but it still qualifies as a high-fidelity unit, and its performance definitely exceeds that of many so-called "high-fidelity" phonograph amplifiers. Using a tapped-screen output transformer of new design, the Model A-7D provides a frequency response of $\pm 1\frac{1}{2}$ DB from 20 to 20,000 CPS. Total distortion is held to a surprisingly low level. Output stage is push pull, and separate bass and treble tone controls are provided. Shpg. Wt. 10 lbs.

MODEL A-7E: Similar to the A-7D, except that a 12SL7 tube has been added for pre-amplification. Two inputs, RIAA compensation, and extra gain.

MODEL A-7D

\$17.95

INCLUDING NEW
EXCISE TAX

\$19.95



HEATH COMPANY

A Subsidiary of Daystrom, Inc.

BENTON HARBOR 15, MICH.

HIGH FIDELITY

Amplifier Kit


This 25 watt unit is our finest high-fidelity amplifier. Using a special design peerless output transformer, and KT-66 output tubes by Genalex, the Model W-5M provides performance characteristics unsurpassed at this price level. Frequency response is ± 1 DB from 5 to 160,000 CPS at 1 watt. Harmonic distortion is less than 1% at 25 watts and 1M distortion is less than 1% at 20 watts (60 and 3,000 CPS, 4 to 1). Hum and noise are 99 DB below 25 watts. Damping factor is 40 to 1. Input voltage for 5 watts output is 1 volt. Tubes employed are a pair of 12AU7's, a pair of KT-66's and a 5R4GY rectifier. Measures 13-3/32" W. x 8 1/2" D. x 8 3/4" H. Output impedance is 4, 8, or 16 ohms. Featured, also, is the "tweeter saver" which suppresses high frequency oscillation, and a new type balancing circuit requiring only a voltmeter for indication. This balance is easier to adjust, and results in a closer "dynamic" balance between output tubes. The Model W-5M provides improved phase shift characteristics, reduced IM and harmonic distortion, and improved frequency response. Conservatively rated high-quality components are used throughout to insure years of trouble-free operation. No technical background or training is required for assembly. Step-by-step instructions are provided for every stage of construction, and large pictorial diagrams illustrate exactly where each wire and component is to be placed. An amplifier for music lovers who can appreciate subtle differences in performance. Just ask the audiofile who owns one!

HEATHKIT SINGLE CHASSIS—WILLIAMSON TYPE HIGH FIDELITY AMPLIFIER KIT

The 20-watt Model W-4AM Williamson type amplifier is a tremendous high-fidelity bargain. Combining the power supply and main amplifier on one chassis, and using a special-design output transformer by Chicago Standard brings you savings without a sacrifice in quality. Employing 5881 output tubes, the frequency response of the W-4AM is ± 1 DB from 10 CPS to 100 kc at 1 watt. Harmonic distortion is only 1.5% at 20 watts. Output impedance is 4, 8, or 16 ohms. Hum and noise are 95 DB below 20 watts.

MODEL W-4AM: Shpg. Wt. 28 lbs. Express only..... \$39.75

MODEL W-4A: Consists of Model W-4AM plus Model WA-P2 pre-amplifier. Shpg. Wt. 35 lbs. Express only..... \$59.50

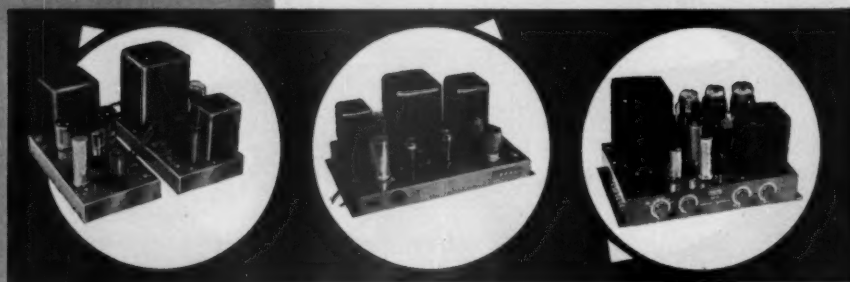

HEATHKIT 20-WATT HIGH FIDELITY AMPLIFIER KIT

This high-fidelity amplifier features full 20-watt output using push pull 6L6 tubes. Built-in preamplifier provides 4 separate inputs, selected by a panel-mounted switch. It has separate bass and treble tone controls, each offering 15 DB boost and cut. Output transformer is tapped at 4, 8, 16, and 500 ohms. Designed primarily for home installations, but also used extensively for public address applications. True high-fidelity performance with frequency response of ± 1 DB from 20 CPS to 20,000 CPS. Total harmonic distortion only 1% (at 3 DB below rated output).

MODEL A-98

\$35.50

Shpg. Wt. 23 lbs.

All prices marked with a † include a new federal excise tax that now applies to receivers, tuners and some amplifiers, even though they may be in kit form. Since the tax is in effect as of July 5, 1956, we have no choice but to reflect it in our kit prices. This note is just to let you know we are not increasing our prices on some kits, but merely including this new tax in them.

Thank you,
HEATH COMPANY

HEATHKIT HIGH FIDELITY

Range Extending SPEAKER SYSTEM KIT

- * High quality speakers of special design — 15" woofer and compression-type super-tweeter.
- * Easy-to-assemble cabinet of furniture-grade plywood.
- * Attractively styled to fit into any living room. Matches Model SS-1.



MODEL
SS-1B

\$99⁹⁵

Shpg. Wt. 80 Lbs.

This range extending unit is designed especially for use with the Model SS-1 speaker system. It consists of a 15" woofer, providing output between 35 and 600 CPS, and a compression-type super-tweeter that provides output between 4,000 and 16,000 CPS. Cross-over frequencies are 600, 1,600, and 4,000 CPS. The SS-1 provides the mid-range, and the SS-1B extends the coverage at both ends of the spectrum. Together, the two speaker systems provide output from 35 to 16,000 CPS within ± 5 DB. This easy-to-assemble speaker enclosure kit is made of top-quality furniture-grade plywood. All parts are pre-cut and pre-drilled, ready for assembly and the finish of your choice. Complete step-by-step instructions are provided for quick assembly by one not necessarily experienced in woodworking. Coils and capacitors for proper cross-over network are included, as is a balance control for super-tweeter output level. The SS-1 and SS-1B can provide you with unbelievably rich audio reproduction, and yet these units are priced reasonably. The SS-1B measures 29" H. x 23" W. x 17½" D. The speakers are both special-design Jensens, and the power rating is 35 watts. Impedance is 16 ohms.

HEATHKIT HIGH FIDELITY SPEAKER SYSTEM KIT



MODEL
SS-1

\$39⁹⁵

Shpg. Wt. 30 Lbs.

- * Special design ducted-port, bass-reflex enclosure.
- * Two separate speakers for high and low frequencies.
- * Kit includes all parts and complete instructions for assembly.

This speaker system is a fine reproducer in its own right, covering 50 to 12,000 CPS within ± 5 DB. However, the story does not end there. Should you desire to expand the system later, the SS-1 is designed to work with the SS-1B range extending unit — providing additional frequency coverage at both ends of the spectrum. It can fulfill your present needs, and still provide for the future. The SS-1 uses two Jensen speakers; an 8" midrange-woofer, and a compression-type tweeter. Cross-over frequency is 1,600 CPS, and the system is rated at 25 watts. Nominal impedance is 16 ohms. The cabinet is a ducted-port bass-reflex type. Attractively styled, the Model SS-1 features a broad "picture-frame" molding that will blend with any room decorating scheme. Pre-cut and pre-drilled wood parts are of furniture grade plywood. The kit is easy-to-build, and all component parts are included, along with complete step-by-step instructions for assembly. Can be built in just one evening, and will provide you with many years of listening enjoyment thereafter.

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 15, MICH.

ORDER BLANK

NOTE: All prices subject to change without notice.

Enclosed find () check () money order for

Please ship C.O.D. () postage enclosed for _____ pounds.

On Express orders do not include transportation charges — they will be collected by the express agency at time of delivery.

ON PARCEL-POST ORDERS include postage for weight shown. ORDERS FROM CANADA and APO'S must include full remittance.

Name _____

Address _____

City & Zone _____ State _____

(PLEASE PRINT)

SHIP VIA

- ☐ Parcel Post
- ☐ Express
- ☐ Freight
- ☐ Best Way

QUANTITY	ITEM	MODEL NO.	PRICE

CENTURY TV TEST EQUIPMENT

- SAVES VALUABLE TIME
- INCREASES YOUR PROFITS
- MAKES TV SERVICING EASIER

SPEAKER SUBSTITUTER

NOW you can pull the chassis and leave the speaker in the cabinet. No more mounting and dismantling... Special speaker connector plugs for RCA, Dumont, Admiral... Also a Signal Tracer and Voltage Checker... \$22.50 net



Model SS-1

Here are test instruments developed and produced by CENTURY to meet your every day service call needs... Brilliantly designed to save your valuable time and make extra dollars for you... Down to earth prices and rugged, durable quality are your assurance of the greatest value in test equipment.

CRT TESTER-REJUVENATOR



Built in power supply enables you to test and repair all picture tubes in or out of set... Check cathode emission... short and open elements. Estimate remaining life of tube... clear inter-element shorts and leakage... restore emission. \$19.95 net

Model CRT-1

ANTENNA LINE TESTER



The only instrument designed to check twin-lead antenna lines with open end antennas for breaks, where a continuity test is not possible. Tests from inside the house whether antenna line is at fault—and locates break even under insulation. \$19.95 net

Model ALT-1

NOW CENTURY INTRODUCES AN ECONOMY LINE

at sensationally low prices


TRANSISTOR CHECK

This new amazingly low priced instrument combines with your VOM to make an accurate and dependable transistor tester. The TC-1 tests all transistors in or out of the set for current gain... leakage... open... short. Checks all crystal diodes for forward to backward gain... Equipped with test leads that enable the serviceman to leave transistor in circuit while checking. \$4.95 net



Model TC-1

REJUVA CHECK

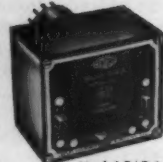

Model RJC-1

The lowest price picture tube test and repair instrument available. Fits snugly in your tube caddy, ready to test, repair and rejuvenate any CRT right in the set. The ingenious RJC-1 powered by TV chassis checks cathode emission—shorts and open elements... Clears inter-element shorts and leakage. Restores emission... No other equipment needed to do the job... \$7.95 net

Century Electronics Co., Inc.

111 ROOSEVELT AVE., MINEOLA, N. Y.

AVAILABLE AT YOUR PARTS JOBBER... Order direct if he cannot supply you.

SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

NEW LIST DI MANY ADDITIONS!

Send stamped, self addressed envelope for List D. Add 25¢ for chart explaining AM nomenclature. DO IT TODAY!

R. E. BOX 1220

GOODHEART BEVERLY HILLS, CAL.

GARAGE DOOR OPENER

Actuator Mechanism \$24.50

EASY TO INSTALL, SAFE, RELIABLE

WRITE for interesting free information... TODAY

P. E. HAWKINS CO.

631 Prospect Kansas City 24, Mo.

LEARN TV

Work on late model sets—using modern equipment and service techniques: under qualified technician instructors. Short resident and correspondence courses—no unnecessary math or theory—also UHF and Color TV. APPROVED FOR VETERANS... day and night classes.

Write for free literature, Dept. IA for residence—Dept. IAC for correspondence.

V.S.I. TELEVISION SCHOOL 4570 Firestone Blvd., Box 359 South Gate, California

Industrial TV Control System

Combines visual observation along with remote control over single coax cable.

A SINGLE-CABLE industrial TV control system, which combines both visual observation and remote control throughout a plant over a closed-circuit TV system, has been introduced by the Jerrold Electronics Corp. of Philadelphia. A unique feature of this system is its ability to carry all functions—two-way pictures, two-way communications, and remote control—over a single coax cable. Previously, a separate cable had been required to carry each of these functions.

This new system permits the use of virtually any closed-circuit TV camera. Cameras of different manufacture can be mixed in the same system and plugged in at any point. While featuring multiple inputs, it also offers an unlimited number of outputs to commercially available television receivers. The system can integrate any of the presently available supervisory control equipment, which can select cameras remotely and adjust them to show the desired picture.

Since the system will provide an outlet in every key area of a factory, various departments can make use of the same camera at different times during the day. No matter where the television camera is plugged into the system, it can be controlled by the user from the point that is most convenient for him.

Control center for mobile closed circuit TV system where visual observation and remote control features are available.



RADIO & TELEVISION NEWS



something wonderful happened

"I don't suppose anyone could have convinced me, beforehand, that the new Fluxvalve would mean so much in the performance of my high fidelity system," says R. W. Sampson, of Princeton, New Jersey.

"Even now, I'm still amazed by the startling clarity of the strings, the richer and fuller range of the basses, the many subtleties that I'd been missing.


"And what makes it all the more satisfying is that *this* time I made the selection myself—without any advice from the 'experts.' I know they have run tests that explain why the Fluxvalve out-performs other pick-ups, but I didn't need this technical data. I *know* how good the Fluxvalve is—because I can *hear* the difference . . . right in my own living room."

Whether you follow the experts—or make your own comparisons—you, too, will find that the new Fluxvalve Pickup gives a new kind of listening pleasure. It can be used with turntables and most of the better changers. So ask your dealer to demonstrate it for you soon. You'll be glad you did.

**WHEN I
CHANGED
TO THE
NEW...**

Fluxvalve

PICKUP

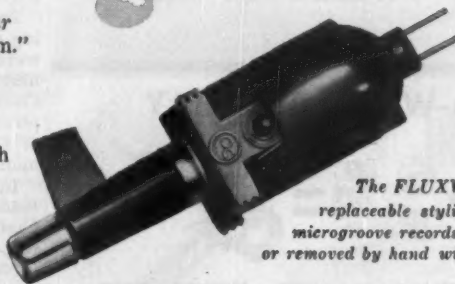

The **FLUXVALVE** features replaceable styli, for standard and microgroove records, that can be inserted or removed by hand without the use of tools.



PICKERING & CO., INC. OCEANSIDE, N. Y.

Professional Audio Components


"For those who can hear the difference"

Demonstrated and sold by Leading Radio Parts Distributors everywhere. For the one nearest you and for detailed literature: write Dept. C-14


EXPORT: AD. AURIEMA, INC., 89 BROAD ST., NEW YORK / CANADA: CHARLES W. POINTON LTD., 6 ALCINA AVE., TORONTO

WIDEST CONTROL COVERAGE EVER ...With New IRC Dealer Parts Stocks

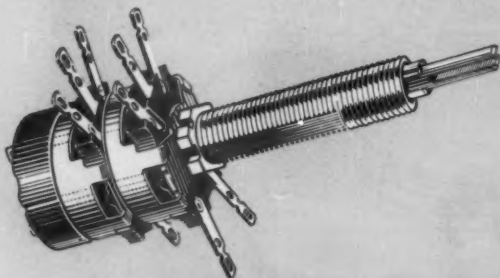New IRC Dealer Parts Stocks put at your fingertips the greatest control coverage ever offered at any price. From these basic stocks of standard parts, you can now assemble most of the controls you need. You're all set for faster service . . . you're safe with IRC quality.



325 EXACT DUPLICATE CONCENTRIC DUALS

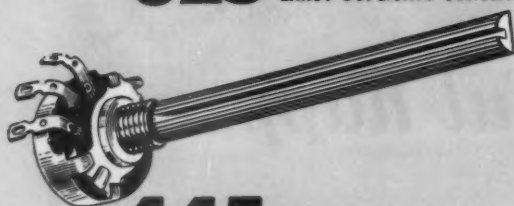

445 SINGLE CARBON CONTROLS



39 SINGLE WIRE-WOUND CONTROLS

TOTAL COVERAGE **809** DIFFERENT CONTROLS COVERING OVER 3700 MANUFACTURERS' PART NUMBERS

"QUICK-AS-A-WINK" ASSEMBLY



BASE-ELEMENT SHAFT INTERCHANGEABLE PARTS COMPLETE CONTROL

Send coupon for all the facts ➡

Wherever
the Circuit Says



INTERNATIONAL
RESISTANCE CO.

Dept. 484, 401 N. Broad St., Phila. 8, Pa.
In Canada: International Resistance Co.,
Ltd., Toronto, Licensee

Spot Radio News

(Continued from page 16)

1500-mile radius, dropping radiosondes at preset points. Although most of the drops are made over oceans and polar regions, sondes are often dropped into the eyes of whirling hurricanes to determine weather there.

A NEW VERSION OF A FLAT TV picture tube for color was described recently in London by Dr. Denis Gabor of the Imperial College of Science and Technology, at a meeting of the Television Society.

The new tube was noted as having the shape of a rectangular glass box, having a total depth of only 4½ inches for a 21-inch screen. The tube is divided into two halves by a metal tray which carries the complete electron optical system, and which also acts as a magnetic screen for the beam. By an ingenious system of electron lenses, the beam is curved to run parallel with the glass faces of the tube, and is finally deflected towards the screen by a series of conductors which run parallel to the screen itself.

Commenting on the construction of the tube, Dr. Gabor said that the flat tube can be made safer than the conventional picture tube, because the glass can be specially toughened, as the glass used in cars. Thus, it was noted, the tubes might dispense with the safety screen in front.

Silicones are used as insulation in the electrode system. This is believed to be the first time they have been applied in a sealed-off vacuum device. In the color models, the separate phosphors are deposited on the glass face through a shadow mask by a method which was described as being more economical than the present technique of depositing a color screen by printing a phosphor in register.

Although the new tube was still in the development stage, it was said that the main problem of making a satisfactory flat tube had been resolved and commercial production should not be too remote.

WITH MORE THAN a million fixed, portable, and mobile transmitters in operation, policing the radio spectrum has become a vast and time-consuming task for the FCC.

In a recent report on the odd problems the Commission is called on to solve through their Field Engineering and Monitoring Bureau, it was disclosed that solutions must be found for situations that might crop up on the sea, in the air, and in such far-off places as Hawaii.

Commenting on the trouble call in Hawaii, the Commission said that a plane en route from these sun-drenched islands radioed a distress call that a fire aboard had disrupted its navigational aid system. FCC monitoring stations obtained bearings which enabled the Coast Guard to guide the plane to safety.

Monitoring fixes from the FCC's field crew also helped to bring in a military transport plane which had developed engine trouble while nearing this country from the Azores.

In another entry, the FCC reported that early one morning operators in New York City police radio headquarters were startled to hear a woman's voice calling: "... running out of fuel ... crash landing ... plane 3417." While Coast Guard helicopters scanned the area, a series of phone calls made it possible to trace the hoaxer; a mother of four children. She was committed to a hospital for mental observation.

In California, interference to radio communications was traced by an FCC mobile monitoring unit to an electronic heater. In Florida, an arc welder in a shipyard was found responsible for disruption of marine radiotelephone service.

Nearly 150 illegal radio stations were discovered and closed by the FCC during the year. One was being used to transmit signals to operate a swing bridge over a Texas waterway. Another was employed by a retired tugboat captain to keep up his contacts with coastal radiotelephone stations.

Elsewhere, the FCC found that even a toy broadcast station can cause trouble. Its very young operator burst into tears when told that his programs were going on the air. The FCC engineer, noting the lad's genuine interest in radio, suggested that he take up amateur radio as a hobby. So this youthful tragedy was compensated by the

boy's new interest in trying to qualify for real two-way contact through ham radio service.

Another listing in the interference book concerned a Pacific coast radiotelegraph carrier who had been complaining that an unidentified strong signal was blotting out its communication with ships. Aided by a monitoring station general fix, an FCC mobile unit got a more definite bearing from a mountain top. This led back to the telegraph company's own station, where a transmitter revealed a faulty exciter unit. The only thing needed here was readjustment.

AS THIS COLUMN was being written during the final weeks of '56, TV's growth along station row was still bottled up by investigations, probes, and petitions. The slow station-grant pace set in the early days of the year continued and as a result authorizations were only trickling out. As the listings on page 12 show, the output continues to be quite meager.

UNUSUAL ELECTRONIC TOOLS involving TV and radio are now in use by oil companies.

In the southwest, a marine sonoprobe has been developed for exploring of the ocean floor and sediments 80 feet or beneath it; useful for offshore oil exploration, submarine pipeline construction, and underwater salvage operations.

The sonoprobe is similar in construction and operation to conventional recording echo sounders used for measuring the depth of water, but it has been specially designed to get echoes from beneath the ocean floor.

The instrument used a special sound source which produces sound pulses of much lower frequency and much greater power than in conventional echo sounders. These pulses have been found to penetrate bottom sediments and are reflected back from layers beneath the bottom.

The sea floor and layers beneath it are displayed on a small TV picture tube and are also recorded as a continuous profile on electrosensitive paper.

The electronic sea probe, intended for use in water-covered areas of the world, where conditions are favorable, can be mounted on shallow-draft boats for use in shallow water or on larger vessels for use in deeper water.

The instrument was originally designed, built, and tested for underwater geological research; it has also been used for mapping the routes of underwater pipelines and in surveying sites for offshore drilling platforms, for which pilings must be driven into the sea bottom.

In addition, the new tool has been used to find buried beds of oyster shells, which are then dredged from beneath the ocean floor for use in road construction and in making cement, chemicals, and fertilizer.

Experience with the new device indicates that it will provide reliable maps of shallow salt domes, shallow faults, buried ancient channels and valleys, and shallow geological structures. It may also give useful information to determine the extent of silting in reservoirs.

ON THE NORTHEAST of Borneo, electronics has also come to the rescue of oil operations. There a remote-control radio installation has been developed to meet difficulties involved in loading oil into tanks 3½ miles off the shore of Sarawak.

Because of the shallowness of the water off Sarawak, tankers are forced to load miles off shore using underwater pipelines, creating many engineering problems. The radio system has solved the problem.

Now, as a tanker approaches the moorings for a loading, a portable transmitter-receiver is taken on board, which in addition to providing a connection with the shore terminal, can transmit on a special pump control channel. Should it be necessary to stop the pumps in an emergency, the depressing of a control button on the panel of the portable set overrides the telephone channel and brings the pump control channel into operation.

Seven portable radio units are employed. They incorporate loud-hailing facilities and a remote-control unit which enables the equipment to be operated up to a distance of three hundred feet from the base. . . . L. W.

February, 1957

97

MOST CONTROL COVERAGE PER \$...With New IRC Dealer Parts Stocks

\$15 worth of
coverage for every \$1
you invest!


No wonder IRC Dealer
Parts Stock #21 is the
biggest bargain in control
history. Two master
stockers contain all the
parts you need for coverage
on 469 different
controls. This wide coverage
would cost you
\$752 in assembled controls,
but Parts Stock
#21 gives it to you for
only \$49.90!



**Dealer Parts Stock
#21—Only \$49.90**

Dealer Parts Stock #22
Widest coverage ever available in a parts kit!

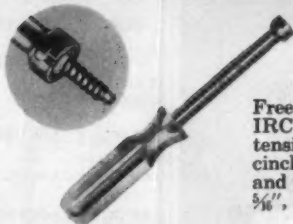Dealer Parts Stock #22 sets you up for practically every
control you'll need. 209 different controls altogether, including
special wire-wounds. It would take \$1245 to buy
the same coverage in factory controls, yet Dealer Parts
Stock #22 sells for only \$99.90!



IRC TENSION-GRIP NUT DRIVERS

Free a hand . . . save your temper with
IRC's non-magnetic nut driver. Vise-like
tension band makes driving or removing a
cinch. Nuts and hex screws won't twist—
and they can't drop. Six socket sizes: ¼",
⅜", ½", ⅝", ¾", and 1½".



INTERNATIONAL RESISTANCE CO.

Dept. 484, 401 N. Broad St., Phila. 8, Pa.

Send the facts about the biggest control coverage bargain in history.

NAME _____

DEALER _____

ADDRESS _____

CITY _____ STATE _____

BUILD THE BEST— BUILD ALLIED'S OWN knight-kits

ALLIED stakes its 36-year reputation in the Electronics field on your complete success and fullest satisfaction with KNIGHT-KITS. Join the thousands who have discovered the ultimate in kit value in...

knight-kits

LOWEST COST because our giant buying power passes biggest savings on to you... you do the easy assembly and your finished instrument is equal in performance and appearance to equipment selling for several times the KNIGHT-KIT cost. (Easy Payment Terms available, too.)

knight-kits

EASIEST TO BUILD because KNIGHT-KIT "Step-and-Chek" instruction manuals are marvels of clarity—it's just like having a good instructor at your side. Proved professional design and premium quality parts help insure your building success.

knight-kits

MONEY-BACK GUARANTEE:
When properly assembled, KNIGHT-KITS fully meet published specifications, or we refund your money.

WHEN YOU BUILD A KNIGHT-KIT
YOU BUILD THE BEST

For a Complete Selection of
Famous knight-kits
SEE PAGES 117-123

Available Only From
ALLIED RADIO
100 N. Western Ave., Chicago 80, Ill.

New Tube Tester Data

New radio and TV tubes are always being introduced. Bring your Eico and Philco tube checkers up to date with the data listed here for the new tube types.

EICO MODEL 625

No.	Shunt	Fil.	Sel.	Up	Down	No.	Shunt	Fil.	Sel.	Up	Down
2BN4	25	2.0	2	2,5,7	1,3,6	6CG8	25	6.3	2	1,2	3,4,8
3B2	100	3.3	4	10	1,3,5,7	(NO shorts test on levers 3 and 8)					
(Good = 500)						6CH8	24	6.3	2	2,3,7	4,6
4BS8	19	3.3	3	1,2	3,4	6CH8	26	6.3	2	8,9	1,4
4BS8	19	3.3	3	6,7	4,8	6CR6	27	6.3	2	5,6,7	1,3
4BX8	16	3.3	1	6,7	4,8	6CR6	30	6.3	1	2	1,3
4BX8	16	3.3	1	1,2	3,4	6DC6	22	6.3	2	1,5,6	2,3,7
5CG8	24	5.0	2	6,7,9	3,4,8	6DQ6	18	6.3	3	4,5,10	2,8
5CG8	26	5.0	2	1,2	3,4,8	12AC6	17	12.6	1	1,5,6	2,3,7
(NO shorts test on levers 3 and 8)						12AD6	16	12.6	1	1,5,6,7	2,3
6BK4	100	6.3	4	10	1,2,3,4,6,8	12AD6	16	12.6	1	1,6	2,3
(Good = 50)						12AE6	18	12.6	1	1,7	2,3
6BN4	25	6.3	2	2,5,7	1,3,6	12AE6	50	12.6	1	6	2,3
6BR8	24	6.3	2	6,7,9	4,8	12AF6	16	12.6	1	1,5,6	2,3,7
6BR8	24	6.3	2	1,2	3,4	12CR6	29	12.6	2	5,6,7	1,3
6BS8	19	6.3	3	1,2	3,4	12CR6	29	12.6	1	2	1,3
6BS8	19	6.3	3	6,7	4,8	12CU5	20	12.6	3	2,5,6,7	1,3
6BX8	16	6.3	1	6,7	4,8	12DQ6	18	12.6	3	4,5,10	2,8
6BX8	16	6.3	1	1,2	3,4	12F8	16	12.6	1	2,3,8	4,7,9
6CB5	20	6.3	3	1,4,5	2,3,6,8,10	12F8	37	12.6	1	6	4,7
6CG8	24	6.3	2	6,7,9	3,4,8	12F8	37	12.6	1	1	4,7
						12K5	16	12.6	1	2,5,6,7	1,3

PHILCO MODELS 7050 and 7051

Tube	Fil.	Tog.	Sw.	Load	Tog.Sw.	Tube	Fil.	Tog.	Sw.	Load	Tog.Sw.	Tube	
Type	Cont.	Short	Cont.	Qual.	Test	Sec.	Type	Cont.	Short	Cont.	Qual.	Test	Sec.
2B3	2	kmop	8	KMOPT			6CL8	6	ABCDEFF	3	BCEF		T
3AF4	4	bnrsAFE	4	BNERS		T				Cannot be tested		P	
3BU8	4	ABCDEF	3	ABE		P1	6X8*	6	ABCDEF	2	BDE		P
			3	AF		P2			2	ABCF		T	
3C2	1	klmneph	4	KLMNEPHT			8AU8	7	ABCDEF	3	A		P
3CE5	4	bnrEFS	14	ABNG					3	B		T	
4BC5	5	bnrAGEF	2	ABGNT			8BA8	7	ABCDEF	4	ABCF		T
4BN6	5	nbAEFG	2	BNRT					4	ABDE		P	
4BU8	5	ABCDEF	3	ABE		P1	8BH8	7	ABCDEF	4	A		T
			3	AF		P2			4	B		P	
4BX8	5	CDEF	3	ADEF		T1	8BN8	7	ADBECF	4			T
			3	BCEF		T2			4	CEF		D1	
4CB6	5	bnrAGEF	4	ABGNT					4	CDF		D2	
4CE5	4	bnrEFS	14	ABNG			8CG7	7	ABCDEF	7	F		T1
4DT6	5	bnAEFGS	14	ABN					7	E		T2	
5AU4*	5	mABDEF	4	MD		D1	8CM7	7	ABCEEF	4	AEF		T1
			4	BM		D2			4			T2	
5BQ7	6	ABCDEF	2	ADEF		T1	8CN7	5	hABCDEF	5	AEH		D1
				BCEF		T2			5	DEH		D2	
5BR8	5	ABCDEF	3	BCEF		T			6	BH		T	
			11	ADEF		P	8SN7	7	csABDEF	2	ABCF		T1
5BZ7	6	CDEF	3	ADEF		T1			2	ABCDSE		T2	
			3	BCEF		T2	9AU7	5	hABCDEF	7	EH		T1
5X8*	5	ABCDEF	2	BDE		P			7	FH		T2	
			2	ABCF		T	9U8	7	ABDEFCF	Cannot be tested		T	
6BU8	6	ABCDEF	3	ABE		P1			3	ACF		P	
			3	AF		P2	12AD7	6	hABCDEF	7	EH		T1
6BV8	6	ACCFBDE	3	ABCF		T			7	FH		T2	
				Cannot be tested		D1	12AE6	8	bnAEFG	4	ABNEFRFT		T
			4	ACDEF		D2			11	ABNE		D1	
6BX8	6	CDEF	3	ADEF		T1			11	ABNF		D2	
			3	BCEF		T2	12AF6	8	bnrAEF	5	BGNS		
6CG8	6	ABCDEF	4	BCEF		T	12AG6	6	bnAEFGS	11	ABN		
				Cannot be tested		P	12D4	8	cAB	4	AC		
6CH8	6	ABCDEF	Cannot be tested			T	12F8	8	ABCDEF	11	BCDEF		D1
			5	ABF		P			11	ACDEF		D2	
									4	ABC		P	

*Revised data

for just **27¢** per day—

PHOTOFACT—the world's finest TV-radio service data comes to you...keeps you right up-to-the-minute on new model releases...is delivered automatically by your Parts Distributor as each new Folder Set is issued. Yes, for just 27¢ per day...

PHOTOFACT can help you double your repair output



Exclusive PHOTOFACT features help you solve any service problem faster...help you earn more

PHOTOFACT offers you complete coverage on over 30,000 TV, Radio, Amplifier, Tuner and Changer models. And PHOTOFACT is a current service—keeps you right up with late model production—brings you these exclusive features...

Full Schematic Coverage: Famous "Standard Notation" uniform symbols are used in every schematic. Diagrams are large, easy to read and handle. Wave forms and voltages are shown right on the schematic for fast analysis. Transformer lead color-coding and winding resistances appear on the schematic. Schematics are keyed to parts lists and to parts on chassis photos.

Full Photographic Coverage: Photos of all chassis views are provided for each model; all parts are numbered and keyed to the schematic and parts lists for quicker parts identification and location.

Alignment Instructions: Complete, detailed alignment data is standard and uniformly presented in all Folders. Alignment frequencies are shown on radio photos adjacent to adjustment number—adjustments are keyed to schematic and photos.


Tube Placement Charts: Top and bottom views are shown. Top view is positioned as seen from back of cabinet. Blank pin or locating key on each tube is shown. Charts include fuse location for quick service reference.

Tube Failure Check Charts: Shows common trouble symptoms and tubes generally responsible for such troubles. Series filament strings are schematically presented for quick reference.

Complete Parts Lists: Detailed parts list is given for each model. Proper replacement parts are listed (with installation notes where required). All parts are keyed to chassis photos and schematics for quick reference.

Field Service Notes: Each Folder includes time-saving tips for servicing in the customer's home. Gives valuable hints for quick access to pertinent adjustments, safety glass removal, special advice covering the specific chassis, etc.

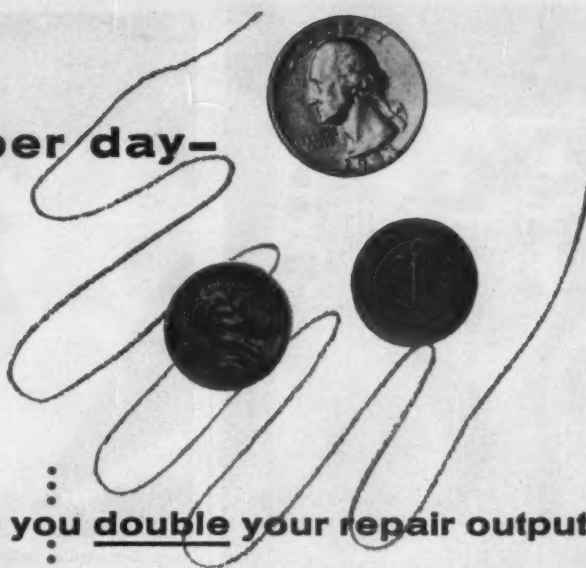with PHOTOFACT by your side, you solve your service problems in just minutes...you SERVICE MORE SETS AND EARN MORE DAILY...



The regular monthly issues of Sam's PHOTOFACT provide you with up-to-the-minute service data on new models as they are produced, for as little as 27¢ per day! And this includes the "bonus" schematic service on new models hot off production lines to give you *immediately* the essential data you need.

With a current PHOTOFACT library at your fingertips, you can actually *double* your repair output, because *you save valuable time on every job. YOU EARN MORE DAILY.*

Learn how easy it is to sign up with your Parts Distributor to receive all Sams' PHOTOFACT Sets regularly as published each month. Learn for yourself how a small investment of only 27¢ per day can mean GREATER income for you.

SPECIAL OFFER: If you return the coupon below and indicate your interest in receiving PHOTOFACT regularly each month, we will arrange to have delivered to you, **ABSOLUTELY FREE**, a valuable and attractive Wall Holder for the "Index to Photofact Folders" as well as the latest copy of the Index. Be sure to give your Distributor's name.

HOWARD W. SAMS & CO., INC.
2203 E. 46th St., Indianapolis 5, Indiana

☐ I am interested in receiving all new PHOTOFACT Sets regularly as published each month. Send full details (I understand there is no obligation on my part, and that I will receive without charge, the latest "Index to Photofact", along with Wall Holder).


☐ I am a Service Technician: ☐ full time; ☐ part time.

My Distributor is: _____

Name: _____

Address: _____

City _____ Zone _____ State _____

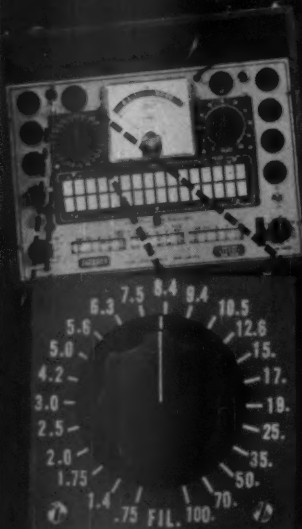

23 Separate Heater Voltages on the Dynamic® JACKSON 648A Assure Accurate Tests for all Series-String Tubes ...The Correct Voltage for Every Known or Presently Planned Type.

YOU CAN MODERNIZE YOUR PRESENT 648

New 648 FV Kit provides same heater voltages as the new 648A Tester. Only four wires to solder. Installs in minutes. Available from your distributor now.

JACKSON
ELECTRICAL INSTRUMENT CO.

*'Service Engineered'
Test Equipment*

16-18 S. Patterson Boulevard • Dayton 2, Ohio
In Canada: The Canadian Marconi Company



Bombardier (left) and navigator (right) operate this 2-man station at master control panel of a later version of fabulous "K-System" bombing-navigation controls.

B-52 Bomb Navigation System...

*First photos of system
that pinpoints any spot
on globe in any weather.*

FAR cry from the relatively simple "bombsight" of early World War II is this later version of the "K-System" bombing-navigation controls in new USAF B-52 Stratofortress bombers. These are first operational views of a master control panel, just released 10 years after the system was initially developed and produced by Sperry Gyroscope for the still-formidable B-47 and B-36 squadrons of Strategic Air Command. First view here reveals, by a selector switch above navigator's helmet (top right), the trans-polar range capability of the bombers.

The K-System automatically measures distance and time to target, computes ballistics of bomb's curve for existing altitude, temperature and crosswinds, permits final hairline adjustment via radar or optical sight, triggers bomb away at proper instant, then helps the navigator to guide the shortest way home.

Originally designed, developed, and produced by Sperry Gyroscope, manufacture of this critical gear was rapidly dispersed through other plants of General Motors, National Cash Register, and IBM. Eastman Kodak, Western Electric, General Mills, Motorola, and Farrand were multiple prime or sub-system sources. Western Electric developed the radar. In all, about one

million factory workers and technicians in 36 states, at 3050 companies large and small, have been directly engaged in this Air Force program to supply needed K-Systems.

More than 70,000 individual parts make up the various computers and other elements of a single K-System for an individual aircraft—about as many parts as a modern automobile with power steering and automatic transmission. Each system contains complex circuitry for hundreds of pre-tested vacuum tubes, over 50 motors, and about 100 relays, with many sealed amplifiers for quick unit replacement while in the air.

The original prototype cost of nearly a half-million dollars was reduced to less than half by manufacturing improvements in volume production. Nearly 900 major improvements for system efficiency through all production channels have been made in the last six years.

Sperry is now "phasing out" its K-System activity, and turning to more advanced gear. Meantime, the Air Force has announced the later-model B-52's will replace the K-System with an improved "Brane" bombing system to be produced by IBM. —(50)—

Bombardier has complete control of aircraft for the final moments of target run.



RADIO & TELEVISION NEWS

it's new!

SEND FOR THIS
FREE
BOOKLET TODAY

your
future
in the
new world of
ELECTRONICS

RADAR • GUIDED MISSILES • SERVO •
COMPUTERS • AERONAUTICAL •
BROADCASTING AM FM TV •
MILITARY • NAVY • CAA •
COMMUNICATIONS •
MANUFACTURING

CAPITOL RADIO ENGINEERING

Turn
this page

See what
the rapidly
expanding
field of
ELECTRONICS
offers you

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed in United States


3c Postage Will Be Paid By

CAPITOL RADIO ENGINEERING INSTITUTE

3224 16th Street, N.W.

Washington 10, D. C.

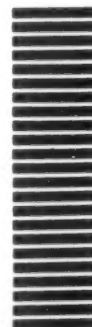1st Class
Permit No. 288-R
Sec. 34.9 P.L.R.
Washington, D. C.



Sales Aids

SELF-SERVICE TAPE DISPLAYS

Minnesota Mining and Manufacturing Co., 900 Fauquier Street, St. Paul 6, Minn. has introduced three new self-service tape merchandisers which are now appearing in stores throughout the country.

Due to the growth of the tape recording industry, magnetic tapes are now easier for the recorder owner to select and buy. Stores now handling tape and recorders include photo stores, music and record shops, high-fidelity equipment dealers, appliance stores, and department stores.

In the past, however, the tape recorder owner has had to ask his dealer whether he sold magnetic tape. With



these new merchandisers the purchaser will be offered a full line of magnetic tape and will find it conveniently displayed for self-service.

PROFITABLE BUSINESS MANUAL

Stromberg-Carlson has prepared a new manual outlining the most important steps in conducting a profitable business.

The 36-page booklet contains a quick and easy method for estimating the market potential and probable sales for an individual dealer in a given area, and suggests a suitable promotional budget based on a percentage of this volume. The dealer is also shown how to make allowances for such factors as competition, cooperation from his supplier, and general buying trends.

Further guidance also is given on the dealer's approach to various media and services commonly used, such as newspaper, radio and television advertising, direct mail, displays, shows, etc., with suggested percentages for each. How to schedule promotions, build mailing lists, answer inquiries, write sales-pulling letters, how to select music for and handle demonstrations, organize shows and "open houses," how to make best use of mats, and suggested copy for newspaper ads, are all



ACTUAL SIZE

PRECISION 110

'THIN-LINE' POCKET-SIZE Model
20,000 ohms-per-volt V.O.M.

Model 110:
Complete with vinyl case, ohmmeter batteries, heavy-duty banana-plug test leads and manual. Dimensions 1 1/4" x 3 1/2" x 5 3/4". Shipping weight 3 lbs. Net Price \$34.95

— Also Available —
Model 100: Similar to Model 110 above, except 1000 ohms per volt AC and DC. Net Price \$29.95

- Full-Range Instrument Performance small-sized instrument convenience
- Fits Your Pocket... Fits Your Tube-Caddy... the ideal extra V.O.M. for field and service
- Extra-High Sensitivity 20,000 ohms per volt DC... 5000 ohms per volt AC
- Extra-Low... Extra-High Voltage Ranges 1.5 volts full-scale extra-low AC and DC 3000 volts full-scale extra-high AC and DC
- Extra-Wide Resistance Ranges self-contained up to 20 megohms
- Complete Current Ranges Up to 600 ma
- Complete Decibel Ranges from -20 to +70 db
- 3 1/2" Full-View Meter... Long, Easy-Reading Scales



Available at leading electronic parts distributors.

PRECISION Apparatus Company, Inc.
70-31 84th Street, Glendale 27, L. I., N. Y.

Export: 458 Broadway, New York 13, N.Y., U.S.A. • Cables: MORHANEX
Canada: Atlas Radio Corp. Ltd. • 50 Wingold Ave., Toronto 10, Ontario

FREE!
 FOR THE
 ASKING

the NEW
 INDISPENSABLE
1957
STANCOR
 TV
 TRANSFORMER
 REPLACEMENT
 GUIDE

to every
 serviceman



JUST RELEASED: 8 new
 exact replacement fly-
 backs for Raytheon, G.E.,
 RCA, Sentinel, Philco, and
 Admiral



The most complete, up-to-date
 TV transformer replacement guide
 published:

- 72 pages of valuable information
- Easy-to-read, easy-to-find listings,
 indexed alphabetically by manufac-
 turer, model and chassis numbers
- Easy-to-find exact replacement
 flyback listing of manufacturer and
 manufacturer's part number
- Schematic diagrams of all flybacks
- Complete specifications on 260
 Stancor TV transformers and
 related components

Get the new Stancor Replacement Guide
 from your Stancor distributor or by
 writing to Chicago Standard . . . NOW!

CHICAGO STANDARD TRANSFORMER CORPORATION
 3503 ADDISON STREET • CHICAGO 18, ILLINOIS

EXPORT SALES: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N.Y.

**college grads get
 ahead faster!**

... have higher incomes ... advance more rapidly.
 Grasp your chance for a better life. Share rewards
 awaiting college-trained men. Important firms visit
 campus regularly to employ Tri-State College gradu-
 ates. Start any quarter. Approved for Vets.

Bach. Sc. degree in 27 months
 Complete Radio Eng. courses (TV, UHF, FM, Elec-
 tronics). Also Mech., Civil, Elec., Chem., Aero., Eng.
 36-months in Bus. Adm. (Gen. Bus., Acctg., Motor
 Transport Mgt.). Superior students faster. More pro-
 fessional class hours. Small classes. Enrollment lim-
 ited to 1650. Beautiful campus. Well-equipped lab.
 Prep courses. Enter Mar., June, Sept., Jan. Earnest,
 capable students (whose time and budget
 require accelerated courses and modest
 costs) are invited to write Jean McCarthy,
 Dir. Adm., for Catalog and "Your Career in
 Engineering and Commerce."



TRI-STATE COLLEGE

1627 College Avenue Angola, Indiana

WANT TO BUY!

BC-224, BC-348 RECEIVERS
 ARC-3 BC-788 R5/ARN-7

Cash or trade. Immediate action.

HARJO SALES CO.

503 N. Victory Blvd., Burbank, Calif.

We pay MOST the FASTEST for:

AIRCRAFT ELECTRONICS
 Transmitters Receivers
 ADF Altimeters
 Indicators Antennas
 Dynamotors Inverters

INSTRUMENTS
 Air Speeds
 Altimeters
 Compasses
 Gyros

NATCO AVIATION

3012-B West Burbank Blvd.


Burbank, Calif.

discussed in simple language that is
 well organized for quick reference.

Copies of the manual have been
 mailed to the company's "Custom Four
 Hundred" high-fidelity dealers, by the
 firm's Special Products Division, Roch-
 ester, N. Y.

RAM COIL DISPLAY

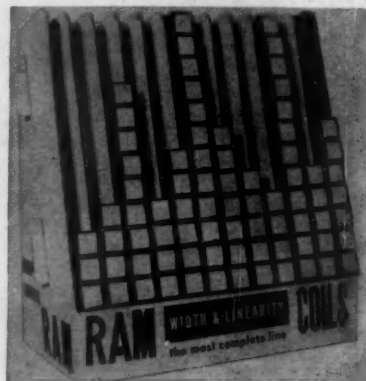RAM Electronics Sales Company has
 created a new counter and wall display
 designed specifically to help distribu-



tors boost the sale of width and lin-
 earity replacement coils.

It stocks, displays, and enables re-
 filling and inventory check in just a
 few minutes.

For further data, write to the com-
 pany at: Irvington-on-Hudson, New
 York.

VACO "TOOL CENTER"

Vaco Products Company has intro-
 duced its "Tool Center" display in the
 form of a "Vari-Board" back panel and
 roomy storage cabinet with sliding
 doors underneath.


The "Vari-Board" perforated back
 panel is 3½ feet high and 4 feet wide,
 offering 14 square feet of display space.
 Over the top is an illuminated canopy
 which gives the tools a dramatic set-
 ting.

The storage cabinet is 48" wide, 15"



deep, and 18" high. The entire unit
 rests on four wrought iron black lac-
 quered legs, pitched at a modernistic
 angle.

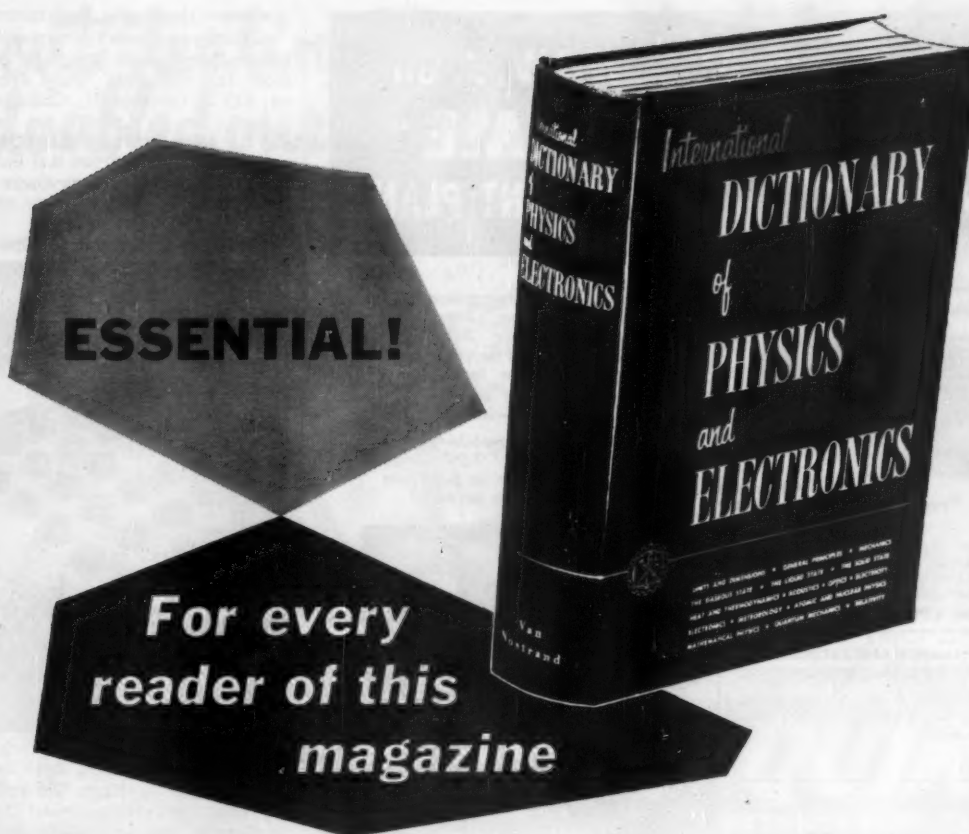The display is furnished with a basic
 assortment of tools containing general
 purpose screwdrivers, nut drivers, pli-
 ers, wood chisels, and screwdriver and
 nut driver kits. All items are self
 priced. This unit may also be pur-



For the first time! A unique new dictionary of physics and electronic terms to meet the demands of our electronic and atomic age.

OVER 12,000 TERMS — OVER 500,000 WORDS — OVER 1000 PAGES

Now you can find all the principal terms in one big book, covering pure and applied science, that will be most helpful in your work.

Each of the more than twelve thousand definitions and articles have been chosen and written to supply quickly and exactly, clear and unambiguous definitions.

They include laws, relationships, equations, basic principles and concepts, as well as the most widely used instruments, apparatus and their components. All defini-

tions, wherever possible, which have been established or recommended by recognized groups are included. Many terms that have been defined from the subject areas bordering on physics will be especially helpful. And, for those without an extensive mathematical background, both explicit and discursive statements and entries are given, as well as the definitions of the more common mathematical terms encountered.

More than five years of planning and preparation by a distinguished group of scientists and educators were needed to produce this important volume. Thumb indexed for convenience, and containing a helpful cross referencing plan, it is perhaps the most valuable addition to your professional library you can make. Order your copy for 10 days free examination. Actually see and use this great book to prove its immense value to yourself.

SPECIAL OFFER

To enable you to quickly and easily acquire this monumental work send only a small first payment of \$5.00 (plus postage) and then just \$5.00 a month for three months until the purchase price of \$20.00 is paid in full. Act now while this offer lasts! Fill out and mail the coupon today. D. VAN NOSTRAND COMPANY, Inc. Princeton, N. J.

Save! Send \$20.00 with order and we pay postage

Mail This Coupon

D. VAN NOSTRAND COMPANY, Inc.
120 Alexander St., Princeton, N. J.

Dept. RTV-257

Gentlemen: Kindly send me your new International Dictionary of Physics and Electronics.

☐ I want it on easy terms. After 10 days I will either remit \$5.00 (plus postage) and then pay \$5.00 per month for three months, or I will return book post paid, and owe nothing.

NAME _____

ADDRESS _____

CITY _____

STATE _____

LAMPKIN FREQUENCY and FM MODULATION METERS

NOW... on TIME PAYMENT PLAN

Enter the lucrative mobile-radio maintenance field—AT LOW COST!



Price \$220.00
Type 105-B Frequency Meter



For free booklet "HOW TO MAKE MONEY IN MOBILE-RADIO MAINTENANCE," and other data—
USE COUPON TODAY

LAMPKIN LABORATORIES, INC.
MFM Division, Bradenton, Florida

At no obligation, please send me free booklet, technical data on Lampkin meters, and time-payment plan details.

Name _____
Address _____
City _____ State _____

Lampkin's new easy-payment plan makes it possible for you to start in mobile-radio maintenance NOW—and the monthly payments for your essential test equipment will be far less than your expected earnings.

You've read how mobile-radio is bursting its seams! NOW—you can start cashing in on this boom...with a low down payment!



Price \$240.00
Type 205-A Modulation Meter

LAMPKIN LABORATORIES, INC.
MFM Division
BRADENTON, FLORIDA

As easy to use as a pencil

WALL
INDUSTRIAL
SOLDERING IRONS
give you

More
BTU's...

Faster
HEAT...

HIGHER HEAT
CONTINUITY

than **ANY OTHER**
soldering irons of equal tip size

Proved 4 times faster on the production lines of America's leading electronics firms. Complete range of sizes... scientifically designed... individually tested... for easier, surer precision work or heavy duty soldering. Operate on 110-120 volts, AC or DC! Model 18T illustrated, \$6.25 list.



Write for FREE Catalog

WALL

MANUFACTURING CO.
Grove City, Pennsylvania

OVER 20,000,000 SOLDERING PRODUCTS SINCE 1864



Exclusive
THERMOSTATIC ACTION...

Guaranteed for the life of the iron!
Prevents excessive tip burning!

chased without the tool merchandise.

A four-page bulletin containing complete information may be obtained from the company. They are located at: 317 E. Ontario St., Chicago 11, Ill.

NEW DISPLAY CARTON

A new display carton has been introduced to dealers everywhere by the Electronic Chemical Corp. of Jersey City, N. J.

This corrugated carton now enables



dealers to show 12 cans each of "No-Noise Volume Control and Contact Restorer" and "No-Noise Tuner Tonic" in one compact arrangement. The display is done in red and black and is self-mounting. Features of the company's two products are prominently shown, together with price.

TRANSISTOR RADIO DISPLAY

Emerson Radio & Phonograph Corp. has introduced a new promotion device especially designed to solve the problem of pilferage of transistor pocket radios from retail counters.

There has been a strong dealer demand for a display fixture that would be durable, attractive, and theft-resistant. The small pocket radios tempt shoplifters and, consequently, dealers have been reluctant to display them.

The new fixture has four radio cabinet fronts (containing no chassis) permanently attached to a display under glass. An additional advantage to the dealer lies in his stock not being tied up for display purposes.

NEW RCA FILM

RCA Institutes, Inc. has made available for high school showings a new 16-mm color motion picture entitled, "Your Career in Electronics."

The purpose of the film is to familiarize the high school student with the role of the technician in the electronics industry. It shows how the student receives instruction in radio-television and electronics at the technical institute, and then puts his knowledge into practice at research and development laboratories, and industrial firms. The movie also illustrates some of the opportunities for electronic technicians, which include broadcasting, communi-

RADIO & TELEVISION NEWS

**"I cut testing time in half"
... "doubled our tube sales" ***

"Adds to my income and saves me unprofitable call-backs."

"We have two... one for the shop and one for house calls."

"Paid for itself several times. Really indispensable."

"Best tube tester I've ever owned. Simple to operate. Saves time."

"Makes lots of money for us. Wonderful instrument."

"Serves my purpose best for speed and dependability."



**FASTEST SELLING TUBE TESTER
IN THE WORLD**

Tests over 95% OF ALL POPULAR TV TUBES—IN SECONDS

Accurately makes each tube test in seconds.
Checks average TV set in minimum minutes

Tests each tube for shorts, grid emission, gas content, leakage, and dynamic mutual conductance.

Ingenious life test detects tubes with short life expectancy.

One switch tests everything. No multiple switching. No roll charts.

Shows tube condition on "Good-Bad" scale and in micromhos. Large 4½-inch plastic meter has two highly accurate scales calibrated 0-6000 and 0-18,000 micromhos

Automatic line compensation is maintained by a special bridge that continuously monitors line voltage.

Built-in 7-pin and 9-pin straighteners are mounted on the panel.

* NAMES ON REQUEST



Makers of Dyna-Quik, CRT,
Dyna-Scan and Calibrator

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

B & K MODEL 500

DYNA-QUIK

DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

One extra tube sale on each of 5 calls a day pays for the Model 500 in 30 days

Enthusiastic comments like those above* come from servicemen all over the country. Actual experience shows an average of close to 2 additional tube sales per call.

Instead of the "trial and error" method of substitution testing, the Dyna-Quik 500 quickly detects weak or inoperative tubes. Cuts servicing time, saves costly call-backs, shows each customer the true condition and life expectancy of the tubes in the set, and makes more on-the-spot tube sales. Helps keep customer good-will, give a better service guarantee, and make more profit.

The B&K Dyna-Quik 500 measures true dynamic mutual conductance. Completely checks tubes with laboratory accuracy under actual operating conditions right in the home... in a matter of seconds. Saves time and work in the shop, too. Simple to operate. Easily portable in luggage-type case. Weighs only 12 lbs. **NET, \$109⁹⁵**

See Your B&K Distributor or Write for Bulletin No. 500-N



Model 1000 DYNA-SCAN
Picture and Pattern Video
Generator. Complete Flying
Spot Scanner. Net, \$199.95



Model 400 CRT
Cathode Rejuvenator Tester.
Tests and repairs TV picture
tubes. Net, \$54.95



Model 750 CALIBRATOR
Designed to check and adjust
test instruments with laboratory
accuracy. Net, \$54.95

ATR THE 'BIG PROFIT' LINE OF HOME PLUG-IN-TYPE

Portable BATTERY CHARGERS

NO INSTALLATION
JUST PLUG INTO
CIGARETTE LIGHTER RECEPTACLE!

NINE PORTABLE PLUG-IN-TYPE MODELS
FOR EVERY HOME USE!

For keeping the storage battery fully charged right in the car, truck, boat, or plane! A storage battery necessity—needed more now than ever before—makes motor starting easy!



- Light in Weight
- Economical
- No Radio Interference
- Portable
- Rugged
- Noiseless
- Long Life

truck clamp-type portable BATTERY CHARGERS

Easily connected directly to storage battery terminals by means of large battery clips. Especially recommended for charging storage batteries in trucks, tractors, boats, and planes.

WRITE FOR COMPLETE CATALOG AND PRICE LIST

ATR AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1951
SAINT PAUL 1, MINNESOTA—U. S. A.
MANUFACTURERS OF DC-AC INVERTERS, PORTABLE BATTERY CHARGERS
"A" BATTERY ELIMINATORS, AUTO RADIO VIBRATORS

BUILD 16 RADIO

Reg. Pat. Off. CIRCUITS AT HOME WITH THE NEW BELUXE PROGRESSIVE RADIO "EDU-KIT"

A Practical Home Radio Course ONLY \$22.95

FREE! Set of Tools, Soldering Iron, Tester, Membership in National TV Club, Consultation Service, TV, Radio, Hi-Fi, Quiz Books, FCC Amateur License Training, Printed Circuitry, Parts-Cutters, Alignment Tool.

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. You will learn radio theory, construction and servicing. You will learn to build radio, solder and wire in a professional manner, trouble-shoot radio. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background in Electronics and Radio, worth many times the small price you pay.

You will receive all parts, tools and instructions necessary to build 16 different radio and electronic circuits, each guaranteed to operate. Our kits contain tubes, tube sockets, variable, electrolytic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc. In addition, you receive Printed Circuit materials, including Printed circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, pliers-cutters, an alignment tool, a professional electric soldering iron, and a self-powered dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, TV, Radio, Hi-Fi and Quiz Books, FCC Amateur License Training.

All parts, components, etc. of the "Edu-Kit" are 100% unconditionally guaranteed, brand new, carefully selected, tested and matched. Everything is yours to keep. The complete price of this practical home radio and electronics course is only \$22.95. Sold only by Progressive "Edu-Kits."

You will learn to trouble-shoot and service radio, using the professional Signal Tracer, the unique Signal Injector, and the dynamic Radio and Electronics Tester. Our Consultation Service will help you with any technical problems.

J. Stasulis, of 25 Poplar Pl., Waterbury, Conn. writes: "I have repaired several sets for my friends, and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your kit."

PROGRESSIVE "EDU-KITS" INC.
497 UNION AVE., DEPT. 62-E, BROOKLYN 11, N. Y.
ORDER FROM AD-RECEIVE FREE BONUS RESISTOR & CONDENSER KITS WORTH \$7

30-DAY UNCONDITIONAL MONEY-BACK GUARANTEE

- ☐ I enclose full payment of \$22.95 for "Edu-Kit" sent postpaid.
- ☐ I will pay postman \$32.95 plus postage for "Edu-Kit" sent COD.
- ☐ Rush me FREE descriptive literature concerning "Edu-Kit." Also send me FREE valuable Radio, TV literature.

NAME _____ ADDRESS _____

Outside U.S.A. No COD. 110v model \$22.95, 220v model \$26.45.

AUDEL'S T.V. RADIO SERVICE LIBRARY TELLS HOW TO ANSWER RADIO T.V. QUESTIONS

HERE IS LATE INFORMATION IN A HANDY FORM FOR TELEVISION AND RADIO REPAIRMEN, SERVICEMEN AND STUDENTS

AUDEL'S T.V. RADIO SERVICE LIBRARY—Highly Endorsed—Over 1500 Pages—1048 Illustrations & Diagrams. 1001 Important Facts & Figures on Modern Television, Radio, Electronic Devices at your finger ends.

INCLUDES TRANSISTORS & Transistor Circuits, Record Changers, Rectifiers, P.A. Systems, Tape Recorders, Phonograph Pick-ups, F.M., Auto Radio; Radio Compass, Short Wave, Radar, etc.

ASK TO SEE IT! IT WILL PAY TO KNOW—
The Basic Principles—Construction—Installation—Operation—Repairs—Trouble-Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems, Methods of Conversion, Terms, etc. Includes Ultra High Frequency—Valuable for Quick Ready Reference and Home Study.

\$6 COMPLETE 2 VOLUMES Get this information for Yourself.

7 DAY TEST—PAY ONLY \$1 A Month

MAIL ORDER

AUDEL PUBLISHERS, 49 W. 23 ST., N.Y. 10, N.Y.

Mail AUDEL'S T.V. RADIO SERVICE LIBRARY (2 Volumes) \$6 on 7 days free trial, if O. K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____

Address _____

Occupation _____

Employed by _____ RN

cations, servicing, aviation, guided missiles, and civil defense.


This film is available for free showing at high schools, educational groups, Boy Scouts, and social service organizations. Running time of the film is 24 minutes.

For information on bookings, contact: Registrar, in care of the school at 350 West Fourth St., New York 17, N. Y.

CAPACITOR SERVICE KITS

Cornell-Dubilier Electric Corp. has introduced two service kits for capacitor replacements.

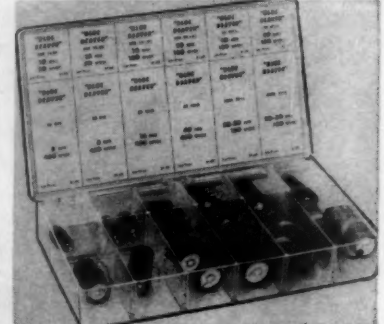The kits are flat, clear plastic, hinged cover (11" x 6 1/2" x 1 1/2") cases that fit into a regular field service bag. The "Cub" kit is made up of 76 molded tubular capacitors of assorted ratings



and types most frequently needed on service calls and bench service. The "Blue Beaver" kit comprises 22 of the most widely used electrolytic types. Each kit also contains a location chart, ratings, and prices of each capacitor, and a guide which lists the complete lines.

These cases are supplied free of charge with the purchase of a pre-selected assortment of capacitors. The service technician pays only for the capacitors in the kit. The company's distributors can furnish additional detailed information, or write direct to the firm at South Plainfield, New Jersey.


NEW MULLARD TUBE PACKING

Mullard, British electronic tube manufacturer, recently introduced a blue-plastic pin protector which guards miniature tubes against the possibility of damage in transit.

These protectors fit snugly over the tube pins, effectively padding them against any damage which might be caused during shipment. When the tubes have been put into use, the protectors can be fastened to the workbench or perhaps a piece of board as a storage rack, thus preventing the breakage that often occurs when tubes roll or are knocked off the table. This is a convenience which is readily appreciated by the experienced and efficient service technician.

For further information, write to the firm's - representative, *International Electronics Corp.*, 81 Spring Street, New York 12, N. Y.

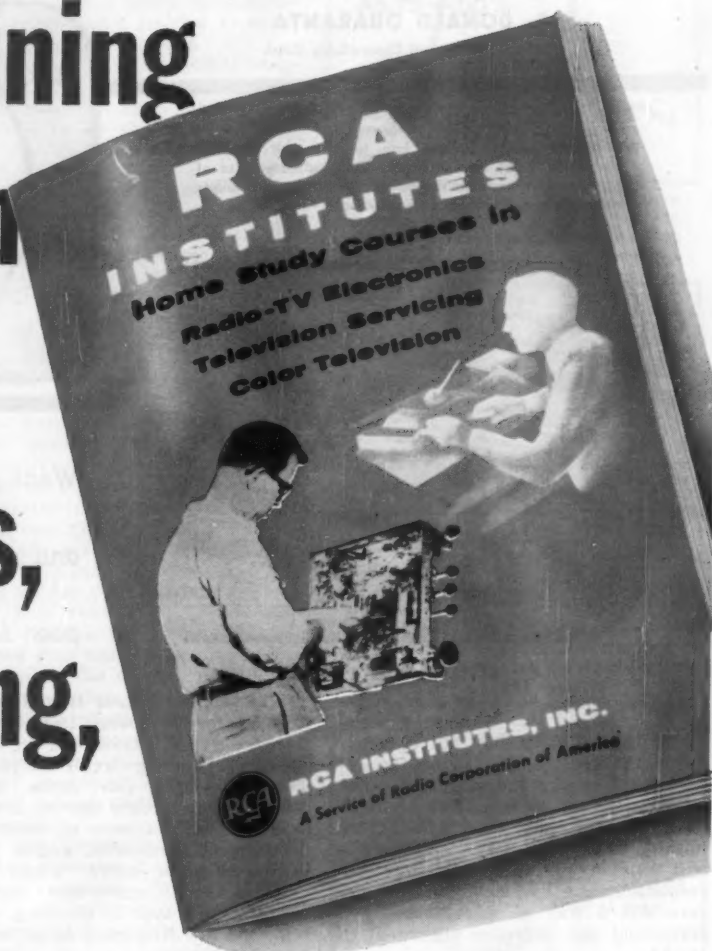**RCA offers you the
finest training
at home in
Radio-TV
electronics,
TV servicing,
Color TV**



**SEND FOR THIS FREE
BOOK NOW!**



RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION of AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

The instruction you receive and equipment you get (and keep) will start you on your way. Pay-as-you-learn. You pay for only one study group at a time. This 52 page book contains complete information on Home Study Courses for the beginner and the advanced student.

RCA Institutes, Inc., Home Study N-27,
350 West Fourth Street New York 14, N. Y.
Without obligation, send me FREE CATALOG
on Home Study Courses in Radio, Television,
and Color TV. No salesman will call.



Name Please Print
Address
City Zone State

VETERANS
KOREAN G.I.
P.L. 550
CHECK HERE
()

Curing TV I.F. Troubles

By DONALD QUARANTA
CBS TV Technical Operations Dept.

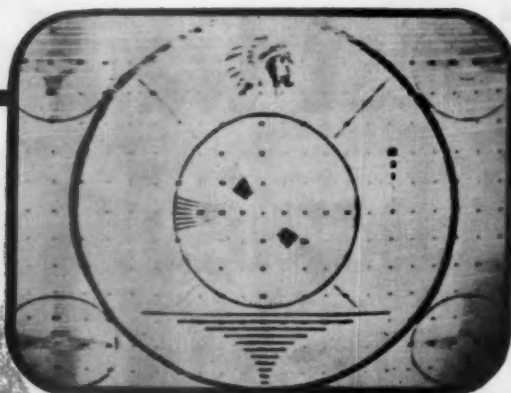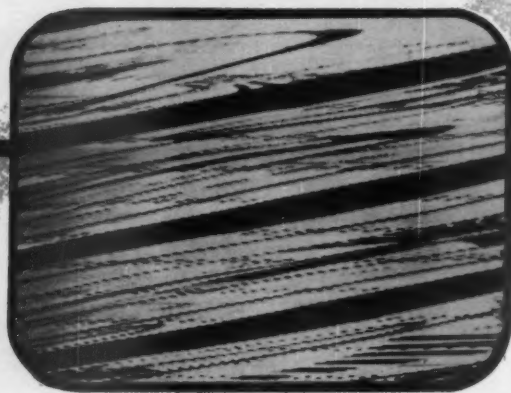A misadjusted i.f. strip can lead to the troubles shown in these two pictures. One indicates loss of horizontal sync with the resulting tearing, the other shows picture which is washed out—loss of detail.



Weak pictures, loss of detail, smearing, and poor a.g.c. action are often due to poor i.f. curve. Here is possible cure.

CHANGES in the i.f. response curve of a TV set due to misalignment of the i.f. strip may not only degrade the picture quality of the receiver but can be the source of other troubles. Weak sync, poor a.g.c., and poor blanking many times result from misalignment of the i.f. This article will explain the effect an improper response curve can have on the picture and a way of interpreting and correcting any improper alignment in the i.f.

Possible i.f. misalignment is a problem because of the critical design of this section of the television receiver. Some television manufacturers use specially chosen tubes for the i.f. strip to obtain optimum picture results. Actually, the alignment of the i.f. circuits of a television receiver determines, to a great extent, the kind of performance which the receiver will give.

When a television receiver becomes inoperative due to a defective i.f. tube, the new replacement tube may cause the picture quality of the receiver to change. This does not mean that every time an i.f. tube is replaced, the receiver needs alignment. However, over a period of years, the picture quality of the receiver may change due to the replacement of a few i.f. tubes and the heating of the i.f. circuit components. The deterioration of the response curve in the i.f. section due to these changes can be seen in the workshop on the sweep scope display.

Variations in the i.f. circuit may oc-

cur to such an extent that it is hard to say beforehand what form or shape the i.f. curve will take with the changing of i.f. tubes or circuit components. These changes can cause among others: high picture carrier, low picture carrier, increase of bandwidth, decrease of bandwidth, and/or tilting of the response curve. These variations in the i.f. curve can eventually result in poor sync or blanking, loss of high and low frequency detail, or poor a.g.c. operation.

To help in the interpretation of these troubles it is important to have a knowledge of the i.f. response curve and its effect on the picture. Fig. 1 shows a normal i.f. response curve with the response down 50% at the picture carrier frequency—the actual bandwidth is determined by the manufacturer's design. If a test pattern were being displayed by the picture tube of a receiver with this response, it would be interesting to note that it would show good reproduction of the fine picture details, good low frequency performance, and a good contrast range.

Fine picture detail can be checked on the test pattern by observing the lower vertical wedge. A normally aligned receiver would show distinct vertical lines far up towards the center of the test pattern before they begin to blend together. Low frequency performance of the receiver can be checked by observing any thick horizontal lines on the test pattern. These thick lines should be clean cut. Good

contrast affords many shades of brightness ranging from white, through grey, to black. By proper adjustment of the brightness and contrast controls the test pattern should show these distinct and different shades.

If the picture carrier were located at 10% of the response curve height, the low frequency response would be reduced and this effect would show up in the receiver as poor blanking, weak sync, and poor a.g.c. operation. It is important to know that major picture components and the blanking and sync pulses represent relatively low frequencies. On a test pattern this condition would show up readily as weak horizontal wedges and smears on any dark lettering or large picture areas.

If the picture carrier were up at 90% of the response curve, the low frequency picture signals would be strong but the high frequencies would be lost and the result would probably be poor picture definition. On a test pattern this would be clearly indicated by the blending together of the vertical wedges at a relatively low frequency and the loss of definition in small picture areas.

I.F. Tests

The frequencies to which the i.f. transformers and traps are tuned in different TV receivers are not the same, therefore it is necessary that the service technician obtain complete service data before attempting i.f. alignment or tests. Also, the procedures to use for different sets vary in

some
grid
peak
son,
this a
rather
ever.
cedur
ger-tu
TV
use o
when
can b
"head
if the
check
curat
descri
exper
The
check
ceiver
1. A
intern
frequ
mined
in ma
gener
before
i.f. re
which
flatne
shown
sweep
least
2. A
frequ
shoul
to-pea
3. A
gener
frequ
4. A
differ
applie
er has
move
the i.f.
ply is
receiv
cuit f
for th
5. A
4, for
the m
signal
and lo
from
load.
ment
and e
satisf
ers. U
the si
shield
neous
signal
the tu
the fi
or an
This
the o
gener
a 75-
shoul
This
four
two p
bined

some respects, such as the amount of grid bias to apply or the method of peaking the i.f. coils, etc. For this reason, the information to be given in this article concerns a basic procedure rather than a specific method. However, as an example, one definite procedure is included for checking a stagger-tuned i.f. strip.

TV manufacturers often recommend use of a particular pad or network when aligning their sets. Valuable time can be lost in making up these special "heads" or detector pads, particularly if the service technician only wants to check the i.f. strip. The quick and accurate method of checking i.f. strips described here is the result of actual experience in servicing receivers.

The basic test equipment needed to check the i.f. strips of most TV receivers includes:

1. A sweep generator covering TV intermediate frequencies. The exact frequency setting should be determined by the use of external or built-in markers. The flatness of the sweep generator output should be checked before making any adjustments of the i.f. response curve. A simple detector which can be used for checking the flatness of the generator output is shown in Fig. 2. The output of the sweep generator should be flat for at least 10 mc.

2. An oscilloscope with good low frequency response. The vertical input should be calibrated to 3 volts peak-to-peak.

3. An accurately calibrated signal generator to cover the intermediate frequency range.

4. A low impedance bias box for different bias levels (0-6 volt) to be applied to the a.g.c. bus. If the receiver has keyed a.g.c., it is best to remove the keyer tube before aligning the i.f. strip. The low impedance supply is necessary to prevent any of the receiver bias from developing. A circuit for a low impedance bias supply for this purpose is shown in Fig. 3.

5. A "spray shield," as shown in Fig. 4, for feeding the sweep signal into the mixer stage of any receiver. This signal injection device is capacitive and looks into the complete i.f. strip, from the mixer output to the detector load. This special piece of test equipment is not only simple in structure and easy to make, but it has proven satisfactory in servicing most receivers. Using it is better than coupling the signal into the regular mixer tube shield. The latter method gives erroneous responses because the sweep signal is not evenly distributed onto the tube elements of the mixer and the final response shows either a tilt or an incorrect carrier position.

This "spray shield" should match the output impedance of the sweep generator. If the sweep generator has a 75-ohm output impedance, the shield should be terminated in this value. This is accomplished by connecting four resistors in parallel across the two parts of the shield to give a combined resistance of 75 ohms. In this

case, four 300-ohm resistors are used.

The "hot" generator lead is connected to the upper part of the shield; the bottom portion accepts the ground lead of the generator. For even distribution of the sweep signal, it is best to use as round a shield as possible and to position each resistor at equal distances around the shield.

Now, let's examine a typical stagger-tuned i.f. strip. On the schematic diagram of such a circuit, Fig. 5, the mixer tube is not shown but it is a 6AT8. The second detector load resistor is R_1 .

Connect the sweep generator output to the "spray shield" and slip the latter over the mixer tube. Next, connect the scope lead through a 27,000 ohm isolation resistor to the top of the detector load resistor. For this particular circuit, insert a -3 volt bias at the top of C_1 and to the tuner a.g.c. terminal.

Turn on the receiver under test, tune it to an unused channel, and adjust the sweep generator to produce a 3 volt peak-to-peak signal on the scope. After the i.f. response curve is observed on the scope, inject the signal generator signal by placing its output lead near the i.f. circuitry. If the response curve shows that the picture carrier (45.75 mc.) is too low and the original trouble with the receiver was that it had weak sync, the trouble could be this low carrier. As a quick corrective step touch up coil T_2 (45.7 mc.) to raise the carrier side of the response and then straighten it out with T_3 which affects the tilt.

If the response curve shows that the carrier is up too high, it would be necessary to adjust T_2 (45.7 mc.) to lower the carrier response at the carrier frequency.

It is not necessary to completely align the i.f. section if only the carrier side of the response curve is wrong. Complete realignment is needed only when the picture quality is exceptionally poor.

Even in cases when the picture quality on a receiver is very poor and the technician may feel that complete realignment is necessary, it is advisable to try the method outlined here first. A simple touchup of the response curve can save lots of valuable time and the results may be very effective. However, if a complete realignment is nec-

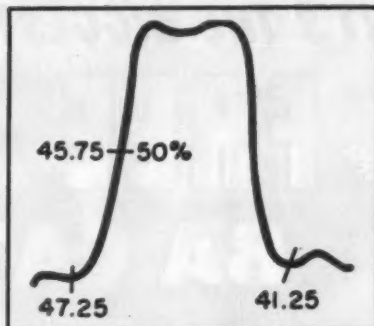


Fig. 1. Normal picture i.f. response curve showing the picture carrier at 50% of the peak amplitude. If this carrier is higher or lower on the curve, the picture suffers.

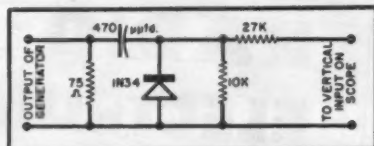


Fig. 2. The circuit shown here is a detector which may be used to check the flatness of the output of a sweep frequency generator.

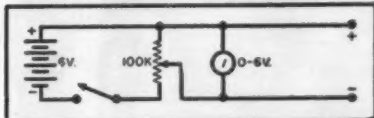


Fig. 3. This low impedance bias supply is useful for supplying the proper a.g.c. bias voltage to the i.f. and tuner circuits during alignment with the a.g.c. disconnected.


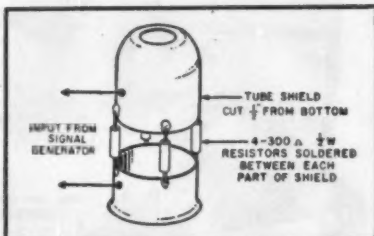


Fig. 4. This modified tube shield fits over the tuner mixer tube and is used as feed-in point for the sweep signal.

essary, be certain to refer to the service data for the receiver under repair to obtain the correct bias and frequencies.

Fig. 5. Schematic diagram of the picture i.f. circuits of a CBS-Columbia TV set.

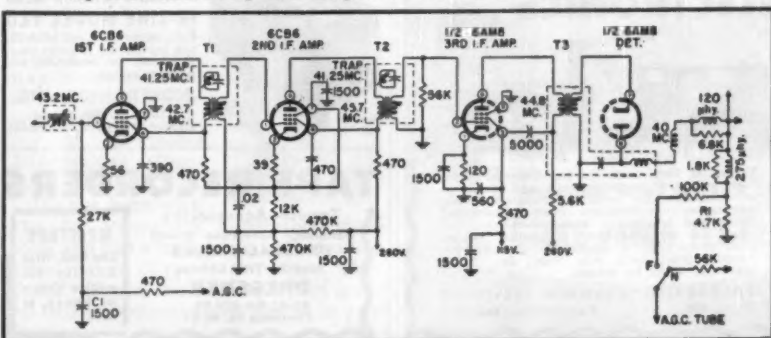

IT'S THE BIGGEST AND BEST EVER

FREE THE GIANT ALL NEW 1957 BA CATALOG

A COMPLETE BUYING GUIDE FOR EVERYTHING IN ...

RADIO • TV ELECTRONICS

1957

ANNUAL CATALOG NO. 571

- ✓ For latest equipment ... for the latest equipment ...
- ✓ Ever complete and up-to-date ...
- ✓ Every B-A Catalog ...

COMPLETE INDEX PAGE 170

BA SINCE 1927

MAKERS, SERVICEMEN, SCHOOLS, ...

RUSH COUPON TODAY!

BURSTEIN-APPLEBEE CO. Dept. M,
1012-14 McGee St., Kansas City 6, Mo.

☐ Send Free B-A Catalog No. 571.

NAME _____

ADDRESS _____

CITY _____ STATE _____


172
KING-SIZED
PAGES

EVERYTHING
IN RADIO
TV AND
ELECTRONICS

100'S OF
NEW ITEMS
LISTED HERE
FOR 1st TIME

21 PAGES
OF BARGAINS
NOT IN ANY
OTHER CATALOG

GET INTO ELECTRONICS

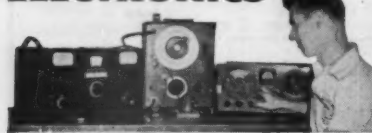

Valparaiso Tech trains for top flight positions. Tech. rep., field engineers, sales and specialists in communications, missiles, computers, radar, automation, color television. Basic and advanced theory and laboratory. Major companies visit school for our graduates. 21 months' course. High school grad. or equivalent. Dormitories—campus. Start April, July, Sept., Jan. G. I. approved. Write for catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana



Audio-
phile

\$23.50

STEREOPHONIC RECORD PLAYBACK HEAD IN-LINE MODEL TLD

For conversion, replacement, new equipment. Includes data, schematics for amplifiers, etc.

ORDER FROM:

NORTRONICS, INC.
1015 S. 6th Street
MINNEAPOLIS 4 MINN.

TAPE RECORDERS

Tapes—Accessories
Nationally Advertised Brands
UNUSUAL VALUES
Send for Free Catalog

DRESSNER
69-02 RA-174 St.
Flushing 65, N. Y.

MERITAPE
Low Cost, High
Quality Re-
cording Tape—
in boxes or
cans.

Within the Industry
(Continued from page 28)

ber of the board of directors of *Kay Lab.* ... **EVERETT S. LEE**, well-known engineer and past president of the American Institute of Electrical Engineers, recently retired after more than 40 years with the *General Electric Company* ... *The Ramo-Wooldridge Corp.* has announced the election of **ROBERT J. HIGHT** as treasurer ... **ALLAN EASTON** has been appointed vice-president and sales manager of *General Transistor Corp.* ... **HENRY F. ARGENTO** has been appointed vice-president, commercial sales, for *Raytheon Manufacturing Company*. He was vice-president and general manager of the firm's former television and radio operations in Chicago ... *The National Company* has named **PHILIP R. HEATH**, recently retired Lt. Commander in the U. S. Navy, to the new post of field service supervisor. He will make his headquarters in Nagoya, Japan ... **HARRY G. MCKENZIE** has been named general sales manager of the *Gray Research and Development Company, Inc.* He was formerly with the *Rudolph Wurlitzer Co.* ... **DR. JOHN T. HENDERSON** has been elected president of the Institute of Radio Engineers for 1957. He is principal research officer of the National Research Council, Ottawa, Canada. **YASUJIRO NIWA**, president of Tokyo Electrical Engineering College, Tokyo, Japan, is the new IRE vice-president. Elected as directors for the 1957-58 terms are: **D. E. NOBEL**, vice-president in charge of the Communications and Electronics Div. of *Motorola, Inc.*, Chicago, Ill., and **SAMUEL SEELY**, professor and head of the Department of Electrical Engineering at Case Institute of Technology, Cleveland, Ohio.

J. P. ARNDT, JR. has been appointed assistant to the vice-president and general sales manager of *Brush Electronics Co.*, division of *Clevite Corp.*, Cleveland, Ohio.

He joined the company in 1935 as a patent engineer. Successively he became manager of the Patent Department, manager of the Crystal Measurements Department, and Crystal Sales manager.

In his new post, he will concentrate his activities on product planning and development.



DONALD B. HARRIS, manager of electron tube research at *General Electric's* Microwave Lab. in Palo Alto, Calif., has been elected chairman of the 1957 Western Electronic Show and Convention.

Vice-chairman in charge of exhibit operations for the show is **Norman H. Moore**, vice-president of *Litton Industries* and managing director of that

RADIO & TELEVISION NEWS

company's electron tube division in San Carlos, Calif.

B. M. Oliver, director of research and development at **Hewlett-Packard Co.** in Palo Alto, has been named vice-chairman in charge of convention activities, and H. Myrl Stearns, vice-president and general manager of **Varian Assoc.** in Palo Alto, was elected secretary-treasurer.

The four additional convention directors are Bruce S. Angwin of the **General Electric Tube Div.**, E. P. Gertsch of **Gertsch Products, Inc.**, C. Frederick Wolcott of **Gilfillan Brothers, Inc.**, and Gramer Yarbrough of the **Elgin Electronics Division**.

DOUGLAS F. HUDSON has been appointed to the position of president of **Permo, Incorporated**, Chicago, Ill., manufacturer of the "Fidelitone" line of phonograph needles and accessories.

During his ten years of association with the organization, he has served as division manager, manager of industrial sales, and most recently as vice-president and director.

Mr. Hudson attended college at U.C.L.A. and prior to his employment with the company served in the U. S. Navy as Lieutenant, Senior Grade.



SYLVANIA ELECTRIC PRODUCTS INC. announced plans for a multi-million-dollar research and development center in Amherst, N. Y., for the company's Electronic Systems Division . . . **CBS-HYTRON**, tube manufacturing division of the **COLUMBIA BROADCASTING SYSTEM, INC.**, has opened a new sales office and warehouse in Seattle, Washington. The new facility is located at 102 West Roy Street . . . **NEWARK ELECTRIC CO.** announced plans to construct a new 35,000 square-foot building in Inglewood, Calif., to house its West Coast headquarters. It will be located at Rosewood and Century Blvds., and occupancy is planned for early fall . . . A branch communications laboratory of **FEDERAL TELECOMMUNICATION LABORATORIES** has been established at 809 San Antonio Road, Palo Alto, Calif. . . . A \$250,000 expansion program has been announced by **KAY LAB.** Completion of this addition to the present plant is scheduled for late spring . . . Construction has begun on an addition to the assembly plant of **SERVO CORPORATION OF AMERICA**, New Hyde Park, L. I., N. Y. . . . **SYLVANIA ELECTRIC PRODUCTS INC.** will construct a 50,000-square-foot addition to the Electronics Division headquarters plant in Woburn, Mass. Completion is scheduled for July, 1957 . . . **MICROTRAN COMPANY, INC.** has moved to its new plant at 145 E. Mineola Ave., Valley Stream, N. Y. . . . A new electronic research and development building, containing 40,000 square feet, will

be constructed by **HOFFMAN LABORATORIES, INC.** in the 3700 block on South Grand Ave., Los Angeles, Calif. Ground is also being broken for a new administrative building immediately adjacent to the present facilities . . . **TRIPLETT ELECTRICAL INSTRUMENT COMPANY** of Bluffton, Ohio, is planning to construct a 10,000-square-foot plant in Oceanside, Calif. . . . **KOESSLER SALES COMPANY**, and its division, **KOESSLER INDUSTRIES, INC.**, recently announced the purchase of a building at 818 North Fairfax Avenue, Los Angeles, Calif. The new housing includes larger offices and demonstration room, more warehouse facilities, and 3000-square-feet of parking. The move into the new quarters was effective October 15, 1956.

RETMA will consolidate and move its Washington headquarters' operations about February 1, 1957.

The trade group will occupy what will be known as the "RETMA Building" at 1721 De Sales Street in Northwest Washington, D. C. Original plans, approved by the Board of Directors, calls for the transfer of the RETMA Engineering Dept., now in New York City, to the new consolidated offices. However, this move is deferred for the time being.

The building is a four-story structure and is being remodeled and modernized to the organization's specifications. A large conference room will be available for committee meetings, and it is felt that a single duplicating and mailing unit will result in substantial economies and greater efficiency.

ETA KAPPA NU ASSOCIATION, national electrical engineering honor society, has named Dr. Jordan J. Baruch as the Most Outstanding Young Electrical Engineer of 1956.

Dr. Baruch is a 1948 graduate of Massachusetts Institute of Technology and is now vice-president and director of New Products Development of **Bolt, Beranek and Newman, Inc.**, Cambridge, Mass.

Robert B. Seidel, president of **Automatic Temperature Control Co.** of Philadelphia, Pa., and a 1948 graduate of Cornell University, was chosen to receive the honorable mention this year.

JOHN J. BURKE, formerly head of the guidance and electronics divisions of the U. S. Government's Jet Propulsion Laboratory, has been elected vice-president in charge of engineering of **Hallamore Electronics Company**, Anaheim, Cal.

He has been with the Jet Propulsion Laboratory since 1948 and had a major role in that unit's development of the U. S. Army's "Corporal" missile, the country's first guided ballistic-missile to be placed in production.



BUILD THE BEST- AND ALLIED'S OWN knight-kits

ALLIED states its 36-year reputation in the Electronics field on your complete success and fullest satisfaction with KNIGHT-KITS. Join the thousands who have discovered the ultimate in kit value in . . .



knight-kits

EASIEST TO BUILD because our latest buying power passes biggest savings on to you . . . you do the easy assembly and your finished instrument is equal in performance and appearance to equipment selling for several times the unit's factory cost. (Easy Payment Terms available, too.)



knight-kits

FASTEST TO BUILD because our latest "Stop-and-Check" instruction manuals are marvels of clarity—it's just like having a good instructor at your side. Proved professional design and premium quality parts help insure your building success.



knight-kits

MONEY-BACK GUARANTEED: When properly assembled, KNIGHT-KITS fully meet published specifications, or we refund your money.

WHEN YOU BUILD A KNIGHT-KIT
YOU BUILD THE BEST



For a Complete Selection of
Famous knight-kits
SEE PAGES 117-123

Available Only From
ALLIED RADIO
100 N. Western Ave., Chicago 80, Ill.

**Take the advice of experts:
Do a Better Service
Job... Get a Better
Price with KRYLON®**

... spray high voltage connections to prevent corona, and arcing caused by moisture.

... spray bell part of picture tube to repel dust and arcing.

... spray antennae to prevent rust, corrosion, pitting, signal loss.

... insulate and moisture proof lead-in connections.

KRYLON RUST RELEASE

... unlocks rusted, corroded, "frozen" parts, etc. Loosens rusted antennae and outside connections. Giant 16.2-oz. can.

KRYLON DULLING SPRAY

... kills glare and reflections from objects in T-V studios, simplifies lighting and arranging problems. Giant 16.2-oz. can.

KRYLON SPRAY ENAMELS

... for maintenance and touch-up... renew tube bells, loud speaker grids, hardware, etc. 18 colors. Giant 16.2-oz. can.

Order from your T-V Parts Jobber or write
KRYLON, INC., NORRISTOWN, PA.

**KRYLON GOES FARTHER IN NEW GIANT CAN...
35% More Product at No Extra Cost to You**



Behind the Giant Brains
(Continued from page 71)

business such a short time ago. Every computer research center in the country is straining at the seams, and every engineering staff is heavily overburdened. Computer engineers and experienced computer programmers have, within the last two years, discovered that they can practically write their own tickets.

Computer research has borrowed heavily from every known science and technology, and has managed to solve many of the most pressing problems. Frequently, however, each solved problem turns, hydra-like, into a hundred more questions. The name *mushrooming technology* is apt: computer research has frequently tried to grow in all directions simultaneously.

Industry and business now have heavy investments in the development of newer and more capable electronic tools, and our economy is gradually accustoming itself to depending on them more and more. Properly used, they can make life simpler and easier for all of us—and more rewarding, too, as the time-consuming and deadly dull repetitive tasks which are part of so much of our commercial and industrial effort are given over to the machines. Their growth was inevitable, because there were too many jobs to be done, and too few manhours to do them in; without manpower, we must inevitably fall back on the machine. And whether for better or for worse, automatic controls and electronic computers are with us to stay.

—50—

RETURNS VIA HAM RADIO

RADIO amateurs throughout New York State combined forces election night in a unique demonstration of the hams' ability to gather detailed information from a large area and forward it swiftly and accurately to its destination.

Participating in the demonstration were members of the N. Y. State Civil Defense Command Nets, N.Y.C. RACES group, Amateur Radio Teletype Society, other cooperating hams. Election returns were gathered by counties and then transmitted via 80 meter c.w. and 75 meter phone to Civil Defense Headquarters. From this point, the reports were put on a high-speed 2-meter radio teletype printer circuit which terminated in Studio C of Stations WNYC and WNYC-FM.

Participating in the demonstration were Robert Link, W2VKE, RACES supervisor; Leonard Nachemov, W2DUP, asst. supervisor, RACES; Clay Cool, W2ZBZ, ARTS who set up and maintained the equipment; Tony Landry, W2IRT, who supplied the teletype and converter at WNYC; David Penner, K2JVB; and Dick Daynard, K2IAD—all at the station. Vincent T. Kenny, W2BGO, state radio officer, and William Knott, W2OGH, Westchester radio officer who supplied the radio teletype at the state control, held down the state headquarters post. Forty-two other hams throughout the state also contributed their time and gear to this project.

—50—

RADIO & TELEVISION NEWS

pfk
pre-finished
Kits

PFK-120/150 PFK-300 PFK-500

designed by
Paul Klipsch

Now you need only a screw-driver to put together a furniture-finished Klipsch speaker enclosure, indistinguishable from factory-assembled Rebel 3, 4 or 5. Also available as conventional, unfinished kits.

Write for Complete Catalog!
36 pages... 16 other hi-fi kits... 29 equipment cabinets... 4 matched speaker systems... 20 hi-fi accessories.

cabinart '57

Cabinart

99 North 11th Street
Brooklyn 11, N. Y.

largest manufacturer of cabinets and kits for hi-fi
a division of G&H Wood Products Co., Inc.

TeleMatic
introduces
FASTER SERVICING
with **TELECHECK**

KIT INCLUDES:

- 8AXP4 Tube.
- Universal yoke with 6-foot leads and insulation piercing-clips.
- 6-foot CRT and anode extensions.
- Leatherette professional instrument case.

Available with or without tube.

FREE! 16-page Booklet "Service Shortcuts"

Please send me FREE booklet!

Name _____
Address _____
City _____ State _____
Distributor _____

TELEMATIC INDUSTRIES, INC.
18 HOWARD AVE. • BROOKLYN 21, N. Y.

BUY THE WORLD'S FIRST COLOR TELEVISION ANNUAL!

136 PAGES COVERING EVERY PHASE OF COLOR TV:

■ **Fundamentals of
Color TV**
(A Complete Course)

■ **Color Sets On The
Market**


■ **Picture Tubes
and Components**

■ **Technical Analysis
of Sets**

■ **Servicing and Installing**

■ **Test Instruments for
Color TV**

■ **Converters, Color
Wheels, Vitascan**

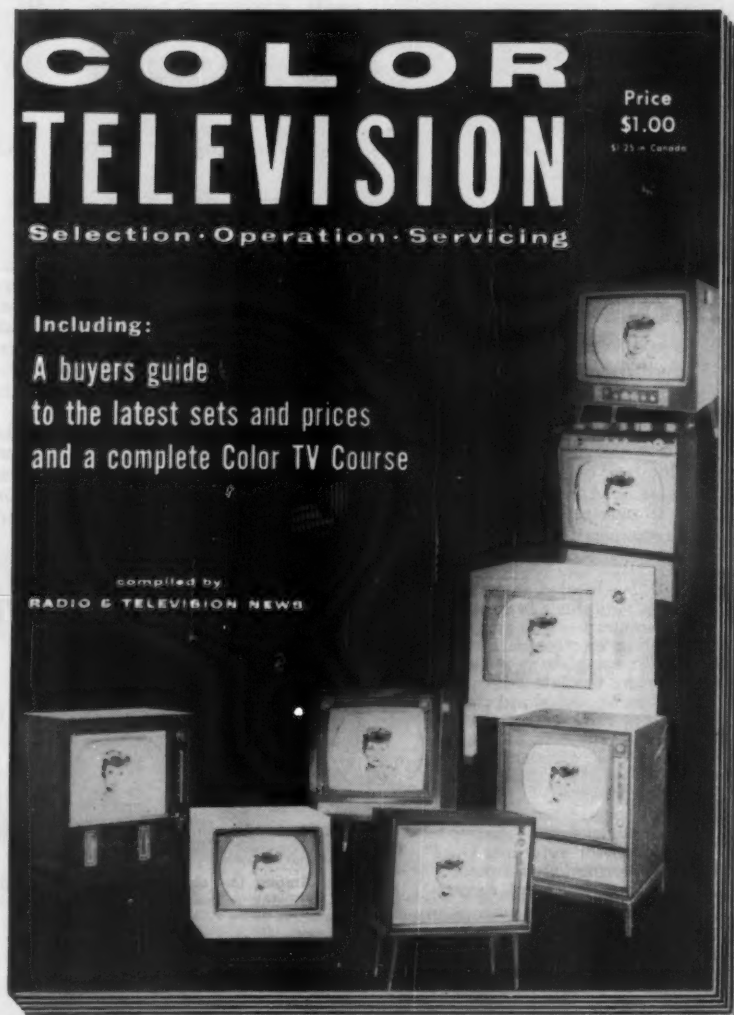

NOW ON SALE AT ALL NEWSSTANDS—ONLY \$1.00



ZIFF-DAVIS PUBLISHING COMPANY—

**Publishers of RADIO & TELEVISION NEWS, POPULAR ELECTRONICS,
AND HI-FI ANNUAL & AUDIO HANDBOOK**

Your choice of school
is highly important
to your career in



INDUSTRIAL
ELECTRONICS



RADIO-
TELEVISION



ELECTRONICS
COMMUNICATIONS

Become an
**ELECTRICAL
ENGINEER**
or an
**ENGINEERING
TECHNICIAN**
at

MSOE in Milwaukee

Choose from courses in:

ELECTRICAL ENGINEERING
Bachelor of Science degree in
36 months. Communications
option (radio-tv) Power option.

ENGINEERING TECHNICIAN
Assoc. in Applied Science degree
— 18 months.

Electronics Communications
Electrical Power.

MSOE — located in Milwaukee,
one of America's largest indus-
trial centers — is a national
leader in electronics instruction
— with complete facilities,
including the latest laboratory
equipment, visual aid theater,
amateur radio transmitter —
offers 93 subjects in electrical
engineering, electronics, radio,
television, electrical power,
and electricity.

Advisory committee of lead-
ing industrialists. Courses
approved for veterans. Over
50,000 former students.
Excellent placement record.



QUARTERS BEGIN OCTOBER,
JANUARY, APRIL, JULY

Choose wisely — your
future depends on it. Write
for more information today!

MILWAUKEE
SCHOOL OF ENGINEERING
Dept. RN-257, 1025 N. Milwaukee Street
Milwaukee 1, Wisconsin
Send FREE career booklet.

I am interested in _____
(Name of course)
Name _____ Age _____
Address _____
City _____ Zone _____ State _____
If veteran, give discharge date _____

MS-57

Rubberized Circuits for Guided Missiles

U. S. Air Force Snark, a guided
missile, roars from its launching
cradle with its rocket boosters
flaming. The Snark couples inter-
continental range with the ability
to carry a first-priority warhead.




*New silicone rubber that cures at room temperature
provides a protective coating for vital circuits.*

USING a new silicone rubber that
cures at room temperature, en-
gineers at Northrop Aircraft, Inc.,
have developed a quick, easy, and al-
most foolproof guarantee of top per-
formance for vital high impedance cir-
cuits in the Snark guided missile, the
F-89 interceptor, and other projects.


After electronic panels in the cir-
cuits are packed with resistors, ca-
pacitors, transistors, and other gear
designed to record or transmit infor-
mation during flight, the panels are

coated with Silastic RTV, the room
temperature curing silicone rubber
developed by Dow Corning Corp. Ac-
cording to Northrop designers a single
coating of the silicone rubber cushions
vibration, provides moisture resist-
ance, improves surface resistivity of
the panels, and protects the assemblies
from rough handling. Individual com-
ponents may be inspected after assem-
bly by simply slitting open the silicone
rubber to expose the unit. Slit is then
patched with the same rubber. —30—

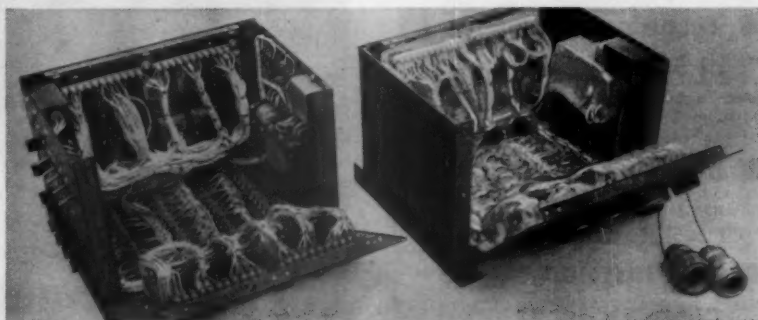

Among the electronic components which Northrop Aircraft protects with the new
silicone rubber are these junction boxes, shown here before and after the potting.

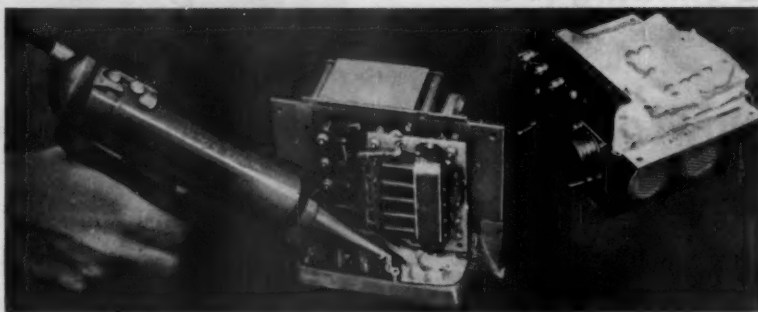The silicone rubber material is applied with an air-pressure gun to many electrical
components of the Snark missile. Here is a filter assembly during and after potting.



RADIO & TELEVISION NEWS



BUILD THE BEST—

get the most for your money in ALLIED'S own

knight-kits!

THE FINEST ELECTRONIC EQUIPMENT IN MONEY-SAVING KIT FORM

LOWEST COST

Our huge buying power means biggest savings for you. You do the easy assembly and your finished instrument is equal in performance and appearance to equipment selling for several times the low KNIGHT-KIT price.

LATEST DESIGN

Months of research, development and field-testing go into each KNIGHT-KIT to bring you proved, advanced design. To assure top performance, premium quality parts are supplied in each kit. KNIGHT-KITS are guaranteed to meet published specifications. ON YOUR BACK.

EASIEST TO ASSEMBLE

All chassis and panels are punched; all parts are clearly marked; even the resistors are mounted on cards, and keyed for easy identification. Each instruction manual is a marvel of "Step-and-Check" clarity. You get professional results even without experience.

MONEY-BACK GUARANTEE: KNIGHT-KITS FULLY MEET PUBLISHED SPECIFICATIONS, OR WE REFUND YOUR MONEY.



**FEATURING PHANTASTRON
LINEAR SWEEP CIRCUIT**

knight-kit LOW-COST GENERAL-PURPOSE 5" OSCILLOSCOPE KIT

Feature for Feature the World's Best Oscilloscope Value

Model F-146

\$49⁵⁰

This new oscilloscope delivers performance equal to wired units costing several times more and defies comparison with any other 'scope kit at anywhere near its price. It's the ideal choice for radio and TV servicing, audio work and hundreds of other applications—meets 90% of all 'scope requirements. Here are some of the features that make this kit a standout in its class: *Phantastron*

Sweep Circuit—versions of this circuit are used in \$1,000 'scopes; provides high linearity of sweep from 15 to 150,000 cps. *Regulated Calibration Voltage*—fully regulated square wave calibrating voltage is injected into signal circuit by spring return switch. *25 Millivolts Per Inch Sensitivity*—three times the sensitivity of other 'scope kits in its price class. *Retrace Blanking*—found only in high-priced 'scopes. *Vertical Amplifier*—frequency response ± 3 db from 3 cps to 1.5 mc (± 6 db to 2.5 mc). Input controls are frequency-compensated. Rise time, .25 microseconds. Impedance, 3.3 meg. and 45 mmfd. Includes positive and negative internal sync. Outstanding construction features: CRT protected by heavy rubber ring; sturdy steel case with disappearing handle. For easy assembly: pre-cut color-coded wire; resistors carded and keyed to match instructions; printed circuit; laced wiring harness; "Step-and-Check" construction manual with wall-size picture diagrams. Supplied with all tubes including CRT, all parts, graph screen, wire, solder. Size, $9\frac{1}{4} \times 13\frac{1}{4} \times 17\frac{1}{4}$ ". Shpg. wt., 26 lbs.

Model F-146. Complete 5" Oscilloscope Kit. Net only..... **\$49.50**

F-148. RF Demodulator Probe Kit. Net..... **\$3.45**

F-147. Low Capacity Probe Kit. Net..... **\$3.45**



Model F-123

\$44⁷⁵

knight-kit TV-FM SWEEP GENERATOR KIT

Guaranteed Linearity • Fool-proof Calibration • Wide-Range • Electronic Blanking

All-new; precision-designed for lab use, TV and FM servicing, production line testing. Covers 300 kc to 250 mc continuous on 4 bands (all fundamentals). Center frequencies of VHF TV channels appear on scales. Exclusive KNIGHT-KIT sweep circuit assures perfect linearity—RF sweep output in excess of 0.15 volts, flat within 1 db, is available on all bands. Sweep width continuously variable, 0-13 mc. Dual crystal marker oscillator and input for variable marker (RF Signal Generator on next page is ideal). Phase control provides blanking shift, 0 to 180°. Step-type and continuous output controls; separate marker amplitude control. Filter connected to 0-50 mc output jack provides 20 db attenuation of frequencies above 50 mc to assure pure, fundamental output. Sweep voltage for 'scopes on front panel. Professional-looking blue-finish steel case with gray panel. Has "disappearing" handle. $8\frac{1}{2} \times 12 \times 7\frac{1}{4}$ ". With all parts, tubes, test cable, solder and multi-color pre-cut wire. Less crystal. Shpg. wt., 13½ lbs.

Model F-123. TV-FM Sweep Generator Kit. Net only..... **\$44.75**

F-286. 4.5 mc Crystal (.005%). Net..... **\$4.80**

F-143. 5.0 mc Crystal (.02%). Net..... **\$3.95**

F-145. 10.7 mc Crystal (.02%). Net..... **\$3.95**

EASY PAYMENT TERMS

If your total KNIGHT-KIT order is over \$25, take advantage of our Liberal Time Payment Plan—only 1% down. Write for application form today.

SEE FOLLOWING PAGES >

order from **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 30, ILL.

ALLIED'S own knight-kits... better by far



knight-kit 5" ALL-PURPOSE WIDE-BAND OSCILLOSCOPE KIT

2 Printed Circuit Boards • 5 Mc Width for Color TV

Model F-144

\$69⁰⁰

Wide-band, 5" Oscilloscope; equals or better the performance of commercially-wired 'scopes costing several times the price. Two printed circuit boards and laced wiring harness assure wiring accuracy and reduce assembly time. Ideal for lab use, color TV servicing and high frequency applications. Provides unusually wide sweep range—from 15 to 600,000 cps. Locks in at frequencies as high as 9 mc. Vertical response, 5 cycles to 5 mc. Response, down only 1 db at 3.58 mc color burst frequency; down only 3 db at 5 mc. High vertical sensitivity of 25 mv/inch. Input capacity 20 mmf and 3.5 mega. Outstanding features: cathode-follower vertical and horizontal inputs; 2nd anode provides 1400 volts high-intensity trace; push-pull vertical and horizontal amplifiers; positive and negative locking; faithful square wave response; frequency-compensated attenuator; Z-axis input for intensity modulation; one volt P-P calibrating voltage; astigmatism control; blanking circuit to eliminate retrace lines; DC positioning control. Complete with CRT, all tubes and parts. Handsome, professional, blue-finished steel case with "disappearing" handles. 14½ x 9½ x 16". Shpg. wt., 40 lbs.

Model F-144. Wide-Band 5" Oscilloscope Kit. Net only... **\$69.00**
F-148. Demodulator Probe. Net... **\$3.45** F-147. Low Capacity Probe. 12 mmf. Net... **\$3.45**



NEW knight-kit VOLTAGE CALIBRATOR KIT

Model F-136

\$12⁷⁵

Permits the use of any scope as a precision peak-to-peak AC voltmeter. Provides a true square-wave voltage on scope screen. Range switch and calibrated potentiometer permit selecting any voltage between .01 and 100 volts, in 4 ranges. Fifth position of switch feeds external signal to scope for comparison. Constant output on line volt. variation from 80-135 v. ±6% on all ranges. Shunt capacitance only 15 mmf. Use any 20,000 ohms/volt VOM or a VTVM for initial calibration. Direct coupling of output provides ground reference for DC scopes. Portable case, 7½ x 5½ x 4½". Ready to build. Shpg. wt., 5 lbs.

Model F-136. Voltage Calibrator Kit. Net... **\$12.75**



knight-kit LOW COST RF SIGNAL GENERATOR KIT

Model F-145

\$19⁷⁵

Build this wide-range extremely stable RF signal generator and save two-thirds the cost of a comparable wired instrument. Ideal for alignment of RF and IF stages in radio and TV sets, and for troubleshooting audio equipment. Delivers output on fundamentals from 160 kc all the way out to 110 mc; useful harmonics to 220 mc. Has built-in 400-cycle sine-wave audio oscillator for modulating RF; audio is also available externally. Features high-stability Colpitts circuit with precision-wound coils—no calibration necessary. Has input for external modulator. Maximum audio output, 10 volts. RF output, over 100,000 micro-volts. Step and continuous-type output attenuators. With all parts, tubes, wire and solder. Portable case, 7 x 10 x 5". Shpg. wt., 10 lbs.

Model F-145. RF Signal Generator Kit. Net only... **\$19.75**




Model F-135
\$26⁵⁰

knight-kit VISUAL-AURAL SIGNAL TRACER KIT

A remarkable value in an instrument which permits visual and aural signal tracing of RF, IF, video and audio circuits—has highest gain in its price class. Traces the signal from the antenna to the speaker. Reproduces signal at plate or grid connection of any stage. Identifies and isolates "dead" stages. Features: usable gain of 91,000; "magic eye" with calibrated attenuators for signal presence indication and stage-by-stage gain measurements; built-in 4" PM speaker; single probe with plug-in head gives instant choice of RF or audio tracing. Provides noise test; built-in watt meter calibrated from 25 to 1000 watts; provision for external scope or VTVM. Blue-finish steel case. Shpg. wt., 13 lbs.

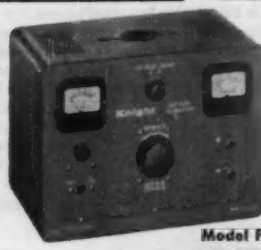Model F-135. Signal Tracer Kit. Net only... **\$26.50**



Model F-129
\$37⁹⁵

NEW knight-kit 6-12 VOLT BATTERY ELIMINATOR KIT

A valuable new unit for servicing auto radios, mobile gear, etc. Delivers continuously variable filtered DC output from 0 to 15 volts. Provides DC output at 0-8 volts or 0-15 volts. Continuous current rating: 12.5 amps at 6 volts, 10 amps at 12 volts. Can also be used as battery charger. Oversize rectifiers and transformer for better regulation and long life. Two meters provide simultaneous current and voltage readings; ranges: 0-15 volts DC; 0-20 amps DC. Doubly protected: fused primary and automatic-reset overload relay for secondary. Heavy-duty binding posts. Blue-finish steel case with "disappearing" handle. With all parts, solder and pre-cut wire. 9 x 12½ x 7¾". Shpg. wt., 20 lbs.

Model F-129. Power Supply Kit. Net only... **\$37.95**



knight-kit AUDIO GENERATOR KIT

Model F-137

\$37⁵⁰

An ideal audio frequency source for checking audio circuits and speaker response. Covers: 20 cps to 1 mc in 5 ranges. Output voltage: 10 volts into 600 ohms impedance. Offers the flat response of a lab standard—±1 db to 1 meg. Generator imp., 600 ohms. Less than .25% distortion from 100 cps through the audible range; less than .5% when driving 600 ohm load at maximum output. Cont. var. step-attenuated output. 17 lbs.

Model F-137. Audio Generator Kit. Net only... **\$37.50**

knight-kit RESISTANCE SUBSTITUTION BOX KIT

Model F-139

\$5⁹⁵

Simplifies determination of resistor values needed in a circuit. 36 standard 1 watt resistance values between 15 ohms and 10 megohms with an accuracy of 10%. 18-position switch; also slide switch for multiplying values by 1000. Extra switch wafer serves as tiepoints, eliminating buss bar. 5 x 3 x 2". Complete with test leads and clips. 2 lbs.

Model F-139. Resin. Sub. Box Kit. Net... **\$5.95**

knight-kit CAPACITANCE SUBSTITUTION BOX KIT

Model F-138

\$5⁹⁵

Makes it easy to find capacitor values needed in a circuit. Provides 18 standard capacitor values from .0001 mfd. to .22 mfd., ±20%. Values are 600 volts, except .15 and .22 which are 400 volt. 18-position switch selects all values quickly and easily. In bakelite case, 5 x 3 x 2". Complete with all parts, test leads and clips. 2 lbs.

Model F-138. Cap. Sub. Box Kit. Net... **\$5.95**

QUALITY ELECTRONIC TEST EQUIPMENT IN MONEY-SAVING KIT FORM

...easiest to build...you get more...YOU SAVE MORE



4 1/2" Meter

Model F-128 **\$16⁹⁵**

knight-kit

1000 OHMS/VOLT VOM KIT

Exceptional accuracy and versatility at amazing low cost. Ideal for service shop, lab and Amateur use. Uses 4 1/2" meter (400 microamp movement) with separate scales for AC voltage and current, DC voltage and current, decibels and resistance. 38 ranges include: AC, DC and output volts, 0-1-5-10-50-100-500-5000 (1000 ohms/volt sensitivity); Resistance, 0-1000-100,000 ohms and 0-1 meg.; Current, AC or DC, 0-1-10-100 ma and 0-1 amps; Decibels, -20 to +69 in 6 ranges. Uses 1% precision resistors. 3-position function switch and 12-position range switch. Complete kit with bakelite case, (6 3/4 x 5 1/4 x 3 3/4"), battery, pre-cut wire, solder and test leads. Shpg. wt., 2 1/2 lbs.

Model F-128. 1,000 ohms/volt VOM Kit. Net only **\$16.95**




Model F-140 **\$29⁵⁰**

knight-kit

20,000 OHMS/VOLT VOM KIT

Outstanding quality and performance at extremely low cost. Features 32 ranges; full vision 4 1/2" meter; accuracy $\pm 2\%$ of full scale; 50 microampere sensitivity for 20,000 ohms/volt input resistance on DC; front panel "zero adjust". Single switch selects function and range. Range: AC, DC and output volts, 0-2.5, 10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg.; DC ma, 0-1-10-100; DC amps, 0-1-10; Decibels, -30 to +63 in 6 ranges. Uses precision 1% multipliers. Moisture-resistant film-type resistors. Complete kit with bakelite case (6 3/4 x 5 1/4 x 3 3/4"), batteries, pre-cut wire, solder and test leads. Shpg. wt., 5 lbs.

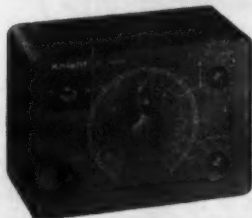Model F-140. 20,000 ohms/volt VOM Kit. Net only **\$29.50**



knight-kit RESISTOR-CAPACITOR TESTER KIT

Model F-124 **\$19⁵⁰** Measures capacitance and resistance by accurate bridge method; checks for opens and shorts in paper, mica and ceramic capacitors; shows power factor of electrolytics.

Large dial shows capacitance and resistance at a glance; balanced-bridge circuit with "magic eye" null indicator measures power factor from 0-50%. Tests capacitors with rated voltages applied. 5 test voltages: 50, 150, 250, 350, 450. Capacitance ranges: 10 mmf to 1000 mfd in 5 ranges. Resistance ranges: 100 to 50,000 ohms and 10,000 ohms to 5 megs. Accuracy, $\pm 10\%$. Automatic discharge feature prevents after-test shock. Blue-finished steel case, 5 x 3 x 2". With tubes and all parts. Shpg. wt., 8 lbs.

Model F-124. Resistor-Capacitor Tester Kit. Net only **\$19.50**



NEW knight-kit TRANSISTOR & DIODE CHECKER KIT

Model F-149

\$8⁵⁰ Checks leakage-to-gain ratio and noise level of all junction, point contact and barrier transistors. Also checks diodes, forward and reverse current conduction of selenium rectifiers; useful for continuity and short checks. Easy-to-read meter. Features: spring-return leakage gain switch; calibration control; separate sockets for PNP and NPN transistors. Headphones or signal tracer may be used with checker for noise measurements. Case, 5 x 3 x 2". With 22 1/2 volt battery. 2 1/2 lbs.

Model F-149. Transistor Checker Kit. Net **\$8.50**

EASY PAYMENT TERMS: If your total KNIGHT-KIT order is over \$45, take advantage of our liberal Time Payment Plan —only 10% down. Write for application blank.

ALL PRICES NET F.O.B. CHICAGO



knight-kit VTVM KIT with Printed Circuit Board

Model F-125 **\$24⁹⁵** An extremely stable, and highly accurate VTVM. Greatly simplified wiring—entire chassis is a printed circuit board. Maximum convenience in arrangement of scales; 3X AC and DC scale design permits utilization of best portion of each scale for most accurate readings. Also measures peak-to-peak for FM and TV work. Ranges: AC

P-P volts, 0-4-14-40-140-400-1400-4000; AC rms volts and DC volts, 0-1.5-5-15-50-150-500-1500; resistance, 0-1000-10K-100K ohms and 0-1-10-100-1000 megohms; db scale, -10 to +5. AC response, 30 cycles to 3 mc. Low-leakage switches and 1% precision resistors. Balanced-bridge circuit. 4 1/2" meter, 200 microamp movement. Polarity reversing switch. Input res., 11 mega. Shpg. wt., 6 lbs.

Model F-125 Printed Circuit VTVM Kit. Net only **\$24.95**

F-126. Hi-Voltage Probe; extends DC to 50,000 Volts **\$4.75**

F-127. Hi-Frequency Probe; extends AC to 250 mc. **\$3.45**



Model F-143

knight-kit LOW-COST TUBE TESTER KIT

\$29⁷⁵ Offers high accuracy, top versatility and convenience at lowest cost. Tests 4, 5, 6 and 7-pin large, regular and miniature types, octals, loctals, 9-pin miniatures and pilot lamps. Features test for new 600 ma series string tubes. Tests for open, short, leakage, heater continuity and quality (by amount of cathode emission). 4 1/2" square meter with clear "GOOD-?-REPLACE" scale. With line-voltage indicator and line-adjust control. Choice of 14 filament voltages from .63 to 117 volts. Blank socket for future type tubes. Universal-type selector switches for any combination of pin connections. Single-unit, 10-lever function switch. Entire switch assembly is installed as a single unit—saves time and greatly simplifies construction. Illuminated roll chart lists over 600 tube types. Shpg. wt., 14 lbs.

Model F-143. Counter Model Tube Tester Kit. Net only **\$29.75**

Model F-142. Portable Model Tube Tester Kit. Net only **\$34.75**

F-141. TV Picture Tube Adapter for above. Net only **\$3.75**



Model F-119

knight-kit LOW-COST

"IN-CIRCUIT" CAPACITOR CHECKER KIT

Tests capacitors while they are still wired in the circuit! Saves time and bother; an essential instrument for the service technician. Just press a button and the "magic eye" instantly shows opens and shorts (not leakage). Tests opens and shorts on any capacitor of 20 mmf or greater capacity, even if it is in parallel with a resistance as low as 50 ohms. Tests for shorts may be made on any capacitor even when it is shunted by as low as 20 ohms. Blue-finish steel case, 7 3/4 x 5 1/4 x 5". With tubes, all parts, wire and solder. Easy to assemble. Shpg. wt., 5 lbs.

Model F-119. Cap. Checker Kit **\$12.50**

order from **ALLIED RADIO**

100 N. WESTERN AVE., CHICAGO 80, ILL.



ALLIED'S own MONEY-SAVING knight-kits

FAMOUS knight-kits FOR HOBBYISTS & EXPERIMENTERS...FASCINATING, INSTRUCTIVE...



knight-kit
"SPACE SPANNER"
BAND SWITCHING
RECEIVER KIT

Model S-243 \$15⁹⁵

Thrilling Short Wave and Broadcast

Famous 2-band AC-DC receiver in easy-to-build kit form at a very low price. Pulls in thrilling short-wave (6 to 17 mc) and standard broadcast. It's fun listening to amateur, aircraft, police and marine radio. Features highly sensitive regenerative circuit. Bandswitch selects broadcast or short wave. Has 4" PM speaker and beam-power output tube for plenty of volume; headphone connectors for weak signal listening; slide switch cuts out speaker. Uses 12AT7 regenerative detector and audio amplifier, 50C5 power output, 35W4 rectifier. Six controls: Bandspread; Main Tuning; Antenna Trimmer; Bandswitch; Regeneration; Audio Gain. Includes tubes and all parts. 7 x 10 1/2 x 6". Shpg. wt. 4 1/2 lbs.

Model S-243. "Space Spanner" Receiver Kit. Net only.....\$15.95
S-247. Matching Cabinet for above. 2 lbs. Net.....\$2.90



Model S-295 \$14⁷⁵

NEW knight-kit TWO-WAY INTERCOM KIT

New low-cost, easy to build intercom system kit. Ideal for use in home or office. Consists of Master unit and Remote unit, each with press-to-talk switch. Remote unit may be left "open" for answering calls from a distance, for "baby-sitting", etc. Remote may also be connected for "private" operation—cannot be "listened-in" on, but it can be called and can originate calls. Master unit includes high-gain 2-stage amplifier; each unit has 4" PM dynamic speaker. Complete with Antique White cabinets (4 3/4 x 6 1/2 x 4 3/4"), all parts, tubes and 50 feet of cable (up to 200 feet of cable can be added). For AC or DC. Shpg. wt., 7 lbs.

Model S-295. Two-Way Intercom Kit. Net only...\$14.75



Model S-740 \$11⁷⁵

knight-kit

"OCEAN HOPPER" RECEIVER KIT

Tops for exciting broadcast, long wave and short wave reception. Highly sensitive regenerative-type circuit. Excellent headphone reception; can be used with 3-4 ohm PM speaker on strong broadcast band stations. Supplied with plug-in coil for standard broadcast; covers long wave and popular short wave bands with coils below. Pulls in thrilling foreign broadcasts, police, amateurs and aircraft. Controls: Main Tuning, Bandspread, Antenna Tuning, Off-On-Regeneration. With all parts and tubes (less extra coils and headset). AC or DC. Shpg. wt., 5 lbs.

Model S-740. "Ocean Hopper" Kit.....\$11.75

EXTRA PLUG-IN COILS

S-741. Long Wave, 155-470 kc. Net.....79¢
S-742. Short Wave, 1.65-470 kc. Net.....79¢
S-743. Short Wave, 2.9-7.3 mc. Net.....65¢
S-745. Short Wave, 7-17.5 mc. Net.....65¢
S-744. Short Wave, 15.5-35 mc. Net.....65¢




Model S-735 \$17²⁵

knight-kit

"RANGER II" SUPERHET RADIO KIT

Thousands have built and enjoyed the "Ranger" Broadcast Band Receiver. Carefully engineered for easy construction and powerful, sensitive performance. Latest Superhet circuit; tunes 540 to 1680 kc; covers entire broadcast band and exciting police calls. Features automatic volume control, built-in preformed loop antenna, ball-bearing tuning condenser. Develops excellent tone quality from Alnico V PM dynamic speaker. Supplied with following tubes: 12SA7GT converter; 12SK7GT IF amp.; 12SQ7GT det.-AVC-audio; 60L6GT audio output; 35Z5GT rect. Complete with handsome brown plastic cabinet (6 x 9 x 5) tubes, speaker, all parts, and instruction manual. AC or DC operation. Shpg. wt., 8 lbs.

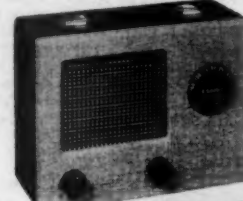Model S-735. "Ranger II" Superhet Radio Kit. Net only.....\$17.25




Model S-730 \$19⁹⁵

knight-kit

3-WAY PORTABLE RADIO KIT

A low-cost portable radio covering the full standard broadcast band from 535 kc to 1650 kc. Delivers excellent reception on AC or DC current or from self-contained batteries. Sensitive Superhet circuit features automatic volume control, economical operation. Includes powerful 5" Alnico PM dynamic speaker, efficient ferrite loop-stick antenna. Supplied with following tubes: 1R5 converter; 1U4 IF amplifier; 1U5 detector-AVC-audio; 3V4 audio output. Complete with attractive portable case (7 3/4 x 10 x 5 1/4"), tubes, speaker, all parts and instruction manual. Shpg. wt., 6 lbs.

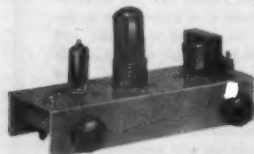Model S-730. 3-Way Portable Radio Kit (less batteries). Net.....\$19.95
J-651. Battery Kit for above.....\$2.50



Model S-790 \$8⁹⁵

knight-kit LOW COST PHONO AMPLIFIER KIT

It's easy to build this fine-performing, low-cost compact phono amplifier. Ideal for use in a portable phono-graph—simply add any record player and a 3 to 4-ohm speaker. Amplifier works with crystal or ceramic cartridges. Inverse feedback circuit for rich, clean tone quality. Delivers full 1 1/2-watt output with less than .25 volt input. Includes efficient tone control; has AC outlet, controlled from amplifier switch. Complete with tubes and all parts. Size only 4 1/2 x 7 x 4"—fits into almost any portable phono case. Shpg. wt., 3 lbs.

Model S-790. Phono Amplifier Kit. Net only.....\$8.95

FAMOUS knight-kit CRYSTAL SET KIT

Model S-261

\$2¹⁵


Thousands of beginners have started in radio and electronics by building the KNIGHT-KIT crystal set. This feature-packed set delivers loud, clear reception of local broadcast stations. A germanium crystal diode detector assures high sensitivity and simple operation—no crystal adjustment required. "Hi-Q" coil boosts sensitivity. Ball-bearing variable capacitor for easy tuning. With all parts and simple-to-follow instructions. Shpg. wt., 1 lb.

Model S-261. Crystal Set Kit. Net only.....\$2.15
S-267. Accessory Kit. 2000-ohm headphones and all parts for outdoor antenna.....\$2.95

Buy with confidence from ALLIED—America's Pioneer in Electronic Kits

finest quality electronic equipment in lowest-cost kit form

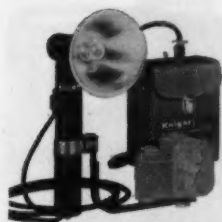EASY-TO-BUILD HIGH PERFORMANCE KITS • WIDELY USED BY MANY LEADING TRAINING SCHOOLS




NEW knight-kit ELECTRONIC PHOTOFLASH KIT

Model S-244 New feature-packed photoflash kit—designed for top quality dependability—available at a money-saving low price. Ideal for black and white or color photography. Xenon-filled reflector-bulb assembly gives over

10,000 flashes at less than $\frac{1}{2}$ ¢ each! 1/700-second flash freezes the fastest action. Has 50 watt-second output. Provides light approximating daylight in spectral quality; permits the use of outdoor-type film indoors. Film guide number for color (ASA10) is 45. Designed for "X" or "O" shutters only. Requires sync cable (available from any photo supply dealer) and either battery or AC supply listed below. Complete outfit with battery weighs only $3\frac{1}{2}$ lbs. Kit includes all parts, carrying case and easy-to-follow instructions. Shpg. wt., 3 lbs.

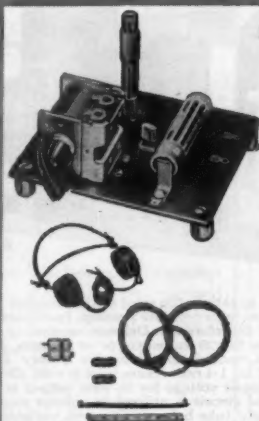Model S-244. Electronic Photoflash Kit. Net.....\$28.50
S-246. AC Power Supply Kit. Easy to assemble.....\$3.75
J-626. Battery for above (Burgess U-200).....\$8.47




knight-kit TRANSISTOR RADIO KIT Printed Wiring • Works from Penlight Cell

Model S-765 \$4.35 Smooth Variable Capacitor Tuning

Experiment with the marvel of transistors! Printed circuit requires no wiring—just assemble with a few solder connections and enjoy excellent reception over the full AM broadcast band. No tubes to burn out—no crystal. Compact—fits in the palm of your hand—operates for months from a single penlight cell. Transistor provides plenty of power for strong headphone reception. Complete with all parts, transistor and penlight cell. Shpg. wt., 8 oz.

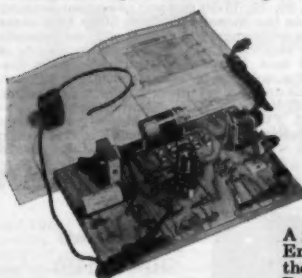Model S-765. Transistor Radio Kit \$4.35
S-266. Accessory Kit. 4000-ohm headphones and all parts for outdoor antenna.....\$3.15




FAMOUS knight-kit LAB KITS

6-IN-1 RADIO LAB KIT

Model S-770 \$7.95 Build Any of 6 Electronic Projects

A fascinating and instructive kit. Enables you to build any one of the following projects: Standard Broadcast Receiver; Wireless Amplifier (for phono or mike); Wireless Phono Oscillator; Home "Broadcast Station"; Code Practice Oscillator; Capacity-Operated Relay, or any one of four other fascinating projects. Low voltages; safe to build and operate. Only tools needed are screwdriver and pliers. Perfect for self-instruction in circuit fundamentals, and packed with practical applications. Kit includes mounting board, tubes, all parts, hardware, microphone, and 12-page builders' manual. Shpg. wt., 10 lbs.

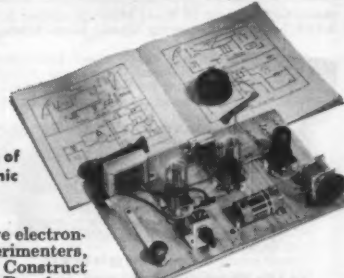Model S-770. "6-in-1" Lab Kit. Net only.....\$7.95
J-112. Single 1000-ohm headphone for above.....\$1.05
C-100. Antenna kit for above.....\$1.05




10-IN-1 LAB KIT

Model S-265 \$12.65 Build Any of 10 Electronic Projects

A wonderfully instructive electronics kit. Ideal for experimenters, beginners—fun to build. Construct a sensitive Broadcast Receiver; Amplifier (for phono or mike); Wireless Phono Oscillator; Home "Broadcast Station"; Code Practice Oscillator; Capacity-Operated Relay, or any one of four other fascinating projects. Low voltages; safe to build and operate. Only tools needed are soldering iron, screwdriver and pliers. Perfect for self-instruction in circuit fundamentals, and packed with practical applications. Kit includes mounting board, tubes, all parts, hardware, microphone, and 12-page builders' manual. Shpg. wt., 10 lbs.

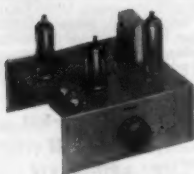Model S-265. "10-in-1" Lab Kit. Net only.....\$12.65
J-112. Single 1000-ohm headphone for above.....\$1.05
C-100. Antenna Kit for above.....\$1.05



knight-kit WIRELESS BROADCASTER KIT

Model S-705 \$9.50 This fascinating unit makes it possible to "broadcast" with phonograph or microphone through any standard radio receiver up to 50 feet away—without any connection to the set. May be used with crystal or magnetic cartridge, or with microphone.

Broadcasts a clear, full-toned signal. High-gain stage permits using magnetic cartridge without need for external preamp. Complete with all parts, tubes, wire and solder (less microphone). $4\frac{1}{2}$ x 5 x 6". Easy to assemble. Shpg. wt., 3 lbs.

Model S-705. Wireless Broadcaster Kit. Net only.....\$9.50
S-356. Microphone for above with 5-ft. cable.....\$3.95



knight-kit PHONO OSCILLATOR KIT

Model S-760 \$5.85 This low-cost phono oscillator may be used with any crystal phonograph for "broadcasting" recorded music through any standard radio receiver up to 50 feet away. Requires no direct connection to radio set. Operates on any frequency between 600 and 800 kc. Has controls for adjustment of modulation level and selection of clear frequency on radio receiver. Uses 50L6GT tube and 35Z5GT rectifier. Complete with all parts, tubes and instructions. $4\frac{1}{4}$ x $4\frac{1}{4}$ x $4\frac{1}{4}$ ". Shpg. wt., 1 lb.

Model S-760. Phono Oscillator Kit. Net only.....\$5.85



knight-kit CODE PRACTICE OSCILLATOR KIT

Model S-239 \$3.95 Transistor Circuit—Powered by Penlight Cell

An ideal code practice oscillator. Uses transistor circuit. Extremely low current consumption—powered by single penlight battery. Provides crisp, clear tone (400 to 600 cps). Has input jack for earphone; screw-type terminal strip for key. In compact bakelite case ($2\frac{3}{4}$ x $3\frac{3}{4}$ x $1\frac{1}{4}$ ") with anodized aluminum panel. Complete with all parts, transistor, battery and easy-to-follow instructions. Shpg. wt., 1 lb.

Model S-239. Code Practice Kit.....\$3.95

See Next Page for Amateur Kits

ALL PRICES NET F.O.B. CHICAGO

order from **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 80, ILL.



ALLIED'S own knight-kits give you the most for your money

BUILD YOUR OWN QUALITY HI-FI AMPLIFIER!

knight-kit BASIC 25-WATT LINEAR-DELUXE HI-FI AMPLIFIER KIT


Model S-755
\$44.50

Williamson-Type Circuit
Printed Circuit Board
Chrome-Plated Chassis



This super-quality hi-fi basic amplifier is designed to satisfy the most critical listener. Intended for use with tuners incorporating built-in preamp or with separate preamp. Incorporates latest Williamson-type circuit and has potted matched transformers. Delivers maximum output of 45 watts. Frequency response is: ± 0.5 db, 10 cps to 120 kc, measured at 20 watts. Harmonic distortion is only .15% right up to 30 watts. Intermodulation distortion is only .27% at 10 watts and only .4% at 20 watts, using 60 cps and 7 kc, 1:4 ratio. Hum level is -85 db below full rated output. Output impedance, 4, 8, 16 ohms. Input voltage for 25-watt output is 1.8 volts. Uses two 12AU7's, two 5881's, and a 5V4. Etched circuit is utilized in voltage amplifier and phase inverter stages to speed assembly. Has output tube balancing control, variable damping control, and on-off switch. Handsome chrome-plated chassis, 14 x 9 x 2". Overall height, 7". A deluxe true hi-fi amplifier equal in performance to amplifiers selling at over twice the price. Complete with all parts and tubes. Easy to assemble. Shpg. wt., 27 lbs.

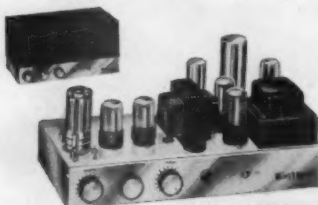
Model S-755. Basic 25 Watt Hi-Fi Amplifier Kit. Net only.....**\$44.50**
S-759. Metal enclosure for above; black finish. 3 lbs. Net.....**\$4.25**



knight-kit 10-WATT HI-FI AMPLIFIER KIT

Model S-753 Chrome-Plated Chassis
\$23.50
Famous for wide response and smooth reproduction at low cost. Only 0.5 volt drives amplifier to full output. Frequency response: ± 1 db, 30-20,000 cps at 10 watts. Harmonic distortion less than 0.5% at 10 watts. Intermod. distortion less than 1.5% at full output. Controls: on-off-volume, bass, treble. Input for crystal phono or tuner. Chromed chassis; punched to accommodate magnetic cartridge preamp. Matches 8 ohm speakers. Shpg. wt., 14 lbs.

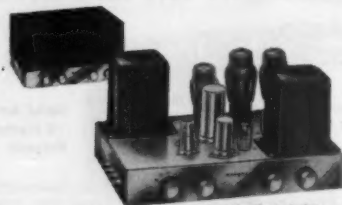Model S-753. Amplifier Kit. Net.....**\$23.50**
Model S-235. Preamp Kit for above...**\$3.10**
S-757. Metal Enclosure. 3 lbs.....**\$3.95**



knight-kit 20-WATT HI-FI AMPLIFIER KIT

Model S-750 Chrome-Plated Chassis
\$35.75
True hi-fi for less! Frequency response, ± 1 db, 20-20,000 cps at 20 watts. Distortion, 1% at 20 watts. Hum and noise level: tuner input, 90 db below 20 watts; phono 72 db below 20 watts. 4 inputs: magnetic phono, microphone, crystal phono or recorder, and tuner. Controls: Bass, Treble, Volume, Selector. With compensation positions for 78 and LP records. Built-in Preamp. Outputs: 4, 8, 16 and 500 ohms. 23 lbs.

Model S-750. 20-Watt Kit. Net.....**\$35.75**
S-758. Metal Enclosure. 3 lbs.**\$4.15**
S-752. Chrome-plated escutcheon for cabinet installation of amplifier. Net.....**\$1.40**

LOW-COST TOP QUALITY KITS FOR THE HAM



knight-kit Model S-255 50-WATT CW TRANSMITTER KIT Built-in Pi-Type Antenna Coupler

\$38.95
Check the features packed into this new transmitter kit and you'll see why it's one of the greatest Amateur values ever offered. Compact and versatile, it is the perfect low-power rig for the beginning Novice or seasoned veteran. Features: 50 watts input to 807 final; high-efficiency 6AG7 modified-Pierce oscillator takes crystal or VFO without circuit changes; bandswitching coverage of 80, 40, 20, 15, 11-10 meters; pi-section antenna output matches line impedances from 50 to 1200 ohms —permits use with any type of antenna; no separate antenna tuner required. Crisp, clean, cathode keying of oscillator and final. Power take-off plug supplies filament and B-plus voltages for other equipment. Copper-finished chassis and cabinet interior, filtering, shielding, bypassing, and coaxial SO-239 antenna connector provide excellent TVI suppression. Meter reads either plate or grid current of final. Jacks for VFO, crystal and key. Supplied with all parts and tubes. Less crystal and key. 8 3/4 x 11 1/4 x 8 3/4". Shpg. wt., 18 lbs.

Model S-255. 50-Watt Transmitter Kit. Net....**\$38.95**



knight-kit SELF-POWERED VFO KIT

Model S-725
\$28.50

Complete with built-in power supply! Careful design and voltage regulation assure high stability. Excellent oscillator keying characteristics for fast break-in without clicks or chirps. Full TVI suppression. Has plenty of bandspread: separate calibrated scales for 80, 40, 20, 15, 11 and 10 meters; vernier drive mechanism. 2-chassis construction keeps heat from frequency determining circuits. Output cable plugs into crystal socket of transmitter. Output on 80 and 40 meters. With Spot-Off-Transmit switch for "no swish" tuning. Extra switch contacts for operating relays and other equipment. With all parts and tubes. 8 lbs.

Model S-725. Self-Powered VFO Kit. Net....**\$28.50**



NEW knight-kit AMATEUR RF 'Z' BRIDGE KIT

Model S-253
\$5.85

Measures standing wave ratio (SWR) and impedance of antenna systems; also for adjusting antenna networks for optimum results. Any VOM may be used for null indicator. High accuracy with 20,000 ohm/v VOM. Correction factor info supplied for other VOM's. With coax input and output connectors. Meters both input and bridge voltage. Calibrated dial gives direct impedance reading; includes 1% precision resistor for precise calibration adjustment. With all parts and handy plasticized SWR chart. 1 1/2 lbs.

Model S-253. "Z" Bridge Kit. Net only.....**\$5.85**

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

our
36th year

ALLIED RADIO CORP., Dept. 01-B-7, 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$_____ enclosed. For parcel post include postage (express is shipped collect).

Name _____

Address _____

City _____

Zone _____

State _____

← *order Today*

LATEST ALLIED knight-kits




NEW for the
Serviceman

knight-kit
**FLYBACK
CHECKER KIT**

Model Y-118 **\$19.50**

Race through TV deflection circuit repairs for extra servicing profits with this new Flyback and Yoke Tester! Instantly checks all types of standard horizontal output transformers as well as linearity and width coils. Positively indicates shorted turns for any coil with a "Q" greater than 1, and inductance between .003 and 2 henries. Determines continuity of any circuit with resistance from zero to .5 meg. Checks wider range of inductances than any other similar unit. Has highly legible $4\frac{1}{2}$ " meter. Uses 684-A pulsed oscillator circuit. Supplied with all parts and test leads. $7\frac{1}{2} \times 5\frac{1}{2} \times 6"$. Shpg. wt. $5\frac{1}{2}$ lbs.

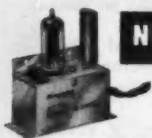Model Y-118. Flyback Checker Kit. **\$19.50**
Net.....




NEW for the Ham

knight-kit
**100 KC CRYSTAL
CALIBRATOR KIT**

Model Y-256 **\$10.50**

New universal frequency calibrator to fit any communications receiver—priced so low every Ham can afford it. Uses hermetically-sealed 100 KC crystal. Generates 100 KC markers all the way up to 35 mc. Compact case is only $3 \times 1\frac{1}{2} \times 1\frac{1}{2}$ "; has universal mounting flanges for mounting in any of several positions. Requires only 6.3 v. at .15 amps and 150-350 v. at 3-6 ma. Includes crystal zeroing trimmer and on-off switch which mounts on case. Connects to receiver input. Uses 6AK6 as electron-coupled oscillator. Complete with formed and punched case, 100 KC crystal, tube, all parts and instructions. Shpg. wt., 1 lb.

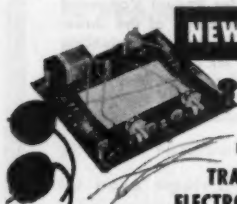Model Y-256. Crystal Calibrator Kit. **\$10.50**
Net.....



NEW for the
Experimenter

knight-kit
**TRANSISTORIZED
ELECTRONIC LAB KIT**

Model Y-299 **\$15.45**

It's sensational—learn how transistors operate—see all the projects you can make with this all-new electronic marvel! You just assemble the basic parts once. Then you complete project after project (10 in all), just by inserting the "plug-in" leads into the proper jacks on the printed-circuit board—without additional soldering! You can complete and enjoy any of these: a fine AM radio; a wireless home "broadcaster"; phono amplifier; code practice oscillator; electronic timer, switch or flasher; voice-operated, capacity-operated and photoelectric relays. It's the most fascinating experimenters' kit ever developed! Includes all parts, two transistors, battery, headphones and special cards showing you how to plug in each project. Shpg. wt., 3 lbs.

Model Y-299. Transistorized Lab Kit. **\$15.45**
Net.....

← use order blank
on opposite page

Sun	Mon	Tue	Wed	Thu	Fri	Sat
			1	2	3	4
						5
						12
						19
						26

CALENDAR of EVENTS

FEBRUARY 1, 2, 3

High Fidelity Music Show. Sponsored by Rigo Enterprises, Inc. Statler Hotel, Detroit, Michigan. Contact the sponsor at Suite 1002, 500 N. Dearborn, Chicago 10, Ill.

FEBRUARY 7-8

Conference on Nucleonics in Industry. Sponsored by American Management Association. Hotel Statler, New York, N. Y. Contact the association at 1515 Broadway, New York 36, N. Y., for full program data.

FEBRUARY 14

Symposium on Recording of Heart Sounds. Sponsored by PGME. University of Buffalo Medical School, Buffalo, N. Y. Godfrey F. Buranich, Bell Aircraft Corp., Buffalo 5, N. Y., program chairman.

FEBRUARY 14-15

Conference on Transistor Circuits. Sponsored by PGCT, Philadelphia Section of IRE, and AIEE, Philadelphia, Pa. Dr. Geo. H. Royer, Westinghouse Electric Corp., 356 Collins Ave., Pittsburgh 6, Pa., program chairman.

FEBRUARY 15-16

Spring Meeting. National Society of Professional Engineers. Hotel Francis Marion, Charleston, S. C. Contact society at 2029 K St., N.W., Washington 6, D. C.

Cleveland Electronics Conference. Masonic Auditorium, Euclid Avenue & East 36th, Cleveland 14, Ohio. D. C. Griffith, conference chairman, 18511 Euclid Ave., Cleveland 12.

FEBRUARY 22, 23, 24

High Fidelity Music Show. Sponsored by Rigo Enterprises, Inc. Hollenden Hotel, Cleveland, Ohio. Contact the sponsor at Suite 1002, 500 N. Dearborn, Chicago 10, Ill.

FEBRUARY 25-27

Special Conference on Electronics in Action. Sponsored by the American Management Association's Finance Div. Statler Hotel, New York, N. Y. Contact AMA at 1515 Broadway, New York 36, N. Y.

FEBRUARY 26-28

1957 Western Joint Computer Conference. Sponsored by the IRE, AIEE, and Association for Computing Machinery. Hotel Statler, Los Angeles, Cal. Information on program from IRE, 1 E. 79th St., New York 21, N. Y.

SENSATIONAL NEW knight-kit HI-FI FM TUNER KIT




knight-kit


HI-FI BASIC FM TUNER KIT

Model Y-751 • Featuring deluxe custom high-fidelity styling
• With latest AFC and Flywheel Tuning Control
• Latest printed circuit—no critical wiring required

\$37.75

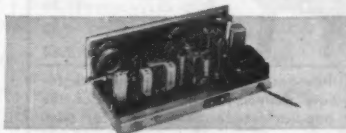

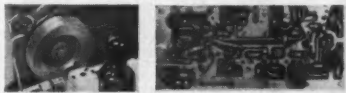Advanced Tuner Circuit—noise-free and highly sensitive. Automatic Frequency Control "locks in" on station; AFC disabling feature helps tune in weak stations.



Flywheel Tuning—Weighted flywheel tuning mechanism—greatly simplifies assembly and reduces wiring time. Circuit board clearly shows placement of basic components.

INCOMPARABLE HI-FI KIT VALUE

Here is not only the best-looking tuner kit your money can buy, but the only FM tuner kit offering all these features: *Printed circuit* for easy assembly; *automatic frequency control* for "lock-in" tuning of stations, with disabling feature for tuning in weak stations; *pre-adjusted RF coils on rigid forms*—no further adjustment required; *pre-aligned I.F.s*; *front ventilation*—an integral part of panel design (no unsightly perforations on cabinet.)

SPECIFICATIONS: Tuning Range: 88-108 mc. Output: 2 volts at 1000 microvolt input. IF Bandwidth: 200 kc. Audio Response: 20-20,000 cps with only .06% distortion. 2 Output Jacks: one for feeding amplifier, the other for tape recorder. Sensitivity: 10 microvolts for 20 db quieting across entire band. Cascade broadband RF amplifier. Drift-compensated oscillator. Ideal for use with the Model S-750 Knight-Kit 20-Watt Amplifier kit (see opposite page), or any amplifier equipped with phono-tuner switch. In beautiful gray cabinet with polished aluminum control panel; $4 \times 13 \times 8"$; illuminated lucite pointer highlights station selection. Complete, ready for easy assembly. Shpg. wt., 12 lbs.

Model Y-751. Basic FM Tuner Kit. **\$37.75**
Net.....

SPECIAL TUNER-AMPLIFIER OFFER

Exclusive hi-fi value—the new FM tuner kit, plus the 20-watt amplifier kit on opposite page (including metal enclosure) for only \$73.65! Buy this matched Hi-Fi combination and save \$4.00! Shpg. wt. 35 lbs. Y-761. Knight-Kit Tuner and 20-Watt Amplifier. Net..... **\$73.65**
Only \$7.37 down on our Easy Pay Plan

← use order blank
on opposite page

QUARTZ CRYSTALS

Fast Service—Unconditional Guarantee

We will grind and etch crystals to your specified frequency at the lowest cost in the industry—supplied in popular FT-243 holders, 1/2" pin spacing, .093" pin diameter—also in DC-34 holders, 3/4" pin spacing, pin diameter .156 or FT-171 holders, pin spacing 3/4" with banana plug pins (fits 5-prong tube socket).



In FT-243 holders from 1100KC to 9000KC. In DC-34 or FT-171 holders from 1100KC to 8000KC (specify holder wanted).

Tolerance:

.05%\$1.35
.01% 1.50
.005% 2.50

With thousands of frequencies in stock for immediate delivery, we list a few of the more popular frequencies. Write for complete listing. Crystals listed are in FT-243 holders but can be supplied in FT-171 holders at 79 cents. (Add 5¢ per crystal for postage and handling.)

2910	6150	7206	8106
2945	6300	7225	8125
3000	6400	7240	8140
3190	6500	7250	8150
3195	6575	7273	8175
3245	6625	7275	8200
3525	6700	7300	8240
3885	6706	7306	8250
3955	6750	7325	8300
3995	6775	7340	8350
4110	6800	7350	8375
4190	6850	7373	8400
4845	6900	7375	8425
5030	6950	7400	8450
5300	7000	7406	8475
5305	7006	7500	8500
5700	7025	7606	8525
5800	7050	8000	8550
6000	7075	8006	8575
6025	7100	8025	8600
6040	7106	8040	8625
6050	7125	8050	8650
6075	7140	8073	
6100	7150	8075	
6125	7200	8100	

WRITE FOR FREE CRYSTAL CATALOG

Novice Crystals 80 meter band within 1KC of specified frequency from 3701KC to 3749KC in 40 meter band from 7152KC to 7198KC within 1KC of specified frequencies 79¢; in DC-34, FT-171 or FT-243 holders (specify holder wanted) 79¢. (Add 5¢ per crystal for postage and handling.)

Stock crystals in FT-243 holders from 5675KC to 8650KC in 25KC steps 50¢.

FT-241 lattice crystals in all frequencies from 370KC to 540KC 50¢.

100KC Frequency Standard Crystals	4.50
200KC Crystals	2.00
455KC Crystals	1.00
500KC Crystals	1.00
1000KC Frequency Standard Crystals	3.50

Jobbers and manufacturers, write for quantity prices and catalog.

Address all mail to Dept. R

Texas Crystals

The Biggest Buy in the U.S.

8538 W. GRAND AVENUE - RIVER GROVE, ILL.
ALL PHONES - GLADSTONE 3-3555

Terms: All items subject to prior sale and change of price without notice. All crystal orders MUST be accompanied by check, cash or M.O. WITH PAYMENT IN FULL. NO C.O.D.s. Postpaid shipments made in U.S. and possessions only. Add 5¢ per crystal for postage and handling charge.

First Guidance System for Satellite Rocket

Honeywell describes operation of inertial guidance system.



First guidance reference system for rockets that will attempt to put man-made satellites in their earth-circling orbits gets the once-over from test pilot Jim Bailey, whose job is testing automatic flight control systems on supersonic jet aircraft.


THE first guidance reference system for the dozen or more proposed earth-satellite-carrying rockets has come off a pilot production line at Minneapolis-Honeywell Regulator Co. more than a year before the Project Vanguard vehicle is scheduled to be launched. Unlike systems that require radio or radar tracking, the Vanguard guidance reference system is entirely rocket-borne. Its job will be to keep the finless rocket from swerving off course because of sloshing fuel, air currents, or other forces, and to gradually "tip" the rocket's trajectory so that it enters a globe-circling course some 300 miles above the earth. Heart of the control system are three highly accurate gyroscopes that will be calibrated to a "memorized" heading reference in the three axes or directions of flight—roll, pitch, and yaw.

Temperature controllers will be used to keep the gyros at operating temperature through built-in heaters. The controllers are all-transistor amplifiers built around a half-dozen H-6 power transistors, which are used for both power and switching functions. There are no relay contacts in the system,

thereby avoiding shock and vibration problems. Signal generator pick-offs and torque generator units are at the ends of the gyro cases.

If the rocket incorrectly rotates—because of sloshing fuel, engine irregularity, etc.—about any of the three axes "memorized" by the roll, pitch, and yaw gyros even an infinitesimal part of a degree, the gyro motor will respond by rotating the gimbal on its jeweled bearings. This movement is sensed by the gyro signal pick-off and sent out as an electrical signal from the gyro through the autopilot amplifier to the error-correcting servo system.


Functional diagram of three-axis guidance reference system for Project Vanguard rocket shows placement of three gyros on platform in second stage of the three-stage rocket. These and other components will be housed in container resembling two derby hats placed brim to brim. Each gyro will have its own temperature regulator, amplifiers, and other electronic equipment. A scheduling device will operate through the pitch gyro only to control the arching path of the rocket.

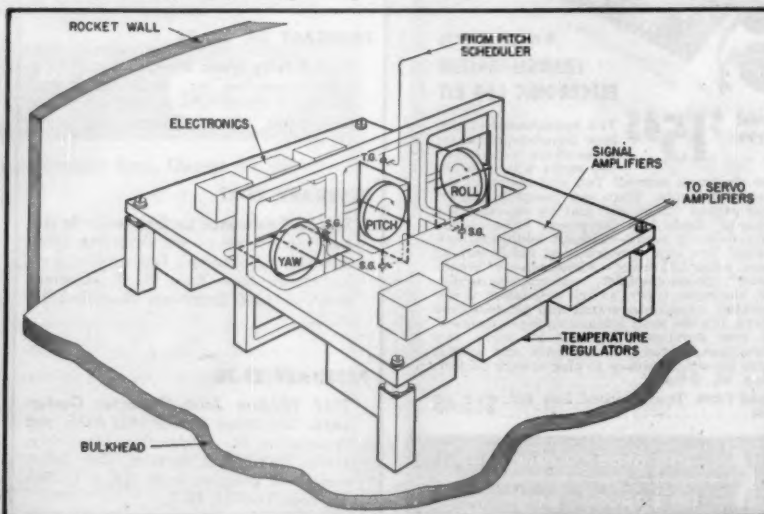

4 Pages of
Mail-Order
Bargains

RADIO

CROSLLEY TRANSISTOR RADIO SALE!

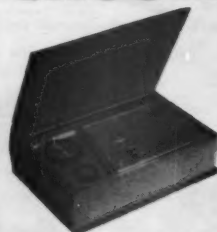

**LEATHER BOUND
TRANSISTOR BOOK RADIO**

Sold
for
\$49.95

\$29⁹⁵

One of the most sensational money-savers we've ever run across. Fabulous CROSLLEY TRANSISTOR BOOK RADIO made to actually net for \$49.95! You save a clear \$20.00 at RADIO SHACK. What's more you get one of the most luxurious, hottest transistors ever built. Lift the cover and radio plays, close cover and radio automatically shuts off. Richly bound in durable top grain leathers with handsome gold embossing. Latest combination transistor and subminiature circuit provides outstanding performance and an amazingly long battery life. Has all of the most desirable electronic developments including printed circuits chassis, alnico V PM speaker, automatic volume control, built-in ferrite antenna, sensitive superhet circuit and push-pull transistor output for greater usable audio level than receivers using a tube in this stage. Ship. wt. 2½ lbs. Order Item A-1E

Order Item A-2E Batteries for Above\$3.95

TRANSISTOR RADIO KIT

Complete with:

**\$1.10 MERCURY BATTERY
\$1.39 CRYSTAL EARPHONE**



Reg. \$22.44 **\$12⁹⁵**

New powerful midget, 2 transistor portable to take with you everywhere! Step-by-step assembly; includes chassis, parts! Ship. 1½ lbs. Order Item A-3E Complete \$12.95

VERDUN EARPHONES!

For Transistor and
Subminiature Use




\$1.39

Just 3 oz. in weight; wide range, sensitive Crystal earphone can be used as tiny mike. Less plug and jack. Ship ¼ lb. Order Item A-4E Sale \$1.39 "Dynamic" — 3000 ohms @ 1000 cps. Order Item A-5E Sale \$1.89

1½" PM SPEAKER

**WORLD'S
SMALLEST**

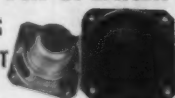

8-ohm voice coil imp. Shallow cone with shielded pot construction, magnet totally enclosed 15/16" depth, 6/32 mag holes. Ship. ½ lb. Order Item A-6E Sale \$1.95 With Matching Output Transformer! Order Item A-7E Sale \$2.90

PORTABLE RADIO AND



**3-SPEED
PHONO**

Reg. \$39.95

\$24.95

Compact, jewel-like molded case holds a fine 3-speed record player with an all-groove cartridge and an AM superhet radio. Ship. 7 lbs. Order Item A-8E Sale \$24.95

DIAMOND-SAPPHIRE for GE RPX-050, RPX-050A



List \$30.00

\$10⁴⁰

NEW-type stylus assembly with slip-on diamond .001" LP tip and sapphire .003" 78 tip. Guaranteed 1st quality whole stone. Ship. ¼ lb. Order Item A-9E Sale \$10.40

**Do You Have
Radio Shack's Complete
212 Page
Catalog?
It's FREE!!!**

PRECISION MICRONTA MULTITESTERS

- ★ ALL WITH SILVER SWITCH CONTACTS!
- ★ ALL WITH RUBBER LEADS, 3" METERS!
- ★ ALL WITH MICRONTA-RETMA GUARANTEES!
- ★ ALL ASTONISHINGLY LOWER PRICED!




NOW WITH 1% WIRE- WOUND RESISTORS

RADIO SHACK's answer to high quality at a sensible price. 5-AC ranges to 1000 volts. 6-DC ranges to 5000 volts. 4-DC current ranges from 50 ua. to 500 ma. 4-resistance ranges to 10 megohms. 2-db ranges — 20 to +36. Not a kit!

Order Item A-12E Ship wt. 4½ lbs.Only \$19.90

Exclusive MICRONTA multitester would cost at least twice our price if made in this country. Same ranges as above except DC current 4-ranges from 250 ua. to 500 ma. 160 ua. jeweled meter. Bakelite case. Completely wired and tested. Order Item A-11E Ship wt. 4 lbs.Only \$14.50

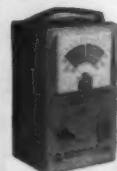Lowest priced high sensitivity (4000 /v DC) multitester in America! 16 ranges: 5-AC ranges to 1000 volts; 4-DC ranges to 1000 volts. 3-DC current ranges from 250 ua. to 250 ma. 2-resistance ranges to 1 megohm. 2-db ranges — 30 to +36 db. Wired, with test leads and batteries. Order Item A-10E Ship wt. 2½ lbs.Only \$9.95




Reg.
\$39.75

\$19⁸⁸

HALF-PRICE SALE! RCP FLYBACKER

Fast, accurate, reliable tester has 3 direct-reading calibrated GOOD-BAD scales for high and low impedance. 4½" illuminated meter. Operates dynamically. Ship. 8 lbs. Order Item A-13ESale \$19.88

FABULOUS TAYLOR WEATHER KIT!!

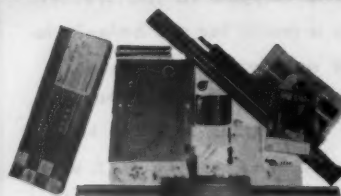

Exclusive Sale!

Made by Taylor
Instrument Co.
to sell for \$24.95

\$9⁹⁵

With \$11.00
Mercury Column

Prepared under guidance of Encyclopedia Britannica
and Chicago Museum of Science and Industry!

- ★ Over \$30 Parts Value!
- ★ Builds 34½" Barometer!
- ★ Builds Hygrometer!
- ★ Builds Max-Min Therm'r!
- ★ Builds Wind and Cloud
Speed Dir. Indicators!
- ★ 48-Page Weather Book!

Save \$15.00 on this lavishly complete weather measurement and forecasting kit! Packed in a huge 37 x 12½ x 2½" carton — an immense variety of parts, instructions, charts, this kit is the ultimate in education, entertainment and useful practicality. Deluxe components of glass, metal and wood. Ship. 10 lbs., Railway Express only. Order Item A-14EComplete \$9.95

RADIO SHACK CORPORATION

167 Washington St., Boston, Mass. • 230 Crown St., New Haven, Conn.


SEE ORDER BLANK
ON LAST PAGE ➡

SHACK

4 Pages of
Mail-Order
Bargains

REALISTIC "AM" TUNER CLOSEOUT!!

**SALE!! \$59.95 RCA
TV REMOTE CONTROL**

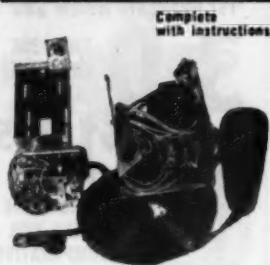


**RELAY ACTUATED
MOTOR DRIVEN \$17.95**

Turns set On-Off, selects channel, adjusts volume, adjusts picture, adjusts fine tuning... at distances up to 30 feet from set! Superbly engineered and built by RCA for installation in VHF TV receivers using KC596 and KC597 series chassis. Also fits most receivers KC566 thru KC592 series chassis. (Complete listing of Sets and Chassis available upon request.) Complete assembly consists of: Relay Unit containing motor relay, on-off relay, local-remote relay and relay transformer; Channel Selector Drive Motor Unit; Remote Control Tuning Head with 30 feet of flat control cable. Official RCA installation booklet included. RCA factory boxed with all necessary parts. RCA Cat. No. 965099. Wt. 12 lbs.
Order Item No. B-1E.....\$17.95

**Do You Have
Radio Shack's Complete
212 Page
Catalog?
It's FREE!!!**

**FAMOUS RECORDING
TAPE BONANZA!**

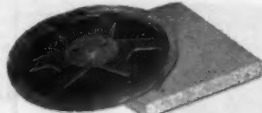

1800-FT ACETATE
ON 5-INCH REEL
Regularly \$2.25 **\$1.99** B-2E

1800-FT ACETATE
ON 7-INCH REEL
WITH NEW 2 1/2" HUB
Regularly \$5.50 **\$2.39** B-3E

2400-FT MYLAN
ON 7-INCH REEL
WITH NEW 2 1/2" HUB
Regularly \$8.95 **\$3.99** B-4E

**Exclusive "Archer" Brand
MIKE SALE!**

'LIPSTICK' CRYSTAL



LIST \$21.00

\$5.95

NEW 4 1/4" long 3-OUNCE mike has hi-fi 50-10,500 cps response! Includes 10 feet of cable, stand attachment for 180° tilt. 100% detachable for hand-mike use. TV-gray and chrome. Ship. 2 lbs.
Order Item B-5E.....Sale \$5.95

'BULLET' CRYSTAL



LIST \$9.00

\$3.85

NEW imported mike has 85-7000 cps response and output 1000 c/s — 48 db. Yet cost 50% less than if made here. TV-gray; 15 feet of cable, swivel neck. 3/8"-27 thread. Ship. 1 lb.
Order Item B-6E.....Sale \$3.85

SI-D DYNAMIC



LIST \$40.00

\$10.95

NEWLY restyled for 1957 with lustrous gray body, gold screen, gray cord. High imp. (30K), hi-fi (50-13,000 cps) SLIM dynamic features built-in on/off switch, tuned cavity design. 12 ft. cable. Has slip-out cradle rest. Ship. 2 lbs.
Order Item B-7E.....Sale \$10.95

**SALE! HI-FI ORGAN
DEMONSTRATION!**

Reg. \$5.95
12" LP } **\$2.95**
RECORD }

List \$10.95
7 1/2 ips } **\$4.98**
TAPE }

A rare record at any price! All classical selections: Farnam, Karg-Elert, Dupre, Vietne, Mulet, Alain, Brahms, Widor. Organist: Adam Hamme, S.M.M. instrument: 3-manual Aeolian-Skinner pipe organ of Zion Lutheran Church, York, Pa. This fine record is exclusive at Radio Shack. All selections are complete and uninterrupted — no speaking. Ship. 1/4 lb.

Order Item B-8E.....Sale \$2.95

PRE-RECORDED TAPE of above organ disc, 7 1/2 ips dual track.
Order Item B-9E.....Sale \$4.98

**1st TIME EVER AT THIS PRICE!
ALL 1956 MODELS MUST BE SOLD**



\$39.95 Value **\$21.95**

1st Available Below \$70

Matching Mate to Realistic FM in size, appearance, controls, electrical specifications. Features: tuned RF stage, superb circuit, built-in AC supply, 5 uv sensitivity, 8 kc bandwidth, response 20-5000 cps \pm 3 db, 530-1650 kc AM range.
Order Item B-10E Ship. 6 1/4 lbs.Closeout at \$21.95

Radio Shack's "FM" Buy of a Lifetime!

**REALISTIC "FM" \$39.95
HI-FI TUNER**

Features Armstrong FM with Foster-Seeley discriminator, 5 uv sensitivity for 30 db quieting, double-tuner limiter, automatic frequency control (AFC), tuner RF stage, built-in AC power supply, 20-20,000 cps response \pm 0.5 db, pilot light, slide rule dial, function switch. Solid 1-piece gold-tone metal front panel. Output 1V for 100% mod. For 117V 60 cycle AC. SUPER-SMALL SIZE: 4 1/4" H x 9 1/2" W x 6 1/4" D!
Order Item B-11E Ship. 6 1/4 lbs.Exclusive at \$39.95

When you think of AMPS, think of the Realistic

**\$29.95 10W
AMPLIFIER**



Realistic "AF" 10 watt hi-fi amplifier, matches Realistic tuners in appearance. Features: 10 watts (18 peak), \pm 1 db 20-20,000 cps \pm 1 watt level, built-in RIAA-equalized preamp, treble control 18 db attenuation @ 18 kc, bass control 15 db boost @ 50 cps, hum 80 db below 10 watts; output 4-8-16 ohms; jack for direct feed to tape recorder; inputs for tuner or crystal pickup, magnetic pickup or high-imp. mike.
Order Item B-12E Ship. 10 lbs.Exclusive at \$29.95

**NEW "REALISTIC"
SUSPENSION CONE
HI-FI SPEAKER**



**\$19.95 COMPLETE
IN FURNITURE-FINISHED
WOOD ENCLOSURE!**

- VERIFIED 50-12,000 CPS!
- ULTRA-COMPLIANT CONE!
- CASE FINISHED ALL 4 SIDES!
- EXCLUSIVE AT RADIO SHACK!
- LIST PRICE IS \$41.50.

Here's compactness — 14 1/2" x 11 x 10 1/2" — for small-space hi-fi systems, for paired stereophonic systems, for school or P.A. use! Here's quality — verified by lab checks and thousands of sales — plus cabinetry that's right out of the audio handbooks: tuned, vented, duct-type Helmholtz resonator. Includes leg rails for use if desired. Solid wood case finished to harmonize either with walnut or mahogany; lumite-type grille cloth front. Sealed wood back with terminal strip connection. Heavy FM-magnet speaker has cone attached to super-soft leather suspension rim for enhanced low frequency reproduction. An exclusive Radio Shack import to save you money.
Order Item B-13E Ship. wt. 12 lbs.Realistic System Complete \$19.95

RADIO SHACK CORPORATION

167 Washington St., Boston, Mass. • 230 Crown St., New Haven, Conn.

**SEE ORDER BLANK
ON LAST PAGE**

4 Pages of
Mail-Order
Bargains

RADIO

SALE! \$40 FAST 35mm f/3.5 CAMERA



Ultra-Compact-and-Light

Reg. \$40
\$18⁹⁵

- ★ Coated f/3.5 Lens!
- ★ Semi-wide Angle, 40mm Focal Length!
- ★ Shutter: Bulb, 1/25, 1/50, 1/100, 1/200!
- ★ Flash Synchronized!
- ★ PC Flash Tip!
- ★ Save At Least 1/2!

Brand new, multi-feature 35mm MICRONTA-guaranteed camera is one of Radio Shack's favorites for color or black-and-white! Solidly built, all metal camera has all the requirements you'd expect in a \$40.00 camera. Takes as many as 36 pictures per roll! LENS: f/3.5-f16, sharp from 3 feet to infinity. Has double-sprocket take-up accessory clip, removable back. A mere handful (4 1/4 x 2 3/4 x 2 3/4") — this imported satin-chrome-and-black beauty is NEWLY restyled for 1957! We believe there's no finer to give or receive at Radio Shack's dollar-stretching price. Ship. wt. 1 1/2 lbs. **\$18.95**
Order Item C-2E **\$2.95**
Order Item C-3E

\$70 35mm CAMERA



Sale

\$37⁵⁰

COUPLED RANGEFINDER AUTOMATIC FILM ADVANCE

- SELF TIMER • FAST 3.5
 - SYNCHRO-FLASH 3 ELEMENT LENS
- Has every wanted feature of \$70 cameras including: coupled rangefinder; 9 SPEEDS: 1, 1/2, 1/5, 1/10, 1/25, 1/50, 1/100, 1/300, bulb; 3-element coated lens; built-in self-timer; double-exposure prevention device INCLUDES 2-PART LEATHER CASE! Ship. wt. 2 lbs.
Order Item C-4E **\$37.50**

Your
Choice **\$19⁹⁵**

MICRONTA 6.5mm F/1.9 CINE WIDE-ANGLE LENS

REG. \$41.50

Gives your 8mm movie camera an extra eye for "area", for shooting in confined spaces, or for extreme depth of field! Pictures are sharp to the very edge without distortion! Fully color-corrected. Standard fixed-focus mount. Coated.
Order Item C-7E **\$19.95**

FAST F/1.4 MICRONTA TELEPHOTO 1 1/8" LENS

REG. \$69.50

SUPER-FAST f/1.4 telephoto lens for all Revere, Bolex, DeJur, Keystone, Kodak and other 8mm movie cameras. Magnificently constructed. Five elements, coated, f1.4 lens yielding 3X magnification... click-stop iris f1.4-f16... focusing mount 3 1/2 ft. to infinity Ship. wt. 1 lb.
Order Item C-6E **\$19.95**

PHOTO ELECTRIC EXPOSURE METER

Most Sensational Meter
In Our 34-Year History!



Reg. \$16.95
\$6⁹⁹

- Outstanding Features:
- "Flick" for Incident, Reflected Readings!
 - New LVS Synchro Compur Readings!
 - ONE HAND Operation!
 - Light and Compact!
 - Apertures f1 to f45
 - 8 sec. to 1/1000
 - YEAR Guarantee!

Preferred by professionals (and praised by amateurs). Meter has 7 movie speeds, push-button control allowing automatic changing of scale for incident reading. Full ASA and shutter ranges for all film emulsions; for movie or still pictures, indoors, or out. Highly accurate even in dim light. Has both standard and new Compur shutter speeds.
Order Item C-5E **\$6.99**

MIRACLE SCREEN SALE

Reg. \$21.95

\$11⁹⁵



'RADIANT' 40x40 SCREEN WITH VYNAFLECT FABRIC

World-famous RADIANT color-slide and movie screen with permanently white million-glass-beaded Vynaflect is washable and flame- and mildew-proof! The 40x40" size is just right for slides and for movies. Latest 1957-type chromed tripod assembly and end bells; full length suspension bar that seals out dust from sturdy metal Radiant screen case; latest-type pressure-adjust levers — no screws to tighten! Fabric covered by 10-YEAR guarantee! Ship. wt. 12 1/2 lbs.
Order Item C-1E **\$11.95**

PRISM BINOCULARS BELOW OUR COST!



\$10⁹⁵ Plus 10% Tax
Never before so low — includes year guarantee! Hard-coated optics; fully color-corrected. Includes pigskin case. Individual focus. Ship. 2 lbs.
Order Item C-9E Sale **\$10.99**

100X,
200X,
300X

MICROSCOPE

ORIG. \$3.99
\$14.95

UNHEARD-OF for \$3.99! PLUS features are 1-year guarantee, all metal construction, ground and polished achromatic lenses, triple objectives. Ship. 3 1/4 lbs.
Order Item C-10E Sale **\$3.99**

STYLUS MICROSCOPE



50-TIME MAGNIFICATION
List \$3.00 **\$1.95** Ship. 4 oz.
Order C-8E

PORTABLE 35mm VIEWER-PROJECTOR

- ★ It's a TABLE VIEWER
- ★ It's a WALL PROJECTOR
- ★ It's PORTABLE
- ★ For COLOR SLIDES
- ★ F3.5 LENS

\$75
Value

\$27⁵⁰



SEMI-AUTOMATIC CHANGER

Projects a direct view image onto its self-contained 5 1/2" sq. ground glass screen. Projects COLOR slides onto any light colored wall. Sharp focus 10 ft. sq. picture. The size of your wall is the only limit to the size of MICRONTA-VUE's picture! Semi-automatic 36 slide changer. Efficient convection cooling. Finest optical parts. F/3.5 lens. All-metal portable carry-case: 7x10x3 1/2" D. Weighs only 4 lbs. With 100 Watt bulb, line cord, instructions. For 115V AC-DC operation. Ship. wt. 5 lbs.
Order Item C-12E **\$27.50**

"PRISMATIC"

Binocular Microscope
1st Available Below \$90

3-D TWIN 30X
OBJECTIVE
LENSES

\$19⁹⁵

EXTRA WIDE
FIELD FOR
COMPARATIVE
STUDIES!



Exclusive industrial and biology lab 3-D microscope has full color-corrected lenses and stereo-binocular vision. Also features adjustable eyepiece tubes, dual optical prisms, ground glass view stage. Complete with hardwood case, Micronta 6-mos. guarantee. Buy-of-a-lifetime. 4 lbs.
Order Item C-11E Complete **\$19.95**

Radio Shack's Great New 1957 Catalog

Has the Latest

Comprehensive Product
Listings Including
Industrial Electronics,
Transistor Components.

Send For Your
FREE Copy Today

RADIO SHACK CORPORATION

167 Washington St., Boston, Mass. • 230 Crown St., New Haven, Conn.

SEE ORDER BLANK
ON LAST PAGE →

RADIO & TELEVISION NEWS

SHACK

4 Pages of
Mail-Order
Bargains

SALE! RCA 45 rpm SLIDE-O-MATIC

FAMOUS MAKE 7" POWER SAW

1 1/4
hp



Reg.
\$44.95
List

\$29⁹⁵

Nationally-famous electric saw features FULL 8 AMPS, 5000 rpm saw arbor speed, helical drive gears, retractable saw guard, power cord at 45° angle. Operating controls are at rear of saw; air-stream blows dust away from saw line. A \$60-\$70 value in everyone's book. Ship. wt. 12 lbs. Order Item D-1E.....Sale \$29.95

5-PC. JEWELERS PLIER SET SALE!

Reg. \$12.95

\$5⁹⁹

- Drop Forged
- Chrome Plated



Magnificent set includes: End Nipper, Diagonal Cutter, Round Nose, Flat Nose, Half-round Flat Nose. Has our Skillman brand. Ship. 1 1/2 lbs. Order Item D-2E.....Sale \$5.99

PRECISION MICRONTA LOG-LOG SLIDE RULE!

\$25.00
Value

\$11⁹⁵




Standard-size! Features 18 different scales. Graduations engraved in ivory-finished veneer body. Includes leather case. Ship. 1 lb. Order Item D-3E.....Sale \$11.95

POWERFUL GE 6 RPM DISPLAY MOTOR KIT

Worth \$11.95

\$3⁹⁵

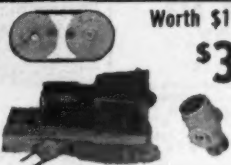

Designed to continuously operate a 30 lb. load on GE's famous revolving shelf refrigerator. Can be adapted to serve a hundred useful functions in display work, hobby and industrial applications. Consists of very heavy duty AC synchronous motor with reduction gear assembly to 6 rpm, 2-3/4" pulleys with spring belt-drive, line cord and light socket AC adaptor. Brand new packed in original GE Box. Ship. wt. 6 lbs. Order Item D-4E.....\$3.49

WILSON "TINY ATOM" REVERSIBLE DC MOTOR

Has Clear
Plastic Case

Reg. \$149
\$2.50



Operates from 1 or 2 flashlight batteries. Ideal for model builders, hobbyists. Precision construction. Alnico V field. Brass sleeve bearings. Speeds from 3500 to 9200 rpm. Instantly reversible. Ship 4 oz. Order Item D-5E.....Sale \$1.49


POWER DRIVE ACCESSORY KIT

Contains all the necessary parts for belt, direct connected, spur gear, and worm drives at a wide range of speeds. Hundreds of hard-to-get power drive parts. Wt. 2 lbs. Order Item D-6E.....\$3.00

14-PART DRAFTING SET!

\$14.00
Value

\$7⁷⁵

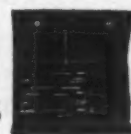


Deluxe set of nickel-plated brass drafting instruments in velvet-lined case. Self-centering style construction. Ship. 1 1/2 lbs. Order Item D-7E.....Set \$7.75

REMOTE CONTROL MODEL BOAT!

Remote Control Functions:

- Forward
- Reverse
- Left Rudder
- Right Rudder
- Running Lights

\$7⁹⁹

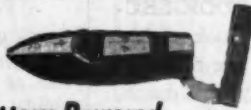

Battery-Powered

WORTH \$35.00 — 2-seater motor boat has all functions controlled by hand-held R/C unit. Built to scale of lightweight woods. Hand made and lacquered. NOT A KIT, but a 15 1/2" long, 5" wide fully wired boat. Uses 3 standard flashlight batteries. Waterproof control cable. 4 lbs. Order Item D-8E.....Complete \$7.99

RADIO SHACK

167 Washington St., Boston, Mass.



RCA "Victrola" Super-Sale

Reg. \$14.95


\$6⁹⁹

- Slide in 45rpm Disk
- Starts Automatically
- Stops Automatically
- For all the Family
- Safe for Children

Below DEALER cost at Radio Shack! Compact 4 1/4" x 7 1/2" x 10 1/2", fully hi-impact plastic encased, has Miss Francis decal. Automatic single-play operation: slip in any 45 rpm disk, flip up Play Bar, concealed arm descends and disk starts automatically; stops automatically after playing! Plug into any amplifier, any radio or TV with phono input. Complete with AC plug, phono cord, RCA guarantee, in orig. Victor carton. Ideal for kids — they can't get at arm or motor, can't damage disk, can't get hurt — everything's enclosed. Sold everywhere for \$14.95, it's over 50% off at Radio Shack. Ship. wt. 7 lbs. Order Item D-9E.....\$6.99

POWER SUPPLY KIT 400 VDC @ 150 MA.

\$9⁹⁵ Worth \$25.00

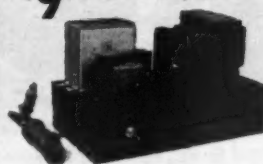


A complete sell-out the last time we advertised this great power supply kit! Designed for continuous operation at 400 VDC-150 MA with less than 1/2% of 1% ripple! Excellent regulation. Makes an ideal power supply for Williamson-type amplifiers and other equipment. Kit includes metal encased power transformer, 400-0-400 @ 200 ma., 5 V. @ 4 A., 6.3 V @ 5.4 A. 2-8 mfd. @ 600 VDC oil filled capacitors, 7 henry @ 150 ma open cased choke, 5T4 rectifier, 100 W. bleeder, line cord, switch, socket and 7x12x3" chassis. Complete with schematic and chassis layout. Ship. wt. 18 lbs. Order Item D-10E.....\$9.95

COLUMBIA SALE!

22-RECORD 45-RPM
PACKAGE—WORTH \$20
With 2 45-EP Discs

\$3⁹⁵

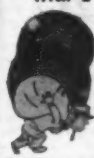

Famous Artists:
Frankie Laine
Rosemary Clooney
Buck Clayton
And Others!

20 Different hit-tune, jazz and other hi-fi 45 rpm discs featuring top Columbia artists! Sale has BONUS of 2 (Reg. \$1.49 ea.) Columbia 45-EP discs! Ship. 3 lbs. Order Item D-11E.....Sale \$3.95

BACH'S MASS IN B MINOR

Reg. \$11.90

\$4⁹⁹

COMPLETE on 2 fabulous hi-fi VANGUARD 12" LP records in an album featuring the complete text in English and Latin. Ship. 2 1/4 lbs. Order Item D-12E

RADIO SHACK CORP. 167 Washington St. Boston 8, Mass.

Please Rush the following items:

Quan.	Item	Net	Quan.	Item	Net	Quan.	Item	Net
	A-1E			B-4E			C-8E	
	A-2E			B-5E			C-9E	
	A-3E			B-6E			C-10E	
	A-4E			B-7E			C-11E	
	A-5E			B-8E			C-12E	
	A-6E			B-9E			D-1E	
	A-7E			B-10E			D-2E	
	A-8E			B-11E			D-3E	
	A-9E			B-12E			D-4E	
	A-10E			B-13E			D-5E	
	A-11E			C-1E			D-6E	
	A-12E			C-2E			D-7E	
	A-13E			C-3E			D-8E	
	A-14E			C-4E			D-9E	
	B-1E			C-5E			D-10E	
	B-2E			C-6E			D-11E	
	B-3E			C-7E			D-12E	

C.O.D. CUSTOMERS: Radio Shack accepts C.O.D. orders of \$5.00 and over ONLY if accompanied by a deposit of at least 25%. It should be noted that such orders cost you more because of postoffice charges on the services involved. Add estimated postage.

NAME

ADDRESS

TOWN

ZONE


STATE

FREE

RADIO SHACK
1957 CATALOG

BUY THE WORLD'S MOST COMPLETE HI-FI GUIDE!

164
PAGES!

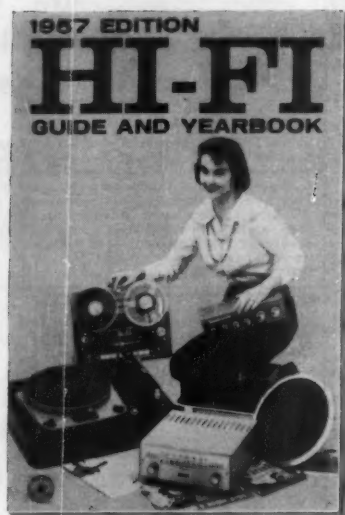

Compiled by the Editors of Popular Electronics

NINE BIG CHAPTERS ON!

- Why and How Hi-Fi
- Tuners
- Tapes
- Record Players and Changers
- Tone Arms, Cartridges and Needles
- Preamplifiers and Amplifiers
- Loudspeakers
- Speaker Enclosures
- Saving Money in Hi-Fi

Also included in this new H-Fi volume is a giant YEARBOOK SECTION covering all the latest trends in high fidelity. This "book within a book" lists the nation's best-selling records and artists, pre-recorded tapes, all FM stations, and contains a new Hi-Fi glossary and much, much more!



BE SURE TO BUY YOUR COPY!

ON SALE FEB. 7 AT ALL NEWSSTANDS AND RADIO PARTS DEALERS!

Bench Puzzlers

By JAMES A. McROBERTS

An assortment of problem repairs, from one technician's experience, may rescue others from headaches.


IN THE spirit of mutual helpfulness, the author offers the following jottings from his service notebook in the hopes that it will save some fellow technician valuable time in tracking down these unusual service faults.

Horizontal Output Blocking

A symptom of a sudden cut-off of the raster, with a period of no raster, followed by an increase to normal raster brilliance, may be due to the blocking of the horizontal output tube.

The trouble originates in the grid of the output tube. This resistor may increase in value to an open circuit, or a nearly open circuit. The schematic diagram of this section of the receiver is shown below.

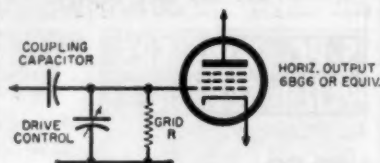When the value of this grid resistor increases, the grid circuit of the hori-



zontal amplifier may block, as occurs, for example, in multivibrator and blocking-oscillator action. When the tube blocks, it obviously cuts off the high voltage (flyback type assumed) and there is no raster. With a gradual turn-on of the tube, the raster will increase in brilliance and also in sweep width.

Wow with Good Capstan

When the Pentron 9T-3C tape recorder exhibited wow and an inspection of the capstan assembly showed no flats or other troubles, the most likely source of the difficulty was the spring which holds the idler wheel in contact with the motor pulley (manufacturer's part #39) or excessive wear of the idler wheel, or both.

Check the condition of the spring even if the trouble is obviously a badly worn idler wheel.

Poor Height-Compression

The Raytheon chassis 21T8 displayed considerable compression at the bottom of the picture together with inability to secure quite enough raster height. A new vertical output tube (6S4, V_{90}) improved matters slightly for a few minutes but the trouble slowly returned.

When this problem is encountered, check and replace C_{507} , the .01 μ f. capacitor connected in series with resistor R_{118} (180,000 ohms, 1 watt). C_{507} and R_{118} are connected from the plate

TELEPHONE & CONTROL EQUIPMENT



• **CONTROL UNIT RM-53**—(Pictured at left.) Used to operate radio equipment and provide remote control and intercom. of such equipment by use of the RM-52 Unit listed below. Up to 1/2 mile, uses 2 flashlight batt. Internal transformer has High-Low impedance Sw. and Sidetone. Also Mic. & Phone Jack & PL-55 & PL-58 Plugs.
USED: \$3.95 NEW: \$5.95

REMOTE CONTROL RM-52—(Pictured at right.) Can be used with RM-53 or used as a separate telephone system. Up to 1/2 mile. Uses 4 flashlight batt. Also can be used as a direct remote control for radio equipment. Provides bias for Mic. & Sidetone to headset. High or Low Imp. Also Mic. & Phone Jacks.
USED: \$2.95 NEW: \$4.95



TS-13 HANDSET for RM-53 or RM-52....Used: \$5.95

EE-3 FIELD TELEPHONE—Ideal for private telephone system for two or more phones, up to 17 miles. Hand ringer, generator with handset, carrying case. Uses 2 flashlight batt. Price—Used, Checked....\$14.95
WIRE—Weatherproof Twisted Pair: 500 ft. \$4.75-135 ft. \$1.00-2500 ft. \$19.95. Per Foot at 1 1/2¢.
COMBAT WIRE—Rubber covered W-130...\$1 per Ft.

PANORAMIC ADAPTER AND OSCILLOSCOPE—ID-60/APA-10

Two Units in One. Panadapter and Scope with three inputs for feeding IF Freq. of 455 KC, 5.2 or 30 MC from Receivers, viewing on 3" Scope. Also can be used as regular scope. Has vertical and horizontal push-pull amplifier inputs. Complete with 21 tubes, instruction book, and schematic. Operates from 115 Volt 400 cycle. (Not demilitarized)
NEW: \$49.50


PRACTICE CODE TAPE:

SETS: INKED PAPER TAPES—For Code practice and training—for Radio Operators, Hams, Amateurs, Beginners, and Telegraphers. 15 lessons to a Set, on 16mm 400 ft. reels that can be reproduced on TG-34A and TG-10 Keyers. Price: SET of 15 Reels in wood case.....**\$18.95**
REELS: Lesson Reels available individually. Order by number desired, 1 thru 15.....Each: \$2.00

BC-1158 TRANS. & MODULATOR

Frequency coverage 53.3 to 95 MC. 50 Watt. RF Doubler, Amplifier and Modulator Sections, using 4/819 and 10/12SN7 Tubes. Can be converted to 2-6-10- or 20 Meters. Complete with Tubes, Meter, Blower, etc.....**NEW: \$39.95 Used: \$29.95**

MICROPHONES & HEADSETS

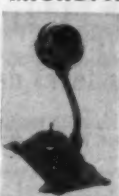

F-1 BUTTON CARBON MIC.—(Pictured at left) High Gain—Can be used on desk, car, hand, or strapped to chest. Complete with on-off Mom.
Switch.....NEW: \$1.95
RS-38 CARBON MIC. with PL-58 Plug.....U: \$2.50
T-17 Carbon Mic. Used, checked.....\$3.95; N: \$8.95
Sound Powered Mic. no cord, used, checked.....U: \$1.50
HS-30 HEADSET—Hearing aid type.....U: \$1.50
HS-18 HEADSET—4000 ohm.....U: \$1.95

Sound Powered—One headphone only.....U: \$1.00
Sound Powered Handset TS-10—Used, checked \$5.95
TS-9 Handset—Push to talk Sw. No plugs.....U: \$5.95
TS-13 Handset—Push to talk Sw. w/PL-58 & PL-55.....U: \$5.95

DYNAMOTORS & GENERATORS:

INPUT VOLTS:	OUTPUT VOLTS:	MA.	STOCK NO.	PRICES:
				USED: NEW:
12 VDC	220	80	DM-34	\$2.95 \$4.95
12	225	100	D-402	5.95 8.95
12	625	225	DM-35	9.95 14.95
12	230	80	PE-133	4.95 6.95
12	480	40	DA-12	14.95 24.95
12	230	100	DA-14	8.95 14.95
14	220	70	DM-24	4.95 7.95
14	1630	250	DM-42	4.95 9.95
14	425	163	WE-377	5.95 9.95
14 VDC	330	150	DM-87	3.95 5.95
14	250	50	DM-25	6.95 8.95
14	1000	350	BD-77	14.95 24.95
14	230	90	DM-21	6.95 9.95
24	250	60	DM-32	2.95 5.95
24	250	60	PE-86	8.95 14.95
24	1000	350	PE-73	8.95 14.95

12 to 24 VDC PM Dynamotor—Supplies 24 VDC 2 A. from 12 VDC, also 500 V 50 MA. @ 6 VDC will supply 12 VDC & 250 V 50 MA.
#0515.....**NEW: \$4.95**

Address Dept. RN • \$5.00 Order Minimum • 25% Deposit on C.O.D.'s • Prices are F.O.B. Lima, Ohio

RADAR TRANS.

Transmitter Frequency 143 to 194 MC. using one 3A5 Tube. In plastic case 4 1/2" x 1 1/2" mounted top of 58" Telescoping Antenna with 14" Dipole. Battery Case for holding 2/BA-30 1 1/2 V. & 2/BA-36 100% Volt "B". Has on & off Sw. Tel. Ant. mounts side of batt. case.
Price: \$4.95

ORDER TODAY!

FM RECEIVERS AND TRANSMITTERS


27 to 38.9 MC. FM RECEIVER
Four Pre-selected Channels & Squelch Circuit. Complete with 16 Tubes and Speaker. Set size: 6 1/2" W x 1 1/2" H x 1 1/2" D. Power required 12 or 24 VDC & 275 VDC 150 MA. BC-923 RECEIVER—Used, Checked.....\$34.95
12 V. DYNAMOTOR for BC-923:.....\$22.50
A.C. POWER SUPPLY for BC-923:.....\$35.95
KIT of Parts & Wiring Diagram for BC-923:.....\$17.50

27 to 38.9 MC. FM TRANSMITTER
30 Watt channel to BC-923 Receiver. Four Pre-selected channels, Voltage regulated by 0 control, using 2/815, 2/6SL7, 1 each 6SL7, 6V6, 6J5, 6AG7, & VR-150 Tubes. Size: 11" x 11" x 18". Voltage required: 12 or 24 VDC & 400 VDC @ 400 MA. BC-924 TRANSMITTER—New: \$24.95; Used: \$14.95
Power & Control Plug for BC-923 or BC-924:.....\$1.00
Mounting Base FT-237 1/BC-923 & BC-924:.....\$9.95

BC-603 RECEIVER—20-28 MC variable tuning, 10 Pre-set push button channels, squelch circuit, 4" speaker; 10 Tubes: 2/12SG7, 2/6SL7, 1/6V6, 1/6J5, 3/6AG7, & 1/6H6. Prices:.....NEW: \$39.95; USED: \$29.95
PLUS for rear of Receiver.....\$1.00
DYNAMOTOR: 12 V input; Output 220 V 50 MA—#DM-34.....NEW: \$4.95; REISSUE: \$2.95
BC-604 TRANSMITTER—20-28 MC, 30 Watt, companion to BC-603 Receiver. Crystal control, 10 Pre-set channels, interphone communication: 8 Tubes 7/1619 & 1/1624.....USED: \$18.95
PLUS for rear of Transmitter.....\$1.00
DYNAMOTOR: 12 V input; Output 635 VDC 225 MA—#DM-35.....USED: \$9.95
FT-237 BASE for mounting Receiver & Transmitter (No Plugs required).....USED: \$9.95

NATIONAL DIAL

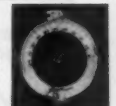TYPE "N" Precision 4" divided scale with decimal vernier drive 5:1 ratio. Planetary drive 8 1/2" shaft, 100-0 scale.
Each: **\$1.95**



COMMAND EQUIPMENT

	USED:	NEW:
550 to 1500 REC., Navy.....	\$14.95	\$19.95
550 to 1500 REC., Navy w/ant. loop. Sw.....	\$14.95	\$19.95
1.5 to 3 MC. REC., Navy.....	9.95	
3 to 6 MC. REC.—BC-454.....	9.95	
6 to 9 MC. REC.—BC-455.....	7.95	
100 to 150 MC. REC.—R-28.....	10.95	13.95
2.1 to 3 MC. TRANS., Navy.....	7.95	9.95
3 to 4 MC. TRANS., Navy.....	5.95	
4 to 5.5 MC. TRANS.—BC-457.....	4.95	
5.5 to 7 MC. TRANS.—BC-458.....	4.95	
7 to 9 MC. TRANS., Navy.....	7.95	
100 to 150 MC. TRANS.—T-23.....	14.95	

TRANSFORMERS AND CHOKES

115 V. 60 CYCLE PRI. TRANS.:	
600 VCT/100 MA.—5 V/3 A; 5 V/5 A.....	\$4.95
240 VCT/35 MA.—24 V/3A; 5.3 V/5 A; 6.3 V/3 A.....	1.75
1500 VCT/260 MA.—6.5 V/3 A.—6.5 V/5 A.—5 V/4.5 A.....	9.95
700 VCT/150 MA.—5 V/3 A; 6.3 V/4.5 A. CSD.....	3.95
2500 V/015 A; 2.5 V/175 A; 6.3 V/6 A.....	5.95
1890 V/12.6 MA.—Tapped 2.5 V 2 A.....	5.95
1100 V/80 MA.—7.5 VCT/3.25 A.....	5.95
720 VCT/50 MA.—5.3 V/2.5 A—5 V/2 A.....	2.50
662 VCT/110 MA.—6.3 V/2 A—5 V/2 A.....	3.95
880 VCT/300 MA.—12.6 V/10 A—5V/3 A.....	6.95
16 Volt 35 Amp. 115/220.....	\$14.95; 24V—1 Amp 1.50
9 Volt CT—35 Amp.—Tapped 4.5 V.....	7.95
12 Volt—Two separate windings—4 amp each.....	5.95
5 V/2 A; 5 V/2 A; 5 V/2 A; & 5 V/6 A.....	2.95
6.3 V/2.1 A. and 5 V/3 A.....	1.75
600-0-600 VAC—500 MA. 12.5 V A & 12.5 V.....	5.95
@ 2 A.; 5 V. @ 3 A.—2H-100—Price.....	8.95
250-0-250 VAC—50 MA. 24 V. 1 A.; and 6.3 V. 1 A.—2H-100—Price.....	4.95

Choke—12.5 Hy/100 MA.....\$1.95
Choke—8 Hy/150 MA—200 Ohm—Open Frame.....1.25
Choke—5 Hy/150 MA—85 Ohm.....1.50
Choke—10 Hy/250 MA—250 x 2 x 3" Potted.....4.95
Choke—5 Hy/400 MA—4 1/2" x 4" x 5 1/2".....4.95
"A" Choke—I Hy @ 1 A. 7 ohm. Size: 2 1/2" x 2 1/2" x 2 1/2".....Price: 1.95

POWER SUPPLY

110 V. For Army/Navy COMM. RECEIVERS
Eliminates set conversion. For use w/BC-453-454-455-946 or any sets requiring 24 V. @ 1 A. & 250 V. @ 50 MA. Ready to use: has 4" speaker, volume control, CW and on-off switches. Complete with cord and plug 1/roo.
Price.....NEW: \$18.95

NOW—OPERATE BEACON RECEIVER FROM 12 VOLT

BC-1206CM BEACON RECEIVER—200-400 KC. 5 Tubes, 135 KC IF, operates from 24 VDC.....**\$9.95**
New.....\$5.95
Used.....\$5.95
For 12 Volt operation, use this PM DYNAMOTOR—12 VDC input, output 24 VDC. Size: 2 1/2" x 4" x 4 1/2".....**\$4.95**
7" Dyn.....Only



AC POWER SUPPLY—To operate BC-1206 from 110 Volt 60 cycle. Complete with Speaker, etc., in same type cabinet as illustrated at top of this column—Price.....**\$18.95**

PE-110 AC POWER SUPPLY

115 Volt 60 cycle Power Supply for BC-669 Rec.-Trans. Complete with Tubes, 25 ft. AC Power Cord, Spare Tubes, Vibrator, Capacitor, Fuses. Housed in wood chest. Brand New.....**\$59.50**

TA-12B BENDIX TRANSMITTER

Frequency 300-600 KC and 3000 to 7000 CW & MCW 100 Watt. Four separate oscillators easily converted to cover 20-40-80 Meters by using crystal for 10 Meter Band. Selector channel switch changes ECO, IPA, and Output Tanks at one time. All controls mounted on front panel. Uses 3/807, 4/12SK7; also has output Meter. Size: 15 1/2" x 10 1/4" x 6 1/2". Complete with Tubes, Plug and Cable.....Used: **\$32.95**
For Conversion—See Surplus Manual 22—Price: \$2.50
MP-28-BA MODULATOR & POWER SUPPLY for TA-12. Modulated Max. Signal Carrier output 75 Watts Class B. Uses 2/807, 1/8F8, 1/6N7. Dynamotor input 24 VDC output 540 VDC 450 MA.
Price.....New: \$14.95—Used: \$10.95

RA-10 BENDIX RECEIVER

150-1100 KC and 2-10 MC. Excellent for range and marine use. 7 Tubes: 3/6SK7, 1/8K7, 1/6CS, 1/8KG6, 1/8KS. Complete with Dynamotor, RA-8 Control Box, Plug, Remote Tuning shaft. Size: 10" x 8 1/2" x 17".
RA-10 DA—24 Volt 150-1100 KC & 2-10 MC. Used.....\$34.95
RA-10 CA—12 Volt 150-1100 KC & 2-10 MC. U: \$39.95
RA-10 FA—24 Volt 150-400 KC & 2-10 MC. U: 29.95
Surplus Conversion Manual—#1 or #2.....Ea.: 2.50
For List of contents in each Manual, send 3¢ stamp.

METERS:

WESTON AC AMMETER:
(Pictured) in portable leather case, with Test Leads, 2 1/2", 0-15.....**\$5.95**
AC and 0-3 AC Scale.....
DC AMMETER HOYT: In portable metal case, with Test Leads, 4 1/2", Fan Mirrored Scale 0-15 ADC.....\$4.95
DE METER—10 to Plus 5, Westinghouse 3".....\$4.95
NC-35 Imp. 600 ohms @ 1000 cycle..... 4.95
0-1 MA Weston 500; 2 1/2" Rd..... 3.95
0-3 RF AMMETER 15-128; 2 1/2" Rd.....NEW: 2.95
0-3 Amp RF w/Thermocouple 15-80; 2 1/2" Rd..... 4.95
0-15 AC-DC—2 1/2" Rd.; 15-122..... 4.95
0-500 MA DC—2 1/2" Rd.; 15-22..... 4.95
0-150 V. 60 cycle; Simpson; 3 1/2" Rd..... 3.95
0-250 MA DC—Dejour, 3" Sq..... 2.95
OUTPUT—5 Ranges, 4000 ohm Imp.—Used..... 4.95

FAMOUS ARMY

SCR-625 MINE DETECTOR

For Prospectors, Miners, Oil Companies, Plumbers, etc. Portable unit for locating all types of buried metal objects up to 24" or more depending on size and ground condition. Detection by means of a tone. Packed in a chest. Operating weight approx. 15 lbs. Shipping wt. approx. 40 lbs. Complete with **\$39.95** batteries

100-156 MC TRANSMITTER & RECEIVER—SCR-522 TRANS. & RECEIVER

100-156 MC, 4 Channel, Crystal Control, AM Voice Operation, 18 Tubes—Trans.: 2/632, 3/12A6, 1/8557, 1/646—Rec.: 1/8082, 1/8003, 3/12A6, 2/12AN7, 1/12C6, 1/12H6, & 3/12SG7. Complete with Tubes, Schematic, and Conversion Info. for ama-
teur use—Good Cond. **\$34.95**
REC.—Chassis Only, w/Tubes \$19.95 without.....\$9.95
TRANS.—Chas. Only, w/Tubes \$22.50 without.....\$9.95
SCHEMATIC and Conversion Info. Only.....\$2.50

FAIR RADIO SALES

132 SOUTH MAIN ST.
LIMA, OHIO

Europe's
largest selling
electronic tubes
... and at standard prices!

TELEFUNKEN

electronic pioneer
since 1903



**NOT A REPLACEMENT
BUT AN IMPROVEMENT!**

**NO
RETURNS
NO
MICROPHONICS
NO
DISTORTION
NO
COMPROMISE
WITH
QUALITY**

Write for your Telefunken Tube Manual and
for the name of your nearest jobber.

Exclusively imported by

AMERICAN ELITE, INC.

Dept. X, 7 Park Avenue, New York 16, N. Y.

Exclusive importers also of Hi-Fi Home Systems,
Microphones and Hi-Fi FM Car Radios.

of the 6S4 to ground, the resistor being next to the tube.

Black Lines on Raster

The customer complained that his *Motorola* TS 292A chassis displayed black vertical lines on the left side of the raster.

Adding a 120-ohm, 1-watt resistor in the screen grid lead of the horizontal output tube V_{15} (6BQ6GT) suppressed the parasitic oscillation which caused this pseudo-Barkhausen effect.

Picture and Raster Stretch

The *Admiral* chassis 20A2 displayed vertical nonlinearity at the top of the raster by stretching or expanding the first twenty or so visible lines. Some variation in the amount of stretch could be obtained by an adjustment of the vertical linearity control, R_{111} , although too much stretching remained at the limits of motion of this control.

The difficulty was traced to C_{104} , cathode-to-chassis electrolytic bypass capacitor for the vertical output tube, V_{105} . This capacitor had lost some capacity, but also had an abnormal power factor when tested with a capacitor checker. Replacement was made with a tubular unit after clipping the lead to the original one, which was part of a multiple unit. This case was a puzzling one inasmuch as the clue furnished by the linearity control indicated something wrong in the circuit associated with the vertical output tube, but shunting the cathode-to-chassis bypass did not cure the trouble and no evidence of excessive leakage showed on an ohmmeter check.

Washed Out Picture

In those cases where the grid of the cathode-ray tube is fed the video signal through a coupling capacitor, leakage in this capacitor will result in increased brilliance of the picture and a washing out of the video information on the picture tube. The case is especially true if the "B+" to the video amplifier is fed through a resistor of relatively high value so that the video

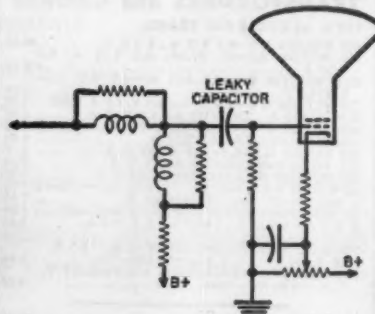


plate voltage drops only a little from normal, and the grid voltage of the CRT is only a trifle more positive than normal. The schematic diagram above shows such a typical case.

As a check prior to direct substitution of the suspected capacitor, have

TERADO Trav-Electric CONVERTERS

MOBILE POWER
Give You
110 A.C. HOUSE
CURRENT
ANYWHERE
You Drive or Cruise

LIST
For 6 and 12 Volt Car Batteries—Capacities: 10 to 125 Watts
\$11.95 UP
NO INSTALLATION
Just plug into cigar lighter on dash of car, truck, or boat—and away we go
• OPERATE PORTABLE TV
• SMALL DO-IT-YOURSELF
• TOOLS WHEREVER NEEDED
One of the great conveniences of our electronic age

101 USES
ALL ELECTRIC SHAVERS
DO-IT-YOURSELF HOBBY TOOLS
SEE YOUR ELECTRONIC PARTS DEALER OR JOBBER

TERADO COMPANY
DESIGNERS & MFGS. OF ELECTRONIC EQUIPMENT SINCE 1927
1058 RAYMOND AVE., ST. PAUL 14, MINNESOTA

GET INTO ONE OF THESE
TOP OPPORTUNITY FIELDS

ELECTRICITY
—Electronics or
TELEVISION
—Radio-Color TV

TRAIN IN THE GREAT SHOPS OF

COYNE OLDEST, BEST EQUIPPED
SCHOOL OF ITS KIND IN U.S.

Veterans and Non-Veterans—Prepare for a better job NOW that offers a real future, too! Get practical training in **TELEVISION—RADIO—ELECTRICITY—ELECTRONICS**—(Refrigeration & Electric Appliance Repair can be included). Learn on real equipment—no advanced education or previous experience needed. Lifetime employment service to graduates.

Finance Plan—enroll now, pay most of tuition later. Part time employment help to students.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. COOKE President **COYNE** FOUNDED 1899
ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. PAULINA ST., CHICAGO, DEPT. 27-2800

ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

B. W. COOKE, Pres., COYNE ELECTRICAL SCHOOL

500 S. Paulina St., Chicago 12, Ill., Dept. 27-2800

Send FREE BOOK and details on:

☐ TELEVISION-RADIO

☐ ELECTRICITY-ELECTRONICS

NAME.....

ADDRESS.....


CITY.....STATE.....

RADIO & TELEVISION NEWS

the set running and tuned to an unused channel (no signal present). Clip off one lead of the capacitor while monitoring the grid voltage of the CRT or the plate voltage of the video amplifier tube with a voltmeter. If the capacitor is good, no change will be noted in the meter reading.

Snow Due to Flux Leakage

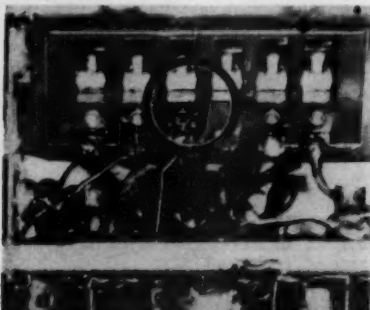The photograph below shows a leakage path between the third and fourth



contacts of a turret tuner. The darker area is soldering flux with its accumulated dirt and grime.

The leakage path resulted in a reduction of the a.g.c. voltage applied to the tuner. Thus the tuner operated at nearly full gain irrespective of the developed a.g.c. As a consequence, more snow was developed since the noise pulses easily overloaded subsequent stages. These pulses were unduly prominent even when overloading did not occur.

Record Changer Trouble

After considerable service the RCA Victor RP 176 record changer may develop an intermittent case of no sound. The symptom will become progressively worse. The trouble spot is the muting switch on the pickup arm which serves to kill the input to the amplifier during the changer cycle. Due to the constant pushing, the switch blade, in time, will jam against the other switch blade to form a permanent, or near permanent, closed circuit.

The remedy is to manipulate the blades of the switch so that they make contact only during the change or reject cycle.

Poor Horizontal Sync

When the report of poor horizontal sync was made on the Philco r.f. chassis R-191, we replaced capacitor C_{100} in the sync feed filter from the video amplifier to the sync separator tube, V_{11} , a 6CS6.

Capacitor C_{100} has a value of 220 $\mu\text{fd.}$ and is located in series with another capacitor, C_{101} (4700 $\mu\text{fd.}$) which is connected to the sync separator (V_{11}) grid, pin 1. C_{100} is shunted by a 150,000-ohm resistor, R_{100} , to form a filter for the sync.

When C_{100} opens, as in this case, the high-frequency (i.e., horizontal) sync pulses are greatly reduced in ampli-

tude. The low-frequency pulses pass with relative ease through the shunting resistor R_{100} , so that the vertical pulse group's flat tops are not appreciably affected. The capacitor, C_{100} , even though disconnected, will leave some capacity in the circuit due to stray wiring so that some horizontal sync action can be effected.

No Sound from KCS-81

Some audio buzz was noted in the RCA KCS-81 when the volume control was touched. The 33,000-ohm resistor connected to pin 6 of the 2nd sound i.f. tube, V_{106} , soon heated up sufficiently to reveal the passage of heavy current through it. Capacitor C_{100A} , part of a dual unit, was the cause of the trouble.

As several complaints have been traced to either this section or its mate in this particular capacitor, replacement of this dual capacitor is a recommended procedure when servicing this chassis, even when the specific complaint doesn't involve this particular component.

Lines and Hiss

The complaint on the Crosley chassis No. 431 concerned a series of beady vertical lines on the left-hand side of the raster with the lines to the far left the most intense. The symptoms were present with or without a picture. A slight hiss could be heard on all stations or in the absence of a station.

The cause of the trouble was a parasitic oscillation at the screen grid of the horizontal output tube, V_{106} , a 25C6. Installation of a 100-ohm, 1-watt anti-parasitic resistor between pin 4 (screen grid terminal) of the horizontal output tube and the dropping resistor, R_{171} (a 12,000-ohm, 3-watt unit) and the bypass capacitor, C_{151} (.05 $\mu\text{fd.}$) cured the complaint.

The resistor damps out the high-frequency oscillation at the second subharmonic of a frequency near the sound carrier in the i.f. passband. The oscillation is started with each horizontal line, hence its steadiness.

Blooming in Admiral 20D2

Blooming, exemplified by an abnormal expansion of the raster area with a change in setting of the brightness control, may be due to trouble in the horizontal output circuit. The resistance in the screen grid circuit increased abnormally in this particular case.

The output tube for this chassis is V_{106} , a 6BQ6GT. The screen grid dropping resistor is R_{100} with a rated value of 8200 ohms and a rated dissipation of 2 watts. The case history revealed that this resistance had changed its value to approximately 17,000 ohms. A 5-watt, 8200 ohm resistor was used as a replacement so as to allow additional dissipation with less likelihood of further trouble due to a resistance change in the circuit.

BUILD THE BEST— BUILD ALLIED'S OWN knight-kits

ALLIED stakes its 36-year reputation in the Electronics field on your complete success and fullest satisfaction with KNIGHT-KITS. Join the thousands who have discovered the ultimate in kit value in...



knight-kits

LOWEST COST because our giant buying power passes biggest savings on to you...you do the easy assembly and your finished instrument is equal in performance and appearance to equipment selling for several times the KNIGHT-KIT cost. (Easy Payment Terms available, too.)



knight-kits

EASIEST TO BUILD because KNIGHT-KIT "Step-and-Click" instruction manuals are marvels of clarity—it's just like having a good instructor at your side. Proved professional design and premium quality parts help insure your building success.



knight-kits

MONEY-BACK GUARANTEE: When properly assembled, KNIGHT-KITS fully meet published specifications, or we refund your money.

WHEN YOU BUILD A KNIGHT-KIT
YOU BUILD THE BEST



For a Complete Selection of
Famous knight-kits

SEE PAGES 117-123

Available Only From

ALLIED RADIO

100 N. Western Ave., Chicago 80, Ill.

BRAND NEW DM35 DYNAMOTORS

12 VOLT INPUT-
OUTPUT 625 V. @ 225 MA \$14.95

SMALL PIONEER DYNAMOTORS

Ideal for Amateur or Commercial Service 3.5 to 6 volt DC input-output 400 volts at 175 MA cont. or 275 MA intermittent duty. Comes complete with A & B filters. HF hash filter & internal cooling fan.....each \$14.95

DYNAMOTOR STARTING RELAY

12V DC coil. Solenoid type fully enclosed. Will easily handle 50 amps. Contacts and winding isolated from ground.....ea. \$1.75 2 for \$3.00

MARION 2 1/2" METER

Basic 0-1 mil has dual scale. 0-100 ma and 0-500 VDC. Complete with 500 Volt Meter Multiplier.....ea. \$3.95

REDMOND BLOWER

110V. 60 cyc. 3 Amp. 1600 Rpm. 3 1/4" Blower wheel-Outlet 2" diameter. Suitable for 0-500 VDC. Transm. tubes, etc.....ea. \$1.95 2 for \$3.00

REVODEX MICROMETER DIAL

1" Diameter dial. Scales Chrome plated. Grad. 0-100 div. Black face front & back. 1.1" Actual counts 1000 div. or 10 turns. Contains mounting hardware and full instructions. For rotary inductors, helixes, or any other device with 1/8" shaft.....ea. \$2.95

MS 1" Miniature Meter
0-1 mil. Scale calibrated in 20 divisions.....\$3.95

Filament Transformer
Pri. 110V. 60 cyc. Sec. secondary 6.3V @ 10 amps. Good quality.....ea. \$1.95

TELEPHONE HANDSET ELEMENTS

Receiving elements fit standard W. E. or 65c Conn. Tel. handsets.....ea. \$1.10 10 for \$9.25

G. E. RELAY CONTROL

(Ideal for Model Controls, Etc.)
Contains a sigma midpoint 5,000 ohm relay (trips at less than 2 MA), high impedance choke, bimetal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total \$1.10 ea. 10 for \$9.25

RELAYS

Scaled Claire SPDT. Norm. closed 3000 ohm coil. 2 1/2" dia.....ea. 95c
Claire Telephone Type 11,300 ohm coil DPDT contacts 10 amp 125V. 5mm. 4RA.....ea. \$3.95
Cutter Hammer Contacter-110V 60 cyc. 4 pole single throw. Norm. open 28 amp contacts.....ea. \$6.95
Hermetically Sealed Relay Coil 110V AC 60 cyc SPDT Contacts 5 Amps.....ea. \$1.85
12 Volt DPDT DC Relay.....ea. \$1.35
Cramer Time Delay Relay, 220V 60 cyc. 45 sec. adj. 2 pole DT.....ea. \$6.95
G.E. Plug In Relay 5 prong 2000 ohm coil 4 mil. SPDT.....ea. \$1.75 2 for \$3.00

OIL CONDENSER SPECIALS

BRAND NEW

2 MFD 600 VDC .50	1 MFD 3000 VDC 1.85
4 MFD 600 VDC .75	4 MFD 3000 VDC 5.95
8 MFD 600 VDC .85	4 MFD 4000 VDC 6.95
8 MFD 600 VDC .85	1 MFD 6000 VDC 6.45
10 MFD 600 VDC 1.10	8 MFD 7500 VDC 1.45
12 MFD 600 VDC 1.50	1 MFD 10,000 VDC 22.00
2 MFD 1000 VDC .85	2 MFD 10,000 VDC 39.95
4 MFD 1000 VDC 1.25	1 MFD 15,000 VDC 29.50
12 MFD 1000 VDC 2.35	1 MFD 25,000 VDC 49.50
1 MFD 1500 VDC .45	8 MFD 330 AC .95
2 MFD 1500 VDC 1.10	1 MFD 1000 DC .95
8 MFD 1500 VDC 3.95	20 MFD 330 AC 3.50
10 MFD 1500 VDC 3.95	8 MFD 680 AC (2000 DC) 2.35
1 MFD 2000 VDC .85	
2 MFD 2000 VDC 1.50	
4 MFD 2000 VDC 3.50	
10 MFD 2000 VDC 6.95	

NEW PANEL METERS

G.E., WESTINGHOUSE, W.E., SIMPSON, etc.
1" METERS 0-5 Amps R.F. 3.95
0-1 Mil. 3" METERS
1 1/2" 0-50 mil 3.95
DC 0-150 Ma (Basic 1.5 Ma).....ea. 3.45
1 1/2" 0-5 Amps 0-1 Amp DC.....ea. 3.95
w/ wxt. Thermocouple 3.95
2" METERS 0-500 Volts DC 4.50
18-36 Volts DC \$1.95
0-50 Microamp. 5.95
0-5 Amps DC.....ea. 4.50
0-300 Mil A.C. 2.95
0-150 MA RF 0-1 Mil.....ea. 3.95
Int. Thermo. 3.49 0-1 1/2 Amps AC 3.95

BUD CE2008

Variable Condenser. Isolantite insulation. Air gap .01 Capacity 300 MMF. Reg. net \$4.95 ea. OUR PRICE.....ea. \$1.45

CHORE-Fully cased, hermetically sealed.
10 HENRY 60 Mil (unshielded).....90c
2 HENRY @ 250 Ma.....\$1.95
2 HENRY @ 315 Ma.....3.50
2 HENRY @ 630 Ma.....2.50
6 HENRY 850 Mil.....4.95

Read 'n' Save Bargains

9 Pin tube pin aligner.....99c
Precision Meter Multiplier-1 Megohm
1% tolerance.....\$1.49 ea.
IRC MPA 1 Mil Resistor 25 Watts.....85c
HEINEMANN CIRC. BREAKER
110 V. 60 cyc. 30 amps. Curve 4.....1.25
.01 MMF 1000 VDC MICAS.....3 for .95
.0004 2500 VDC MICAS.....5 for .95
.025 600 V MICAS.....5 for .95
1 MFD OH Condenser 400 VDC.....29c ea.
Thorndarson Filament Transf. pri 115V. 60 cyc. Secondary 2 1/2 V. 10 amps. 7500V Insul. 3 V. 3 Amps.....3.25


All merchandise sold on a 10 day money back guarantee basis

Min. Order \$3.00-25% with Order-F.O.B. New York
PEAK
ELECTRONICS COMPANY
66 W. Broadway, New York 7, N. Y., WO-2-5439

Antenna News

HIGH-GAIN WIDE-BAND ANTENNA

Winegard Company, Burlington, Iowa, has announced another antenna, the "Color Beam Deluxe," incorporating the "Electro Lens" feature. The result, according to the manufacturer, is an all-channel antenna with performance comparable to separate cut-to-channel yagis, yet retaining the small physical size and good mechanical design of the yagi. It has been designed to meet the requirements of color reception. Factory-assembled, it

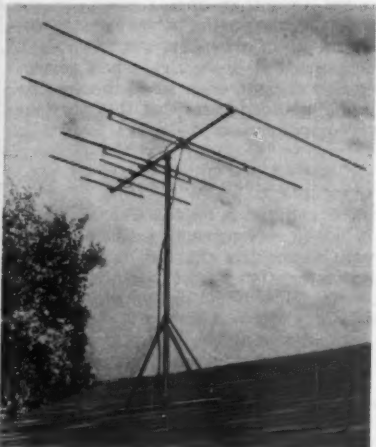

opens like an umbrella at the installation site, setting up the possibility of convenient, one-man installations. Completely anodized in gold, the unit is corrosion-resistant and weather-protected.

Included with the "Color Beam Deluxe" is the "Jigger Mount" device, a universal mount that permits quick attachment to any type or pitch of roof. Also included is lead-in wire with attached terminal clips and other material needed for the complete installation.

SALES REORGANIZATION

Snyder Manufacturing Company, Philadelphia, Pa., will reorganize its sales program in its Automobile Accessories Division during coming months. According to President Ben Snyder, sales representatives will be established in all areas. Establishment of a sales representative organization for this division closely follows a similar, successful reorganization of sales for the Antenna Division.

Newly appointed representatives for the Antenna & Electronics Division include J. W. Lehner Co., 367 Brynhild Rd., Columbus, O., to cover Ohio, western Pennsylvania, and W. Va.; also Herbert L. Dienes Co., 1505 Paper Mill Rd., Erdenheim, Pa., to cover

eastern Pennsylvania, southern New Jersey, Maryland, Delaware, District of Columbia, and Virginia.

INDOOR ANTENNA

Radio Merchandise Sales, Inc., 2016 Bronxdale Avenue, New York 62, N. Y., claims for its new "Focus," model F-38K, that it has the gain of three separate switch-type indoor antennas stacked together. Features include the exclusive diamond phasing loops, a criss-cross phasing element, and a 12-position all-channel phasing switch. The mahogany-finished base has a felt pad to prevent damage to furniture surfaces.




Edward E. Wineblatt, general manager of the firm, has announced the appointment of Ed Martin as representative in the state of Virginia.

MAGNETIC AERIALS

Brach Electronic Division, General Bronze Corporation, 711 Stewart Ave., Garden City, N. Y., is seeking new applications for the magnetic antenna materials already introduced in a top-of-the-set indoor antenna that has no conventional elements protruding from its modest-sized, radio-like cabinet. It is presently conducting development in the direction of aircraft antennas, miniature in size and low in weight, that maintain the same operating efficiency of aircraft antennas currently in use.

LIGHTWEIGHT ANTENNA

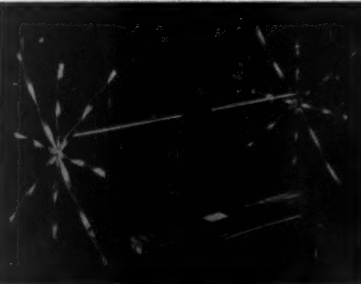Starbeam Company, Box 5087, Waco, Tex., uses a new principle in its "Starbeam" antenna, in which eight twisted aluminum elements are arranged in a star pattern on each end of a 34-in. two-piece aluminum




beam. Its designer is Dr. Corlett, a nuclear physicist who once studied under Albert Einstein and who believes that TV waves are composed of individual particles of energy. He states that the twisted antenna elements use more of the bouncing rays, which have heretofore been a source of annoyance in TV reception.

Since the unit is light (9½ oz.) and relatively small in size, it may easily be disassembled and reassembled for portability, and may be used indoors, as in an attic, or outdoors.

TUCK-AWAY INDOOR ANTENNA

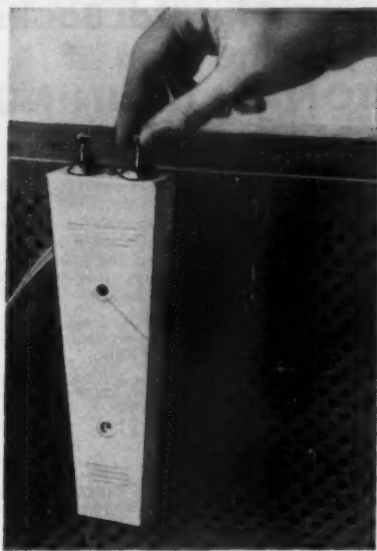JFD Manufacturing Company, Inc., 6101 16th Avenue, Brooklyn 4, N. Y., offers an indoor dipole antenna, the "Periscope," that mounts to the back




of the TV receiver. When not in use, it can be telescoped out of sight. The balled-socket nickeled brass telescoping dipoles pivot in any direction in use, drop out of sight behind the set when not in action.

Encased in a high-impact styrene housing and available in a choice of four colors, models of the "Periscope" are available in either special or deluxe versions to fit portable, table, or console receivers of various sizes.

6-METER MOBILE ANTENNA

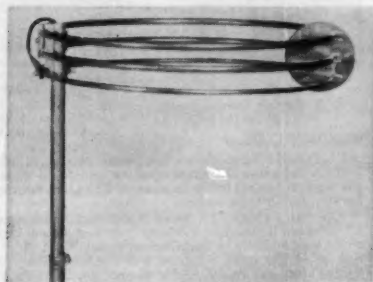Hi-Par Products Company, Fitchburg, Mass., offers the "Saturn 6" for the many amateurs who have gone over to horizontal polarization in the 6-meter band. Design center is 50.5



mc. but a trimmer permits resonating between 50 and 53 mc. As compared to vertical whips, the antenna shows improved results, especially over hilly terrain, with less flutter and swish, and less ignition noise. A universal bumper mount is available. -TV-


Weller soldering guns make safe repairs to Heat-Sensitive Components

A Weller Soldering Gun gives you precise control of heat. This feature is especially important when replacing heat-sensitive components. Here are some typical applications:



1 REPAIRING PLASTIC-MOUNTED I-F TRANSFORMERS. Your Weller Gun gives you precise heat control for this delicate operation. Prevents melting of plastic sockets; enables you to repair loose contacts and hair-thin coil-winding wire without damage.

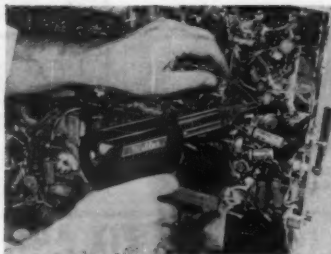
2 SOLDERING VOICE COIL CONNECTIONS. Heat-control characteristic of Weller Guns enables you to repair loose or broken voice coil connections on the reflecting surface of paper resonating cone. The slightest mishandling of a soldering iron would burn cone.



4 REPAIRING REMOTE-CONTROL TUNING UNITS. Your Weller Soldering Gun fits neatly into the small spaces between the terminal tabs on telephone-type relay stacks. Also, heat shut-off feature of gun prevents damage to insulation.



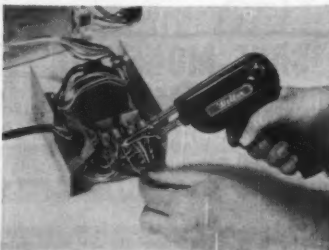3 REPLACING CRYSTAL OSCILLATOR. Controlled heat is imperative for replacing crystal oscillator in color demodulator circuits. With a Weller Soldering Gun you get perfect heat control, thus avoid damage to delicate crystal element.



There are professional model Weller guns
for every type of service work



Your choice of models ... ranging from 100 to 250
with single heat and 100 to 275 dual heat types.
Suitable for every kind of service operation.
All models heat in 5 seconds; provide instant,
triggermatic control of temperature.

ORDER FROM YOUR ELECTRONIC PARTS DISTRIBUTOR

Weller

ELECTRIC CORP.

401 Stone's Crossing Road, Easton, Pa.

radio and television receiver

radio and television troubleshooting & repair

SAVE \$1.25!

Make your service library complete! Have the needed data at your fingertips **WHEN YOU NEED IT!**

If broken into "lessons" and sent to you as a "course," you'd regard this new Ghirardi training as a bargain at \$100 OR MORE! Instead you buy BOTH big books at the bargain price of only \$13.00. (you save \$1.25!)

A. A. Ghirardi
More servicemen have trained from Ghirardi books than any other books or courses of their kind!

FIX ANY TV or

These 2 Great Ghirardi Books bring you the kind of PROFESSIONAL TRAINING THAT REALLY PAYS OFF!

Let these two up-to-the-minute Ghirardi books make it easy for you to handle ALL types of AM, FM and Television receiver service by the very best and latest methods! Learn to handle jobs faster, better . . . and with less testing! Whether you're a service beginner or an experienced technician you'll find the speedy, professional methods that are so clearly explained can give BOTH your service efficiency and your earnings a big boost!

Almost 1500 pages and over 800 big, clear pictures and diagrams explain EVERY troubleshooting and repair operation so simply it's next to impossible to go wrong.
Books are sold separately at prices indicated. Better yet, you can save

\$1.25 by buying both together! Send no money. Practice from these great books for 10 full days FREE.

Mail coupon today to Rinehart & Co., Inc., Dept. RN-27, 232 Madison Ave., New York 16, N. Y.

COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS!

Radio & Television Receiver 1 Circuitry & Operation

by Ghirardi & Johnson
669 pages, 417 clear illustrations, \$6.75

It's lots easier to repair ANY radio or television set when you know all about its circuits and just why and how each one works! You locate troubles in much less time and with less testing. You repair them faster, better—more profitably!

That's why **Radio & Television Receiver CIRCUITRY AND OPERATION** is invaluable to servicemen who want to be well equipped to handle today's complicated receivers! First it gives a complete understanding of basic circuits and their variations. It teaches

you to recognize each one quickly. Then it shows how to eliminate useless testing and guesswork in making repairs.

Throughout, this book gives you the kind of above-average training that takes the "headaches" out of servicing—the kind that fits you for the better-paid jobs. Covers all basic circuits used in modern TV and radio as well as phono pick-ups and record players.

Sold separately for \$6.75—or see big MONEY-SAVING OFFER.

Radio & Television Receiver 2 Troubleshooting & Repair

by Ghirardi & Johnson
822 pages, 417 clear illustrations, \$7.50

Backed by the how-to-do-it methods and procedures so clearly explained in this big book, you can breeze through television and radio service jobs easier and faster than you may have thought possible!

Throughout its 822 pages, **Radio & Television TROUBLE-SHOOTING AND REPAIR** is an amazingly complete, how-to-do-it guide to professional service methods . . . the kind that help you handle jobs lots faster and make more money doing it!

For beginners, this big book is an easily understood course in locating troubles fast and repairing them r-i-g-h-t. For ex-

perienced servicemen, it is a quick way to "brush up" on specific jobs; to develop better methods and shortcuts; or to find fast answers to tough service problems.

Modern troubleshooting is clearly explained—from quick "static" tests to dynamic signal tracing and all the rest. Special hard-to-find troubles are fully covered. Step-by-step charts demonstrate exactly what to do on different operations. A big, television section includes everything you need to know for fast, accurate work on any TV receiver model or make.

Sold separately for \$7.50 or see MONEY-SAVING COMBINATION OFFER.

SAVE MONEY ON INSTRUMENTS!



BASIC ELECTRONIC TEST INSTRUMENTS
254 pages,
171 illus.,
Price \$4.95

Work better with fewer instruments—get more work out of your old ones

Here, at last, is an instrument book especially for servicemen, amateurs and experimenters!

Basic Electronic Test Instruments helps you work better and faster with fewer instruments; shows how to increase the usefulness of old instruments; how to choose the right instrument for each job; how to understand instrument readings and put them to practical use; how to avoid buying unnecessary instruments . . . and lots more.

Over 60 instruments from the old standbys to the very latest ones are fully described and explained. Work-saving shortcuts are outlined.

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's, V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes; R-F test oscillators; signal generators; audio test oscillators; R-F and A-F measuring devices; signal tracers; tube testers and many others.

This handy book is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators; TV linearity pattern generators, square wave generators, distortion meters, etc. Dozens of time-saving "tricks" help you put old instruments to new uses.

Check Basic Electronic Test Instruments in coupon for 10-day FREE trial.

Now! FIX ANY ELECTRIC MOTOR!



TRAIN FOR BETTER PAY IN A FIELD THAT ISN'T CROWDED!

do-it diagrams side by side so that you learn fast, easily and right. Every job is explained so clearly you cannot fail to understand it. Over 100,000 copies in use in motor repair shops, schools and for home study. Fully approved by repair specialists, unions and instructors.

It's the ideal book whether you want to train for a good-pay motor repair job or simply want to fix motors as a sideline or hobby!

Order **ELECTRIC MOTOR REPAIR** in coupon. Price only \$6.95.

Handle ANY job from minor repairs to complete rewinding


550 pages—Over 800 how-to-do-it pictures

It pays to train for something different! **ELECTRIC MOTOR REPAIR** is a complete guide that helps you cash in on this vast, rapidly growing field. Shows step by step how to handle all repair jobs (including complete rewinding) on practically ANY AC or DC motor or generator in common use—from fractional horsepower to giant industrial motors. Special duo-spiral binding brings text and related how-to-do-it diagrams side by side so that you learn fast, easily and right. Every job is explained so clearly you cannot fail to understand it. Over 100,000 copies in use in motor repair shops, schools and for home study. Fully approved by repair specialists, unions and instructors.

It's the ideal book whether you want to train for a good-pay motor repair job or simply want to fix motors as a sideline or hobby!

Order **ELECTRIC MOTOR REPAIR** in coupon. Price only \$6.95.

SHORT CUT TO TELEVISION REPAIRS

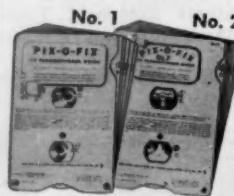

Pix-O-Fix TV Trouble Finder Guides
Only \$2 for the two

repairing . . . presto! . . . you've got your clue.

PIX-O-FIX then shows the causes of the trouble. Next it indicates the exact receiver section in which the trouble has probably happened. Then it gives step by step repair instructions.

The two PIX-O-FIX units No. 1 and No. 2 cover 47 different television troubles . . . just about anything you're likely to be called on to fix. No. 1 identifies 24 of the most common troubles and gives 192 causes and 253 remedies for them. No. 2 covers 23 more advanced troubles not included in No. 1. Together, they are a comprehensive guide to quick "picture analysis" servicing of any TV set . . . AND THE PRICE IS ONLY \$2.00 for the two. Money refunded if you are not more than satisfied. Specify PIX-O-FIX in coupon.

Eliminate useless testing . . . Fix sets twice as fast!

Just turn the dial of the handy, pocket-size Ghirardi & Middleton PIX-O-FIX TV Trouble Finder Guide. When the picture in the PIX-O-FIX window matches the screen image on the television set you're

USE COUPON FOR **10-day Free Trial!**

RADIO EVER MADE

**FAST!
EASY!
R-I-G-H-T!**

Cash in on HIGH-FI SERVICE and BUILDING



HIGH FIDELITY TECHNIQUES
By John H. Newitt
494 pages,
\$08 illus.
Price \$7.60

A complete guide to better High Fidelity methods and results

Get better results from "Hi-Fi" by having all the facts and latest ideas at your fingertips!

This big book brings you complete data on modern sound reproduction methods and equipment. It shows how to get better results at lower cost; how to build your own; how to service hi-fi equipment; discusses all details of components; compares different methods—AND IS CRAMMED FULL OF HOW-TO-DO-IT TIPS AND IDEAS.

Here are just a few of the many subjects: How to get the right hi-fi equipment for your needs; Hi-fi versus P.A. type speaker; Loudspeaker construction and performance; Adjusting bass-reflex cabinets; Controlling distortion; Getting rid of "hang-over"; Selecting a woofer-tweeter; Sound-proofing materials; All about output transformers; Special hi-fi circuits; Ways to suppress noise; Negative feedback and how to use it; Amplifier construction hints; Minimizing tuner distortion; Avoiding chatter; Limiter-discriminator vs. ratio detector FM circuits; Avoiding record wear; Tips for custom builders; Bass-reflex charts; Acoustical horn design data; special installation problems; pre-amps and equalizers; pick-up resonance; a novel horn system . . . and literally dozens of other subjects.

Order **High Fidelity Techniques** in coupon today for 10-day FREE trial!

Here's How to Get Started in RADIO-ELECTRONICS!



RADIO PHYSICS COURSE
by Ghirardi
978 pages,
\$08 illus., \$68 self-test questions
Price only \$8.50

More service experts got their basic training from this big book than any other of its type!

Here's basic training you can really understand—written by A. A. Ghirardi who has probably trained more service experts than any other man living today! From start to finish, it is practical training that can help fit you for a BIG PAY job in any branch of radio-television-electronics work.

Ghirardi's **RADIO PHYSICS COURSE** is the oldest book of its kind—and still a best seller BECAUSE IT IS SO AMAZINGLY CLEAR AND COMPLETE. You can understand it, even without any previous radio or TV training!

36 COURSES IN ONE!

Starts with Basic Electricity. Then it takes you step by step through the entire field from basic circuits, components, instruments, etc. to their final application in radio-electronic equipment. You can buy newer, costlier training—but you can't buy better training at anywhere near the price. Ask the men who know!

Order **RADIO PHYSICS COURSE** in coupon.

DON'T THROW OLD RADIOS AWAY!



RADIO TROUBLESHOOTER'S HANDBOOK
Covers every model made by 202 mfrs. from 1925 to 1942

Here's the data you need to fix old sets in a jiffy!

Just look up the how-to-do-it data on that old radio you want to fix!


Four times out of 5, this giant, 3½-pound, 744-page Ghirardi **RADIO TROUBLESHOOTER'S HANDBOOK** tells what is likely to be causing the trouble . . . shows how to fix it. No useless testing. No wasted time. Using it, even beginners can easily fix old sets which might otherwise be thrown away because service information is lacking. With a few simple repairs, most of these old sets can be made to operate perfectly for years to come.

THE ONLY GUIDE OF ITS KIND!

Cuts service time in half!

Included are common trouble symptoms and their remedies for over 4,800 models of old home, auto radios and record changers. Airline, Apex, Arvin, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G-E, Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Sparton, Stromberg and dozens more. Includes hundreds of pages of invaluable tube and component data, service short cuts, etc.

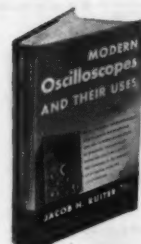Specify **RADIO TROUBLESHOOTER'S HANDBOOK** in coupon. Price only \$6.95. 10-day trial.



The book that really teaches you how to use 'scopes on all kinds of electronic service

Here's everything you need to know ABOUT OSCILLOSCOPES!

Oscilloscopes are "gold mines" if you learn to use them fully on every job.

THIS BIG BOOK TEACHES YOU HOW!

Here, in a big, revised 2nd edition, is THE book that really shows you how to use oscilloscopes!

Clearly as A-B-C, **MODERN OSCILLOSCOPES AND THEIR USES** gets right down to "brass tacks" in telling you exactly when, where and how. You learn to locate either AM or FM radio or television troubles in a jiffy. Even tough realignment jobs are made easy. No involved mathematics! Every detail is clearly explained—from making connections to ad-

justing circuit components and setting the oscilloscope controls. And you learn to analyze patterns fast and RIGHT!

Includes latest data on use of 'scopes in color TV, industrial electronics, teaching . . . even in atomic energy work. Over 400 helpful pictures including dozens of pattern photos make things doubly clear. Price \$6.50.

Practice 10 days free. Order **MODERN OSCILLOSCOPES** in coupon.



Oscilloscope experts get the BIG PAY jobs!



LICENSE MANUAL for Radio Operators
by J. R. Johnson (W2BDL)

A complete, practical study guide for getting your "ticket" as a commercial operator

Now! PASS FCC LICENSE EXAMS easier! faster!

Train for big pay in communication's most interesting jobs

Here, at last, is a guide to FCC License Examinations . . . written so you can easily understand AND REMEMBER it. Covers ALL EIGHT exam elements . . . not just some of them. Reviews almost 2200 typical exam questions with straight-to-the-point answers. Includes full data on the recent changes in examination elements 1 and 2. (Many folks do not even know these changes exist!) Covers all necessary examination data from electrical-radio fundamentals to navigation and related subjects. Anyone who has basic radio training will find Johnson's **LICENSE MANUAL** the ideal training book for making this all-important step ahead in his career! Price only \$5.00. Use coupon.

TRY ANY BOOK 10 DAYS FREE!

Dept. RN-27, Rinehart & Company, Inc.,
232 Madison Ave., New York 16, N. Y.

Check here for MONEY-SAVING COMBINATION OFFER

. . . on Ghirardi's **Radio & TV Receiver CIRCUITRY AND OPERATION**, and **Radio & TV Receiver TROUBLESHOOTING AND REPAIR**. Price only \$13.00 for the two books plus postage. (Regular price \$14.25 . . . you save \$1.25). Payable at rate of \$4 (plus postage) after 10 days and \$3 a month for three months until \$13.00 has been paid. If not satisfactory, return books in 10 days and owe nothing.

Check here to order INDIVIDUAL BOOKS

- | | |
|---|--|
| <input type="checkbox"/> Radio & TV Receiver CIRCUITRY AND OPERATION \$6.75 | <input type="checkbox"/> HIGH FIDELITY TECHNIQUES \$7.50 |
| <input type="checkbox"/> Radio & TV Receiver TROUBLESHOOTING AND REPAIR \$7.50 | <input type="checkbox"/> MODERN OSCILLOSCOPES AND THEIR USES \$6.50 |
| <input type="checkbox"/> BASIC ELECTRONIC TEST INSTRUMENTS \$4.95 | <input type="checkbox"/> RADIO TROUBLESHOOTER'S HANDBOOK \$6.95 |
| <input type="checkbox"/> ELECTRIC MOTOR REPAIR \$6.95 | <input type="checkbox"/> RADIO PHYSICS COURSE \$6.50 |
| <input type="checkbox"/> PIX-O-FIX TROUBLE-FINDER GUIDES (Nos. 1 and 2) \$2.00 | <input type="checkbox"/> LICENSE MANUAL for Radio Operators \$5.00 |

If cash is sent with order, we pay postage—same 10 day return privilege. Otherwise, postage is extra. To order **OUTSIDE U.S.A.**—Special combination offer, \$14.00 for both books. For all other books, add 50¢ each to above prices for handling through customs, etc. Sold for cash only. Any book may be returned in 10 days and money will be refunded.

Name
Address
City, Zone, State

AIREX

THE ELECTRONICS
SUPERMARKET

ROCK
BOTTOM
PRICES

NEW HI-FI EQUIPMENT YEAR BOOK

Most complete guide in the industry. 128 pages crammed full of technical information of 100 mfrs. Lists over 700 items, 400 photos of the latest Hi-Fi merchandise, with costs. This is a limited edition!

\$1.95

with Mde
bought from
Year Book

RECORD CHANGER BARGAINS

WEBSTER NEW 4 SPEED: changer with Magic Mind. Automatically changes from 33 1/2 to 45 RPM as the record drops. New 16 RPM speed. With ceramic cart, dual sapphire stylus. **\$24.95**

WEBSTER NEW 3 SPEED
With 4 pole motor & GE RPX050A Reluctance cart & dual sapphire stylus. **\$27.95**

NATIONALLY FAMOUS CASER RELUCTANCE CARTRIDGE TYPE RPS OS2A. Triple play .003 mil sapphire & .004 mil diamond. Clip-in stylus. Stylus pressure 6-8 grams. **\$17.95**

NATIONALLY FAMOUS RELUCTANCE CART TYPE OS0A. Triple play sapphire needles for all records, clip-in stylus. Stylus pressure 6-8 grams. **\$6.95**

45 RPM SPINDLES GARRARD \$3.49 MARCHAL \$2.95 WEBSTER \$2.49 COLLARO \$3.75

DYNAKIT MARK II

The most compact high fidelity 50 watt amplifier made. 100 watt peak. Intermodulation distortion less than 1% at 50 watts, less than .25% below 35 watts. Response 6-60KC ± 5 db ± 1 db 20-20KC. Input 1.5 volts for 50 watt output. Damping factor of 15. 8 and 16 ohm taps. Uses 2-EL34, 6AN5 and 6U4GB. Complete with all components. Prewired XXXP circuit board. Only top quality parts used throughout. **\$69.75**
With bottom cover and cage. 27 lbs.

Grommes Hi-Fi Amplifier Kits
10 Watts, 18 watts peak. Resp. 20-20,000 cps ± 1 db. Presamp. 1 input. Hum-80 db. 2% Harm. Dist. 10 watts. Complete with detailed step by step instruction manual, all resistors, condensers, tubes, wire & solder. Easy to make. 2-12AX7, 3-6V6, & 5Y3. Bass & Treble boost. Limited quantity. **\$24.95**

New 20 watt Grommes amplifier kit, mdl. 61PGK. 30 watts peak. Response 20-20,000 cps ± 1 db, hum-80 db, full equalization & compensation. Complete with cage & 7 tubes. **\$59.50**

FM-AM TUNER KIT

Easy to assemble. Professional quality performance. 3 double tuned IF stages. Foster-Seely discriminator, automatic frequency control & defect. 7 tubes plus rectifier. Distortion less than 10%. Hum level -70dB. Sensitivity 5 microvolts for 20 dB quieting on FM & 20 microvolts on AM. FM selectivity 200Kc band width 8 DB down; AM SEC band width 6 DB down. 5 1/2" high x 9 1/2" wide x 8" deep. Complete with step-by-step instructions. **\$29.95**

FM TUNER ONLY—\$23.95 • COVER—\$3.95
These units are ideal in combination with the Grommes Hi-Fi Amplifier. Kits listed above.

MULLARD HI-FIDELITY TUBES

Type	Replaces	Price	Type	Replaces	Price
EL34	KY88; 6CA7	\$4.35	6X4	12AU7	\$2.20
EL37	6L6; 6BA1	\$3.50	6X4	12AX7	\$2.50
EL34	KY88	\$3.50	6X4	12AX7	\$2.50
EL34	6BD6	\$2.40	6X4	12AX7	\$2.50
EL34	12AT7	\$2.60	6X4	12AX7	\$2.50

FAMOUS UTAH SPEAKERS

12" coaxial, exclusive built-in crossover network assures a frequency response from 35 to 17,500 cps, 12 watt cap. 8 OHMS impedance. Reg. \$24.95. **\$12.88**
15" woofer-response 30 to 8,000 cycles, 21.5 c. magnet, 35 watt capacity, 1 1/2" voice coil, 8 OHMS impedance. Reg. \$34.95. **\$19.95**
3" super tweeter-response 2000 to 19,500 cps, 25 watt capacity, 3/4" voice coil, 8 OHMS impedance, with built-in crossover network. **\$7.95**

JENSEN SPEAKER ENCLOSURE KITS

Now you can build any of the basic Jensen speaker enclosures at tremendous savings. All kits are cut from 3/4" plywood panels and all baffles are pre-cut. All hardware, glue, sound absorbing material and complete simple instructions are included. You need only a screwdriver. Brochure available.

K-101, Imperial Cabinet Kit.....	\$89.00
K-103, Tri-Plex Cabinet Kit.....	\$48.00
K-105, 15" Base Ultra-Flex Cab Kit.....	\$48.00
K-107, Concerto Cabinet Kit.....	\$39.00
K-109, 12" Base Ultra-Flex Cab Kit.....	\$39.00
K-111, 8" Base Ultra-Flex Cab Kit.....	\$23.00
K-113, Treasure Chest Cab Kit.....	\$18.00

Standard Coil Cascade TV Tuner

Replacement for any type TV set. 41 MC. IP. Shaft length 3 1/4". **\$9.95**
Knobs to match—69¢. In lots of 2, \$6.95 ea.

Building Your Own Hi-Fi System? Write Us FOR PRICES ON OUR PACKAGE DEAL QUOTATION.

All merchandise is brand new, factory fresh & guaranteed. Mail & phone orders filled on receipt of certified check or MO of 20% of items as a deposit. Balance C.O.D. F.O.B. factory N.Y. Prices & specifications subject to change without notice.

AIREX RADIO CORP.

64 Cortlandt St. N.Y. 7, N.Y. CO 7-2137

Electronic Agitator

(Continued from page 43)

appear on C_1 . When switch S_1 is closed, full line voltage is connected across the plate-cathode circuit, but the tube does not fire because of the negative charge present on C_1 . This charge blocks space current until it has dissipated through R_1 . Resistor R_1 functions as a coarse adjustment by shifting the operating point.

The tube fires at the expiration of the timed period and applies rectified a.c. to the relay, RL_1 . The tube continues to pass current and hold RL_1 closed until S_1 is opened. Plate current then ceases, RL_1 opens, and C_1 begins to charge. After a second or so the cycle may be repeated. R_2 protects the grid by limiting the current during the charge and firing periods. R_2 connects the cathode to L_2 . Fuse F_1 is used to prevent tube failure if C_1 or the relay become shorted.

In operation the film reel is clipped to a string which passes through the string guide and is attached to the motor drum. The drum on the motor shaft need not be grooved as shown in the illustration. A short piece of 1/4" diameter dowel with a hole drilled into the end to accept the motor shaft and a screw tapped into the side is sufficient. The string guide will keep the cord from running off the drum.

The string guide is made from a short length of coat hanger wire bent

sharply at one end and soldered closed at the other. The slot left should be sufficient to pass the string, but not the knotted string. After assembling the switch onto the chassis, the string guide is soldered to the switch lever.


When the timing circuit fires and closes the relay, the motor begins to wind the string and raise the film reel out of the solution. This is the draining period. The lower knot in the string is unable to pass through the string guide, thus raising the guide and opening switch S_1 . The motor then stops, allowing the film reel to coast down into the solution. As the reel enters the solution, a second knot located above the string guide, about three inches from the motor drum, pulls the string guide down, closing S_1 and starting the timing cycle again. The period for which the film is draining may be changed by varying the distance between the lower knot and the string guide. The "in solution" period is adjusted by means of the two controls on the front panel.

The completed unit is supported by a board which hooks onto a shelf above the sink.

This agitator has given daily service for over two months. It has operated perfectly and assures us of consistent results in our color film processing. The advantages of automatic agitation will also prove valuable to the careful black-and-white processor.

Agitation is an important detail and, unlike a person, this mechanical unit is almost infallible. —30—

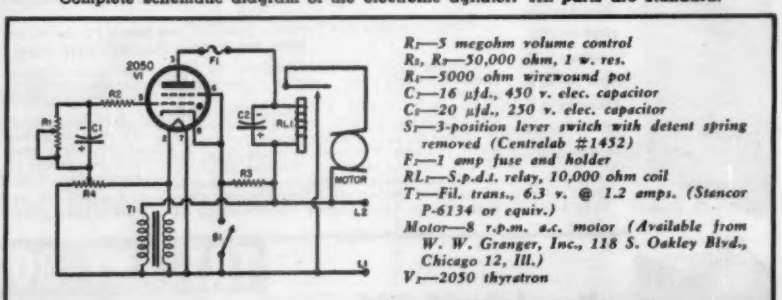Complete schematic diagram of the electronic agitator. All parts are standard.



Over-all view of the chassis and the back of the front panel with the motor and 2050 thyatron tube removed. Top of unit is at left. Plywood is easy to work but the builder can use any material for constructing the agitator.



RADIO & TELEVISION NEWS

only LAFAYETTE can do it!

OUR DIRECT IMPORTATIONS

YOU SAVE IMPORTERS PROFIT!

SAVE 33 1/3-50

PROFESSIONAL TRANSCRIPTION TURNTABLE AND VISCOUS-DAMPED TONE ARM

THE FINEST TRANSCRIPTION TURNTABLE AND TONE ARM FOR THE PROFESSIONAL USER AND THE AUDIOPHILE



PK-100A TRANSCRIPTION TURNTABLE
New 3-speed instrument with built-in stroboscope and viewer for exact speed determination, and magnetic brake for instantaneous speed variation. Precision engineered to meet professional standards for wow, rumble and flutter content. Heavy 12" cast aluminum rim-driven turntable. Variable speed control permits adjustment of each speed within $\pm 7\%$ using efficient frictionless magnetic brake. Heavy-duty constant speed 4-pole induction motor freely suspended and isolated by shock-mountings to eliminate vibration transfer. R-C filter network suppresses "pop" in speaker. Truly a delight for the connoisseur. Size: 13 1/2" x 14" and requires 2 1/2" clearance above and 3 1/2" below motorboard. For 110-130V and 60/50 cycle AC. Power consumption 12 watts. Handsome hammertone gray finish. Shpg. wt., 20 lbs.
PK-100-A Net 49.50

PK-90 VISCOUS-DAMPED TONE ARM
This transcription arm assures dependable and stable operation, utilizing the "floating action" principle of "viscous-damping." The arm is supported at a single point by a pivot and jewel bearing having negligible friction. Damping is accomplished by a silicone fluid occupying the gap between a ball and socket. This damping control permits high compliance and negligible tracking error, and prevents damage to either record or stylus should the tone arm be accidentally dropped. Low frequency resonance, skidding and groove-jumping are likewise minimized. The tone arm accepts all records up to 16" and accommodates virtually all hi-fi cartridges by means of precisely engineered adapters which simplify installation and provide proper stylus pressure. This tone arm is a quality companion to the PK-100 with matching finish. Shpg. wt., 2 1/2 lbs.
PK-90 Net 15.95




NEW! HIGH FREQUENCY TWEETER WITH ACOUSTIC LENS

DIRECT IMPORTATION MAKES THIS PRICE POSSIBLE!

- FREQUENCY RESPONSE FROM 2000 CPS TO BEYOND AUDIBILITY
- LOUVERED ACOUSTIC LENS FOR UNIFORM SOUND DISPERSION
- HANDLES 25 WATTS OF POWER
- PRICED EXCEPTIONALLY LOW

New high frequency tweeter featuring a louvered acoustic lens for uniform sound dispersion and capable of handling up to 25 watts of distortion-free power. The directional tendency of high frequency notes is overcome by the natural wide dispersion angle of the short horn and the acoustic lens which disperses and radiates the high notes smoothly throughout the entire listening area. The lens is detachable for panel mounting, with a separate base for the tweeter furnished for external mounting where desired. Aluminum voice coil has 16 ohms impedance. Size: 4 1/4" long x 3" diameter, lens extends 2 1/2". Requires a crossover network, preferably one with a level control, such as the LN-2. With full instructions. Shpg. wt., 5 lbs.
HW-7 Net 14.95

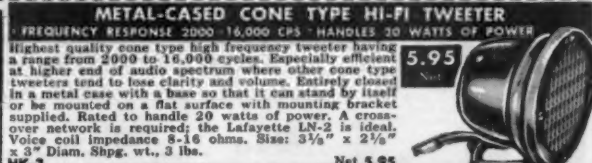

METAL-CASED CONE TYPE HI-FI TWEETER

FREQUENCY RESPONSE 2000-16,000 CPS - HANDLES 30 WATTS OF POWER

Highest quality cone type high frequency tweeter having a range from 2000 to 16,000 cycles. Especially efficient at higher end of audio spectrum where other cone type tweeters tend to lose clarity and volume. Entirely enclosed in a metal case with a base so that it can stand by itself or be mounted on a flat surface with mounting bracket supplied. Rated to handle 30 watts of power. A crossover network is required; the Lafayette LN-2 is ideal. Voice coil impedance 8-16 ohms. Size: 3 1/2" x 2 1/2" x 3" Diam. Shpg. wt., 3 lbs.
HW-3 Net 5.95



3 WAY CROSSOVER NETWORK


Carefully designed and engineered to Lafayette's own specifications. Insertion loss is well below the acceptable minimum. Crossover is at 500 and 5000 cycles. Permits full enjoyment of any 3 way system. Properly balances woofer, mid range speaker and tweeter inputs. Complete with 2 continuously variable "presence" and "brilliance" controls for tonal adjustment and full instructions. 8 1/2" x 3 1/2" H x 2 1/2" W. Shpg. wt., 7 lbs.
LN-3 Net 14.95



NEW! IMPORTED 12" HI-FI COAX. SPEAKER

- FREQUENCY RANGE 30-15000 CPS
- HANDLES 20 WATTS OF POWER
- COMPLETE WITH LEVEL CONTROL
- POWERFUL TSK-5 MAGNETS
- SPECIAL SHEEPSKIN-EDGED CONE

A Lafayette exclusive import and exceptional value. Consists of a 12" woofer, coaxially mounted 2 1/2" tweeter and a built-in crossover network. The specially processed fibre cone has a sheepskin edge to suppress unwanted nodal vibrations and insure beautiful tone quality. Highly efficient TSK-5 magnets. Level control provides variation to 6 db cut. Maximum input 20 watts. Impedance 8 ohms. Rugged all-metal frame. If made in this country, would cost at least \$49.50. Shpg. wt., 11 lbs.
SK-38 Net 29.50

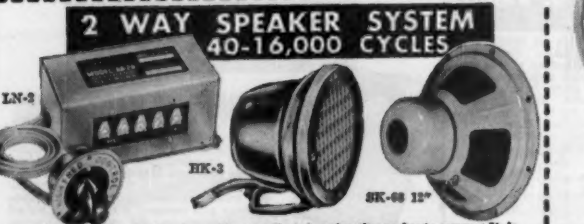

2 WAY SPEAKER SYSTEM 40-16,000 CYCLES
This 2-way speaker system is another excellent buy for the moderate purse. It is basically the same as the SK-38 system described at the top of the page, but incorporates the deluxe SK-65 speaker with 31.5 oz. Alnico V magnet. This results in more efficient reproduction and extension of the lower register. Complete system includes the RK-68 12" 25 watt woofer, HW-3 cone type tweeter and LN-3 crossover network with level-brilliance control. Range of system 30-16,000 cycles. Shpg. wt., 18 lbs.
SK-67 Net 27.50
SK-68 Net 34.50



3 WAY HI-FI SPEAKER SYSTEM
A complete 3-way system capable of performance heretofore found only in systems at many times this price. The components were specially selected by Lafayette sound engineers to offer the maximum in audio fidelity at the lowest price possible. Includes continuously variable presence and brilliance controls. Offers superb reproduction across the entire audio spectrum. Shpg. wt., 25 lbs.
SK-74 Net 55.50


LAFAYETTE RADIO

DEPT RB-1

JAMAICA 33; N. Y. 165-08 Liberty Ave. Write for FREE Bargain Packed Catalog!

100 SIXTH AVE., NEW YORK, N. Y.
BOSTON, MASS., 110 Federal St.
PLAINFIELD, N. J., 139 West 2nd St.
NEWARK, N. J., 24 Central Ave.
BRONX, N. Y., 542 E. Fordham Rd.

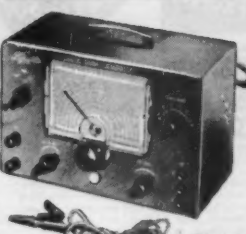LAFAYETTE SENSATIONAL VALUES! IN COMPLETELY WIRED TEST EQUIPMENT at LESS than the PRICE of KITS!



LAFAYETTE SIGNAL GENERATOR
NEVER BEFORE HAS A COMPLETELY WIRED AND TESTED INSTRUMENT OF SUCH ACCURACY AND QUALITY BEEN OFFERED AT SUCH A PRICE!

- FREQUENCY 120 KC TO 260 MC
- 120 KC TO 130 MC ON FUNDAMENTALS
- LABORATORY ACCURACY AND QUALITY

A completely wired and tested instrument not to be confused with units sold in kit form at almost the same price, but with a quality and accuracy of instruments 3 to 4 times its price. Six overlapping ranges generate signals of 120KC—320KC, 320KC—1000KC, 1MC—3.2MC—11MC, 11MC—38MC and 37MC—130MC all on fundamentals with calibrated harmonics from 120MC to 260MC. Selector switch gives instant choice of ranges. Switch gives choice of internal modulation of 400 CPS or use of any external source at other frequencies. For audio testing the 400 cycle signal can be used separately.

Outputs are unmodulated RF, modulated RF and 400 CPS audio. RF output is in excess of 100,000 microvolts and jacks are provided for choice of either high or low RF output. Stability is insured by special circuit design. Has a fine adjustment RF control. AF output is 2-3 volts, AF input is 4 volts across 1 megohm. Large clear 5 inch etched dial plate and pointer are protected by transparent plastic bezel. Common AF terminals for EXT-HIGH input and INT-LF for audio tests eliminate need for special AF output connectors. Machine engraved panel lettering. Handsome gray metal case with carrying handle. Measures $6\frac{1}{2}'' \times 10'' \times 4\frac{1}{2}''$. Comes complete with pair of leads. AC line cord and plug. Operates on 105-125V 50-60 cycle AC. Shpg. wt., 8 lbs.

LAFAYETTE L50-10 SIGNAL GENERATOR

22.50

NEW!

LAFAYETTE CAPACITANCE-RESISTANCE TESTER WITH "IN-SET QUICK CHECK"
COMPLETELY WIRED AND TESTED



- TWO INSTRUMENTS IN ONE
- CHECKS ELECTROLYTIC, PAPER, MICA AND CERAMIC CONDENSERS
- 4 DIRECT READING CAPACITY SCALES FROM .00001 MFD TO 1000 MFD
- CHECK FOR OPEN SHORTS, LEAKAGE AND INTERMITTENTS
- 2 RESISTANCE RANGES FROM 100 TO 5 MEGOHM

Here is a "must" for servicemen and lab technicians. A completely self-contained instrument with integrated capacitance and resistance bridge, plus a quick check for in the set testing. Large 5 direct reading scale has 4 ranges of .00001-.005 MFD, .001-.5 MFD, .1-50 MFD and 20-1000 MFD. Resistance ranges are 100-50,000 OHMS and 10,000 to 5 megohm. Quick check feature enables you to check capacitors for shorts, open or intermittent while in circuit—no need to remove them from the set till you're sure they need replacement. Leakage test switch gives scales after setting magic eye to maximum. Completely self-contained power supply. Attractively finished steel case with etched panel and rounded corners. Measures $14\frac{1}{2}'' \times 8\frac{1}{2}'' \times 5\frac{1}{2}''$. Shpg. wt. 19 lbs.

you choice of 25, 150, 250, 350 or 450 volts for checking leakage under correct potential. Separate power factor control with continuous settings from 0 to 50%. Operation is simple and accurate, using a magic-eye tube as the null detector. Attractively finished steel case with etched panel and rounded corners. Measures $14\frac{1}{2}'' \times 8\frac{1}{2}'' \times 5\frac{1}{2}''$. Shpg. wt. 19 lbs.

MODEL LC-4

NET 34.50

NEW!

LAFAYETTE CAPACITOR-RESISTANCE TESTER
COMPLETELY WIRED AND TESTED



- COMPLETELY WIRED AND TESTED
- CHECKS ALL TYPES OF CONDENSERS FOR CAPACITY, LEAKAGE, OPEN SHORTS OR INTERMITTENT CONDITION
- DIRECT READING SCALES FROM .00001 TO 1000 MFD AND 100 TO 5 MEGOHMS

A stable and accurate bridge type circuit measures capacitance in 4 ranges of .00001-.005 MFD, .001-.5 MFD, .1 to 50 MFD and 20 to 1000 MFD. Two resistance ranges of 100-50,000 and 10,000 to 5 megohms. Check leakage under actual load with choice of 25, 150, 250, 350 or 450 volts available by selector switch. Power factor control from 0 to 50%. Checks for leakage, open, short, or intermittent operation. All readings taken directly on scales after setting magic eye to maximum. Completely self-contained power supply. Attractively finished steel case with rounded corners and etched panel. Operates from 110V AC. Size $9\frac{1}{2}'' \times 7\frac{1}{2}'' \times 5\frac{1}{2}''$. Shpg. wt. 10 lbs.

MODEL LC-15

NET 21.50

4 AND 6 TRANSISTOR SUPERHET KITS POCKET AND HOME RADIOS FOR SPEAKER AND EARPHONE OPERATION



Completely self-contained, pocket size portable set which operates a miniature earpiece so only you can hear. The circuit uses 4 transistors (2 high frequency and 2 audio) plus a germanium diode, 2 IF stages and built-in high gain ferrite core and antenna. The result is a sensitive, stable and selective receiver covering the entire broadcast band. It requires no outside antenna or ground connection. The kit is supplied complete with transistors and all parts, including battery, and drilled and punched chassis. Pictorial and circuit diagrams are included with simple, easy-to-follow instructions. (Note: Earpiece and carrying case are not supplied.)

- KT-94—Complete Kit. Shpg. wt., 2 lbs. Net 19.95
- MS-311—Leather Carrying Case. Net 1.95
- MS-260—Super Power Dynamic Earpiece. Net 3.95

7 TRANSISTOR PUSH-PULL OUTPUT KIT WITH SPEAKER SELF-CONTAINED IN BEAUTIFUL PLASTIC CASE

Converts 4-Transistor Kit KT-94 into a 6-transistor home radio with speaker. Transistorized push-pull audio stage plugs into 4-transistor kit, suitable for group listening. Performance equal or superior to commercially wired sets selling at much higher prices. Kit includes 3 transistors, 3 transformers, 2 8" PAI speaker, pre-punched chassis, and speaker case (holds all components), battery, hardware, instructions and diagrams.


KT-94—Shpg. wt., 1 lb. Net 11.50

LAFAYETTE RADIO

JAMAICA 33; N. Y. 165-08 Liberty Ave. Write for FREE Bargain Packed Catalog!

NEW POCKET AC-DC VOM MULTITESTER
2,000 ohm per volt Sensitivity on both DC and AC

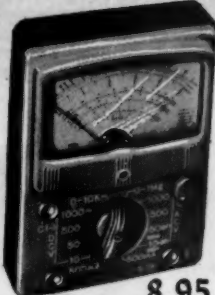160 ua 3" METER
1% PRECISION
RESISTORS
SILVER CONTACT
SELECTOR SWITCH



FULL SCALE RANGES
DC Volts: 0-10; 0-50; 0-500; 0-1000 Volts—AC Volts: 0-10; 0-50; 0-500; 0-1000 Volts—DC Current: 500 ua and 500 ma—Resistance: 0-10K; 0-1 Meg—Decibels: -20 to +22 +20 to 36 db (0 db = 0.775 V)—Capacity: 250 mmfd to .2 mfd—.005 mfd to 1 mfd—Output Range: 0-10; 0-50; 0-500; 0-1000 volts


8.95

Best Buy in America! A very accurate and sensitive VOM. This Multitester is a complete instrument (not a kit) with high quality and sensitive 160 microamp meter; 2000 ohm per volt on both AC and DC. Single selector switch, 1% precision resistors, 3" meter. Features extreme versatility, accuracy and ruggedness. In attractive plastic front panel, with metal bottom for ruggedness and shielding. First capacity range requires 50 volt AC source. Second capacity range requires 10 volt AC source. Size $4\frac{1}{2}'' \times 3\frac{1}{2}'' \times 1\frac{1}{2}''$. Complete with test leads and batteries. Shipping weight 4 lbs.

RW-27A

Complete 7.95

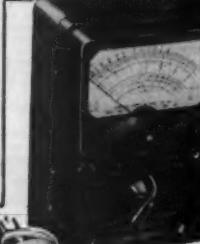HIGH SENSITIVITY 20,000 OHM PER VOLT DC 10,000 OHM PER VOLT AC MULTITESTER



LOOK AT THESE FULL SCALE RANGES!
D.C. Volts: 0-5; 0-30; 0-120; 0-600; 0-1200 Volts—A.C. VOLTS: 0-5; 0-30; 0-120; 0-600; 0-1200 Volts—RESISTANCE: 0-10K; 0-100K; 0-1 Meg; 0-10 Megohms—D.C. CURRENT: 0-60 Microamp; 0-6; 0-60; 0-600 Milliamps—D.B. 18dB; -20 to +17 db (0 db = 0.775V)—CAPACITY: .0001-.01; .005-.15 mfd—INDUCTANCE: 20-2000 millihenry—OUTPUT RANGE: 0-30; 0-120; 0-600; 0-1200 Volts

19.95

The new Lafayette high sensitivity Multitester is a complete instrument (not a kit). In addition to its unusual sensitivity of 20,000 OHMS PER VOLT on D.C. AND 10,000 OHMS PER VOLT ON A.C., and the extraordinary number and scope of its ranges, it is packed with features that would make it cost at least twice as much if made in this country. Uses 1% precision resistors, silver contacts on selector switch, 36 ua 3" meter. Dependable, rugged and accurate. Even the test leads are heavy duty with high voltage insulation. Voltage source required for low capacity range is 120V A.C. for high range capacity and inductance scale is 6V A.C. Attractive plastic front with metal bottom. Size $6\frac{1}{2}'' \times 4\frac{1}{2}'' \times 2\frac{1}{2}''$. Complete with batteries and leads. Shipping weight $4\frac{1}{2}$ lbs.

RW-30A

NET 19.25

3 TRANSISTOR SUPERHET POCKET RADIO KIT



- A TRULY POCKET SUPERHET RECEIVER NO EXTERNAL ANTENNA
- NO EXTERNAL SPEAKER

A remarkable sensitive, super-selective pocket superhet receiver with astonishing performance over the complete broadcast band. Uses 2 high-frequency and one audio transistor plus efficient diode detector and features 2 specially matched IF transformers for maximum power transfer. The components are housed in a professional looking beige plastic case.

The receiver's appearance enhanced by attractive maroon and silver station dial. Sensitive built-in ferrite antenna eliminates need for external antenna. A designer's dream in a true pocket superhet receiver! Complete with all parts, transistors battery, case, dial and easy to follow step-by-step instructions. $4\frac{1}{2}'' \times 2\frac{1}{2}'' \times 1\frac{1}{16}''$. Shpg. wt., 1 lb.

- KT-116—Complete Kit, less earphone. Net 16.95
- MS-260—Super Power Dynamic Earphone. Net 3.95

100 SIXTH AVE., NEW YORK, N. Y.
BOSTON, MASS., 110 Federal St.
PLAINFIELD, N. J., 139 West 2nd St.
NEWARK, N. J., 24 Central Ave.
BRONX, N. Y., 542 E. Fordham Rd.

DEPT RB-2

RADIO & TELEVISION NEWS

FREE! LAFAYETTE CATALOG



ELECTRONIC CATALOG PACKED WITH MONEY SAVERS

Packed with the largest selection of Electronic, Radio and T.V. Parts and equipment. PA, Hi-Fi systems, tubes, antennas, Transistor Kits, parts and components. Test Equipment, new build your own kits, tools, books, Microscope, drafting equipment, Binoculars, Telescopes, All Radio, TV and Ham supplies — ALL AT GREAT SAVINGS — For the economy minded servicemen, dealer, engineer and technician. **CHUCK FULL OF BUYS! SEND FOR YOUR FREE COPY TO-DAY.**

35 WATT HI-FI AMPLIFIER KIT WITH METERED OUTPUT AND 4 PUSH-PULL PARALLEL NEW EL84 TUBES

New Lafayette high power amplifier kit with a host of features not in any other single amplifier. Calibrated output meter permits use as either a recording or reproducing amplifier. EL84 power pentodes provide high peak power and low distortion required for better audio quality. Features exceptional control versatility and ample inputs for all associated custom hi-fi equipment. DC operated preamp filaments and balancing adjustment to minimize hum. Meter can be switched to indicate either recording voltage or output level of amplifier. Features rumble filter, loudness control, separate bass and treble controls, silencing switch, speaker selector switch, output balancing adjustment and monitoring jack.




SPECIFICATIONS

FREQUENCY RESPONSE: ± 1 db 20-20,000 cps. **HUM:** 85 db below rated output. **POWER OUTPUT:** 35 watts with 4% total distortion at full rated output. **INPUTS:** TV Sound, Radio, Magnetic Phono, Crystal Phono, Tape. **OUTPUT IMPEDANCE:** 4, 8 and 16 ohms; high impedance for tape recorder. **TUBE COMPLEMENT:** 3-12AX7, 1-12AU6, 4-EL84, 1-5U4. **FEEDBACK:** Negative feedback loops virtually eliminate distortion. **POWER:** 117V, 60 cps. 80/150 watts with auxiliary power receptacles. Removable screwdown. Size 12 1/2" L x 9 1/2" D x 4 1/2" H. A combination of high power, high fidelity, gleaming beauty and advanced engineering features unmatched at even twice the price. Supplied in complete kit form with simplified easy-to-follow instruction sheets. Shpg. wt., 25 lbs.

KT-115—Complete kit, Net 59.50
LA-66 completely wired Net 79.50

LAFAYETTE'S FM-AM TUNER KIT

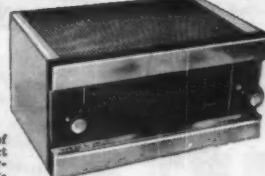- SIMPLIFIED DETAILED INSTRUCTION MANUAL
- MEETS FCC REQUIREMENTS FOR RADIATION
- GROUNDED GRID TRIODE AMPLIFIER
- ARMSTRONG FM CIRCUIT WITH FOSTER-SEELEY DISCRIMINATOR
- AFC DEFEAT CIRCUIT WITH FRONT PANEL CONTROL



The excellence of its design and the quality of its components combine to provide this compact high-fidelity FM-AM tuner with superb characteristics normally found in units costing several times as much, and with performance unbelievable at this low price. Features Armstrong FM circuit with limiter and Foster-Seeley discriminator. Simplified tuning with slide-rule dial and flywheel counterweighted mechanism. AFC defeat circuit combined with tuning control. Attractive etched copper-plated and lacquered finish.

SPECIFICATIONS

FREQUENCY RANGE: FM, 88-108 MC; AM, 530-1650 KC. **ANTENNA INPUT:** FM, 300 ohms; AM, Ferrite loopstick and high impedance external antenna. **CONTROLS:** 2—a function control for AM, FM, PHONO, TV and a tuning/AFC defeat control. **DISTORTION:** Less than 1% rated output. **FREQUENCY RESPONSE:** FM, ± 5 db 20 to 20,000 cps; AM, ± 3 db 50 to 5000 cps. **SENSITIVITY:** FM, 5 μ V for 30 db quieting; AM, Loop sensitivity 80 μ V/meter. **SELECTIVITY:** FM, 200 KC bandwidth, 6 db down — 375 KC FM discriminator peak to peak separation; AM, 8 KC bandwidth, 6 db down. **IMAGE REJECTION:** 30 db minimum. **HUM LEVEL:** 60 db below 100% modulation. **TUBE COMPLEMENT:** 2-12AT7, 1-6BA6, 1-6BE6, 2-6AU6, 1-6AL5 plus 1-6X4 rectifier. **SIZE:** 5 1/4" high x 9 1/2" wide x 9 1/2" deep (excluding knobs). **CONSUMPTION:** 30 watts. For 110-120V 60 cycles AC. Less metal case. Shpg. wt., 9 lbs.
KT-100 kit, less case Net 34.95
LT-10 — Completely wired, Less metal case Net 52.50
MT-100 — Metal cage for above, shpg. wt., 3 lbs. Net 5.00



LAFAYETTE MATCHED HIGH FIDELITY PHONO SYSTEM

**NOTHING
FINER AT
THIS PRICE!**

Reg. Value
~~158.55~~
SALE!
119.50

NEVER—in the annals of HIGH-FIDELITY has a phono system of this quality—at this price—been offered. A Lafayette "best buy" system designed around the new Lafayette LA-59 amplifier. The performance of this Phono system surpasses the most critical requirements of music lovers. Twenty-four combinations of record equalization provide an almost endless variety of tone compensation to match varying recording characteristics. This system includes the famous Garrard RC-121 "Renown" 3 speed automatic and manual record changer, LAFAYETTE LA-59 18 watt amplifier with features found only in the most expensive amplifiers, G.E. triple-play—turnover cartridges with genuine G.E. DIAMOND SAPPHIRE STYL, and LAFAYETTE 3K-58 12" coaxial Hi-Fi speaker. All units are supplied with plugs, jacks and prepared color-coded interconnecting cables for quick easy installation. For 110-125 volt, 60 cycle AC. Shpg. wt. 50 lbs.

MF-154—Complete Phono System Net 119.50

LAFAYETTE DELUXE FM-AM TUNER Completely Wired

- 2 1/4" Tuning Meter
- Armstrong FM Circuit—Foster-Seeley Discriminator
- Cathode Follower Output
- Tuned RF Stage



SPECIFICATIONS

FREQUENCY RANGE: FM, 88-108 MC; AM, 530-1650 Kc. **ANTENNA INPUT:** FM, 300 ohms; AM, Ferrite loopstick and low impedance external antenna. **FREQUENCY RESPONSE:** FM, $\pm 1/2$ db 20-20,000 cps; AM, ± 3 db 20-5,000 cps. **SENSITIVITY:** FM, 3 microvolts for 30 db quieting; 15 on AM. **HUM LEVEL:** 60 db below 100% modulation. **SELECTIVITY:** FM, 200 Kc bandwidth, 6 db down, 375 Kc FM discriminator peak to peak separation; AM, 8 Kc bandwidth, 6 db down. **IMAGE REJECTION:** 50 db. **DISTORTION:** Less than 1% at rated output. **OUTPUT LEVEL:** 3 volts for 100% modulation, 1 volt for 30% modulation. **TUBE COMPLEMENT:** 2-6AU6, 6BE6, 6AU6, 12AT7, 6AL5 and 6X4 rectifier. **POWER REQUIREMENTS:** 110-120 V, 60 cycle AC; 35 watts. Size: 4 1/4" H x 12 1/2" W x 9 1/4" D. Shpg. wt., 9 lbs.

LT-20 FM-AM Tuner, Including Federal Excise Tax, less cage Net 62.50
ML-110 Metal Cage for above. Shpg. wt., 3 lbs. Net 5.00

Lafayette Radio
DEPT RB-3 165-08 Liberty Ave.
JAMAICA 33, N. Y.

NAME _____
ADDRESS _____
CITY _____
ZONE _____
STATE _____

**SEND FREE
LAFAYETTE
CATALOG**

**CUT OUT
AND MAIL
TODAY!**



FIELD ENGINEERS:

HERE'S THE GOOD WORD—

Bendix Radio
IS CONTINUING ITS RAPID EXPANSION AND NEEDS YOU!

Bendix Radio, the leader in its field, has numerous, excellent opportunities for Field Engineering Personnel for both U.S. and overseas assignments. You will be responsible for the installation, overhaul and maintenance of long-range Bendix radar equipment.

ACT NOW! YOU'LL OBTAIN THESE IMPORTANT ADVANTAGES:

- ★ The prestige of representing the leader in its field.
- ★ Opportunity for professional development & advancement.
- ★ Excellent salary.
- ★ Overseas allowance.
- ★ Field allowance.
- ★ Relocation expenses.
- ★ Many other company benefits

It is preferable that you have had a minimum of two years college, plus at least four years engineering experience in radar or communications systems.

Send resume to: MR. O. A. BOWMAN
Field Engineering
Dept. R

Bendix Radio

DIVISION OF BENDIX AVIATION CORP.
BALTIMORE 4, MARYLAND



Portable 90-Degree CRT

(Continued from page 49)

picture tube's external coating. The 8XP4 has no external coating, so on receivers that require the capacitor, a 500- μ fd., 20-kv. capacitor may be connected from the high-voltage terminal on the receiver to chassis ground.

Housing the yoke and check tube in a small cabinet or box makes a handy test unit for mounting above the service bench or carrying along on service calls. Leads with battery or alligator clips connect the yoke to the yoke terminals in the receiver. The 8XP4 tube is self-focusing and without ion trap, so the service technician need not worry about focus or ion-trap adjustments. With this unit, all parts of the receiver chassis are readily available for servicing. There is no possibility of important parts on the chassis being covered by the picture tube, as is the case with vertical chassis. Because the picture tube need not be especially supported or braced, the chassis can be tilted to any position for repair.

On a few TV sets, it is actually easier to remove the picture tube from the chassis and leave the chassis in the cabinet. For a situation like this, the 8XP4 can be inserted in the chassis and still leave room for servicing. It's a good idea, therefore, to make a door on the box holding the 8XP4 tube and yoke so the tube can be removed for direct use.

While the 8XP4 will work satisfactorily for the deflection system in nearly any receiver, it is particularly useful in 90-degree systems, especially where such deflection-circuit problems as width and linearity are under examination. In such 90-degree systems, therefore, it has broader application than its useful companion and forerunner.

Like its predecessor, however, this CRT is subject to development of a small dark area—ion burn—at the center of the faceplate. This spot will not impair the usefulness of the 8XP4 in its intended application or shorten its life. The use of low brightness settings will retard this burn. —50—

PICTURE FLICKER

By JAMES A. McROBERTS

WHEN the volume control was advanced on the Sylvania Chassis 1-504, a flicker was noted in the picture with any loud passage of the sound. Some slight evidence of a hum bar was present on the picture and even more so on the plain raster.

The presence of the hum bar suggested improper filtering of the "B+" to the video or the video i.f. stages. This coupled with the symptom of flicker caused by loud sounds pointed to the common feature of trouble in the sound "B" supply.

Bridging capacitor C_{111} , a 40 μ fd. unit, eliminated the hum bar and sound interference. Replacing C_{111} (the "B+" bypass of the audio amplifier output stage) proved to be the permanent remedy. —50—

Another Sencore Time-Saver

SENCORE TUBE and CAPACITOR LEAKAGE CHECKER

A MUST FOR SERVICING GRID CIRCUITS

A highly accurate tester for detecting leakage between tube elements.

MODEL LC-2

A reliable instrument for indicating capacitor leakage with 50 volts applied. Quickly indicates • Grid to cathode leakage • Grid emission • Heater to cathode leakage • Gassy tubes.

Only \$24.95
DEALER NET KIT — \$19.95

"Two Testers in One"

Checks 70 Critical Tube Types AT LEADING DISTRIBUTORS EVERYWHERE

Mfg by **SENCORE SERVICE INSTRUMENTS CORP.**
(formerly SENCOR)
171 OFFICIAL RD., ADDISON, ILL.

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

Rauland

'Golden Series' HI-FI

The "GOLDEN GATE" AM-FM Tuner...with an FM sensitivity of 3 microvolts for 20 db of quieting—and a host of other remarkable features...

one of a complete line of advanced design high fidelity tuners, amplifiers and components...


hear these quality RAULAND units at your HI-FI dealer or write for details...

RAULAND-BORG CORPORATION
3515 W. Addison St., Dept. T, Chicago 18, Ill.

Superior's New Model 670-A

SUPER-METER

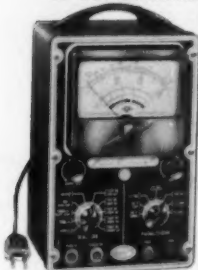A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY, REACTANCE, INDUCTANCE AND DECIBEL MEASUREMENTS.



ADDED FEATURE:
Built in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.

SPECIFICATIONS

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms

CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Good-Bad scale for checking quality of electrolytic condensers.)

REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms

INDUCTANCE: .15 to 7 Henries 7 Henries to 7,000 Henries

DECIBELS: -6 to +18 +14 to +38 +34 to +58

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions.

\$28 40
NET

Superior's New Streamlined Model TD-55

TUBE TESTER

FOR The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester.
The Professional Serviceman, who needs an extra Tube Tester for outside calls.
The Busy TV Service Organization, which needs extra Tube Testers for its field men.



Speedy, yet efficient operation is accomplished by: 1. Simplification of all switching and controls. 2. Elimination of old style sockets used for testing obsolete tubes (28, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minor types.

CHECKS FOR SHORTS AND LEAKAGES BETWEEN ALL ELEMENTS - Model TD-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. **"FREE-POINT" ELEMENT SWITCHING SYSTEM** - Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap." **ELEMENTAL SWITCHES ARE NUMBERED IN STRICT ACCORDANCE WITH R.M.A. SPECIFICATION** - The 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Model TD-55 comes complete with operating instructions and charts. Housed in rugged steel cabinet. Use it on the bench - use it for field calls. A streamlined carrying case, included at no extra charge, accommodates the tester and book of instructions.

\$26 95
NET

Superior's New Model TV-60

20,000 OHMS PER VOLT

ALL METER

SPECIFICATIONS

8 D.C. VOLTAGE RANGES (At a sensitivity of 20,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500/30,000 Volts.
7 A.C. VOLTAGE RANGES: (At a sensitivity of 5,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500 Volts.
3 RESISTANCE RANGES: 0 to 2,000/200,000 Ohms. 0-20 Megohms.
2 CAPACITY RANGES: .00025 Mfd. to 30 Mfd.
5 D.C. CURRENT RANGES: 0-75 Microamperes, 0 to 7.5/75/750 Milliampers, 0 to 15 Amperes.
3 DECIBEL RANGES: -6 db to +58 db.
R.F. SIGNAL TRACER SERVICE: Enables following the R.F. signal from the antenna to speaker of any radio or TV receiver and using that signal as a basis of measurement to first isolate the faulty stage and finally the component or circuit condition causing the trouble.



AUDIO SIGNAL TRACER SERVICE: Functions in the same manner as the R.F. Signal Tracing service specified at right except that it is used for the location of cause of trouble in all audio and amplifier systems.

FEATURES

Giant recessed 6 1/2 inch 40 Microampere meter with mirrored scale. Built-in Isolation Transformer. Use of the latest type printed circuit and 1% multipliers assure unchanging accurate readings.

Model TV-60 comes complete with book of instructions; pair of standard test leads; high-voltage probe; detachable line cord; R.F. Signal Tracer Probe and Audio Signal Tracer Probe. Plug-in bag for all above accessories is also included. Price complete. Nothing else to buy. ONLY

\$52 50
NET

Superior's new Model TW-11 STANDARD PROFESSIONAL

TUBE TESTER



• Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Sub-Minors, Proximity fuse types, etc. • Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary. • The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. • Free-moving

built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

• **NOISE TEST:** Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

• **SEPARATE SCALE FOR LOW-CURRENT TUBES**-Previously, on standard emission type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the standard scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

\$47 50
NET

SHIPPED ON APPROVAL NO MONEY WITH ORDER - NO C.O.D.

We invite you to try before you buy any of the models described on this and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate. (See other side for time-payment schedule details.)

**NO INTEREST
OR FINANCE
CHARGES ADDED!**

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

SEE OTHER SIDE!
Cut out and mail TODAY! ▶

All prices net, F.O.B., N.Y.C.

FIRST CLASS

Permit No. 61430

New York, N. Y.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the U. S.

VIA AIR MAIL

POSTAGE WILL BE PAID BY -

MOSS ELECTRONIC DIST. CO., INC.

3849 TENTH AVENUE

NEW YORK 34, N. Y.

Superior's
New
Model

76

For the first time ever: ONE TESTER PROVIDES ALL THE SERVICES LISTED BELOW!



IT'S A CONDENSER BRIDGE

with a range of .00001 Microfarad to 1000 Microfarads (Measures power factor and leakage too.)

IT'S A SIGNAL TRACER

which will enable you to trace the signal from antenna to speaker of all receivers and to finally pinpoint the exact cause of trouble whether it be a part or circuit defect.

IT'S A RESISTANCE BRIDGE

with a range of 100 ohms to 5 megohms

IT'S A TV ANTENNA TESTER

The TV Antenna Tester section is used first to determine if a "break" exists in the TV antenna and if a break does exist the specific point (in feet from set) where it is.

SPECIFICATIONS

✓ RESISTANCE BRIDGE SECTION

2 Ranges: 100 ohms to 50,000 ohms; 10,000 ohms to 5 megohms. Resistance can be measured without disconnecting capacitor connected across it. (Except, of course, when the R C combination is part of an R C bank.)

As Design Engineers, we the undersigned would like to say that the Model 76 is in our opinion the best combination unit of its kind we have been privileged to design. Although it is comparatively a low-priced tester, it will, after you become acquainted with its multiple services, be your most frequently used instrument.

S. LITT
L. MELENKEVITZ

✓ CAPACITY BRIDGE SECTION

4 Ranges: .00001 Microfarad to .005 Microfarad; .001 Microfarad to .5 Microfarad; .1 Microfarad to 50 Microfarads; 20 Microfarads to 1000 Microfarads. This section will also locate shorts, and leakages up to 20 megohms. And finally, this section will measure the power factor of all condensers from .1 to 1000 Microfarads. (Power factor is the ability of a condenser to retain a charge and thereby filter efficiently.)

✓ SIGNAL TRACER SECTION


A built-in high gain pentode voltage amplifier, plus a diode rectifier, plus a direct coupled triode amplifier are combined to provide this highly sensitive signal tracing service. With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc. Provision has been made for use of phones and meter if desired.

✓ TV ANTENNA TESTER SECTION

Loss of sync., snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? The Model 76 will enable you to locate a break in any TV antenna and if a break does exist, the Model 76 will measure the location of the break in feet from the set terminals. 2 Ranges: 2' to 200' for 72 ohm coax and 2' to 250' for 300 ohm ribbon.

Model 76 comes complete with all accessories including R.F. and A.F. Probes; Test Leads and operating instructions. Nothing else to buy Only

\$26⁹⁵
NET

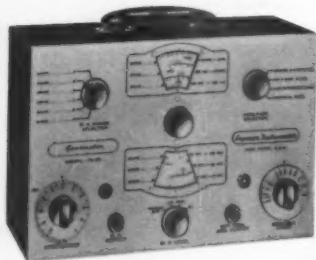

Superior's New Model TV-50

GENOMETER

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:
A. M. Radio • F. M. Radio • Amplifiers • Black and White TV • Color TV

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator

- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

R. F. SIGNAL GENERATOR: Provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

CROSS HATCH GENERATOR: Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.

BAR GENERATOR: Projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

MODEL TV-50 comes absolutely complete with shielded leads and operating instructions. Only

\$47⁵⁰
NET

MARKER GENERATOR: The following markers are provided: 189 Kc., 252.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.)

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C.O.D.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-311 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance or interest charges added. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- | | |
|--|--|
| <input type="checkbox"/> Model TD-55..... Total Price \$36.95
\$6.95 within 10 days. Balance \$3.00
monthly for 4 months. | <input type="checkbox"/> Model TV-50..... Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months. |
| <input type="checkbox"/> Model TV-60..... Total Price \$52.50
\$12.50 within 10 days. Balance \$8.00
monthly for 5 months. | <input type="checkbox"/> Model 670-A..... Total Price \$28.48
\$7.48 within 10 days. Balance \$3.50
monthly for 6 months. |
| <input type="checkbox"/> Model TW-11..... Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months. | <input type="checkbox"/> Model 76..... Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00
monthly for 4 months. |

Name.....
Address.....
City..... Zone..... State.....

All prices net, F.O.B., N.Y.C.

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

SEE OTHER SIDE!

➤ Cut out and mail TODAY!

'56 G-E TV: Many Symptoms-One Cause

By LLOYD B. HUST

A single bad connection causes several different defects in various sets.

CHASSIS in the G-E "ST" line tend to suffer from a fault that shows up in many different and puzzling ways. Knowing about it in advance may save considerable time spent in troubleshooting, as it is not otherwise likely to be suspected as the cause.

The symptoms noted here which may occur as a result of this single defect are by no means a complete list. On one set, it appeared as though the picture tube were at fault, with low emission as the chief symptom. On another set, the fault manifested itself mainly as sync trouble. In yet another case, the high-voltage section of the receiver seemed involved, as there was severe raster blooming. In one, the video circuits appeared to be involved, with a very snowy picture resulting. In most cases, the set plays best when first turned on, with the trouble becoming worse after warm-up.

On all of these sets, the trouble was traced to one point—a poor ground connection at the point where the filament leads from the power transformer are grounded to the chassis. This defective grounding would affect some tubes more than others on the various sets, since not all tube filaments are returned to ground in exactly the same way.

The cure for this condition is obvious—make a good ground connection between the chassis and the transformer leads which should be grounded. On this set, these leads are soldered to a terminal which is riveted to the chassis. Heat seems to develop at this point, and the result is oxidation of the area around the rivet as well as on the surface of the rivet itself.

To make a good connection, first clean the chassis and the rivet, then flow a good grade of solder all around the junction with plenty of heat. Let the solder flow in and around the rivet. At the same time, it is a good idea, while the job is under way, to re-solder other transformer heater leads to their respective terminals.

So much time was spent in localizing this trouble in the different sets with different symptoms that now, on every set of this series that comes into the shop, the writer solders these connections as a matter of routine. On many, this procedure has saved time by immediately curing the complaint on which the set was brought in, thus eliminating the need for further testing. The practice has paid off. —30—

February, 1957

\$100,000

Hi-Lo is covered by a \$100,000.00 insurance policy issued by one of the largest insurance companies.*

GUARANTEED PERFORMANCE

Each and every Hi-Lo is backed by a money back guarantee. For the best reception, unsurpassed clear pictures, specify Hi-Lo, with the exclusive highest gain, spiral designs which are covered by the following U.S. patent numbers: 2,495,579; 2,583,745; 2,724,773; 2,748,387; 2,755,466; and Canadian Patents 1951 and 1956; other patents pending.

**New...
Just what
you asked
for!**




Hi-Lo Model 505 — Channels 2-83
The spiral antenna that is designed for maximum performance featuring the NEW TELESCOPING DIPOLES. This versatile antenna swivels on ball and socket in any direction. Gold spirals, plastic base blend with any room. LIST... \$14.95

**New...
For every
TV
owner**



Hi-Lo Model 404 Channels — 2-83.
NEW INDOOR ANTENNA
that swivels with a gentle touch of your little finger. Dipoles swivel on ball and socket in every direction. Golden spirals and decorative plastic base blend with all furniture. RECEPTION IS GUARANTEED. LIST... \$12.95


*name upon request

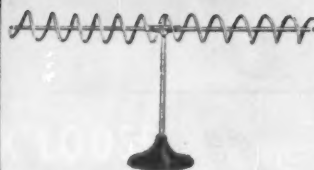

Hi-Lo Model 101 — Channels 2-13.
The original and world famous antenna that is wanted, demanded and used for GUARANTEED FINEST RECEPTION. No rods to adjust. Provides clear-est pictures faster. LIST... \$9.95



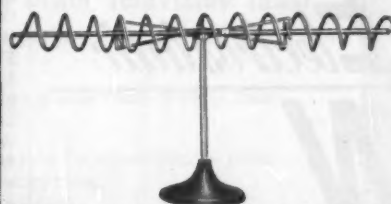Hi-Lo Model 303 — Channels 14-83.
The UHF ANTENNA with the highest signal gain that is specially designed for ALL UHF areas. Luxurious gold upright and crossbar. LIST... \$5.95



Hi-Lo Model 202 — Channels 2-83
PEAK PERFORMANCE which is unsurpassed is guaranteed with this antenna... for ANY and EVERY area. The gleaming gold upright, shiny spirals, bakelite base, aluminum bars, modern design

... all make this YOUR BEST ANTENNA BUY.

LIST... \$9.95

INSIST ON THE GENUINE Hi-Lo Spiral Antennas!

Known and accepted everywhere, Hi-Lo is manufactured and GUARANTEED by the best antenna manufacturer in the world. Hi-Lo is consumer accepted and approved.

Hi-Lo

TV ANTENNA CORP.
3540 North Ravenswood Avenue
Chicago 13, Illinois

The Most Nearly Perfect Loudspeaker Ever Made —Period!

J A N S Z E N

JANSZEN
PRODUCT OF
NESHAMINY ELECTRONIC CORP.
NESHAMINY, PA.
Export Division: 25 Warren St., N. Y., 7
Cable: Simonrice, N. Y.

Common-Sense Service (Continued from page 59)

positive, we can be sure that leakage is taking place through the capacitor. Other clues can be obtained by removing a tube from its socket. Assuming that the tube is the only component in a given circuit through which current can be drawn, as is usually the case, there should be no current and therefore no voltage drop across plate and screen resistors with the tube out of its socket. This means that plate and screen voltages should rise to the full value of their "B+" source. If this action is not observed, further checking is indicated in the components of the tube's associated circuit.

Series-string filament chassis need not be excluded from this type of test. Even with a tube removed, thus opening the filament continuity, voltages hold up long enough (thirty seconds to two minutes) to permit a check.


Parts Replacement

The replacement of a power transformer, a can-type filter, a concentric control, or an i.f. transformer is a time-consuming, often tedious project due to the usual maze of wires and attached small parts on terminals or tie points. However, much of the time can be saved and heat damage prevented by cutting out some steps.

For instance, when replacing power transformers, many technicians will patiently tag for identification each and every wire and tie point to which the replacement is to be connected. But if a technician knows his business, is this multiple tagging really necessary? Or is it only that that is the way he has always done it?

For, when he unsolders the wires coming from the defective power transformer, it should be obvious to the technician what function each has. For example, transformer wires going to pins 4 and 6 of the 5U4 rectifier are high-voltage plates; pins 2 and 8 are 5U4 5-volt filament connections; one wire of the 6.3 filament secondary goes to pins 2 or 7 of most octal tubes with the other going to ground or chassis, etc. It does not take much to see

Fig. 8. This cathode-coupled multivibrator is an example of a circuit where the leakage voltage through a defective capacitor might be disguised by stage operation. Killing the stage by withdrawing the tube permits useful readings.

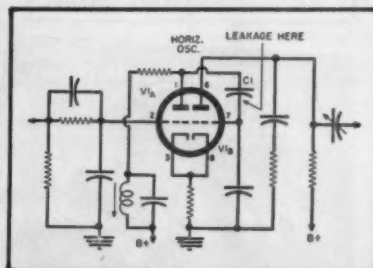

BUTTONS AND BOWS BELL TELEPHONE'S CARBON MICROPHONE

We take a bow for this button at only 49¢. We don't have to tell you about the quality of a WESTERN ELECTRIC P1 MICROPHONE UNICARB because you hear it every time you answer your telephone. Its response curve was worked out at Bell Labs for maximum speech clarity. It is "big" in diameter, so it catches lots of air waves and puts out lots of decibels, yet it fits just right in the palm of your hand. Hermetically sealed. Solder a wire to each of its two silver-plated contacts (ring and center) and connect in series with a switch, two flashlight batteries, and the 50 to 100 ohm primary of any grid input transformer. Or tickle an audio transistor with it. Shpg. wt. 1/2 lb.

Cat. 115MC10RN. Only..... **49¢**
Get 10 of them still cheaper. Ask for..... **\$3.95**
Cat. 408MC10RN. Ten for only..... **\$3.95**
MIKE-TO-GRID Transformer for above. Shpg. wt. 1/2 lb.

Cat. 150TR22RN. Only..... **79¢**
CD-508 MIKE CORD 5' lg with 3-circuit mike plug PL-66 and hand-held press-to-talk switch with hanger hook. Mount the P1 button on the switch molding and you have it made. Shpg. wt. 1 lb. **99¢**
Cat. 108CCRN. Only..... **49¢**
If you have a PL-66 or won't use a plug, buy the above less the PL-66.

Cat. 150K1RN. Only..... **49¢**
SC-709 IS A CARBON-MIKE AMPLIFIER, complete in compact aluminum box, with mike input xfrmr, instant-heating 384 tube, 2 jacks for PL-66, output xfrmr to high-impedance headphones or lines, new and ready to use. Has holders for 2 flashlight cells and for a 67 1/2 V battery. Shpg. wt. 3 lbs. **\$2.95**
Cat. 308AX1RN. Only..... **\$2.95**
67 1/2 V BATTERY, guaranteed good and fresh, priced \$1.00 under any U.S. make. Shpg. wt. 1 lb. **\$1.85**
Cat. 2088A1RN. Only..... **\$1.85**

RECEIVER: 46ACJ has double-conversion. Uses 13 tubes. Three 446-A Lighthouse Tubes tune 450-600 mc, and you retune only the converter. We give schematic and instructions. First IF of 55 mc is amplified in 2 stages. Second IF of 16 mc has 4 stages. Detector is followed by two stages. Brand new. Includes 8-6AC7, 3-446A, 1-6AG7, 1-6H6. Only..... **\$9.95**
If you have lots of 6AC7's get it less these only **\$1.00**

TRANSMITTER: 30 WATT Transmitter..... **\$6.95**
4-8025, 2 as 250-385 mc P-P osc. driving the other two as PA. The PA is grid modulated by a 3-tube video ampli. and plate-mod by a 3-tube sync ampli. New with all tubes, schematic and instructions for easy conversion to 420. Only..... **\$18.75**
COME, DEAL! Rev & Xmt. new, with tubes, both for only..... **\$23.50**

FREE! Big Bargain Catalog!
Send for your copy.

All shpts. FOB whse. Send 25¢ dep. with all CDS orders. Item sub. to prior sale & change of price without notice. Min. order \$2.50.

ARROW SALES, INC.

Western Mailing Address:
Box 30078 NORTH HOLLYWOOD, CALIF.
Central Mailing Address & Sales-Showroom
2441 S. WICH. AV., Dept. R., CHICAGO 16, ILL.
California Distributors:
G. L. Electronics, Inc., 1632 Venice, Los Angeles
P.A.R.T.S., Inc., 2005 Empire Ave., Burbank

THE BEST TV BUSINESS BUILDER



Your Own
TV
Magazine
at
Surprisingly
Low Cost

YOUR NAME Appears on all 4
Covers! Front, Back and Inside!

EACH MONTH TV TREND BRINGS:

- 3 Pages of well-illustrated, hard-hitting TV Sales and Service advertising—with plenty of space for any special message of your own.
- Original TV feature articles.
- Highlights of outstanding programs of the coming month, which keep the magazine in the home for 30 days.
- Double-Page Photo of a popular TV Star, ideal for scrapbooks.

ALL EXCLUSIVELY YOURS
IN YOUR TERRITORY!

MAIL COUPON NOW—
For Full Particulars

TV TREND,
4950-R Marine Drive, Chicago 40, Ill.

Without any obligation on my part, please rush sample copy and full particulars on how I can have my own TV business building magazine.

Name.....
Firm.....
Address.....
City & State.....
(Please print clearly)

RADIO & TELEVISION NEWS

what the function of each wire is just by where it connects.

The practical and sensible way for an experienced technician to replace power transformers is this: Cut each wire coming from the old transformer, leaving about a two-inch stub of wire on each pin or tie point to which it connects. Raise these stubs upright so that they will be easy to locate later on.

Tag nothing! Slip out the old transformer and mount the new one. If it is an exact-brand replacement, its color coding will be the same so that no special effort is needed to match leads. If it is a commercial replacement, it will be supplied with a chart identifying the function and color coding of each wire.

Hook up the easiest and more obvious windings first, such as the four 5U4 connections, the two from the a.c. primary, and the two or three that go to ground (check with the schematic). The destination of the two or three remaining wires, if not immediately obvious, require but little tracing. Clip off each stub of wire remaining from the original transformer as each new wire is installed. This may at first appear to be a reckless system. After a technician tries it once he may wonder why he had ever bothered to tag eight or ten wires when all along he knew exactly where they should go.

The tagging of wires or the sketching of an involved wire color code and layout diagram is a common sight, too, when many technicians replace concentric controls, can-type filters, and even some i.f. transformers. These components have multiple wires and small parts attached to their terminals, making it confusing to wire in new units. Some technicians will unsolder each wire and small part, usually melting the plastic wire insulation and occasionally breaking the lead off a resistor or capacitor in the process. And they may patiently tag each wire and small part or make a diagram for identification. But the practical and direct approach is not to remove all wires and parts from their terminals and ground lugs. Instead, *remove the terminals* with all their wiring intact and undamaged. Just clip them off the old units, which are being discarded anyhow. You can cut off these terminals with a pair of diagonal cutters and leave each one in its relative position. Install the new unit and simply sweat-solder each old terminal to the corresponding one on the replacement part.

Where it may require twenty to thirty minutes to replace a concentric control, with this method the job can be finished neatly, without wire insulation damage, in less than five minutes.

There is probably no end to the number of direct-approach servicing and replacement techniques that are in use today. Few technicians can afford to ignore all of the satisfactory and time-saving results achieved with them.

—50—

February, 1957

WHEN STORMS BREAK LOOSE PERMA-TUBE STAYS UP

... and so does your reputation!

J & L
M

Look for this brand mark
—only genuine Perma-Tube
gives you this protection.

Here's why ... sturdy steel PERMA-TUBE is stronger than any other television mast

1. Its resistance to bending is *five times stronger* than structural aluminum.
2. Its resistance to deflection is *three times stronger* than structural aluminum.
3. Its resistance to destruction by wind-force is *twice as strong* as structural aluminum.

ADDITIONAL REASONS FOR USING PERMA-TUBE EVERY TIME

PERMA-TUBE IS CORROSION PROOF... it's treated with vinsynite—then coated *inside and outside* with a metallic vinyl resin base.

PERMA-TUBE IS EASILY INSTALLED... it's the *only mast* with *both ends* of the joint machine fitted.

ONLY GENUINE PERMA-TUBE GIVES THIS PROTECTION AND SERVICE... look for this brand mark... accept no claims from substitute materials.



For complete information and scientific data write to: Jones and Laughlin Steel Corporation, Department 495, 3 Gateway Center, Pittsburgh 30, Pa.

Jones & Laughlin
STEEL CORPORATION • PITTSBURGH

AMERICA'S FINEST VALUES IN "LOW COST" HIGH FIDELITY

ECONOMY 20 WATT AMPLIFIER \$22.95

\$24.95

Push-Pull 6L6 Output Tubes
Response 30-15,000 cps
Bass and Treble Tone Controls
Input for Xtal or Dynamic Mike
Input for Xtal or V. R. Phono

A tremendous High Fidelity amplifier value. Response 30 to 15,000 cps. Electronic bass and treble boost by separate tone controls. Use this amplifier with any record changer having crystal or variable reluctance cartridge, radio tuner or high impedance crystal or dynamic microphone. 30-watts power output. Use with any 8-ohm speaker. Chassis size 7 1/2" x 10 1/2" x 7 1/2". High. Complete with tubes: 2-6X4, 2-6C4, 12AX7 and 5046. This is a terrific value. A ready to use High Fidelity amplifier at less than the cost of a kit. Model HF-21, 20-watt Hi-Fi amplifier. Sale Price \$24.95.

Model HF-21
NEW IMPORTED MONARCH HIGH FIDELITY AUTOMATIC CHANGER

WITH RONETTE #222 HI-FI turn-over crystal cartridge with separate sapphire needles.

SALE PRICE \$27.95

Monarch Model UAS new imported high fidelity 4-speed automatic record changer, size 10 1/2" x 12 1/2". Plays 7", 10" and 12" records automatically. Interchange records of the same speed in any order. Features a 4-pole high fidelity motor eliminating rumble and wow. 9" turntable with high fidelity rubber molded cushion dynamically balanced. Counter balance tone arm with adjustable weight to any desired cartridge—adaptable for O.E. cartridge. Ship. wt. 15 lbs. Model UAS Monarch automatic record changer with Ronette No. 222 crystal cartridge. Price \$29.95. With Goldring No. 500 Var. Rel. cartridge—Sale Price \$29.95. 45 rpm spindle, \$1.95 extra.


12" COAXIAL PM SPEAKER
RESPONSE 25-17,000 CPS
\$9.95

Model 12X3Y, new 1957 12" Coaxial PM Speaker. has high efficiency 12" woofer with Alnico V magnet and coaxially suspended 3 1/2" Alnico V tweeter. Built-in crossover with variable brilliance control on an 18" lead for remote control of the tweeter volume. 10-watts, response 25 to 17,000 cps. Ship. wt. 12 lbs. Model 12X3Y, 12" coaxial PM Speaker. Sale Price \$9.95.

SPECIAL MONEY SAVING COMBINATION PACKAGE DEAL

Model HF-21, 20-watt Hi-Fi Amplifier.
 Model UAS, MONARCH Hi-Fi Automatic Changer, and
 Model 12X3Y, 12" Coaxial PM Speaker as described above.

SPECIAL PRICE \$59.95

3-1957 MODEL HI-FI SPEAKERS
• COMPLETE SYSTEMS WITH 4 SPEAKERS
• ACOUSTICALLY LINED ENCLOSURES

The new 1957 Hollywood, 4 speaker high fidelity speaker systems are expressly designed to give realistic reproduction from your Hi-Fi amplifier or FM radio. Juke box bass response with brilliant, middle and high range response. All 3 models have general LC crossover networks and variable brilliance controls. Only 2 wires to connect to the 4 or 8 ohm tap on your Hi-Fi amplifier. A fine speaker system to use with our Imperial 20, 30 and 34 high fidelity amplifiers, and all FM-AM chassis in our Radio & TV News offerings. Adjusting the twin tone controls on our Imperial amplifiers along with the brilliance control on the Hollywood speaker systems you can have fidelity of your own personal taste. All 3 Hollywood models are housed in the same fine cabinet. Choice of either blond or mahogany finishes. Baffles are fully enclosed and acoustically lined. Small enough in size for the average room, yet large enough for proper baffling. 25" high, 19" front to back, 35" wide. Specify cabinet finish when ordering, otherwise we will ship mahogany finish. Take \$3.00 discount when you order with any of the Imperial amplifiers or Espey FM-AM chassis offered in this 3 page ad.

Model M-4H, Hollywood 4 speaker high fidelity speaker system. 30 watts, response 30 to 17,500 cps. Choice of blond or mahogany finish enclosure. Features a 12" General Electric 6.8 ohm Alnico V magnet, aluminum voice coil woofer, plus 6" mid-range and 2-5" tweeters. Built-in variable brilliance LC crossover network. Model M-4H. Ship. wt. 55 lbs. Price \$39.95.

Model Y-4Y, Hollywood 4 speaker high fidelity speaker system. 35 watts, response 30 to 17,500 cps. Choice of blond or mahogany finish enclosure. Features a 12" General Electric 6.8 ohm Alnico V magnet, aluminum voice coil woofer, plus 6" mid-range and 2-5" tweeters. Built-in variable brilliance LC crossover network. Model Y-4Y. Ship. wt. 55 lbs. Sale price, \$44.95.

Model Z-4Z, Hollywood 4 speaker high fidelity speaker system. 25 watts, response 30 to 17,500 cps. Choice of blond or mahogany finish enclosure. Features a 12" General Electric 6.8 ohm Alnico V magnet, aluminum voice coil woofer, plus 6" mid-range and 2-5" tweeters. Built-in variable brilliance LC crossover network. Model Z-4Z. Ship. wt. 57 lbs. Sale price, \$49.95.

NEW IMPERIAL SPEAKER SYSTEMS

Imperial IV with 8" G.E. High Fidelity Speaker
\$19.95

3-Way Imperial VI with 12" G.E. Speaker
\$29.95

New 1957 Model IMPERIAL IV, High fidelity speaker system with General Electric 8" speaker. Housed in a high quality leatherette covered plywood cabinet 10" x 10" x 10 1/2" deep. Fully enclosed, covered on all sides except back. Use as an auxiliary speaker or with any high fidelity radio, amplifier or home music system. The IMPERIAL IV contains a General Electric Model 950 or 9770 Motorola 8" extended range high fidelity 8" PM speaker and 6.8 ohm Alnico V magnet and 6.8 ohm voice coil and a 5" tweeter. Response 30 to 15,000 cps. Model IV Imperial \$19.95.

1957 Model Imperial VI, 3-way speaker system. Baffle is of heavy wood, leatherette covered. Similar in appearance to the Imperial IV pictured above, except 4" taller and 1" deeper. Equipped with 3 matched speakers. A 12" G.E. Model 1203 with 6.8 ohm Alnico V magnet, plus 5 1/2" PM for middle range and 2" tweeter. Simple to connect to any high fidelity amplifier. (8 ohms impedance). Stock No. IMP-VI, Sale price, \$29.95. Ideal for use with HF-20 and IMP-30 amplifiers described above.

THEATER QUALITY HIGH FIDELITY SPEAKER SYSTEM \$39.95
15" WOOFER PLUS—ELECTROVOICE MODEL B47
MID-HIGH RANGE SPEAKER—600 CYCLE LC CROSSOVER.

A theatre quality, powerful speaker system for homes and sound demonstration rooms. This speaker arrangement will connect to any high fidelity audio amplifier (8 ohms impedance) Features a 15" electro-dynamic heavy duty woofer which is equal to a PM speaker with up to 50 lbs. of Alnico V magnet. This woofer reproduces the low audio register from 600 cycles down to 20 cps. An Electro-Voice Model B47 horn type speaker is used for the middle range and high range of audio. These two speakers are connected to a 600 cycle inductive-capacity crossover network. Built in the network is the field exciter for the 15" woofer. You would spend over \$100 for a speaker system and not beat this one. Stock No. EV-15047A, McGee's sale price, \$39.95.

McGEE RADIO COMPANY

PRICES F.O.B. KANSAS CITY
 SEND 25% OR FULL
 REMITTANCE WITH ORDER.
 BAL. SENT C.O.D.

TELEPHONE VICTOR 2-5092
 1903 McGEE ST., KANSAS CITY, MISSOURI

NEW 1957 MODEL

Push-Pull 6L6 Output Tubes
Response 15-20,000 CPS
Bass and Treble Tone Controls
Compensated Gain for G.E. Carl.
Input for Xtal or Dynamic Mike

With CU-14Y, 12" Coax Speaker. \$39.95


With P15-CR, 15" Coax Speaker. \$49.95

With Imperial IV Speaker System. \$46.95

With Imperial VI. \$55.95

With HF-33GE. \$76.95

New 1957 model 7 tube Imperial 30 watt High Fidelity audio amplifier. A \$100.00 list value for only \$39.95. Features a heavy 4 lb. specially wound high fidelity output transformer with 15% inverse feedback; push-pull 6L6 output tubes and frequency response from 15 to 20,000 cps. Matches 8 or 16 ohm speakers. You can center your entire custom music system around this low cost 30 watt amplifier. This Imperial 30, 30 watt amplifier may be used with any radio tuner or record player. It will drive any speaker system that you may have. Use from one to ten 8" speakers or any 12" or 15" coaxial speaker or any 3-way speaker system. Tone compensated input for either a crystal phone pickup or a dynamic microphone. A reluctance pickup. Also, has input for crystal or high impedance dynamic microphone. 4 controls are mix gain, phone gain, treble tone and bass boost tone control. The amplifier weighs 21 lbs. The transformer components would cost you up to \$18.00 if purchased separately. Gold color chassis is 12 1/2" x 7 1/2" x 7 1/2" high. Complete with 7 tubes and diagram. Model IMP-30, 30 watt high fidelity amplifier. Stock No. IMP-30, 30 watt Imperial High-Fidelity amplifier complete with tubes and diagram. Ship. wt. 23 lbs. Sale price only \$39.95.

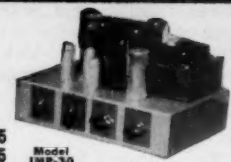
Model IMP-30
NEW IMPERIAL 24 WATT AMPLIFIER \$39.95

PUSH-PULL EL-34 ENGLISH MADE MULLARD OUTPUT TUBES

WILLIAMSON TYPE CIRCUIT

RESPONSE 15-20,000 CPS

With CU-14Y, 12" Coax Speaker. \$49.95

With P15-CR, 15" Coax Speaker. \$59.95

With Imperial IV Speaker System. \$56.95

With SP1215CR. \$65.95. With HF-33GE. \$86.95. Model IMP-34X

1957 model Imperial 24, 24 watt high fidelity amplifier for the audio enthusiast who want McGee's finest amplifier. This amplifier features push-pull EL-34 English made Mullard output tubes in a Williamson circuit. Heavy duty 6 lb. specially wound Mullard output transformer in potted case has a response from 15 to 20,000 cps. Matches 8 or 16 ohm speakers. Amplifier has input for crystal pickup and built-in pre-amplifier for the popular General Electric and Goldring variable reluctance cartridges; as well as input for crystal or high impedance dynamic microphones. 4 controls are microphone gain, phone gain and separate variable treble and bass boost tone control with off-on switch. Chassis size 12 1/2" x 7 1/2" x 7 1/2" high. Complete with 7 tubes and diagram. Model IMP-24X, 24 watt high fidelity amplifier, ideal for use with any of our high fidelity coaxial or multiple speaker systems. Ship. wt. 26 lbs. Sale price, \$39.95.


McGEE'S NEW 1957 MODEL
25 WATT 12" COAXIAL SPEAKER

★ 14 1/2 oz. G.E. 12" WOOFER—
 ★ 3 1/2" COAXIALLY SUSPENDED TWEETER—
 ★ BUILT-IN CROSSOVER—
 ★ ALUMINUM VOICE COIL WOOFER—
\$18.95

McGee's new 1957 model, GE-120XT, 12" 25 watt high fidelity coaxial PM speaker. No frills or dummy pot cover. It's a speaker value. Features a General Electric 12", 14 1/2 oz. Alnico V woofer with aluminum voice coil and exponential, milled scandium cone. The tweeter is a specially made 1.47 oz. Alnico V, 3 1/2" speaker which accept only the upper register of audio. It is electrically connected to the tweeter input of the amplifier. Only two wires connect this complete high fidelity speaker to any 8 ohm amplifier. Ship. wt. 8 lbs. Stock No. GE-120XT. McGee's sale price, \$18.95. New 1957 model, 20 watt coaxial 12" coaxial PM speaker. Only 2 wires to connect to any 8 ohm Hi-Fi radio or amplifier. Features an aluminum voice coil General Electric 12" PM speaker with 16 oz. Alnico V magnet, plus a coaxially suspended built-in tweeter. Responds up to 17,500 cps. Ship. wt. 8 lbs. Sale price, \$14.95.

TREMENDOUS McGEE VALUE
NEW 1957 HI-FI SPEAKER SYSTEMS ON BAFFLE BOARDS

Model B-125, high fidelity 20-watt, 3-way speaker system, mounted on an 18" square baffle board. Has 12" G.E. woofer, 2-4x6" mid-range speakers, plus a 4" high-range and 3" tweeter; all with Alnico V magnets. Built-in LC crossover network with variable brilliance control. Ship. wt. 11 lbs. Stock No. B-125, 3-way, 20-watt Hi-Fi speaker system. AUDIOPHILE VALUE \$30.00. SALE PRICE \$18.95.

SALE PRICE \$18.95


Model B-236, high fidelity 24-watt, 4-way speaker system, mounted on a 24" square baffle board. Has 12" 9-oz. woofer, a new high fidelity extended range 6x3" speaker, plus 2-5" tweeters; all with Alnico V magnets. Built-in LC crossover network with variable brilliance and presence controls. Ship. wt. 16 lbs. Stock No. B-236, 4-way, 24-watt Hi-Fi speaker system. AUDIOPHILE VALUE \$49.95. SALE PRICE \$27.95.

SALE PRICE \$27.95


Model B-347, high fidelity 30-watt, 5-way speaker system, mounted on an 30" x 24" baffle board. Has 15" UTAH 2 1/2-oz. woofer, 2-new high fidelity extended range 6x3" speakers, plus 2-5" tweeters; all with Alnico V magnets. Built-in LC crossover network with variable brilliance and presence controls. Ship. wt. 22 lbs. Stock No. B-347, 5-way, 30-watt Hi-Fi speaker system. AUDIOPHILE VALUE \$59.95. SALE PRICE \$39.95.

SALE PRICE \$39.95


Mount these Hi-Fi speaker systems in your own cabinet or use for custom installation. Ideal for use with any radio or amplifier. Ready to connect to any 8-ohm output.

TV-to-Radio Wireless Oscillator

By
HAROLD REED
Research and Engineering
U. S. Recording Company

Over-all view of transistorized oscillator unit. Note the use of a small rod antenna.



You can still enjoy the non-visual portions of favorite TV programs by using a small portable and this oscillator.

PHONO oscillators and "wireless" microphone devices, whereby music or voice-modulated radio frequency carriers are transmitted over short distances to radio receivers, have been popular for many years. Providing their radiation range is limited and does not cause interference, as prescribed by FCC regulations, the experimenter and hobbyist may construct and operate such devices.

Transistors are especially suited to this application due to the miniaturization advantages possible by their minute size and small power requirements. A novel approach to this limited "wireless" transmission is presented in this article.

In the two applications just mentioned, the voice picked up by the microphone, or music from a record player, is transmitted to the radio receiver and heard on the receiver loudspeaker. The idea presented here is to transmit voice and music from a television set to the home broadcast radio receiver.

The author has observed that there are many television programs such as music, speeches, etc., which may be enjoyed or are informative without actually watching the television picture. This can prove to be quite a convenience. For instance, the listener may be in a room remote from the television set location and engaged in

work in which music may not only be unobjectionable, but beneficial. In other cases, he may be occupied with duties that can be accomplished while listening to television speech. A portable radio set is quite handy for this arrangement.

The transistor oscillator, as shown in Fig. 1, employs the Colpitts type circuit, using a CK722 junction transistor. The necessary feedback to sustain oscillation is provided by connecting the emitter to the junction of the two capacitors in the tuned circuit. The Hartley circuit may also be used with a single capacitor, connecting the emitter to a tap on the coil, usually near the center.

The coil L_1 is a "Loopstick" antenna with adjustable iron core. Capacitors C_2 and C_3 each have a value of 270 μfd . With these values in the tuned circuit, and with the "Loopstick" adjusting screw set to about mid-position, the oscillating frequency was slightly above 700 kc. This was a "quiet spot" on the radio set at the author's location. The constructor may vary the capacitor values and iron core adjustment to produce a carrier frequency to suit radio broadcast conditions at his particular location.

A rod antenna is connected to the tuned circuit at the collector end of the inductor. Different antenna lengths will change oscillator frequency slight-

ly. Longer lengths will provide greater r. f. radiation, but if too long, may prevent oscillation. An 18-inch rod seems about right to cover the average home.

Choke coil RFC_1 is included, of course, to prevent r. f. current from flowing through the power supply.

Audio frequency modulation of the r. f. carrier is introduced from the television receiver through the resistive network composed of R_1 , R_2 , and R_3 . The transistor base circuit is connected across the 1000-ohm resistor, R_1 , which is shunted by the two 10,000-ohm resistors, R_2 and R_3 , and the TV speaker voice coil in series. Thus, the 10,000-ohm resistors bridge the speaker voice coil, and as their value is very high in relation to the low impedance of the voice coil, no undesirable loading of the speaker circuit results and TV sound is not affected. The audio signal level to the oscillator may be adjusted by varying the values of R_2 and R_3 . The value of each resistor should remain identical and increasing the value of each will decrease the sound level to the oscillator, while decreasing the value of these resistors increases the audio level. These resistors should be selected so that oscillator modulation is satisfactory when the TV set controls are adjusted for normal listening conditions at the TV receiver. The magnitude of the audio modulating signal should not be so great as to produce over-modulation of the r. f. carrier which will result in distortion of the sound reproduced by the radio loudspeaker. The author found the 10,000-ohm resistors

show
of his
tortu
recei

The
in a
Felt
of th
the t
is pla
type
match
copper
lead i
"Loop
on th
to the
jack
stick"
as far
faces
met-e
end o
justm
Anoth
provi
conne
voice
with
across
place
physi
critic
extre
For i
may

Bat
the so
of th
type
Colle
at thi
satisf
down
ages
oscilla
An
also
Figs.
range
ple ci
hum
versio
plug
hum
inter
side
not b
box v

The
less
tion
could
forme
volta
filter
Best
with
trans
shock

The
suppl
vide,
about
an a.c.
Other
varyin
ever,
of th

Febru

shown just right for normal operation of his TV set, while providing undistorted sound reproduction in the radio receiver.

The component parts are assembled in a standard 3" x 4" x 5" metal box. Felt tabs are cemented to the bottom of the box to prevent scratching of the top of the TV set where the device is placed. A small insulated banana type jack is fitted to the top and a matching plug is soldered to the #10 copper wire rod antenna. A flexible lead is connected from the jack to the "Loopstick." All parts are mounted on the 2 1/4" x 4" plastic shelf attached to the front panel, except the antenna jack and "on-off" switch. The "Loopstick" is mounted in the center to be as far as possible from all metal surfaces of the cabinet. A rubber-grommet-equipped hole is provided at one end of the metal box to allow for adjustment of the "Loopstick" iron core. Another hole fitted with a grommet is provided to pass the wire leads for connection to the TV loudspeaker voice coil. These leads are equipped with alligator clips for connection across the TV speaker. Other than placement of the "Loopstick," the physical arrangement of parts is not critical. No attempt was made toward extreme miniaturization of the unit. For instance, some of the capacitors may be of the 6-volt type.

Battery power supply is indicated in the schematic diagram and photograph of the device. A 15-volt hearing-aid-type battery may be used as shown. Collector current runs about 0.8 ma. at this voltage. The oscillator operated satisfactorily with a supply voltage down to about 7 volts. Higher voltages will result, of course, in greater oscillator output.

An a.c.-operated power supply may also be employed. The diagrams of Figs. 2A and 2B give two circuit arrangements the author tried. The simple circuit of Fig. 2A resulted in some hum modulation of the carrier. Reversing the power supply line cord plug in the a.c. outlet produced less hum in one certain position. In the interest of safety, the plus, or ground, side in the transistor circuit should not be connected directly to the metal box when using this a.c. supply.

The circuit of Fig. 2B introduced less hum even without the line isolation transformer. This transformer could just as well be a filament transformer with an appropriate secondary voltage. It will be seen that additional filtering is provided in this circuit. Best results were obtained hum-wise with the addition of the isolation transformer and it also eliminates the shock hazard.

The resistors given in these power supplies are of such value as to provide, depending on their tolerance, about 12 volts to the oscillator, with an a.c. supply line voltage of 117 volts. Other potentials may be obtained by varying the values of R_1 and R_2 . However, in order not to exceed the rating of the 1N34 diode, the a.c. voltage

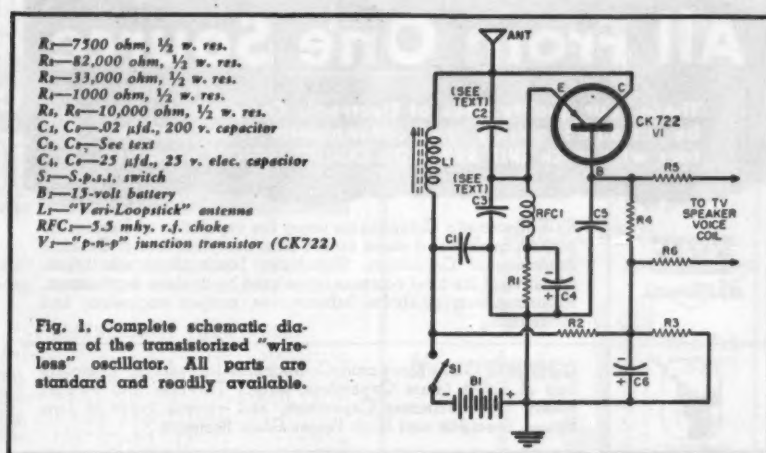


Fig. 1. Complete schematic diagram of the transistorized "wireless" oscillator. All parts are standard and readily available.

across R_5 should be held to not over about 20 volts.

The TV-to-radio oscillator performed very well. There appeared to be negligible frequency drift. With the TV set operating normally in the author's den, the sound was picked up clearly and undistorted on a kitchen radio receiver, a distance of 35 feet. The oscillator carrier, if of the same frequency as a radio station carrier, will beat with same, causing a heterodyne "whistle" in the radio. A "quiet spot" on the radio dial must be chosen.

When using a portable radio, the directional characteristics of the built-in antenna of the set may be used to advantage when necessary at extreme distances, by orienting the radio for maximum pickup.


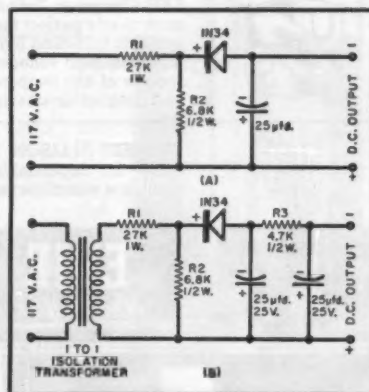


Fig. 2. Alternate supplies, refer to text.

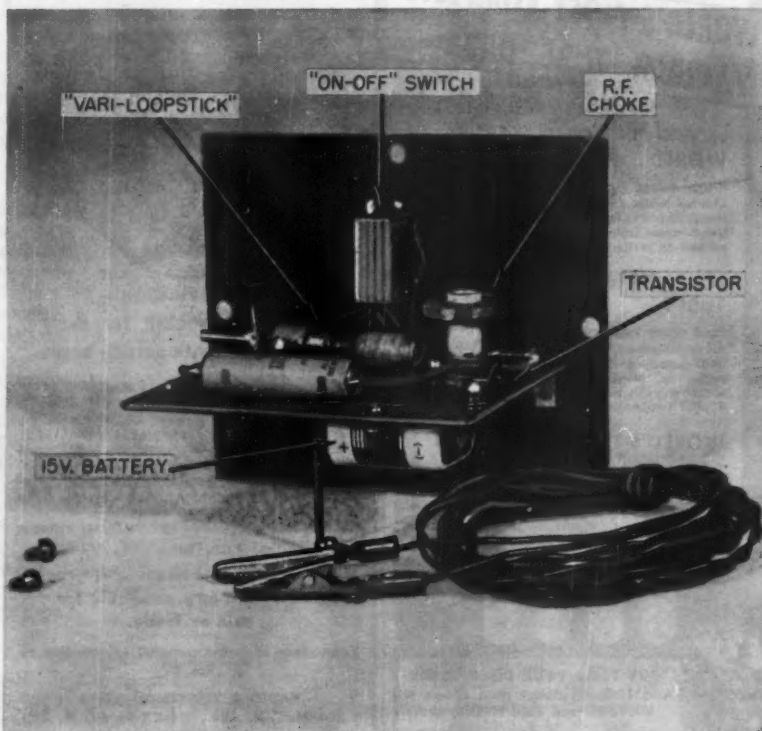Rear view of unit removed from case. Parts are mounted on shelf fastened to panel.



All From One Source

These four quality lines of Electronic Components may be obtained quickly and conveniently from Distributors who stock ERIE RESISTOR CORPORATION products.



ERIE Electronic Components enjoy the reputation of having the highest quality and make up the most complete line of Ceramic Replacement Capacitors. Distributor Stock items are representative of the most common types used by dealers, servicemen, experimenters, amateurs, laboratories, project engineers, and industrial.



CORNING Glass Electronic Components include the complete line of Fixed Glass Capacitors, Direct Traverse and Midget Rotary Glass Trimmer Capacitors, and various types of Low Power, Precision and High Power Glass Resistors.



ERIE-Chemelec Teflon Electronic Components are made of the most nearly perfect insulating material available, and are ideally suited to withstand high humidity, high or low temperatures, high altitudes, high voltages, and high frequency operation. It is serviceable at any temperature from -110°F to 550°F for long periods with negligible change in critical electrical characteristics.



GRIGSBY-ALLISON Switches are known throughout the industry for dependable quality and smooth performance. They include a complete variety of styles for all types of applications.

ORDER NOW
from Your
ERIE
DISTRIBUTOR

ERIE
electronics

ERIE ELECTRONICS DISTRIBUTOR DIVISION
ERIE RESISTOR CORPORATION
Main Office: ERIE, PA.
ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO

WORLD'S MOST COMPLETE VACUUM TUBE DATA —

Characteristics and Comparisons WORLD'S RADIO TUBES

Radio Tubes Vade Mecum
Characteristics of all tubes from all countries. World's largest list of tube data. Listed numerically and alphabetically. Base connection section. **\$5.00**

WORLD'S EQUIVALENT TUBES

Equivalent Tubes Vade Mecum
All replacement tubes for a given type, both exact and near-equivalents (with points of difference detailed). Military tubes and commercial equivalents. Over 43,900 comparisons. **\$5.00**

WORLD'S TELEVISION TUBES

Television Tubes Vade Mecum
Characteristics of all TV picture, C.R., and special purpose tubes. A "must" for all specialists. **\$5.00**



BUY FROM YOUR DISTRIBUTOR
Add 10% on direct mail orders to
EDITORS and ENGINEERS, Ltd.
Summerland 2, California

WANTED



Willing to pay cash for Early
Phonographs with outside horns

WANT Coronet (illustrated), Double Bell Wonder, Victor Types A, D, and O, Monarch Special, and Improved Monarch. Also Edison Idella, Excelsior, and Treadle Phonographs. Want early Bell-Tainter, American Gramophones, Multiphone, Multinola, Scott Magazine Phonograph, Peerless, Sovereign, Wizard Phonograph, Regina Hexaphone, and Graphophones. Also catalogues or old literature on phonos made prior to 1906. Want unusual machines and coin-in-slot cylinder phonographs.

A few duplicate Edisons and graphophones are now available for sale or trade.

Send clear snapshot and full information to Box 50

RADIO & TELEVISION NEWS
366 Madison Ave., New York 17, N. Y.

Strategy of Color Service

(Continued from page 41)

Admittedly, a factory service branch has certain advantages over the independents. Its technicians become well-versed specialists on the relatively few models they handle while the independent struggles with a variety of makes and models. But their alleged advantage can help out the independent too.

The factory branch men run into the tough ones, too—often sooner than the independent. After they have worked out the solution, the independent can cash in on this experience and thus save a tremendous amount of time, money, and customer goodwill. The help is there for the asking—don't be embarrassed or ashamed to seek it.



One of the troublesome cases encountered by a factory branch involved a 21" receiver which displayed a smeary picture. It seemed to be a classic illustration of frequency response distortion, as if a peaking coil or something in the video amplifier circuits had let go. The circuit was checked carefully and thoroughly but no defective component was found. The chassis was pulled and after a lot of group "conferences" it was decided that components would be changed one at a time until the trouble was located. The job was started with the tubes. When the 6U8 noise inverter was replaced, the picture cleared up!

The tube was checked carefully and it was found that there was a cathode-to-control-grid short in the triode section. A glance at the schematic, Fig. 6, showed that the noise inverter was hooked into the video detector, the cathode of the first video amplifier, and the grid of the second video amplifier through some peaking coils and the delay line. This was a real stumper.

The experience of the technicians at the factory branch paid off for the writer when he encountered an identical case which was cleared immediately when the 6U8 was replaced.

Save yourself hours in color work by taking advantage of every possible source of servicing information—from books to experienced technicians' friendly tips!

Fig. 6. Poor h.f. response (smeary) was caused, not by a defective peaking component, but by the load placed on the detector from another defective circuit.

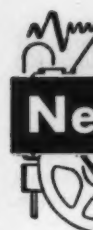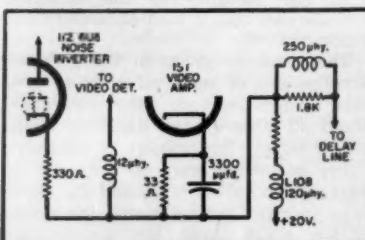

TAP
Telec
St., Lon
announc
magnetic



which ha
studio a
cations.

The M
track ma
producer
and repr
which op

Frequ
cps ± 2
cps ± 2
minute
Model 10
60 cycles


The un
clad ply
to withs
also be
covered

Jensen
Laramie
added a
to its pr
ers for c
tional, an


The R
with rect
from gla
resin. T
on car t
wall cor



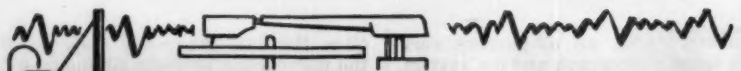or vertic
tical con
mounted
clusters
ing hard
platform



New Hi-Fi-Audio

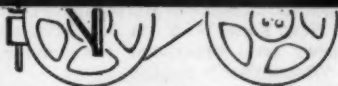

Equipment

TAPE RECORDER-REPRODUCER

Telectro Industries Corp., 35-18 37th St., Long Island City 1, N. Y., has announced the availability of a new magnetic tape recorder-reproducer



which has been designed for broadcast studio and other high-fidelity applications.

The Model 1000 is a portable dual track magnetic tape recorder and reproducer. The sound is recorded on and reproduced from a 2400 foot reel which operates at 7½ or 15 ips.


Frequency response is 30 to 10,000 cps ± 2 db at 7½ ips and 30 to 15,000 cps ± 2 db at 15 ips. Rewind time is 1 minute for 2400 feet of tape. The Model 1000 operates at 117 volts a.c., 60 cycles.

The unit is housed in two aluminum clad plywood cases, especially designed to withstand portable usage. It can also be supplied in gray Fabrikoid covered plywood cases, if desired.

RECTANGULAR HORNS

Jensen Manufacturing Co., 6601 S. Laramie Ave., Chicago 38, Ill., has added a rectangular horn, the RT-20, to its professional series line of speakers for commercial, industrial, institutional, and p.a. applications.

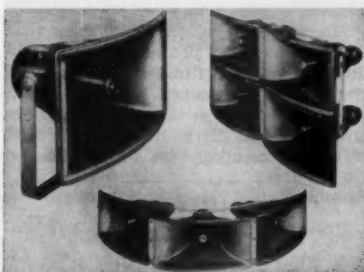The RT-20 is an axial projector horn with rectangular mouth section molded from glass fiber re-inforced polyester resin. The speakers can be mounted on car tops, used singly or doubly in wall corners, or installed horizontally



or vertically, depending on the acoustical conditions. The speakers can be mounted with a minimum of rigging, clusters are readily joined with stacking hardware and require no special platforms.

For full information on these new horns, write the manufacturer direct.

PROFESSIONAL TURNTABLE

Intersearch, 7 Arcadia, Cincinnati, Ohio, is acting as the exclusive U. S. importer of a new Japanese-built turntable for hi-fi applications.

The I/S Model TP-50 features a magnetic eddy current speed adjustment which permits a 23% speed adjustment and a neon illuminated stroboscope which is viewed through an observation window in the motor plate. One speed adjustment corrects all three turntable speeds.

A separate "flip switch" permits instant selection of 33½, 45, or 78 r.p.m.



The 12-inch cast aluminum turntable is rim driven by a new two-phase capacity type motor. The motor can be operated for long periods of time with very little rise in temperature. Complete U. S. servicing facilities are available.

NEW "INTERADIOCOM"

Stratford Corporation, 745 Fifth Ave., New York, N. Y., has recently introduced a new intercommunications system for home use.

Known as the "Interadiocom," the new unit combines an intercom and radio. It can service five relay stations within the home, permitting simultaneous radio and inter-room communication at each or any of the outlets.

The master control panel includes a radio, intercom, clock, electric timer, a.c. socket, five-position switch, safety interlock, jewel pilot light indicator, and phono jack. The set includes four relay stations, each with a powerful 5-inch PM heavy-duty speaker, and an entry door relay station with a push-button bell.

CALIFONE "DIRECTOR"

Califone Corporation, 1041 N. Sycamore Ave., Hollywood 38, Cal., is currently in production on its new 1957

NEW \$70.00

SHURE SLENDYNE

OMNIDIRECTIONAL
DYNAMIC
PROBE
MICROPHONE

IS 5
Microphones
IN 1

Model
"535"
List
Price
\$70.00



For Public Address
Remote Broadcast
Theater-Stage
Sound Systems

A completely versatile probe microphone of excellent frequency range (60-15,500) that combines ruggedness, beauty and reliability.

Versatility: Can be used (1) on a floor stand; (2) on a desk stand; (3) quickly removed for use as a hand-held microphone; (4) furnished with lavalier cord for wearing around the neck; (5) impedance switch permits use as high or low impedance microphone. Accessory on-off switch requires no wiring.

Ruggedness: Built to withstand hard usage and extremes of temperature and humidity.

Beauty: Slender, convenient shape, finished in brushed satin chrome.

Reliability: High efficiency magnetic materials and circuits assure years of consistent high quality performance. Shure quality control techniques result in an exceptionally high degree of uniformity for microphone interchangeability and multiple use.

SLENDYNE Model "530"

This deluxe version of the Slendyne has a frequency range of 50-15,000 cps and is furnished with a Cannon XL-3-11 broadcast connector. Strikingly attractive non-reflecting black and gold anodized finish. LIST PRICE \$110.00

The Mark of Quality

SHURE SHURE BROTHERS, INC.


210 HARTREY AVENUE • EVANSTON, ILLINOIS

THE HARTLEY TELLS ONLY THE TRUTH!

The Hartley 215 may prove embarrassing in some cases, but if YOUR installation is good the absolutely true reproduction of our speaker will prove it.

FAITHFUL REPRODUCTION ... THAT'S ALL

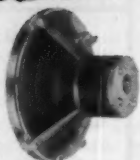The Hartley 215 is completely free from distortion and resonance (confirmed by laboratory tests). If you're happy with the quality of your records and playback equipment, you will want the Hartley. Nothing is added to the sound that is fed to this speaker, you'll get only faithful reproduction. The perfection of its unique construction is assured by 28 hand operations.



SPECIFICATIONS

Frequency response: 1 to 18,000 cps (without resonance)
Impedance: 4 ohms
Magnet: 5 lbs. Alcomax II
Peak power capacity: 20 watts
Diaphragm movement: 1/2"
(reproduces the lowest notes of any musical instrument)

HARTLEY 215 SPEAKER SYSTEMS



The renowned Hartley Baffle, with one, two, three or four drivers. Prices start at \$115.75 for the complete system. At franchised dealers or write for details:

HARTLEY PRODUCTS CO.

Dept. 55, 521 East 162nd Street
New York 51, N. Y. • LUdow 5-4239

Now available at

Walters Home Appliances
7335 McGraw
Detroit, Mich.

Valley Engineering Co.
601 Cedar St.
Los Alamos, N. M.

Audio Center, Inc.
1633 Westheimer
Houston 6, Texas

Hi-Fi Music Haven
2651 N. Federal Highway
Ft. Lauderdale, Fla.

Leonard Radio
69 Cortlandt St.
New York, N. Y.

G. L. Electronics, Inc.
1632 Venice Blvd.
Los Angeles 6, Calif.

"Director" unit, an all-purpose variable speed phonograph and p.a. system.

The Model 12V-7 features a center-driven, continuously variable speed turntable (having a range of from 16




to 84 r.p.m.) which eliminates cones, idlers, and rollers and provides for exact setting of speed without drift from a cold start to continuous running; a "Strobeselector" which is a combination of single knob speed control and illuminated stroboscope; and a precision machined cast aluminum turntable with a cork cover and pop-up 45 r.p.m. centering device. An all-aluminum pickup arm features double wrist action. A counterbalanced weight adjustment controls needle pressure at the pickup head while the entire arm lifts for easy handling and needle replacement.

An 8-page catalogue describing this and other of the company's new units is available without charge from the manufacturer.

MICROPHONE CALIBRATOR

Brush Electronics Company, 3405 Perkins Ave., Cleveland 14, Ohio, is now offering a microphone calibration unit which is manufactured by Bruel & Kjaer and is catalogued as the Model BL-4119.

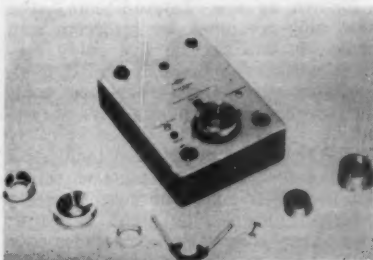Designed for the accurate calibration of the firm's condenser microphone Model BL-4111 as well as the condenser microphone cartridge MK-0002, the apparatus enables both a calibration procedure which is a simplified form of the standardized reciprocity calibration technique and the determi-



nation of the complete frequency response curve of the microphone by means of an electrostatic actuator.

The first measurement yields the accurate absolute sensitivity of the microphone at any arbitrary frequency without the use of any precalibrated standard by using three condenser cartridges. The second measurement


gives the total frequency response of the microphone between 20 and 20,000 cps.

NEW RONETTE MIKE

Ronette Acoustical Corp., 135 Front St., New York, N. Y., is now offering a new, semi-directional microphone, the "Ronomike."

The microphone is housed in a slim, sturdy die-cast housing that is fully chrome plated. Its modern, convenient shape adds strength and attractiveness and its performance is especially suitable for use with tape recorders, p.a. systems, and ham transmitters.

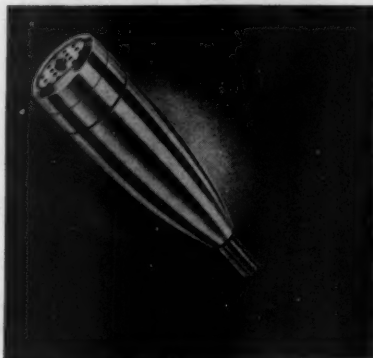A high impedance instrument, the new unit requires a high value of load resistance. It has a sensitivity of -55.4 db. The flat response from 30 to 10,000 cps is peak-free when matched to a



500,000 ohm to 1 megohm input of a triode stage. IM distortion is negligible.

The microphone cable, of special design, has a minimum of 90% shielding and is included along with a fully shielded telephone-type plug.

HI-FI GRILLE SCREEN

General Cement Mfg. Co., 400 South Wyman St., Rockford, Ill., has introduced a new heavy metal grille screen designed especially for hi-fi system applications.

Featuring a style suitable for any modern or period enclosure, this grille screen is designed for high-fidelity systems, juke boxes, TV consoles, p.a. speakers, and other similar applications.

The screen is of the rigid type that affords maximum protection for an enclosure and is finished in brushed brass, then lacquered for extra durability. The screen comes in five sizes ranging from 12" x 18" to 36" x 48". Write the company for full details.

EQUALIZER-PREAMP

McIntosh Laboratory, Inc., 320 Water St., Binghamton, N. Y., has released a new equalizer-preamplifier unit which is designed to serve as an accurate and versatile control center of a hi-fi home music system.

The C-4 provides separate bass and treble accentuate and attenuate controls, five input channel selectors for tape, tuner, microphone, and two

phono cartridges, and a master "on-off" switch with volume control.

This unit features low distortion, good stability, and wide frequency response. Full specifications on this equalizer-preamp are available without charge from the manufacturer on request.

REPLACEMENT CARTRIDGE

Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Ill., has announced production of a replacement pickup cartridge for the Chrysler "Highway Hi-Fi" system.

The WC20, a direct replacement for the PC20A used in these Columbia-built record players, will track at extremely low pressures. This ceramic cartridge has a minimum needle force of 2½ grams and frequency response to 12,000 cps.

Additional information on this replacement unit is available from the manufacturer or any of its authorized distributors.

NEW KLIPSCH "SHORTHORN"

Klipsch and Associates of Hope, Ark. has introduced a new corner horn loudspeaker system which is known as the "Shorthorn" Model "T".

Designed to be used to provide full range sound reproduction for television as well as for record players, tape players, and radio, the dimensions of the new unit are such that it can be used as a stand for table model TV sets.

Extending from below 40 cps to above 20,000 cps, the new system provides good efficiency from 45 to over 16,000 cps. The Model "T" is available



with the company's "K-Ortho" 3-way drive system, consisting of three drivers with a choice of a 12- or 15-inch bass cone driver and crossover network. The bulk of the unit is, the bass horn and, mounted inside it, are the mid-range and high-frequency horns.

The mahogany enclosure is of simple classic design which fits into any type of modern or traditional decorative scheme.

IMPORTED MICROPHONES

Intersearch, 7 Arcadia, Cincinnati, Ohio, is handling the U. S. distribution of two microphones manufactured by

Genalex THE ORIGINAL KT66



The name GENALEX on the tube and carton is your guarantee that you are buying the original KT66... world-famous power tetrode, often referred to as the finest audio tube ever made! The GENALEX KT66 is the hallmark of the finest amplifiers. It is original equipment in the famous HEATH ULTRA LINEAR AMPLIFIER KIT, No. W-5M. Identical pins and connections as 6L6 tubes.

Only \$3.50 net

For complimentary fact sheet, write Dept. XB-47



Quality endorsed product of the British Joint Industrial Council

BRITISH INDUSTRIES CORPORATION
Port Washington • New York



TOP CARTRIDGE

The latest Audio League Report on pickups* again acknowledges that no cartridge excels the ESL Professional and Concert Series.

Audio League tests show that the ESL is unsurpassed in smoothness, clarity, and naturalness of reproduction, and that the ESL will meet the most exacting requirements for broadcast, recording studio, or laboratory use.

Is your pickup obsolete? You're missing plenty if you don't have the world's most advanced cartridge. Write for free details, and buy the ESL at your dealer's.




FOR LISTENING AT ITS BEST

Electro-Sonic Laboratories, Inc.

Dept. R • 35-54 Thirty-sixth Street • Long Island City 6, N.Y.

Soloist Series from \$14.95 • Concert Series \$35.95 • Professional Series arm and cartridge \$106.50

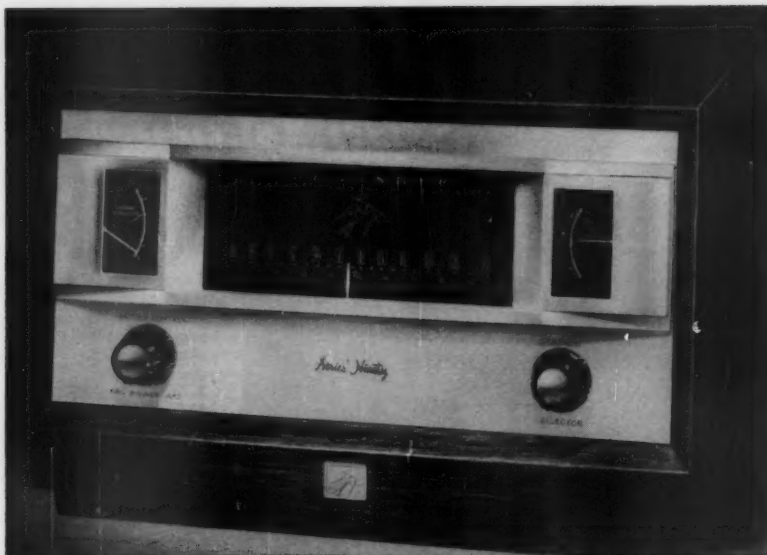*Vol. 2, No. 3 (December 1956). Authorized quotation No. 60. Please consult The Audio League Report, Vol. 1, No. 6-7 (March-April 1955) for the complete technical report and listening evaluation of the ESL. Subscription: 12 issues, \$4, from P. O. Box 262, Mt. Vernon, N. Y.



AMERICA'S LEADING FM TUNER • IN SENSITIVITY, APPEARANCE AND WORKMANSHIP

ANOTHER FISHER FIRST!

THE REVOLUTIONARY

FISHER FM-90X

Gold Cascode FM Tuner

HARD ON THE HEELS of the new Model FM-90, we are proud to present the Model FM-90X with its revolutionary GOLD CASCODE RF amplifier. Precision manufactured, this tube is the costliest of its type in the world! It carries a *two-year warranty*. The use of the gold cascode and special circuitry has brought the FM-90X to the theoretical limits of sensitivity — an achievement never before possible. *Only the FISHER has it!* The standard FM-90, with its silver-plated RF shield, already surpasses ALL other FM tuners — excepting the FISHER GOLD CASCODE 90X.

Basic Features of the Series FM-90

- TWO meters, for micro-accurate tuning. • Revolutionary, dual dynamic limiters, assure noise-free reception where all others fail. • Full wide-band detector for maximum capture ratio. • *Exclusive*, variable inter-station noise eliminator. • Full limiting on signals as low as 1 microvolt. • Dual triode, cascode-tuned RF stage, four IF stages. • Uniform response, 20 to 20,000 cycles. • Three outputs (Main, Recorder and Multiplex). • Dual antenna inputs (72 ohms or 300 ohms balanced). • Four controls. • 10 tubes plus four matched germanium crystal diodes. • Special circuits for meter operation. • Chassis completely shielded and shock-mounted. • Beautiful, die-cast, brushed brass escutcheon and control panel. • Dipole antenna supplied. • SIZE: 13 7/16" w. x 6 1/4" high x 8 3/4" deep (plus 1" for knobs). • WGT: 15 lbs.

FM-90X • Gold Cascode FM Tuner • \$159.50

FM-90 • Professional FM Tuner • \$149.50

MAHOGANY OR BLONDE CABINET: \$17.95


Prices Slightly Higher in the Far West

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORP., 21-23 44th DRIVE • L. I. CITY 1 • N. Y.

Tokyo Tsushin Kogyo, Ltd., and imported from Japan.

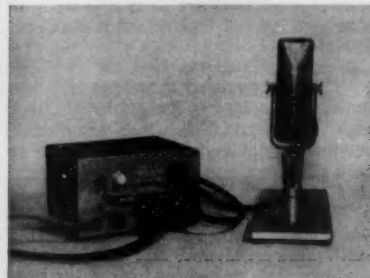The "Sony" Model C-27-A condenser microphone is a polydirectional unit. A switch selects unidirectional or omnidirectional operation. It features a



new type of titanium diaphragm designed to provide stable operation and smooth response from 30 to 20,000 cps. The output impedance is 200 ohms. The output level is -73 db non-directional and -70 db directional. Three frequency responses may be selected by a switch on the panel of the power supply.

The second unit, the Model 10, is a moving coil microphone designed especially for tape recording applications. Response is smooth from 50 to 12,000 cps. The output level is -62 db and the impedance is 10,000 ohms.

Write the distributor for additional details and prices.

ELECTROSTATIC TWEETER

Pampa Electronics Corp., 7354 Frankford Ave., Philadelphia 36, Pa.,

is now offering a single-ended, non-powered electrostatic tweeter in a finished wooden cabinet as its Model 5-20.

Frequency coverage is substantially flat from 5000 to 20,000 cps. The tweeter is designed to be used with amplifiers rated at up to 25 watts output. The distribution angle is 360 degrees in the horizontal plane. The impedance matches 4, 8, and 16 ohm sources. A divider network and matching transformer are built into the tweeter itself, eliminating the necessity for external networks.

The housing for this tweeter measures 4 1/2" wide, 4 1/2" deep and 12" high. The company will mail a specification sheet on request.

BRITISH-BUILT TAPE DECK

Truvox Limited, 15 Lyon Road, Harrow, Middlesex, England, is now offering the "Mark III" in its "U" series of tape decks for high-fidelity system applications.

The deck is powered by three shaded-pole a.c. motors, with electrically and mechanically interlocked push-button control. A separate push-button brake is of the patented elec-

RADIO & TELEVISION NEWS

tric type. There is drop-in tape loading and the machine will handle 60 minutes on each track of half-track 3½ ips or 30 minutes each track at 7½ ips. A visual playing-time indicator operates at either speed to show lapsed time and balance of time to run on the reel. The deck will take all standard tape reels up to 1200 foot sizes.

With a suitable amplifier, the equipment covers a frequency range from 50 to 10,000 cps at 7½ ips. Write the company for a data sheet containing full specifications.

DUOTONE SPEAKER LINE

The Duotone Company, Locust St., Keyport, N. J., manufacturer of a complete line of needles for high-fidelity phonograph applications, has entered the loudspeaker field with seven units.

The line ranges from a 15-inch woofer (the "Supreme") to four coaxial units and two tweeters. The 12" "Royal," for example, has a frequency response of 35 to 18,000 cps. It will handle 25 watts of power and has a



magnet weight of 1.5 pounds. The efficiency is 14% at 400 cps and the resonating frequency is 45 cps.

Write Dept. PR-2 of the company for complete details on this entire line of moderately priced "DFF" speakers.

NEW "KONTAK" MIKE

Amperite Company, Inc., 561 Broadway, New York 12, N. Y., is now offering a new "Kontak" mike designed to be used for all fretted and stringed instruments, including the piano.

The Model KKH-3 can be used with any p.a. amplifier, tape or wire recorder, and all electric guitar amplifiers. A fingertip volume control is conveniently mounted on the microphone and supplied with a large knob for ease of operation. Frequency range is 40 to 10,000 cps ± 2 db. The output level is -55 db. The unit is not affected by temperature, pressure, or moisture.

FREQUENCY DIVIDER

Colbert Laboratory, Inc., 160-09 Hillside Ave., Jamaica 32, N. Y., is now offering a three-channel electronic frequency divider for high-fidelity reproducing systems.

February, 1957



ON ONE COMPACT CHASSIS! FISHER FM-AM TUNER, AUDIO CONTROL AND 30-WATT AMPLIFIER!

New!

THE FISHER "500"

EVERYTHING YOU NEED!
ON ONE SUPERB CHASSIS!

THOUSANDS have asked us for it—and here it is! An extreme-sensitivity FM-AM tuner, a powerful 30-watt amplifier, and a Master Audio Control—all built on one compact chassis. Simply add a record changer and loudspeaker to the FISHER "500" and, as easily as that, you have a complete high fidelity system. Its quality—in the finest FISHER tradition. Its appearance—the timeless beauty of classic simplicity. Here is the most economical form in which you can own FISHER equipment.

Chassis Only, **\$239.50**

Mahogany or Blonde Cabinet, **\$19.95**

Outstanding Features of THE FISHER "500"


- Extreme sensitivity on FM and AM. Meter for micro-accurate tuning.
- Full wide-band FM detector for maximum capture ratio.
- Powerful, 30-watt amplifier; handles 60-watt peaks.
- Uniform response, 16 to 32,000 cycles.
- 4 inputs, including separate tape playback preamp-equalizer.
- 4, 8 and 16-ohm outputs match all existing speakers.
- Recorder output ahead of volume and tone controls.
- 7 Controls, including 9-position Channel Selector (AM, FM, AES, RIAA, LP, NAB, TAPE, AUX 1 and AUX 2), Loudness Contour (4-position), Volume, Bass, Treble, AC-Power, Station Selector.
- Beautiful, die-cast, brushed brass escutcheon and control panel.
- Pin-point, channel indicator lights.
- Smooth, flywheel tuning.
- Largest, easy-to-read, slide-rule dial, with logging scale.
- High efficiency FM and AM antennas supplied.
- 14 tubes plus 2 matched germanium diodes.
- SIZE: 13 7/16" w. x 12 3/4" d. (excluding knobs) x 6 1/4" h.

Prices Slightly Higher In The Far West

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORP., 21-23 44th DRIVE • L. I. CITY 1 • N. Y.

*Friction
Free
as a
Feather
in air*



REK-O-KUT
TURNTABLE ARM

Pat. Pending

A-120 for records up to 12" \$26.95
A-160 for records up to 16" \$29.95
slightly higher west of Rockies

LATERAL FREEDOM FROM FRICTION
achieved by unitized sealed-in
twin-bearing pivot.

FRICTION-FREE VERTICAL SUSPENSION
between 1 mm chrome-steel
bearings... sealed in cross-shaft!

ENDS NEED FOR STYLUS PRESSURE
GAUGE! With cartridge mounted
and arm in state of balance...
turn micrometer-action counter-
weight to build up stylus pressure.

See your dealer or write:
REK-O-KUT
COMPANY, INC.

30-01 Queens Blvd., Long Island City 1, N. Y.
EXPORT: Morhan Exporting Corp., 458 B'way, N. Y. 13
CANADA: Atlas Radio Corp., 50 Wingold Ave., Toronto 10

The Model 3-CFD divides the frequencies before amplification to increase definition and clarity of the reproduced sound. The unit features variable crossover controls for low-, mid-, and high-ranges, permitting exactly right adjustment for every conceivable combination of components. Individual level controls are provided for each sound channel. Since separate amplifiers are used for each frequency range, the frequency response each amplifier is asked to deliver is limited. Designed for use on two- or three-way systems, the Model 3-CFD in-



cludes a 10-watt "Ultra-Linear" amplifier using the latest-designed, low-noise audio tubes developed by Mullard.


A data sheet on this new unit, including complete specifications, is available without charge from the manufacturer.

DELUXE CONTROL AMPLIFIER

Sargent-Raymont Co., 4956 E. 12th St., Oakland 1, Cal., has added another item in its new line of hi-fi components, the SR-200.

This deluxe control amplifier includes a preamp, tone control, and 20-watt "Ultra-Linear" amplifier in a single housing. Among the unique features of "The Claremont" are a variable rumble control, a variable scratch filter, and a nine-position amplifier control dial.

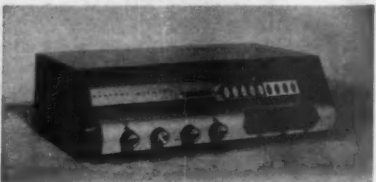The instrument uses six tubes; has output impedances of 4, 8, and 16 ohms; and operates from 110-120 volt



a.c., 50 or 60 cycles. The housing measures, 4½" high, 15" wide, and 11½" deep.


An illustrated brochure on this equipment is available without charge from the company.

TRANSISTOR-MIXER

Lab-Tronics, Inc., 3656 N. Lincoln Ave., Chicago 13, Ill., is now marketing a new transistor-mixer which is designed to meet the needs of the p.a. and recording industries.

Compact in size, the Model No. TR-36 has a built-in transistor preamp and can provide an over-all gain on each of its three channels of better

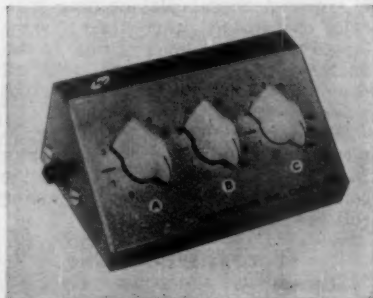than 6 db. Three input phone jacks mix any three channels of microphones, phonographs, or tuners, mak-



ing possible great flexibility. The unit is humless and has an extremely low noise level.

Frequency response is from 20 to 20,000 cps, ± 2 db. The inputs will mix any combination of three high-impedance microphones, crystal phonograph cartridges or tuner outputs, as well as magnetic cartridge preamp outputs.

The circuit uses a low-noise *n-p-n* 2N35 transistor and is powered by three mercury cells.

AMPLIFIER IN KIT FORM

Quality Electronics, Inc., 319 Church St., New York 13, N. Y., has introduced a 12-watt amplifier kit for the "do-it-yourself" contingent.

The circuit incorporates a built-in preamp; a 5-position switch with three



equalizer positions; output impedances of 4, 8, and 500 ohms; and four separate input jacks on the rear apron of the chassis.

The amplifier uses six tubes, including three multi-purpose tubes, which provide nine-tube performance.

Housed in a mahogany case with an ivory and gold front panel, the Model 2000 kit comes with a 25-page illustrated assembly instruction manual.

AUDIO CATALOGUES

"ULTRA-LINEAR" THEORY

Keroes Enterprises, 369 Shurs Lane, Philadelphia 28, Pa., has just issued a new 24-page booklet which presents a detailed study of the theory and operation of the "Ultra-Linear Circuit."

Included in the booklet are the mathematical analysis of the circuit's operation and a typical amplifier design using this circuitry.

The small booklet is priced at 25 cents a copy and can be ordered direct from the company.

West Coast Hi-Fi Shows

Institute to sponsor Los Angeles and San Francisco events early in February.

THE Institute of High Fidelity Manufacturers will be duplicating the successful format of its 1956 New York High Fidelity Show at Los Angeles and San Francisco early in February.

The Institute has scheduled the Los Angeles show February 6th through 9th at the Ambassador Hotel. The public will be admitted, at a nominal charge, between the hours of 2 and 10 p.m. on the first three days of the show and from 10 a.m. to 6 p.m. on Saturday, February 9th.

February 4th, from 10 a.m. to 7 p.m., will be given over to Audio Components Representatives Assn. Conference Day. This will consist of a meeting of sales reps, dealers, and manufacturers. No exhibits will be open during this session. At 7 p.m., the AES will hold its banquet at the Coconut Grove of the Ambassador Hotel.

February 5th has been left open to enable exhibitors to set up their displays. The dealer preview of the exhibits is set for February 6th from 9 a.m. to 1 p.m. before the general public is admitted.

Among the special features of the show will be Oliver Read's (publisher of RADIO & TELEVISION NEWS) "Replica of an 1890 Recording Studio"—an outstanding hit of the New York Show. In this exhibit, original equipment of the period is shown "in use" in a realistic setting.

A series of seminars, "The Ins and Outs of High Fidelity," will be conducted under the direction of C. G. McProud. The same editors who participated in the New York Show seminar will repeat in Los Angeles.


From Los Angeles the Show will move to San Francisco where it will be held from February 15th through 18th at the Hotel Whitcomb. Show hours will be from 2 to 10 p.m. each day. A special preview for the trade only will be held on February 15th from 10 a.m. to 1 p.m. Special features at this Show will include an "Information Room," staffed by experts, who will answer questions on hi-fi posed by visitors.

The scheduling of the two shows one week apart was done to permit manufacturers to call on the trade during the week between. Exhibits can be shipped direct from Los Angeles to San Francisco.

Additional information on either or both of the Shows is available from Sanford L. Cahn, executive secretary, Institute of High Fidelity Manufacturers, P.O. Box 284, Mineola, New York.

—50—

February, 1957

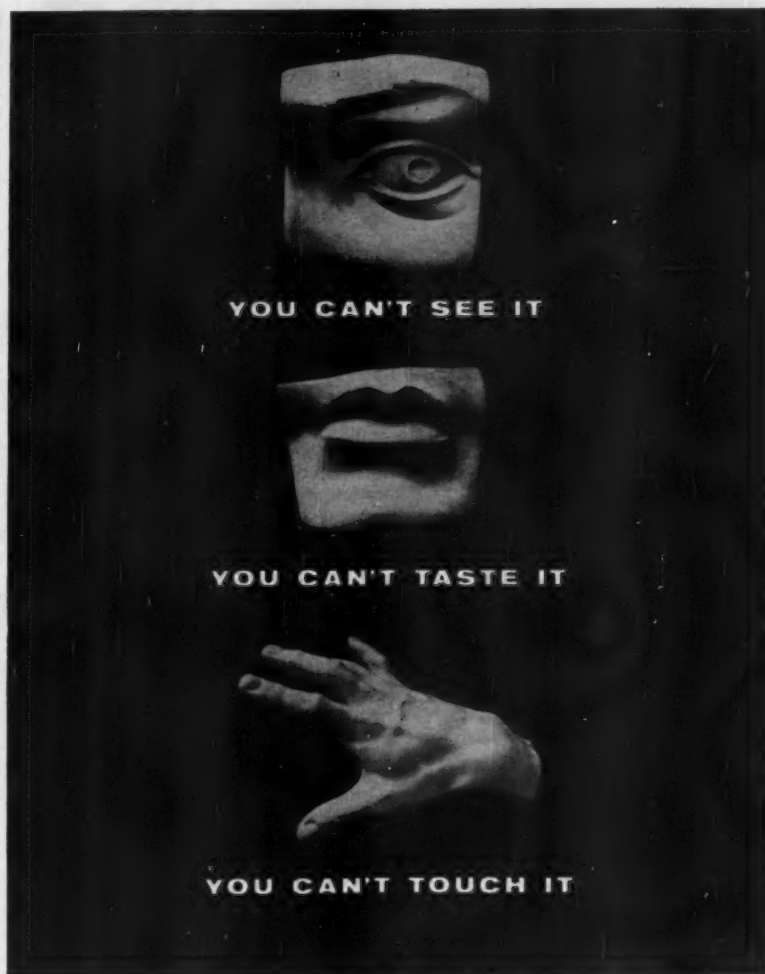

... But it's the most important asset a company can have

A modern plant, a well-stocked inventory, a good shipping department—these things are important. But, more important than all of these, is the *integrity* of a firm... that sense of moral responsibility that demands that you do your best and stand behind what you do.

Integrity starts at the top and filters down, enhancing everything it touches. It serves notice on its customers that every product bearing its label has a team of responsible people behind it.


And something happens to the *product* too! Integrity seems to be built right into it... in ways that you can see and in many more ways that you can't.

In addition to a close check on the quality of the various parts, we, at University, do not tolerate any "sweeping under the carpet." Even those parts which are completely enclosed and hidden from view are as carefully finished as the exposed parts, guaranteeing trouble-free performance.

That's why everyone is saying...

LISTEN

University sounds better

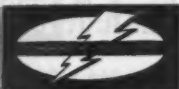

UNIVERSITY LOUDSPEAKERS, INC., 80 SOUTH KENSICO AVENUE, WHITE PLAINS, N. Y.

Build with the BEST

Enjoy the ease and economy of
Systematic Growth, the Sustained
Satisfaction, possible only with

BOZAK

Quality
Loudspeakers

The one-line, one-quality Bozaks are never outgrown or outclassed—never discarded as you build your Speaker System into ever-greater power and realism. From the B-207A to the magnificent B-310 and B-400, in a wall or infinite-baffle enclosure, each for its size unrivalled in quality of sound—The Purest Voice for a Fine Music System!

Step 1 - B-207A

B-199A + B-200X
+ 4-mfd. Filter.
40 cps to 16 kc.
8 Ohms, 15 Watts.



Step 2 - B-302A

B-207A + B-209
+ N-10102.
40 cps to 16 kc.
8 Ohms, 20 Watts.



Step 3 - B-305

2 B-207A + B-209 + N-10102.
35 cps to 16 kc
16 Ohms, 30 Watts.



Step 4 - B-400

4 B-199A + B-209 + B-200XA.
Below 28 cps to beyond 16 kc
N-10102 + N-25
8 Ohms, 50-50 Watts.



May be arranged vertically
to form the B-310A.

All Bozak Products are Designed and
Built by The R. T. Bozak Mfg. Co.

The R. T. **BOZAK** Sales Co.

BOX 966 • DARIEN • CONNECTICUT
EXPORTS: ELECTRONICS MANUFACTURERS'
EXPORT COMPANY, PLAINVIEW, NEW YORK

Tone Compensator

(Continued from page 67)

of the compression curve on broadcast transmitters).

In Fig. 1, C_5 is the capacitor that determines the amount of effective "bass-boost" at low volume levels. R_5 controls the amount of d.c. feedback from the plate to grid of the control tube and, hence, the rate of expansion or control. The values shown will give an operating range in excess of 20 db, with a 1 kc. to 50 cps ratio of about 2 to 1.

The principle of operation is as follows: V_{1A} functions as a diode rectifier, providing a negative, filtered d.c. voltage on the grid of V_{1B} proportional to the amount of applied audio signal. As this voltage increases, less current flows in V_{1B} , resulting in a higher plate impedance. As this impedance is in series with C_5 , the increasing impedance reduces the effectiveness of C_5 , and, hence, provides a more nearly flat response to all frequencies at the output. A portion of the voltage present at the plate of V_{1B} is applied through a voltage divider network to its grid return, giving a sort of d.c. negative feedback, to control the sensitivity of the circuit and, to a certain extent, its linearity.

In order that the level that determines the amount of control is primarily from the middle and higher frequencies, C_1 is made small so the amount of signal reaching the rectifier (V_{1A}) is reduced at the lower frequencies. R_5 is a limiting resistor, whose purpose is to prevent undue loading of the input with sudden dynamic increases. C_5 , C_6 , and R_4 form an RC filter network. R_5 determines the recovery rate (in conjunction with C_5 , C_6 , C_1 , and R_4 ; R_5 and R_1 , the d.c. feedback, or expansion rate. Because R_7 must be kept large (because it is effectively in parallel with R_5 and the plate impedance of V_{1B}), R_5 is the determining component.

The unit pictured was built on a small subchassis to be mounted under the main chassis of an amplifier. With the layout shown, all but three of the necessary connections are made by the component leads themselves. This simplifies the wiring and also reduces the problems of hum and noise. There is no reason why this unit could be built only in this manner, though. Any method where good audio construction practices are employed, should be satisfactory.


It should be remembered that there is a minimum loss of 15 db, also, that the unit should be inserted in an amplifier at a point where there is about 5.0 volts r.m.s. of audio present during normal programming. This circuit must follow any equalizers and precede any tone controls. The volume control should be prior to this compensating device, so that manual adjustment of the volume level will have the same effect as will changes in the intensity of particular passages of sound from the record or radio.

The curves of Fig. 3 show the measured performance of the unit over a 20 db range. It can be seen how closely it follows the change in the human ear response over the same range (obtained from information supplied by the Acoustical Society of America). In taking these measurements, C_1 is shorted out, so that the control frequency and the controlled frequency can be the same. In actual operation, the controlling frequencies are primarily above 500 cycles because of the RC circuit used in the input of the rectifier. Using different tube types and various changes in C_1 and/or R_5 , various amounts of control, over a wide range of frequencies, can be obtained.

A switch can be inserted in the cathode of V_{1B} , if desired, to disable the circuit's operation. In this manner, the effectiveness of automatic tone compensation can be more easily realized by comparison. If the cathode of V_{1B} is opened, the plate impedance will rise to its maximum, and the response of the circuit will be nearly flat over the audio range, with an insertion loss of 15 db. Closing the switch (grounding the cathode of V_{1B}) will leave the response and insertion loss unchanged at high volume levels, but will increase the insertion loss at the middle and high frequencies on low volume levels. This, in effect, provides an increase in the bass boost at lower volume levels, compensating for the non-linear intensity response of the human ear to low-frequency sounds.

This circuit should not be considered the solution to all audio problems, but rather as a building block, in the continuing search for the reproduction of sound in a small, acoustically imperfect room in our home, that will closely resemble the original sound as recorded in an acoustically treated room, at a much louder sound intensity. When considered in this light, it performs its function simply and inexpensively.

Fig. 3. Measured performance of compensator over a 20 decibel range. The dotted line is change in human ear response over a similar range of intensity. See text.

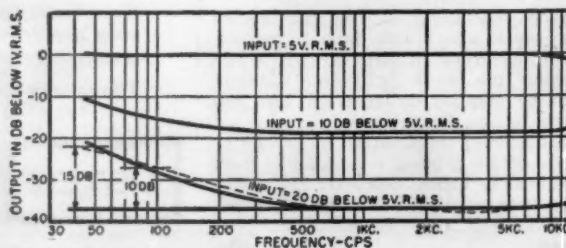

Compact Amplifier (Continued from page 63)


output transformer terminals be made exactly as shown or the feedback circuit will cause the amplifier to oscillate. For the same reason it is also important that the 6CM6 which is connected to terminals 1 and 3 of the transformer is the one whose grid is connected to pin 1 of the 6AN8 through C_5 . If a different transformer than the one specified in the parts list is used, it may be necessary to ground the 8-ohm tap of the secondary and connect R_{10} to the common terminal. This should be done if the amplifier oscillates.

The parts layout of the power supply is shown in Figs. 5 and 6. As in the amplifier, the parts layout is not critical and perhaps a smaller chassis could be used. R_{11} is mounted by connecting its leads to pin 2 of the 5Y3 and to the positive terminal of C_5 . R_{12} is connected between the positive terminals of C_5 and C_6 . The fuse holder is secured to the chassis with one of the screws holding the power transformer. Although the filter circuit is very simple, the noise voltage at the 8-ohm output tap is only one millivolt, or about 77 db below 6 watts.

If the amplifier is to be used with an external speaker to improve the audio quality of a radio tuner or as a playback amplifier for a record player or tape recorder that is equipped with an output jack, it is only necessary to connect a shielded lead between the output jack and the input to the amplifier. As an isolating capacitor is usually furnished in the set in such cases, the input resistor, R_1 , should be used. If the amplifier is to be used with a TV or radio set without an output jack, connect a shielded lead between the volume control of the set and the input jack of the amplifier. The lead should be connected to the arm of the volume control and the shield to the ground lug of the control. In this case, R_1 is not needed.

The gain of the amplifier is high enough so that only 0.7 volt of audio is required for the full six watts of output.


Fig. 7. Total harmonic distortion of audio amplifier is 1.6 per-cent at 6 watts output.

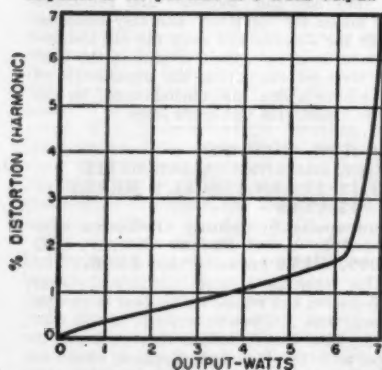

ARKAY Kits . . . lead the field

New! ANOTHER ARKAY WINNER!!

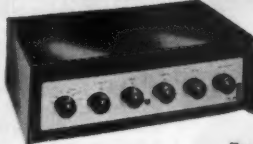SPECIFICATIONS:
POWER—30 watts @ 1% TH.
FREQ. RESPONSE $\pm 1/2$ db.—
10-50,000 cps.
HUM—120 db. below rated output (Actually zero)
CONTROLS—(6) Fm. selector, loudness, bass, treble, level set, 5-position level compensation control.
• 2 E2-34/SCA7 Super-Lin Williamson
• Special output for simultaneous tape recording and monitoring.



ARKAY Model FL-30 Hi-Fi AMP-PRE-AMP

Featuring a transistorized front end for use with a reluctance pick-up, this engineering masterpiece assures the finest in Hi-Fi reproduction. Record equalization for more than 30 labels (LP, RIAA, and EUR). Complete with rose gold panel and black cabinet.

\$49.95



ARKAY Model FL-10 Hi-Fi AMPLIFIER

A super lin. Williamson 12-watt Hi-Fi amplifier with built-in pre-amp. 18 watt peak with a frequency response of 20-40,000 cps. 4 controls including record equalization (LP, RIAA, EUR). Output impedances, 4, 8, & 16 ohms. Special output for simultaneous tape recording and monitoring.

\$29.95

ANOTHER ARKAY FIRST!!

SPECIFICATIONS:
ELECTRICAL RATING—9-volt transistor energizer.
OPERATING FREQUENCIES: Tuning range—540 to 1620 KC. LP amplifier—455 KC.
POWER OUTPUT—275 + milliwatts.
SPEAKER—large alnico V permanent magnet.

TRANSISTOR COMPLEMENT: X1 oscillator-converter; X2 1st LP amplifier; X3 2nd LP amplifier; D1 diode detector-AGC take-off; X4 class B driver; X5 class B output; X6 class B output.
Federal Excise Tax Included **\$37.50**



ARKAY Model B-8 Hi-Fi Speaker System

Frequency Response: 10 to 20,000 cps. Crossover Frequency: 1600 cps. Power Rating: 25 watts. Impedance 16 ohms. Features a bass reflex, ducted port enclosure equipped with a low frequency speaker and a compression driven horn of special design. A variable balance control w/network provides smooth continuous adjustment of the H/F speaker.
Fed. Ex. Tax Incl. . . . **\$35.95**



ARKAY Model 14T21 NEW! TV KIT

Very latest design used in sync. circuits results in excellent stability with extremely low noise characteristics. A.G.C. circuit results in maximum sync. hold characteristics. The only vertical chassis construction, series-string-heater type tubes, vertical retrace blanking circuits, and many more features. **\$79.50**

FREE! Get the new, big catalogue & specifications of the remarkable ARKAY line—Now at your local dealer!
Prices 5% higher West of the Mississippi

ARKAY 120 Cedar Street • N. Y.

MUST MOVE OUR WAREHOUSE

Set Builders—Experimenters

GIANT SURPRISE KIT \$4.95

25-30 lbs. of brand new RADIO PARTS . . . no junk . . . Transformers, Filter and Bypass Condensers, Resistors; Wirewound, Carbon, Volume Controls, Sockets, Wire, Variables, Chassis and Gang Switches. Parts that every Service Man, Experimenter or Ham needs. Express or Freight Shipments Only. No C.O.D.

NEWARK SURPLUS MATERIALS CO.
324 PLANE ST., Newark, N. J.

Top Pay Jobs in TV-ELECTRONICS-RADIO

High pay, opportunity, prestige, security . . . all yours, as a qualified Electronics Technician! Get your training NOW in the big, recognized shops, labs, and TV-Radio Studios at National Schools in Los Angeles, foremost since 1905. Here you work with latest Electronics equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school. Part time job while you learn. Mail coupon NOW, TODAY . . . for full information.

NATIONAL SCHOOLS

National Schools Dept. RXN-27
4000 So. Figueroa Los Angeles 37, Calif.
Send Free Electronics Opportunity Book Today

Name _____ Age _____
Address _____
City _____ State _____

hi-low

with ATLAS

high quality
low price



PAGING & TALK-BACK SPEAKERS
6 sizes and types.
All impedances
from 4 to 45 ohms.
From 5 to 15 watts.
From \$15.00 to \$24.00 NET.



WEATHERPROOF LINE MATCHING TRANSFORMERS
For constant impedance
or constant voltage systems.
\$5.00 NET.



HIGH-POWERED PUBLIC ADDRESS SPEAKERS
Four sizes from 2 1/2' to 6' air column.
From \$10.00 to \$39.00 NET.



U-I APPROVED EXPLOSION-PROOF SPEAKERS
For hazardous applications.
Several sizes, all classes.
From \$66.00 to \$75.00 NET.



SUPER-POWER DRIVER UNITS
For all purposes,
powers, frequencies.
From \$15.00 to \$30.00 NET.



MIKE STANDS & ACCESSORIES
All sizes and types:
boom stands, desk stands,
adapters, fittings, etc.



NEW! SWITCHBOARD MIKE SUPPORT
Adjustable 12" goose
neck. Use as desk support,
for dispatcher office,
dais, table, etc.
#SB-1 ... \$7.80 NET.



NEW! "CHESTY" NECK-SUPPORTED MIKE STAND
Quick, easy 3-way
adjustment. Lightweight.
Multiple uses.
#NS-1 ... \$3.00 NET.



NEW! MIKE FOOT SWITCH
Hand, foot or knee
operation—shielded,
grounded, noise-free,
dependable, damage-proof.
#FS-1 ... \$7.20 NET.



SEND FOR COMPLETE
FREE CATALOG
ATLAS SOUND CORP.
1446 39th St., Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp.,
Ltd., Toronto, Ont.

Certified Record Revue

(Continued from page 50)

percussive but properly so for most of this work. All orchestral elements are nice and clean, frequency and dynamics are wide in range, acoustics live and spacious. Unhappily most of this fine sound is for naught as in the over-all picture the impression is that orchestral weight is insufficient. I can't be sure of this, but offhand I'd say the orchestral forces employed were on the thin side, definitely not at full complement. Still, if you want the best sounding version of this work, this will have to be your choice.

JANACEK

SINFONIETTA TARAS BULBA (RHAPSODY FOR ORCHESTRA)

Pro-Musica Symphony of Vienna conducted by Jascha Horenstein. Vox PL9710. RIAA curve. Price \$4.98.

This recording is a few months old and somehow got mislaid. It is more than worthy of being brought to your attention, despite the time lapse. "Taras Bulba" is a somewhat programmatic work depicting some highly dramatic scenes in the life of a 15th century Cossack hero. The music is a rather odd admixture of romanticism with a liberal admixture of atonalities and dissonances strictly 20th century in origin. It is quite entertaining to listen to and easily assimilated and, incidentally, is a first rate vehicle for hi-fi treatment.

Quite another matter is the "Sinfonietta". A very powerful work with a highly astringent flavor, the first, third, and the allegro of the 4th part calls for incredibly massive orchestration. Most of the instrumentation is doubled and there are extras beyond that as well. As you might expect, this is productive of some mighty sound, and the sonority of the massed brass in the opening bars is, to put it mildly, impressive. Good clean sound and fine balance throughout the two works and it is recommended to you as an interesting "off-beat" musical experience.

TCHAIKOVSKY

SYMPHONY #2 ("LITTLE RUSSIAN")

L'Orchestre de la Societe des Concerts du Conservatoire de Paris conducted by Georg Solti. London LL1507. RIAA curve. Price \$3.98.

Here is a gem of a recording. For Tchaikovsky buffs who have had a surfeit of the 4th, 5th, and 6th symphonies, this delightful work is like a refreshing sea breeze. This ingratiating score deserves much more exposure in the concert hall. It has all the elements so dear to the lover of Tchaikovsky's music. It is tuneful and melodic . . . it has infectious rhythms . . . it generates excitement in its surge and sweep. I find Solti's reading at least the equal of the Beecham/Columbia disc of several years ago. Beyond this Solti has the advantage of some of London's very top engineering. This is a sensational hi-fi work in almost every movement and especially in the ebullient scherzo. Here you will find percussion to gladden the hi-fi heart, including a really tremendous bass drum that on a big speaker system will give forth with a candle-snuffing, windy WHUMP! All elements are beautifully clean and articulate, frequency response and dynamics very wide, acoustics very live and spacious. Highly recommended.

TCHAIKOVSKY

FRANCESCA DA RIMINI CAPRICCIO ITALIEN

London Symphony Orchestra conducted

by Anthony Collins. London LL1441. RIAA curve. Price \$3.98.

More Tchaikovsky from London and a real hi-fi dazzler! If you like these two works coupled together, there is no question of superiority over the only other such coupling on the *Allegro* label. Taken separately, there is a divergence of opinion. Collins is rather slow-paced in "Francesca da Rimini" and also misses some of the essential passion of the work. His reading of the "Capriccio" is competent and workmanlike, but he is out-gunned in drive and excitement, notably by Beecham and Dorati. And the Dorati/Mercury even outguns it in hi-fi terms, although it must be admitted that I am really referring to kind or type of hi-fi sound rather than degree of "hi-fi-ness" in itself. "Francesca" has a much clearer field in the sound department being demonstrably superior to the fine Capitol version or London's own earlier efforts. Good clean string work here, with the annoying edginess that has plagued earlier recordings of "Francesca" happily absent. Exceptional cleanness and wide dynamics throughout both scores.

MASSENET

MANON (COMPLETE OPERA)

Victoria de Los Angeles, Henri Legay, Michel Dens, and other soloists with the chorus and orchestra of the Theatre National de l'Opera-Comique conducted by Pierre Monteux. Victor LM6402. RIAA curve. Price \$15.92. Four discs.

The big news here is Papa Pierre Monteux at the conductorial helm. Under his skillful baton we are given a performance that is ravishingly beautiful and I predict that few opera lovers will be able to resist this recording. All the elements are most happily French, a frame of reference where they belong, except of course, Victoria de Los Angeles. And what an exception! This role is almost tailored for the sweet-voiced lady of Spain and she makes the most of it. Throughout the work she traverses all difficulties with consummate ease and at all times is clear-voiced and completely articulate. Legay is a solid and convincing Chevalier, Jean Borthayre as the Count Des Grieux, is a compelling and believable figure and Michel Dens essays the role of Lescaut, with a voice of considerable beauty although his weak top register was annoying at times. All other soloists were well suited to their roles.

The choral and orchestral scoring was a revelation in the hands of Monteux. His acute sense of balance, his deft handling of tonal masses and textures, his pacing and phrasing contribute mightily to the enjoyment of this opera. Soundwise this is an outstanding job. Vocal and orchestral balances were smooth and complementary. Frequency response and dynamic range was as wide as I've ever heard in an opera recording. Acoustics were intelligently employed, so that there was nice crisp definition to the voices and instruments, yet they had the "liveness" and roundness that makes for "presence" and easy listening. While the London and even the old Columbia recordings have their virtues, in the final and over-all evaluation the superiority of this album is clear and unchallenged. An absolute "must" for the opera lover.

STRAUSS, RICHARD

DER ROSENKAVALIER SUITE TILL EULENSPIEGEL'S MERRY PRANKS

Minneapolis Symphony Orchestra conducted by Antal Dorati. Mercury MG 50099. RIAA curve. Price \$3.98.

This recording is quite fantastic. If your hi-fi system can reproduce all that is on this record, man . . . you've arrived! It will take a very fine system indeed to even begin to cope with the incredible dynamic range of this disc. Fair warning to all who play this

RADIO & TELEVISION NEWS

record . . . don't start this disc at what you would consider "normal room volume", otherwise later on you will find yourself being blown out into the street! This is especially true with "Der Rosenkavalier", and in fact there are several parts of this recording where if you encounter tracking difficulties, you had better suspect your system rather than the record. "Der Rosenkavalier" has long been a Dorati specialty and his reading of it on this disc is quite stunning. In it he combines the sharp pungency, and weighty power of the score with the beautiful lilting waltzes and the exquisite melodies in a manner that betokens complete mastery of his idiom. Oh, there are several other conductors one could name whose readings have more of the old "gemutlichkeit", but I feel this attitude should really be reserved for the opera itself and that the "Rosenkavalier" suite should be treated almost as a separate entity. And an entity which demands much more robust handling.

"Till Eulenspiegel" is somewhat less successful in performance. Dorati's fast pace and rhythmic drive are certainly not lacking in excitement, or exhilaration, but some of the final drama is missing that characterized the reading of the late great Clemens Krauss. But I quibble on minute points . . . this is such an orchestral *tour de force* that it leaves one breathless. Here you will find strings that sound clean and smooth but which also have a hard and incisive bite when called for, woodwinds mellow in their sonic contour or sharp and piercing as the score demands . . . and the brass resounds mightily throughout both works. The opening of "Der Rosenkavalier" heralded by the French horn and trombones is impressive and then a few bars later the incredible sound, so typically "Straussian", of the French horns in that unison triplet figure in an impossibly high register really floors you! Percussion throughout both scores is thunderous and in parts of "Rosenkavalier" it hits like a battering ram. Add the usual spacious acoustics favored by *Mercury* and the over-all result is an overwhelming musical experience. I can't recommend this too highly.

BACH, J. S.
DOUBLE CONCERTO IN D MINOR
FOR VIOLIN, OBOE, AND
STRINGS
TRIPLE CONCERTO IN A MINOR
FOR FLUTE, VIOLIN, HARPSI-
CHORD, AND STRINGS

Solisti di Zagreb conducted by Antonio Janigro. Vanguard BG-562. RIAA curve. Price \$4.98.

The Solisti di Zagreb is a chamber orchestra made up of thirteen strings played by performers of virtuoso caliber. They are still another of the musical groups from Europe that have been touring the United States and embellishing our local music scene. *Vanguard* has recorded this splendid ensemble and issued four discs containing generous samples of their art. This disc concerns itself with old master Bach and I can't urge you too strongly to listen to it. This is certainly one of the finest chamber recordings ever issued. The performances are superbly executed, with Janigro lovingly revealing the inner depths of the scores. He and the Solisti show us the flawless symmetry, the subtleties and nuances of dynamics and phrasing, the fullsome expression, the unalloyed beauty of these works.

The cleanness of tone and the precision and warmth of the playing of the Solisti is something at which to marvel. *Vanguard* has clothed them in a rich tapestry of sound and from every aspect of frequency range, dynamics, transient response, balance and acoustics the disc is well high perfection. If you are one of those people who instinctively



NOW... there's a
GARRARD
 Auto-Manual
 Record Changer
 for every
 hi-fi system



Full manual and automatic positions. True-turret drive... uses no belts. 4-pole "Induction Surge" motor. Foot-proof Garrard Pusher Platform.

World's Finest
 RECORD PLAYING EQUIPMENT
 from Manual Players to
 Professional Transcription
 Turntables

New
RC 88
Deluxe Changer
\$54.50
 net




New
RC 121
Mini Changer
\$42.50
 net

Garrard's most compact, economical changer - fits any cabinet. Simpli-Mix Operation permits stacking all record sizes together. 4-pole motor. Manual position.



New
RC 98
Vulgar Changer
\$67.50
 net

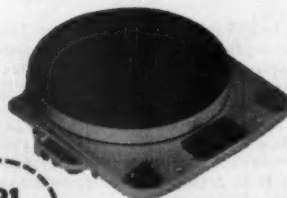All RC 88 features, including full manual position and true-turret drive, PLUS continuous + or - variable speed control on all 3 speeds.



301
Turntable
\$89.00
 net

Supreme in its class. Individual card gives performance measurements for each unit. Dynamically balanced cast aluminum turntable. Heavy-duty 4-pole shaded motor.



Model T
Manual Player
\$32.50
 net

This is the answer for a quality budget system. Incorporates all record playing features of the famed RC 80 record changer. 4-pole motor; automatic stop.

MAIL THIS COUPON TODAY

All Garrard and other B.I.C. components are illustrated and described fully in the B.I.C. High Fidelity Plan Book, a useful guide in planning any hi-fi system.
 A quality-endorsed product of the B.I.C. Group



To: British Industries Corporation Dept. GB-47
 Port Washington, N. Y.
 Please send B.I.C. High Fidelity Plan Book.

Name _____
 Address _____
 City _____ Zone _____ State _____

ZYTRON "QUALITY BRAND"

RADIO & TV RECEIVING

TUBES

BRAND NEW
 INDIVIDUALLY BOXED

Terrifically LOW PRICED!
 Send TODAY for Complete Catalog

ZYTRON TUBE COMPANY

270 West 42nd Street - New York 36, N. Y.

Learn About SOLAR POWER

Complete booklet tells how to build electric and photometric devices powered by the SUN

See how easy it is to make solar-powered devices using INTERNATIONAL RECTIFIER CORPORATION's sun-generating SUN BATTERIES. Start this exciting hobby now by getting your copy of "The Use of Selenium Photo-cells and Sun Batteries."

CONVERT SUN POWER INTO USEFUL ELECTRICITY - by building devices powered with sun batteries that will last indefinitely. Put the sun to work for you. Build sun-powered radio receivers, automatic lighting controls, photometric devices and many other practical devices by using the sun for power.

INTERNATIONAL RECTIFIER CORPORATION
 81 Segundo, California

This booklet is available through your favorite electronic parts distributor at \$1.50 per copy, or if he is temporarily out of stock, send check or money order today!

Concert Orchestra conducted by Prof. Klaus Liepmann. Unicorn UNLP1032. RIAA curve. Price \$3.98.
BEETHOVEN

PIANO SONATAS #30 AND #31
Ernst Levy, pianist. Unicorn UNLP1033. RIAA curve. Price \$3.98.

These three recordings are the most representative of a group of six issued under the generic title, "Music at M.I.T." by Unicorn Records. "M.I.T." is of course the abbreviation for the famous Massachusetts Institute of Technology. These recordings were made at the new Kresge auditorium and M.I.T. Chapel and are of more than passing interest. Both are super-modern structures which have been designed for specific acoustic balance by famed M.I.T. acoustic authority Leo Beranek and colleagues Bolt and Newman. Space is too limited to go into a detailed explanation of the design and construction which, however, is covered at some length on the back of the record jackets. Suffice to say that nearly ideal reverberation characteristics have been produced for recording purposes. Such is the design that the acoustic "climate" for a given piece of music can be fairly well controlled.

These discs, as recorded and mastered by expert Peter Bartok, are indeed impressive. I still feel that the acoustics, however idealized, would not be perfect for all types of music. Usually, in the new auditoriums which have been designed for maximum intelligibility in the speech frequencies, there is trouble in obtaining a good solid bass and in keeping higher frequencies from becoming hard and overbright. Perhaps this will not be true of the new M.I.T. structures . . . in subsequent issues with the possibility of larger repertoire we will be in a better position to judge.

The brass recording has works by four modern composers including the great Paul Hindemith. There is a great deal of atonality and dissonance here with the Berezowski "Brass Suite", the most listenable and easily assimilated. There are some truly remarkable brass textures and sonorities on this disc. The sound is very sharp and bright, transient response is superb, the over-all acoustic impression is that it affords extreme clarity and instrumental definition with spaciousness for a great deal of that elusive thing called "presence". There is also a little niggling thought that good as these acoustics are, there is a sort of "dry" overtone, that some may like and others find too "sterile".

The Handel concerti performed with fine competence by Moe on the Holtkamp Baroque organ installed in the Chapel, are models of clean sound. In spite of Mr. Moe's somewhat excessive use of staccato, definition is sharp throughout and the orchestral parts are projected with equal clarity.

Levy, the pianist in the Beethoven sonatas, is somewhat heavy handed and many will take exception to this while others will admire his robustious thundering. The piano is magnificently delineated. Albeit the tone is a little hard, this is razor sharp, crystalline clear piano sound, with extraordinary transient response. The harmonic structure is quite easily discerned and, all in all, one looks forward to hearing piano concerti from this hall.

Summing up . . . these are musically acceptable performances recorded with exemplary sound quality, with the reservation that the type of sound may not appeal to all tastes.

THE TONE POEM

Victor LM6129. RIAA curve. Price \$11.94. Three discs.

This is a miscellaneous collection of what is generally described as "tone poems", some of which are new to records and others which have appeared in previous editions. The


February, 1957

A NEW CONCEPT IN SPEAKER DESIGN


...From Altec Lansing Laboratories

Exceeding the expectations of even those engineers who worked on the design and development of Altec Lansing's new Biflex speakers, the principle of "multiple concentric compliances" has provided almost unbelievable new performance at very nominal cost. By separating a single cone into two segments with a flexible connection, Biflex speakers achieve a smoother and more extended frequency range than any other single cone loudspeaker.

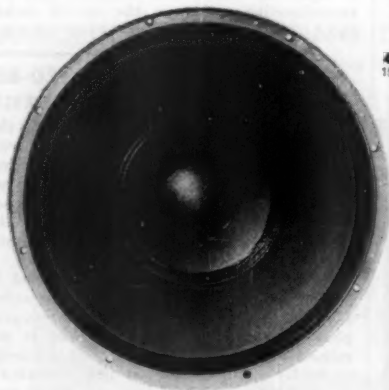To convince yourself of the truly remarkable performance of Biflex speakers selling for as little as \$27.00, you have only to listen for yourself. Only by hearing the Biflex can you believe that so much high fidelity can be yours for so little.



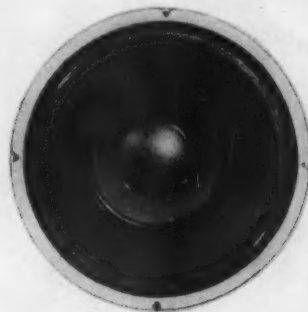415A
15", 25 watts, 30-14,000 cycles, \$83.00



412A
12", 20 watts, 40-15,000 cycles, \$48.00



408A
8", 15 watts, 60-16,000 cycles, \$27.00

These guaranteed frequency responses, measured in Altec's anechoic chamber, are minimum specifications and will be met or exceeded by the Biflex speaker you buy.



ALTEC FIDELITY IS HIGHEST FIDELITY

Dept. 2 T
1515 S. Manchester Ave., Anaheim, Calif.
161 Sixth Avenue, New York 13, N.Y.



ASTOUNDING PERFORMANCE

FROM

20 to 20,000 CYCLES

WITH

GOODMANS

AXIOM 80


free suspension

LOUDSPEAKERS

and ARU

friction loaded

ENCLOSURES

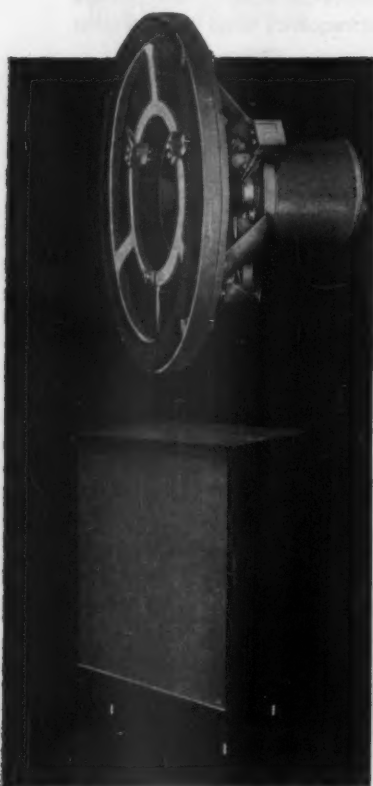

ROCKBAR CORPORATION Dept. ZB-5
430 Halstead Avenue, Mamaroneck, N.Y.
In Canada: A. C. Simmonds and Sons, Ltd.
Toronto, Ontario

Please send me complete details on
Goodmans Axiom 80 speakers and
ARU Enclosure Kits.

Name _____

Address _____

City _____ Zone _____ State _____

standout works are superb performances of Liszt's "Mephisto Waltz" and Strauss' "Don Juan" under Fritz Reiner and the Chicago Symphony. Also of much merit is Copland's "El Salon Mexico" and Ravel's "La Valse", as well as Ibert's "Ports of Call" as done to a turn by Stokowski. Five other varied works fill out the six sides and throughout most of the scores the sound is good and clean with some outstanding realism in the works mentioned. An ideal album for those beginning to assemble a record library.

JOHNNY DUFFY

Theater organ. Liberty SL9003. RIAA curve. Price \$3.98.

CARNIVAL IN RIO

Leo Arnaud and his orchestra. Liberty LRP3020. RIAA curve. Price \$3.98.

THE BROTHERS NASH

Liberty LJH6011. RIAA curve. Price \$3.98.

VIBE-RATIONS

Red Norvo. Liberty LJH6012. RIAA curve. Price \$3.98.

SMORGASBORD

Liberty LJH6008. RIAA curve. Price \$3.98.

CALENDER GIRL

Julie London. Liberty SL9002. RIAA curve. Price \$3.98.

An enterprising new company in Hollywood by the name of *Liberty Records* has been turning out material that deserves mention for the musical content and especially for the outstanding sound quality. All the listed recordings are prime examples of the kind of work they do. The organ recording is superb in clarity and definition and the accompanying notes on the record jacket about the organ and the recording are very

well done. In their respective fields the recordings listed have some of the best sound I've heard. Notable particularly is the transient response and the wide frequency and dynamic range. Their brass is really sharp and pungent, percussion has impact and is always crisp and completely articulate. They have chosen acoustic perspectives which allow for a maximum of "liveness" and "presence" and good instrumental separation without the excessive and objectionable echo chamber overhang found in so many pop recordings. These records make ideal demonstration material of the pop variety. If you go for this sort of thing these are definitely worth looking into and there are other titles in the *Liberty* catalogue you might find rewarding.

GRIGG

LYRIC SUITE

TCHAIKOVSKY

MARCHE SLAV

SIBELIUS

FINLANDIA

LISZT

HUNGARIAN RHAPSODY #4

Danish State Radio Symphony Orchestra conducted by Eric Tuxen. London LL1313. RIAA curve. Price \$3.98.

A potpourri of potboilers, but all expertly played by the superb Danish orchestra and recorded with sound of sumptuous quality. The "Marche Slav" sounds better here than in any competing version and the performance is all one could desire. An outstanding record of its type.

Stereophonic Tape

PROKOFIEFF

ROMEO AND JULIET (EXCERPTS)

A SIMPLIFIED GATED-BEAM FM DETECTOR CIRCUIT

By CHARLES ERWIN COHN

THE gated-beam FM detector using the 6BN6 tube has gained some popularity in this country. It uses a tuned circuit in the quadrature grid of the tube on which a voltage, 90 degrees out-of-phase at center frequency with that on the limiter grid, is induced by electrostatic induction within the tube.

There is, however, a circuit used in England with the EQ80 "nonode" seven-grid tube, in which the 90 degree phase difference between grids is obtained much more readily. This circuit is easily adaptable to the American-made 6BN6 and will give excellent performance, especially since the 6BN6 limits more readily than the EQ80.

The circuit is shown in the diagram. It will be noted that the limiter grid of the 6BN6 is fed from the secondary of the last i.f. transformer, while the quadrature grid is fed from the primary. The voltage on the secondary of the transformer will be 90 degrees out-of-phase with the primary voltage at the center frequency due to the transformer action, with the phase difference departing from 90 degrees away from the center frequency.

As in the conventional circuit, this phase difference determines the width of the pulses of plate current occurring at the signal frequency, which are integrated in the plate circuit to yield an audio signal.


This circuit is somewhat less critical to build than the conventional circuit since the latter must have a quadrature coil with a very high "Q" and a very high L/C ratio in order that sufficient voltage be developed across it by electrostatic induction. In the circuit diagrammed here, any i.f. transformer

suitable for quality FM reception may be used, except that it must not be overcoupled. If an overcoupled transformer is the only one available, its coupling must be brought below the critical point by proper damping of the primary—a step which can be done most easily by adjusting the value of the quadrature grid resistor. Capacitive coupling between the primary and secondary must be avoided, both in the transformer and in the external wiring since such coupling would upset the phase relationships. In order to get proper performance, the i.f. amplifier must provide an ample signal at the 6BN6 to give good limiting.

This circuit is very easy to align. The transformers need only be peaked up on an AM signal or on noise. The secondary of the detector transformer might have to be touched up for best sound on an actual signal. As in the conventional circuit, the cathode pot should be set for the most advantageous AM rejection.



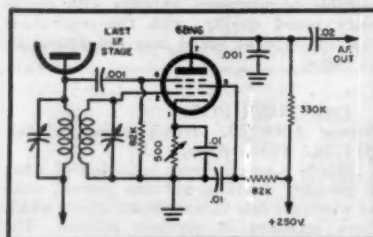An adaptation of a British FM detector circuit using an American-made 6BN6 beam tube.



NBC Symphony Orchestra conducted by Leopold Stokowski. Victor DCS-18. 7" reel, NARTB curve. Price \$12.95.

Repeated listenings to this tape convince me that this is one of the very finest stereo-tapes yet to appear. This is an extraordinary musical and sonic experience. The music is quite wonderful, surely one of the best things Prokofiev has done. It combines the elements of exquisite melodies spiced with typical Prokofiev atonalities, with moments of drama of searing intensity. As a vehicle for the talents of Stokowski it is nigh perfect and he makes the most of it and elicits a stunning performance from the NBC men. As for the sound . . . it is tremendous. I wouldn't be at all surprised if the presence of Stokowski was partly responsible for this excellence. He has experimented more with sound than any other conductor and is generally acknowledged to have made some important contributions to the recording art. He has always had an intense interest in stereophonic reproduction, as witness the early efforts with "Fantasia" (which is not really true stereo, but is fairly effective nonetheless). Because of his interest in the subject I have had the pleasure of recording stereophonic tapes with Dr. Stokowski on a number of occasions. One that comes to mind was really something . . . a Monteverdi "Vesper Mass" with full orchestra, several hundred voices and organ. I hope some day he can do this work for commercial issue.

The general cleanness of this tape and the breathtaking instrumental clarity and definition are something to hear. The sense of directivity is excellent, and once again, the "hole-in-the-middle" effect was minimal. Some of the brass sonorities on this tape are astounding in their weight and brazenness, and in the first section some low, low bass drum thuds of exceptional power. Some of the strings here are bowed so intensely and in such a high register that I am sure that in any other medium except stereo, they would have an edginess that would be unbearable. Here they are not only bearable but add immeasurably to the drama of certain sections. Balance both orchestrally and acoustically was excellent and tape hiss, while still noticeable was down considerably from the last Victor tape I have played. Nuff said. If you are a stereo fan, this will surely become one of your most oft-played tapes.

TUBE REJUVENATION

By CHARLES ERWIN COHN


IT HAS been common practice to reactivate weak picture tubes by subjecting them to an above-normal filament voltage for a short time.

This technique can be easily extended to ordinary receiving tubes, using an ordinary tube checker. If a tube tests weak, turn up the filament voltage control while holding down the test button. At each step, see if the needle rises into the "good" scale. When it does, hold the setting until the needle stops moving. Then turn back to normal filament voltage and see where the needle again comes to rest. If it remains in the "good" scale, the reactivation can be considered successful.

Go through the shorts check again to see if any shorts have been induced by the process and if the tube checks out on this, return it to service. Don't be afraid to pour on the filament voltage as most tubes, except battery types, can stand over twice their normal voltage without blowing. However, since a weak tube would be discarded anyway, it is a risk worth taking. Results with this process will be found extremely variable, some tubes responding well and some not at all.


FAIRCHILD

PRECISION

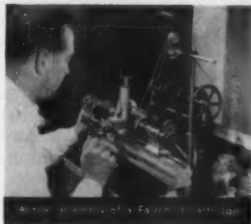

The marked similarity between the watchmaker's art and the craftsmanship required to produce a precision cartridge can be aptly illustrated by an examination of the famous FAIRCHILD Micrad-just Cartridge.

Meticulous care and delicate assembly are basic to both products. In addition, adjustments are provided in the finest of watch movements to regulate performance by compensating for minute differences in manufacturing tolerances as well as variations in material. Similarly the MICRADJUST feature permits regulating the magnetic gap to precisely fit the moving coil assembly.* The result is uniform flux gap, proper centering of stylus arm and correct damping. It assures best possible cartridge performance which is immediately apparent to the critical listener.

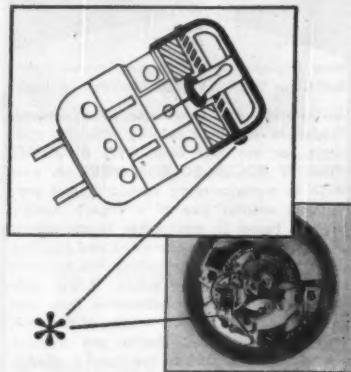

Write for details on FAIRCHILD audio products.

FAIRCHILD RECORDING EQUIPMENT COMPANY

10-40 45th Avenue, Long Island City 1, New York

NOW! HI-FI (FM) IN YOUR CAR!

Only BLUE SPOT offers all these features!

Concert Hall Sound under bridges, through short tunnels, next to high power lines, even in lightning storms!

Constructed to outlast your car.

Coaxial Speakers, 6" x 9", full-range tone control, built-in rear speaker plugs, separate amplifier, 6 to 12 volt convertibility.

Compact design fits most American and foreign cars. Service throughout the U. S.



BLUE SPOT Köln Mark I

Selectomagic Tuner—the first FM "one touch" signal seeker in a car radio.

FM—3 microvolts for 20 DB quieting; AM, 3 microvolts. Response 40-16,000 c.p.s.—image rejection 25 DB.

HI-FI—15 tuned circuits FM and AM.

BLUE SPOT Frankfurt Mark I

FM—plus HI-FI, AM and Pushbutton Selectometer. De luxe, yet economy-priced version of the Köln Mark I.

BLUE SPOT Hamburg

Luxury AM car radio—economically priced. Magnificent sound, pushbutton station selector, ruggedly engineered.

AMERICAN ELITE, INC.

7 Park Avenue, New York 16, N. Y.

Importers of Telefunken and Audio Elite home Hi-Fi Sound Systems, Tubes, Components, Microphones . . . and Blue Spot car radios.

Write Dept C for free pamphlet and information.

Introducing



DFF


**DUOTONE
FIDELITY
FOCUS
Loudspeakers**

New Engineering Technique Assures You—
Bell-Clear Highs; Vibrant-Undistorted Lows.

DUOTONE—For a quarter of a century, leader in the high fidelity industry, presents for the first time, **DFF, DUOTONE FIDELITY FOCUS LOUSPEAKERS**. A new high in manufacturing standards and procedures assures you of a superb quality seldom found in most other loudspeakers. Rigid specifications adhered to and exacting field trials were made before this fine line was presented to the public. It was only the results of these exhaustive tests that assured us of a product worthy of the HI-FI enthusiasts interests. Whether you choose a coaxial speaker such as the Royal or Medallion, or a woofer-tweeter combination like the Supreme and the Duchess, you will be more than satisfied with the excellent response these speakers afford. Stop into your HI-FI dealer's showroom and ask to hear them. Your reward will be the self-satisfaction of hearing excellent high fidelity sound reproduction. There's a **DUOTONE FIDELITY FOCUS LOUSPEAKER** to match your system and they are priced to \$53.97.


Write today for our **FREE** new booklet, "An Objective Study of Loudspeakers". It's designed to help you choose and install your speaker system.

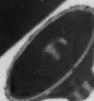12 in. Coaxial
Cat. No. 12CX-62
35 to 18,000
cps. Power:
25 watts Imp:
8



The ROYAL

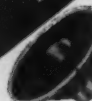12 in. Coaxial
Cat. No. 12CX-60
35 to 18,000
cps. Power:
15 watts Imp:
8




The MEDALLION

8 in. Coaxial
Cat. No. 8CX-50
50 to 20,000
cps. Power:
10 watts Imp:
8



The MARQUIS

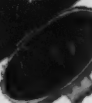8 in. Coaxial
Cat. No. 8CX-70
75 to 19,000
cps. Power:
6 watts Imp:
8




The VISCOUNT

4 in. Tweeter
Cat. No. 4-TX
1000 cycles to
beyond aud.
Power: 5 watts
Imp: 8



The DUKE

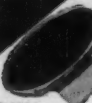7 in. Tweeter
Cat. No. 7-TX
350 cycles to
beyond aud.
Power: 10 watts
Imp: 8



The DUCHESS

DUOTONE
KEYPORT, NEW JERSEY

Realistic High Fidelity (Continued from page 53)

are!). You can mark off a rule of stiff paper, starting 1,2,3 etc. from a center point O, eleven millimeters apart on the left and nine millimeters apart on the right, which will enable you to pick the right load line position for 5% distortion, by putting the center zero of the rule on the mean grid voltage curve. Swinging the rule about point O on the 6L6 curve will indicate that you can't dodge that 5% distortion anyhow. If you moved the operating point O from the -15 volt curve to the -30 volt curve you only need to look at Fig. 38 to see that the distortion would become excessive owing to the crowding of the characteristic curves. And before I go on to the next step, remember that precisely the same rules apply to the curves of the tube when used as a tetrode. The curves have a different shape, but the "family" of curves is subject to the same considerations.

But, of course, you have heard that push-pull operation cancels out second harmonic distortion. Why should it do this? If you imagine the load line *XOY* bent upwards in its lower half so that it runs roughly parallel to the dissipation curve, you can also see that it would cut the grid voltage curves in a much more regular manner, and so reduce distortion. This is what, in effect, happens with push-pull operation, and is illustrated by Fig. 39, which shows two 6L6's in class A triode push-pull. This diagram is simply two Fig. 38's joined back to back, with the 400-plate-volt ordinates (the operating point) coinciding. The dotted families of curves are those of Fig. 38, but new solid lines (composite "curves") take up positions exactly between the corresponding pairs of curves of the two single tubes. These solid lines are the characteristics of the combined pair, and are cut by the load line *XOY*. This is the equivalent of the load line *XZ* shown in the upper half of the diagram, being that imaginary curved load line I mentioned before. I have also drawn the load line *AOB*, which will give a greater power output than *XOY*, but this particular value was chosen to show a considerable trespass into the region greater than 25 watts dissipation, so the tubes would be overloaded on large signal inputs.

In practice the position of the load line affects the distortion at third and fourth harmonics as well as second. The amount of distortion of each harmonic can be calculated from data on the diagram, but the easiest way to check this point is to refer to the distortion charts given in many tube manuals, where distortion harmonic and total is frequently given for any value of load line with related power output.

When the load is a speaker, as it must be if we are to get any sound

LMB BOX CHASSIS OFFERS FREE inside LMB boxes

10 tested kit diagram projects for the builder. Each one of these kit diagrams built by a recognized expert. Kit projects are complete in every detail. Circuit diagram, photo of project both front and rear photo. Rear photo shows wiring and parts. Detailed instructions for building, complete parts list and approximate cost. Complete to build except parts and your distributor can supply the parts. Ask your distributor for the list of LMB kit Diagram Projects. If he does not have them, write to

LMB 1011 Venice Blvd.
Los Angeles, 15, Calif.

INVENTORS

Have you developed any new test instruments which you would like to have manufactured on a liberal royalty basis? We have complete manufacturing facilities and a top-notch nation-wide sales organization to assure maximum distribution. Write and give non-confidential disclosure of invention.

Box 555 RADIO & TELEVISION NEWS

NEW PICTURE TUBES

12 MONTHS GUARANTEE

10BP4B \$ 9.80	17LP4 \$21.50
12LP4A 12.85	17TP4 20.00
12BP4 18.00	19BP4B 25.40
14BP4 17.60	19DP4B 25.60
16BP4A 17.60	20CP4 20.90
18BP4A 18.59	20DP4 23.90
18BP4A 18.59	21AP4 25.60
18BP4A 18.70	21AP4 29.00
18BP4A 18.70	21EP4 25.50
18BP4 16.95	21FP4 26.50
18BP4 16.95	21WP4 27.65
18LP4 16.50	21WP4 26.95
18FP4 16.95	21YP4 26.50
18WP4 19.95	21ZP4 25.50
18BP4 19.95	24CP4 45.95
17CP4 20.00	24DP4 45.95
17DP4 20.00	24VP4 45.95
17BP4 20.00	24VP4 45.95
27" TUBES \$55.95		

Aluminized—\$3.50 extra except—24" tubes which are all aluminized

PRECISION ELECTRONIC MANUFACTURING CO.
218 E. 69th St. Chicago 37, Ill. VI. 6-5646

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

1957 PHOTOGRAPHY ANNUAL

A collection of the world's greatest photographs for the artist of Popular Photography



NOW ON SALE EVERYWHERE!

RADIO & TELEVISION NEWS

from the audio power generated, the load is partly resistive, partly inductive, and partly capacitive. In practice, the capacitive component is not usually considered important (although capacitances are shown in so-called equivalent circuits of loudspeakers). The reactance of the inductive component depends on the frequency and combining the resistive component with the reactance involves consideration of the phase of the reactance. The inductive load line is elliptical, and the major axis can be considered to coincide with the zero current ordinate of Fig. 39. Combining this with the pure resistive load line will produce an elliptical load resultant whose major axis is at an angle with respect to the original major axis, but not at the same angle as the resistive load line. To explain how this comes about would involve a fairly long mathematical discussion, but a little reflection will indicate that at certain frequencies the load on the output stage will be seriously out even if the slope of the major axis has been set for minimum distortion. As tetrodes and pentodes are more critical as to exact loading for maximum power output than triodes, the bias against the former has resulted in the fairly widespread belief that only triodes can be considered for really true fidelity.

Triodes, Tetrodes and Pentodes

This belief is founded on misapprehensions as to what is involved. The accuracy of load for tetrodes and pentodes is only of importance when the maximum possible "undistorted" power is needed, and early in this part I have suggested that for normal listening fewer watts than many people say they want is all they really need. On the other hand it is undeniable that the high plate impedance of tetrodes and pentodes does not give a good damping factor, and if feedback hadn't been invented, then the triode would be absolutely essential for the best results. But feedback can reduce the plate impedance of a pentode to a figure comparable with that of a triode—provided you remember my warning that feedback is not a cure-all for every amplifier ailment.

A triode amplifier can sound very good indeed without any feedback at all. It can be made better with feedback, but triode amplifiers as well as those using beam power tubes can be badly designed and made to sound respectable by adding as much feedback as possible. In the process low-frequency instability can be set up, due to the excessive phase shift caused by several voltage amplifier stages, for the basic disadvantage of triode output tubes is that they need plenty of volts applied to the grid to get the maximum output power. The performance of a well designed triode amplifier without feedback can be paralleled by using a pentode output stage with feedback across the output stage only. I made such amplifiers more

HOBBYISTS... EXPERIMENTERS!

LEARN HOW TO BUILD:

- Your Own Hi-Fi Tuner
- Thermistor Fire Alarm
- Electronic Gardening Gadgets
- A Device That Kills TV Commercials
- Electronic Toys
- Geiger Counter
- Transistorized Light Meter
- Your Own Lie Detector
- PLUS DOZENS OF OTHER HANDY ELECTRONIC DEVICES



Compiled by the Editors of
POPULAR ELECTRONICS

ON SALE EVERYWHERE FEBRUARY 19!




ZIFF-DAVIS PUBLISHING CO.

366 Madison Ave., New York 17, N. Y.

MF MADISON FIELDING *means...* **MAXIMUM FIDELITY**

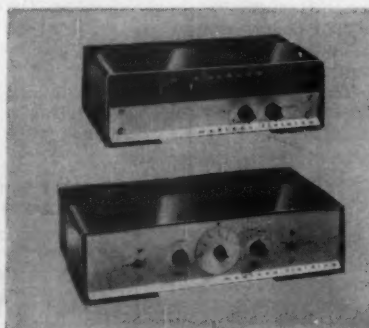MAXIMUM FIDELITY • The most advanced circuits...new transistor designs...incorporated into distinctive hi-fi instruments that are unsurpassed in appearance and lasting performance.



MADISON FIELDING FM TUNER • Series FM-15 with MICRO-BEAM! TUNING

Exclusive Micro-Beam—newest system of positive dynamic tuning. Sensitivity: better than 0.9 microvolts for 20 db of quieting...insures exceptional performance...reception range increased to over 150 miles. Stability: less than 20 kc drift from cold start—professional laboratory standards! Shielded front-end eliminates spurious radiation well within FCC regulations. 12" x 3 1/2" x 6 1/4".

ONLY \$79.95

MADISON FIELDING Integrated Amplifier • Series A-15 with EXCLUSIVE All-Transistor Preamplifier All-Transistor front-end guarantees zero hum and no microphonics. Frequency Response within .5 db, 20 to 20,000 cycles. 16 watts (32-watt peaks) of clean audio power at the speaker terminals. Seven input facilities. Loudness-Balance Control and sharp cut-off Rumble Filter. Control layout on front panel designed for real operating ease. 14 1/2" x 3 1/2" x 7".

ONLY \$89.95

Better Sound with your Present Tape Recorder...Phonograph...PA System!

MADISON FIELDING All-Transistor Matching Amplifier • Series 30 Perfect for phono use—matches low-level, low-impedance cartridges to any preamp. Also permits use of high quality, low impedance mikes with any tape recorder (even a home machine). Hi-Fi or PA system—dispenses with low-fi crystal microphones. Micamp improves overall frequency response, reduces distortion, eliminates hum pickup—even with 1500-foot cable. More than 30 db gain. Battery powered; coil lasts over a year in normal operation.

ONLY \$11.25 with battery



MF MADISON FIELDING CORPORATION

Creators of Distinctive Audio Instruments

869 MADISON STREET • BROOKLYN 21, N. Y.

for

LOWEST hum...noise... microphonics

in a high- μ dual triode...



the
Amperex®
ECC83 A PLUG-IN
REPLACEMENT FOR THE 12AX7

MICROPHONICS:

Negligible in amplifiers requiring an input voltage of at least 50 mv for an output of 5 watts. No special precautions against microphonics necessary even though the tube is mounted in the near vicinity of a loud-speaker with 5% acoustical efficiency.

HUM AND NOISE LEVEL:

Better than -60 db relative to 50 mv when the grid circuit impedance is no greater than 0.5 megohms (at 60 cps), the center tap of the heater is grounded and the cathode resistor is by-passed by a capacitor of at least 100 mfd.

OTHER Amperex TUBES FOR HIGH-FIDELITY AUDIO APPLICATIONS:

EL84/6BQ5	9-pin power pentode; 17 W PP
6CA7/EL34	High-power pentode; 100 W PP
EF86/6267	Low-noise high- μ pentode
ECC81/12AT7	Low-noise medium- μ dual triode
ECC82/12AU7	Low-noise low- μ dual triode
GZ34	Cathode-type rectifier; 250 ma.
EZ80/6V4	9-pin rectifier; cathode; 90 ma.
EZ81/6CA4	9-pin rectifier; cathode; 150 ma.

At All Leading Electronic
Parts Distributors

Amperex
ELECTRONIC CORP.
230 Duffy Ave., Hicksville, Long Island, N.Y.

than 20 years ago, when the beam power tube was still a novelty, and they sounded pretty good.

Also, using output tetrode or pentodes, the smaller amount of voltage amplification required usually saves one stage in the whole amplifier, so if feedback is applied across the whole amplifier, more can be used with pentodes than with triodes because of the smaller phase shift. I state in all seriousness that it is possible to design an amplifier with pentode output tubes with at least as refined a performance as one with triodes and, provided certain steps are taken to deal with the pentodes in a special way, the results can be better than any triode amplifier, for with at least one stage fewer the distortion over the whole amplifier can be less and the stability greater.

Practical Amplifier Circuit

Fig. 40 gives the circuit layout of my own amplifier referred to earlier in this part. It can be shown that if the screen voltage on a beam power output tube is held constant, whatever the input, the distortion is much less. If you examine the data sheets for the 6L6 you will find that curves are given for various values of screen voltage. The plate characteristics alter as screen volts are changed. At the same time you will find, from the tube manual data, that values are given for plate and screen current for zero signal and maximum signal. The plate and screen supplies originate in the rectifier tube and have to pass through the resistances of the smoothing choke and the output transformer primary winding. There is a voltage drop across these resistances, the drop depending on the current. Since both plate and screen currents change as the input grid volts change, the voltages on the plates and screens of the output tubes also change. Change of plate voltage is by no means as critical as change of screen voltage, and if the latter can be held constant, the almost chaotic conditions under which the output tubes have to work can be reduced to regulated order.


There are various ways by which the supply voltage can be regulated, a usual method involving a gas tube

shunted across the supply. This operates by providing a variable leak so as to keep the total current drawn from the supply constant; but it is not necessary to regulate the plate voltage; only the screen voltage is important. In Fig. 40 I use a 6J5 tube connected in a special way so that it acts as an automatic variable resistance in series with the screen supply, and has the effect of maintaining the screen voltage absolutely constant whatever the variation in plate or screen current. A separate 6.3 volt winding on the power transformer must be provided for the heater of this tube, since the whole tube is "hot" with respect to ground.

Other refinements will be noticed in the circuit. The screen supply is taken to a potentiometer, the ends of which are connected directly to the screens. By this means the output tubes can be balanced perfectly by slight compensating changes of screen voltage. In practice all that is needed for balancing is to connect a voltmeter across the whole of the output transformer primary winding. The potentiometer is adjusted until the meter shows zero reading indicating that there is no out-of-balance current in the transformer. This adjustment takes care of almost any pair of tubes; there is no need for buying them in matched pairs, and if only one tube has to be replaced at any time, the "set zero" adjustment is all that is needed.

Each output tube is provided with screen and plate suppressor resistors, connected directly to the tube sockets, and an r.f. bypass capacitor to each plate. These form supersonic oscillation filters, for the output stage is very efficient and could oscillate at r.f. if precautions such as these were not taken. Such oscillation is not audible (although sometimes visible when smoke comes from the speaker) but it can ruin the response of an otherwise fine amplifier. Associated with these two filters are series grid resistors. Again these should be connected directly to the tube sockets. The phase splitter is the conventional split load device, frowned on by some engineers, but I have always found it to be very reliable. The plate load is shown as two

Fig. 40. Schematic diagram of the Hartley 20-watt audio amplifier with stabilized voltage supply to screens of the power output tubes. For discussion, refer to text.

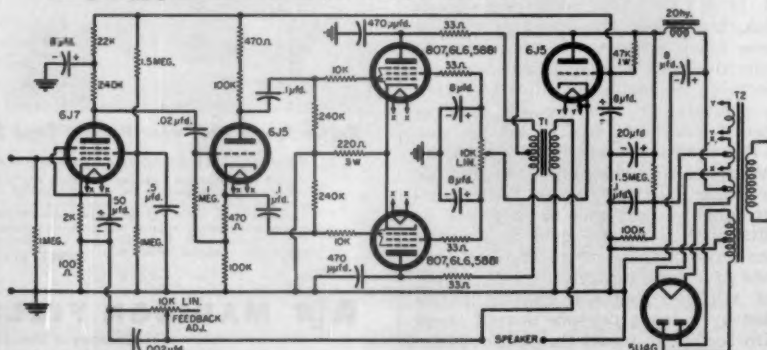

NOTE: T1, T2 TO SUIT TUBES AND SPEAKER IMPEDANCES

resistors. These need not be separate (in production this was found convenient) but what is more important is that the total plate resistance must equal the total cathode resistance. Similarly the output coupling capacitors and following grid resistors must be equal. Their exact value is not important; they must *match*.

If 807's are used to get maximum power, then, owing to the heat from the tubes (which have the plate connection on the top of the bulb) and the operating conditions, the 470 μ fd. plate bypass capacitors have a very rough time of it and should be at least 2000 volt ceramics. Alternative tubes are 6L6 and 5881, and the r.f. capacitors can be the ordinary molded mica type.

Apart from the voltage control complication in the power supply, the circuit is very simple indeed, with the minimum number of stages. Because of this I have been able to apply as much as 28 db of feedback without running into trouble with low-frequency instability. The response is +1 db at 20 cps, -1 db at 50,000 cps and dead flat in between. Intermodulation distortion is negligible (almost unmeasurable) up to 15 watts, and only 1% at 20 watts. These figures may appear to be unimpressive, compared with some claims, but they are factual. Twenty watts is developed with an input of 1 volt r.m.s.

The now famous "Ultra-Linear" output stage was first described by Hafler and Keroes (*Audio Engineering*, Nov. 1951) and used conventional pentodes with taps on the output transformer connected to the screens of the tubes, thus distributing the load between plates and screens. This forms a hybrid sort of output stage, for the devisers of the circuit found that in altering the ratio of screen load to plate load from zero (pentode operation) to unity (triode operation) a point was reached when most of the disabilities of the pentode disappeared and the output stage took on the characteristics of triodes, without losing the high efficiency of the pentode. In a practical sense, therefore, the high power output and stage efficiency of pentodes is retained, but the tubes, from a low plate impedance and damping factor point of view, behave like triodes, and with a carefully designed amplifier, the distortion is less than can otherwise be obtained. The latest development of this circuit has been described by Hafler in *RADIO & TELEVISION NEWS* (June 1956) and need not be repeated here.

The design cannot be applied indiscriminately, for the amplifier as a whole has to be considered carefully. The design of the output transformer is critical, and only components specified for use with particular tubes should be used. The authors' original article suggested that a new tube was really wanted to get the best from the scheme, and such tubes are now available in the Mullard EL34 and the Tung-Sol 6550.

-30-

February, 1957

Why
use
ordinary
tape...

...now that
FERRO-SHEEN
costs you no more?

irish BRAND GREEN BAND

is now made by the exclusive
FERRO-SHEEN
process!



FERRO-SHEEN is the exclusive **irish** tape manufacturing process which astounded the audio world when it was introduced 18 months ago and has rendered ordinary tape old-fashioned, if not obsolete. **irish FERRO-SHEEN** process tape has by far the smoothest and most homogeneously bonded magnetic oxide surface of any recording tape ever made. It ends your worries about wearing or gumming up your recorder heads with the abrasive, easily shed oxide coating of ordinary coated tape. It gives you unprecedented fidelity because the mirror-smooth **FERRO-SHEEN** surface makes for vastly improved head-to-tape contact. It is simply the best-engineered tape in the world.

Write for **FREE** **irish** Comparator Card, a sampler of mounted strips of top-brand tapes, showing at a glance "Which Tape Has the Smoothest Surface."

If not available
at your favorite
dealer, write
directly to:

• **ORRADIO INDUSTRIES, INC., OPELIKA, ALABAMA**
• World's Largest Exclusive Magnetic Tape Manufacturer
• Export Division: Morhan Exporting Corp., N. Y. C.
• In Canada: Ailus Radio Corp., Toronto



**irish
GREEN BAND**

1200 feet.....\$3.50

THE ONLY
PREMIUM QUALITY TAPE
AT THE
STANDARD PRICE

Send for MusiCraft's **FREE** high fidelity catalog



Just off the press!
Jam-packed
with latest
hi-fi values!

Here's a *special* high fidelity catalog that you'll find particularly useful, because we have included *only* equipment which we at MusiCraft consider the *best*—from the standpoint of *compatibility* and stable operating efficiency—in every price range.

Page after page pictures the newest high fidelity equipment with detailed information about characteristics and specifications.

Whatever you want—whatever you need—speakers, tuners, amplifiers, turntables, "do-it-yourself" kits, etc.—MusiCraft's new catalog features all the top quality components from leading manufacturers.

Send now for your free copy of the new **MUSICRAFT HIGH FIDELITY CATALOG**:

MusiCraft

48-A East Oak Street
Chicago 11, Illinois

Delaware 7-4150

name _____

address _____

city _____ zone _____ state _____

FREE!

DESIGN DATA on Transistor Receivers

... including 9 schematics! (with each Transistor Loopstick)

**EXPERIMENTERS!
Servicemen!**

NEW TRANSISTOR LOOPSTICKS

The **ONLY FLAT** Loopsticks with
FULL SLIDE ADJUSTMENT
for perfect match!

FLAT for more pick-up, COMPACT to fit better in smaller places... the powerful Superex Flat Wound Transistor Loopsticks are perfect for the Experimenter, ideal universal replacement for most transistor sets. Use with or without mounting... contains full instructions including 9 suggested circuits.

Regular Radio Loop Replacement model now available in new superior flat style.



2 1/4" — 3 1/4" — 5 1/4" sizes

\$2.75

List

7" Loopstick \$3.00

**At Your Radio
Parts Supplier**

Superex

successor to Graybart
Radford Pl. Yonkers, N.Y.



INDUSTRY FACT BOOK

The Radio - Electronics - Television Manufacturers Association, 1721 DeSales St., N. W., Washington, D. C., has issued a new edition of its electronics industry "Fact Book" which will be of wide interest.

The booklet contains information on radio and television receivers, including production and sales figures; picture and receiving tube statistics; with special chapters devoted to military and industrial electronics, tubes, and export data on the industry.

Those whose work involves statistics of this sort will find this slim volume a wonderful reference source. Copies are available for 50 cents each direct from the Association.

DIGITAL TECHNIQUES

The Electronic Instruments Division of Burroughs Corporation, 1209 Vine Street, Philadelphia 7, Pa. has issued a 16-page booklet on the art of using digital techniques for testing, information handling, and control.

Entitled "Four Dimensions in Digital Design-Pulse Techniques for Modern Control," the booklet is basic enough to serve as an introduction to digital techniques. The publication shows how digital techniques, as applied through the company's pulse control systems, provide increased measures of precision, control, and many other functions of research and manufacturing.

Free copies of the booklet are available on letterhead request to the manufacturer.

"DOLLAR SAVINGS THROUGH STANDARDS"

A proof of the value of standardization in the electrical manufacturing and electronics field is stressed in an extensive survey report, "Dollar Savings Through Standards," which highlights economic benefits to American industry resulting from the use of standards.

The 40-page survey is being made available by the American Standards Association, 70 East 45th St., New York 17, N. Y. as a public service. This report is an up-to-date version of the original edition of 1951 and contains 79 documented case studies covering 27 industrial fields.

MINIATURE VOLTMETER DATA

International Instruments, Inc., P.O. Box 2954, New Haven 15, Conn. has announced the publication of a new engineering data sheet covering its line of miniature, expanded-scale a.c. voltmeters.

The meters are available in standard ranges of 90-120, 90-130, and 90-140 volts a.c. Other ranges with the

RADIO & TELEVISION NEWS



JBL signature



great speakers...

All that it takes to make a speaker great — excellent basic design, precision-made parts, painstaking craftsmanship, meticulous assembly — goes into JBL Signature Loudspeakers. The JBL Signature Model D130 is the only fifteen-inch extended range speaker made with a four-inch voice coil of edge-wound aluminum ribbon. It has a rigid cast frame, silvery dural dome, highly refined magnetic circuit. The D130 is distinguished by its clean, smooth coverage of the complete audio spectrum... crisp, clean bass; smooth, extended highs. It is the most efficient speaker made anywhere.



**PRECISION
HIGH FREQUENCY
UNITS**

The greatest single improvement you can make in your high fidelity system is to add a JBL Signature High Frequency Unit. The popular 175DLH is made with all of the precision necessary to retain the subtleties which are the essence of high frequency reproduction. In addition it has an acoustical lens — an exclusive JBL Signature feature — which disperses sound over a 90° solid angle with equal intensity regardless of frequency.

lowest starting at 80 volts a.c. can be supplied on a custom basis. Minimum scale span is 30 a.c. volts.

The data sheet covers all information pertinent to the expanded scale feature of the line. Supplementary information such as mounting dimensions, case descriptions, standard and special resistances, etc. is contained in additional data sheets covering each specific model.

Free copies of any of these data sheets are available on request.

"ELMENCO" CAPACITORS

Arco Electronics Inc., 64 White St., New York 13, N.Y. has issued a 24-page catalogue covering the complete line of "Elmenco" capacitors which the firm is able to deliver immediately from stock.

Included in the listing is a complete line of micas, tubulars, ceramics, compression micas, and a line of capacitor kits for various applications. The information is presented in tabular and easy-to-use form. Photographs and dimensional diagrams of prototype units have been included.

POWER SUPPLIES

Lambda Electronics Corp., 11-11 131 Street, College Point 56, N.Y. has just released a new 34-page catalogue covering its line of power supplies for industry and laboratory use.

Nearly fifty models are pictured and described in some detail, including special features and complete specifications. Bench, portable, and rack-mounted regulated supplies are included in the line and in the catalogue.

Copies of Catalogue 57 are available on request. Write the manufacturer on your company letterhead.

1957 ZACK CATALOGUE

Zack Radio Supply Company, 1424 Market St., San Francisco, Cal., has announced the availability of its new 1957 general catalogue.

This 224-page publication, which includes a 64-page high-fidelity section, was prepared by *Electronic Publishing Company, Inc.* of Chicago. Copies of the catalogue are available from the parts distributor.

INDUSTRIAL TV DATA

General Precision Laboratory, Inc., 63 Bedford Road, Pleasantville, N.Y. has issued a four-page general application brochure on its closed-circuit television equipment for industrial and institutional applications.

The booklet pictures and describes the various components used in such a system and lists typical applications for such equipment. Copies of the new booklet are free on request to the manufacturer.

MAGNETIC SHIELDING


A new 33-page technical brochure which completely describes the construction features, performance characteristics, and typical applications of non-shock sensitive non-retentive



If you are to hear fundamental bass tones, your speaker must be properly enclosed. JBL Signature Enclosures are engineered to make full use of the great sound potential in Signature Speakers. They are handsome to look at, wonderful to listen to. A wide range of types — bass reflex and folded horns — and sizes is available. All are superbly engineered, superbly designed, superbly built. Panels of specially selected plywood are precision cut. Joints are lock-mitred and wood-welded. An unusually wide choice of fine, hand-rubbed finishes is offered. It is even possible to order an enclosure from the factory to exactly match a sample supplied by you. If you want to build your own, you can get detailed blueprints of most Signature Enclosures from your audio dealer or the manufacturer.

superb enclosures

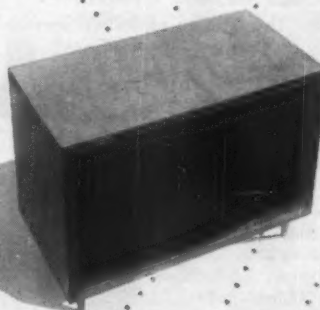Below is shown the new JBL Signature "Harkness," a back-loaded folded-horn in lowboy console styling. Although its proportions are such that it will be welcome in any living room, the Harkness encloses an ingeniously folded six foot horn path for smooth, crisp, deep-down bass.



THERE IS A JBL
SIGNATURE SPEAKER
SYSTEM FOR
EVERYONE... ONE IS
JUST RIGHT FOR YOU.

Write for free catalogue and technical bulletins and the name of the authorized JBL Signature Dealer in your community.



JAMES B. LANSING SOUND, INC.
2439 Fletcher Drive, Los Angeles 39, Calif.

KESTER



Absolutely non-corrosive and non-conductive, KESTER "RESIN-FIVE" CORE SOLDER contains an activated type of resin that gives you that fast, positive action on all your jobs . . . including the most difficult.



KESTER SOLDER COMPANY
4235 Wrightwood Ave. • Chicago 39, Ill.
Newark 5, N. J. • Brantford, Canada

SOLDER

3 big reasons why QUIETROLE
Reg. U. S. Pat. Off.

is "The Choice of Better Service Dealers Everywhere"

- 1 MERIT
- 2 QUALITY
- 3 RELIABILITY

The original product for quieting noisy controls and switches . . . the universal lubri-cleaner for TV and radio . . .

Say "QUIETROLE" to your distributor . . . be sure you get it.

NO GUM! NO GOO! NO GRIME!

Carried by recognized jobbers . . . everywhere!

manufactured by

QUIETROLE COMPANY INC.
Spartanburg, South Carolina

IN CANADA: Active Radio & TV Distributors
58 Spadina Ave. Toronto 28, Ont.

Perma-Power
GOLDEN C-BRITE TV BRITENER

Series or Parallel Booster!

At All Distributors

manufactured by
Perma-Power COMPANY
4727 N. Damen Ave., Chicago 25, Ill.
manufacturers of electronic equipment since 1928
Export: SCHEEL INT., Chicago

"Fernetec" and "Co-Netec" magnetic shielding has been released by *Magnetic Shield Division, Perfection Mica Company*, 20 N. Wacker Drive, Chicago 6, Ill.

Included are twelve pages of technical data, five pages of performance graphs, and fourteen pages of illustrations in addition to a two-page comprehensive index.

Write the company for copies of Data Sheets 101 (1957) or details on how the brochure may be obtained.

"HEATHKITS FOR 1957"

Heath Company has just released an elaborate 55-page catalogue entitled "Heathkits for 1957."

The new publication pictures and describes some seventy kits and includes a complete line of hi-fi equipment, amateur radio gear, and service test instruments in kit form.

One item of particular interest to the audiophile is the new "Legato" speaker system kit featuring *Altec-Lansing* speakers. The new system is being offered in either contemporary or traditional design.

Copies of this new catalogue will be supplied without charge upon direct request to the company at 305 Territorial Road, Benton Harbor, Mich.

MORE RETMA STANDARDS

The Engineering Department of RETMA has released three new standards of interest to the electronics industry.

RS-166 covers miniature waveguide flanges, unpressurized contact type. This standard is priced at 40 cents. Type designations for receiver type tube sockets is available at 80 cents a copy as the RS-167. The third standard covers thermoplastic insulated and jacketed hook-up wire. This standard, 60 cents, has been designated as RS-169.

Copies of any or all of these standards may be ordered direct from the RETMA Engineering Office, 11 West 42nd Street, New York 36, N. Y.

TRANSITRON BROCHURES

Transitron Electronic Corporation of Wakefield, Mass., has issued two new bulletins describing its products.

Bulletin TE 1351 covers high-temperature silicon rectifiers and consists of a series of data sheets providing pertinent electrical, mechanical, and circuit specifications. The second publication, Bulletin TE 1342, covers the firm's "TD" series of silicon rectifier stacks and provides complete specifications.

Either or both of these publications are available upon direct request to the manufacturer.

SPRAGUE WALL CATALOGUE

Of interest to service technicians is the new "wall catalogue" recently issued by *Sprague Products Company*, 51 Marshall St., North Adams, Mass.

The company's complete line of capacitors for radio-TV replacement has been compiled in an easy-to-read,

RADIO & TELEVISION NEWS

Make Money! You can sell these at a profit.

JUNEERO Miniature MACHINE SHOP

Save \$\$\$ Pays for itself with one use.

The Made-in-England Marvel
Bends, Shears and Punches
Flat Strip Metal



Stock No.
TL-125
\$3.93

Makes your own hard-to-get brackets for condensers, terminal boards, resistors, transformers, etc. EASILY. Complete with stock of strip steel and instructions. The Juneero Multi-purpose tool is a correctly designed and engineered device for making, modeling and repairing metal. Any angle bracket with complex bends, holes and slots can be made in minutes. The Juneero is equipped with cutting shears for strip metal, cutting shears for rod, bending jig for rod, bending die for making angle brackets, a punch and a vice. Size: 10x4x3". Comes complete with a good supply of strip steel for making any bracket.

Deluxe Model
Same as above plus a stock of rod material and a thread cutting die.
Stock No. TL-128... \$5.11

POCKET METER

Volts, Ohms, Mills

With Big 3" Meter



Stock No.
TE-98
\$8.46

3 for \$24.00

An Olson best buy. Has all the best features found in more expensive meters. Has 1000 ohms per volt rectangular meter. 1% precision resistors. D'Arsonval microamp movement. Ranges: AC & DC volts: 0-10-50-250-500-5000; DC ma: 0-5-50-500; Ohms 0-10-100-1 meg. Also 2 ranges for DB. Beautifully finished in gray. Complete with test leads. Size 4 1/4 x 3 1/4 x 1 1/2".

Smallest AUTOMATIC CHANGER

RCA Type
45RPM



\$14.88

Stock No. RP-31

Just imagine a fully automatic changer only 10" w. x 7" d. x 7" h. Plays up to 12-78 records automatically with one loading. Equipped with low pressure tone arm mounted in smooth working bearing. Has reject button. Cartridge is the famous 1.5 Volt Ronette with sapphire stylus. Work with any radio, amplifier or TV. Operates on 110-125 V. 60 Cy. AC. Shpg. wt. 8 lbs.

Continuous Play TAPE MAGAZINE

Repeats Recorded Messages
Endlessly



\$1.89

Stock No.
X-443

3 for \$5.00 Reg. Price \$12.50

Makes and plays recorded messages endlessly. Can be erased and re-recorded as many times as desired. Brand new. Offered at this low, low price because we can't supply mounting hardware. Can easily be mounted on recorder with homemade bracket. Repeat messages in stores, carnivals, rehearsals, etc. Each magazine is loaded with 100 ft. of finest double coated tape. Will record and play both sides consecutively. 10 minutes at 3 1/2 IPS or 5 minutes at 7 1/2 IPS.

All Purpose Semi-Directional CRYSTAL MICROPHONE



REG.
\$29.50
\$4.25

Stock No.
M-105
3 for \$12.00

High impedance; response 100 to 8,000 cps. Output level—55 DB at 1,000 cps. swivel lifting head permits semi or non directional positions. Attractive baked green enamel with chrome-plated front. Overall size: 2 1/2" dia. x 4 1/4" long. With 5 ft. shielded cable.

TELEPHONE PICKUP

STOCK NO. M-80

\$2.95

EACH
3 FOR \$8.00
10 FOR \$25.00



Records both sides of telephone conversation. Use disc, wire, tape recorder or amplifier. Simply lay pickup under any green type telephone and connect lead to recorder or amplifier. Operates by induction. Regular \$5.95 value.

RCA VICTOR Combination Portable RADIO—"45" PHONOGRAPH

Only Olson dares to cut the price so low. Cash in during our sale. This famous RCA Victor Portable Radio-Phonograph is completely battery powered and works anywhere.

LOOK AT THESE FEATURES
Plays all 45 RPM discs. Constant speed motion on 4 flashlight batteries. Radio is super-hot, iron-core IF with automatic volume control, powered by one 45 battery. RCA Victor "Golden Throat" Speaker system. Built-in Ferrite antenna pulls in distant stations full range 540-1600 KC. Lightweight RCA tone arm with Sonotone cartridge and precious tip needle. Record storage compartment under lid. Size 5 1/4" x 11" x 12" d. Carrying handle folds into grille.
A-B Battery Pack—RCA V80-64 or Burgess V80-36 or Burgess No. 2.
FLASHLIGHT CELLS, 4 required RCA V80-36 or Burgess No. 2.
Stock No. RA-25, Ea. \$106

Model 48Y4
"Golden Throat"
Battery Operated
Reg. Price
\$59.95

\$29.88

3 for \$88
Stock No.
RA-263



Portable Transistor RADIO KIT



LIST
PRICE
\$20.00
\$12.94
EACH

Stock No.
KB-38

Complete with loudspeaker

Build a powerful radio which will provide excellent loudspeaker reception over the entire broadcast band. Circuit consists of one type detector plus dual transistor audio stages. Feature built-in high-Q loop antenna and overdriven PM speaker. Housed in a clear plastic case with convenient carrying handle, over all size: 7 1/4" x 5" x 1 1/2". Kit supplied complete with 2 transistors, germanium diode, plastic cabinet and all other necessary components, ready to assemble. Full illustrated detailed instructions make assembly easy and fast. Ideal for picnics, beach parties, football-baseball games—anywhere that electric power is not available. Very low drain battery tests and lasts.
BA-37 Battery for above 69¢

1 1/4 Meter Transceiver



Stock No.
RA-252
\$3.93

2 for \$7.00

BUILD YOUR OWN
A Brand new complete RT-92/AM unit designed to receive and transmit signals from 215 to 225 MC. Contains wealth of parts all built into an aluminum case, 3 1/2" x 9 1/2" x 5 1/2" with removable cover. Included are 5 tubes (worth over \$8.00 wholesale), 1-92S, 6X4, 6AR5 and 1-92A, 10 resistors, 10 condensers, SPDT Toggle Switch, 4 mica filled sockets, chokes, a variable condenser, a potentiometer, 3 diode antennas, battery box, battery plugs, and a removable chassis. Wiring diagram included. Can be rebuilt into a transceiver, receiver, field strength meter, etc. Shpg. wt. 5 lbs.

PHONO MOTOR & ARM

Stock No. AS-205

\$5.78



Monarch (Famous Made-in-England Brand) 3 speed motor and turntable plus a genuine Webster tone arm with turnover cartridge and dual precious tipped needles.
Brand new 100% guaranteed. Reg. \$15.00 Value.

Masco Wireless

ELECTRONIC NURSE

One Unit No Wiring Needed
No Installation



\$19.47
Ea.
Stock No.
AM-38

A very sensitive wireless microphone, designed to pick up even a whisper and retransmit to any radio within 300 ft. tuned to its frequency. Easy to use, just plug in and flip the switch. Acts like a miniature broadcasting station. No matter where you are in the house—wherever you have a radio, battery or electric, you will know at once when the baby cries. Also makes an excellent wireless PA system when used with one or more radios. Its frequency is adjustable and can be tuned to any unused spot on your radio dial. Housed in an attractive metal case with convenient carrying handle. For 110-120 Volts AC or DC.

NORELCO TICONAL

SPEAKER New FRS Series

Plus New
ARGOS
BASS
REFLEX
CONSOLE

\$26.00

Stock No.
AS-237

The famous Norelco 9770M Ticonal Eight made by Philips of Holland is teamed with the new Argos Bass Reflex Enclosure. The result is unbelievably fine reproduction. The Norelco speaker has a Ticonal magnet with twice the power of an Alnico 5. Frequency range 45 to 12,000 cps. Equipped with a high frequency "whizzer" or sound disperser for the high frequencies. The enclosure is made of solid 1 1/2" wood, internal acoustical padding. Back is fully enclosed. Exterior of cabinet is beautiful mahogany wood grain plastic material. Size 23 1/2" h. x 19 1/4" w. x 13 1/4" d. Impedance 4 ohms. Shipping Wt. 30 lbs.

HOW TO ORDER

Mail your order to 279 E. Market St., Akron 8, Ohio. Send remittance with order (add for postage 2¢ for each dollar's worth ordered—10¢ for each dollar's worth if you are more than 100 miles away). OLSON REFUNDS EVERY CENT NOT USED. Or—send no money—we'll ship C.O.D. and you pay mail or express for merchandise and postage. ALL MERCHANDISE LOWEST PRICED. PLEASE—MINIMUM ORDER \$5.00.

ATTENTION MANUFACTURERS! If you have large quantities of surplus electronic parts you wish to sell, call or write OLSON at once. We pay top prices!

SEND FOR NEW FREE CATALOG

OLSON RADIO WAREHOUSE

279 EAST MARKET ST. • AKRON 8, OHIO

OLSON BARGAIN STORES IN:


CHICAGO—623 W. Randolph St.
CHICAGO—123 N. Western Ave.
CLEVELAND—2020 Euclid Ave.
PITTSBURGH—5918 Penn Ave.
MILWAUKEE—423 W. Michigan
BUFFALO—711 Main Street

XCELITE Hand Tools
PREFERRED BY THE EXPERTS

TRANSPARENT ZIPPER KIT

NEW!

**CK-20
Pocket
Kit**

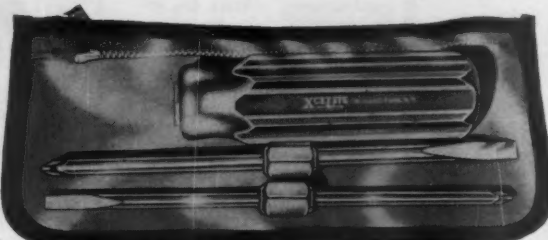

That big, husky Xcelite handle and tough, precision-pointed blades for quick change to Nos. 1 & 2 Phillips, 3/16" & 1/4" regular blades—instantly visible in durable plastic pouch with zipper! Fits hip pocket, tool box, glove compartment, any 4" x 8" space! What a kit to own, and what a gift idea! Ask your supplier.

Only \$4.40 LESS DISCOUNT

Combination Handle is also 7/16" hex nut driver!

XCELITE, INCORPORATED

Dept. E, Orchard Park, N. Y.

In Canada—Charles W. Pointon Ltd.
6 Alicia Ave., Toronto, Ont.

For Originality
LOOK TO XCELITE

315 Different STAMPS — 25¢

Grace Kelly - Rainier
Royal Wedding, Monaca U. S.
President Set—F.D.R., Lincoln,
Washington, Eisenhower.

You also get Bulgaria Complete Motor Show; St. Thomas Explorer; San Marino Airmail Triangle; Dutch New Guinea 1st Stamp issued and hundreds more!

Grand total of 315 all-different stamps. Catalog value \$6.95—yours for 25¢ to introduce our Bargain Appraisal. Included FREE, Midget Encyclopedia of Stamps.

Send 25¢ Today. ASK FOR LOT PW-1

ZENITH CO., 81 Willsoughby St., Brooklyn 1, N. Y.

TALK - LISTEN - AROUND THE WORLD!

Portable 2 Way Radio Set
SENDS AND RECEIVES THOUSANDS OF MILES on Amateur 80 and 40 meter bands—also, Aircraft and overseas broadcasts (3 to 8 mc.) PORTABLE SELF-CONTAINED BATTERY POWERED! NO AC PLUG-INS. NO DANGEROUS HI-VOLTAGES. Low cost battery lasts for MONTHS. Crystal controlled transmitter—Power input up to 5 watts—ENOUGH TO TALK 1 MILE OR 1000. REGENERATIVE RECEIVER pulls in weakest stations. Front Panel Send-receive switch—Uses standard antenna. Size only 6" x 4" x 4". Wt. 3 lbs. TESTED—PROVEN—SIMPLIFIED—PRACTICAL—SAFE for radio beginners. Easy to get license. Full information included.

SEND ONLY \$5.00 (bill, check, m.o. and pay postman \$9.95 C.O.D. postage on arrival or send \$14.95 and we will send postpaid. Complete kit includes all parts, tube, coil, cabinet, full instructions, less batteries and crystal—or COMPLETELY WIRED AND TESTED FOR \$19.95! Compare! A real \$49.95 value. Available only from

WESTERN RADIO
DEPT. BNT-12 KEARNEY, NEBRASKA

easy-to-handle catalogue. Made up in the popular wall-calendar style for hanging near the telephone or work bench, Catalogue C-455 makes ordering simple.

Covering all capacitors needed for radio and TV replacement, the catalogue eliminates all extraneous items which do not fall into this category. Copies of the catalogue will be supplied by the company's distributors without charge but can be ordered direct from the manufacturer for 10 cents, if more convenient.

PIC CATALOGUE

Pic Design Corporation, a division of Benrus Watch Company, Inc., 477 Atlantic Avenue, East Rockaway, Long Island, N.Y. has announced the release of its Catalogue #11.

Listing over 4000 precision instrument and servo parts which are available from stock, the catalogue includes 128 pages of compact and concise engineering data for use in the electronic and instrumentation fields.

The company will supply a copy of this publication upon letterhead request.

"VIKING" HAM RADIO GEAR

E. F. Johnson Company, Waseca, Minnesota has issued an 18-page, two-color catalogue covering its complete "Viking" line of equipment for the radio amateur.

Designated as publication 956, the catalogue features the firm's new "Five Hundred" transmitter which covers the entire amateur spectrum from 80 through 10 meters. The new transmitter provides 600 watts c.w. and 500 watts on phone.

In addition, the catalogue pictures and describes nine other transmitters and a series of accessories, antennas, and rotators. The company will forward copies of this new publication upon request.

RCA "REFERENCE BOOK"

RCA's Tube Division distributors are now offering copies of the 1957 edition of the division's "Reference Book," a pocket-size book containing 200 pages of information on tubes, semiconductor devices, and electronic components, together with a daily reminder calendar, and a collection of world maps in color.

The section on tubes includes a "Quick Selection Guide" of the company's power, CR, phototubes, and special tubes for radio and industry; an interchangeability directory of tubes for communications and industry; and 37 pages of receiving tube characteristics with base and envelope connection diagrams. Picture tube characteristics and socket connections occupy 12 pages.

Contact local RCA tube distributors for copies.

TRANSFORMER REPLACEMENTS

Rogers Electronic Corp., 49 Bleecker St., New York 12, N.Y. has established a new TV transformer replacement manual and subscription service

TELEVISION



Industry needs Electronic Trained Men Now! Qualify for BIG PAY JOB, 9 short months. No other type of training can compare with actual shop practice you get at Healds under expert instructors.

Bachelor of Science Degree, 27 Months

- ☐ Electronics Engineering (B.S. Degree)
- ☐ Electrical Engineering (B.S. Degree)
- ☐ Television Technician (9 Months) ☐ Color TV
- ☐ Electronics Technician (12 Months)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES
Register Now. Write for Catalog.
(No Obligation.)

AT HEALDS YOU LEARN
BY DOING IN MODERN
ELECTRONICS LABORATORIES

HEALD
ENGINEERING COLLEGE

Van Ness at Post, RTN
San Francisco, Calif.

Your Name
Address
City
State

THE MOST IMPORTANT ISSUE

SPECIAL—3 Page Fold of U. S. Military Aircraft

**FLYING**

THE WORLD'S MOST WIDELY READ AVIATION MAGAZINE

FEBRUARY, 1957
50 CENTS



**50 years
of
airpower**

A SEARCHING LOOK AT A REVOLUTIONARY ERA

OF **FLYING** EVER PUBLISHED!

In view of the current world crisis, no American can afford to miss this vital issue of **FLYING**, the world's most widely read aviation magazine.



February **FLYING** discusses the role of *concept* in airpower, analyzes America's past successes and failures in aviation . . . pulls no punches in appraising United States strength in the air today!

Be sure to buy your copy of February **FLYING. NOW ON SALE AT ALL NEWSSTANDS**

FEBRUARY 'BEST-SELLER' FESTIVAL!

63 of our Biggest-Selling Values — Available ONLY at Lektron!

ANY \$1 ITEM
FREE!

WITH \$10 ORDER!

FEBRUARY BUY-OF-THE-MONTH
GIANT SOLAR BATTERY
NEW! Giant sun battery in 2 1/2 x 1 1/4 x 1 1/4 in. sealed case w/ plastic window. Operates 1 or 2 transistor radio from sun, daylight or even a 60 W lamp! Buy several at this fabulous price.
\$2.98



8-PAGE FLYER
FREE!

HUNDREDS OF BARGAIN
AND BONUS ITEMS. Write Today!

LEKTRON'S FAMOUS DOLLAR BUYS! EXCLUSIVE WITH LEKTRON!

- | | | |
|--|--|---|
| <p>HOBBY TRANSFORMER. 115VAC, 60 cycle to 24V @ 3 Amps. Full transformer for shop, surplus gear, hobbyists. Wt. 3 lbs. Reg. \$6.
\$1</p> <p>2 TRANSISTOR LOOP. STICKS, tapped. Match trans. input impedance for better selectivity.
\$1</p> <p>APPLIANCE MOTOR. 3,000 rpm, 115VAC, 60 cycles. For fans, blowers, hobby uses. Fan blade, 35¢ extra. Wt. 2 lbs. Reg. \$1.
\$1</p> <p>FOUR G-E 1N69 DIODES. Germanium, superior to commercial. Reg. \$3.
\$1</p> <p>2 TRANSISTOR COMB. LENS. Eliminate trans. & r/c coupled amp. stages. 100K imp., 5000 DC ohms, center tapped. 1/2" x 1/2" x 1/2". Reg. \$3.
\$1</p> <p>1 HOBBY TRANSISTOR. TOR. Scopel 2 plug-in type printed circuit. Transistors Reg. \$3.75.
\$1</p> <p>WORLD'S SMALLEST RADIO KIT. 2 1/2 x 1 1/4 x 3/4". Permeabloc type, 100 ohm, pre-drilled case. All parts, instructions. Reg. \$1.
\$1</p> <p>SUN BATTERY & photo-cell. 1 1/2" x 1 1/4" x 1 1/4". Not fused. Reg. \$1.
\$1</p> <p>128 RESISTORS. Carbon, 1/2 to 5W, 40 values. 5% tol. Reg. \$15.
\$1</p> <p>3 OUTPUT KFMERS. (Choose any 3) 500K, 550K, 500K, 50K to 3-4 ohms. Reg. \$1.50
\$1</p> <p>7 PILOT LIGHT ASSEMBLIES. 1/2" x 1/2" x 1/2". Jewel, enclosed. Miniature bayonet. Reg. 75¢
\$1</p> <p>3 LBS. HARDWARE. 2000 pcs. ass'd. screws, springs, washers, etc. \$1
\$1</p> <p>APPLIANCE CLOCK-TIMER. Turns radio, TV, appliances "ON" or "OFF" within 15-30 min. Low hardware. Reg. \$2.50
\$2.50</p> <p>MULTI-PURPOSE POWER SUPPLY KIT. 115 VAC. Out 250 VDC @ 70 ma. Incl. smftr., condensers, resistors, w/ cord, etc. switch, tube. Wt. 3 lbs. Reg. \$8.
\$3.33</p> <p>FOUR TUNING MECHANISMS. 3 seconds. Hand, multi-gear, precision units. Reg. \$3 each.
\$1.00</p> <p>3-TUBE AC/DC AMPLIFIER. Wired. Lowest price ever! For phones, P.A. etc. Sup. vol & tone controls. Reg. \$3. Tube, \$2.91 extra.
\$2.91</p> <p>SUPER-POWERED HEADSET. 5,000 ohms. W/ cord & tips. Strongest weak signals. HI-FI quality. Reg. \$5.
\$2.50</p> <p>TRANSISTOR "ADD-A-STAGE." Transistorize your crystal set easily, simply, by adding an amplifier stage. All parts, instructions.
\$2.50</p> | <p>G-E PREAMP KIT for magnetic cartridges. Chassis, parts, diagram. Less 68CT (88¢ extra). Wt. 1 lb. Reg. \$4.50.
\$1</p> <p>175-FT. HOOKUP WIRE. In 25-ft. rolls. Ass'd. colors, stranding, insulation. 218 to 24. Wt. 1 lb. Reg. \$2.75.
\$1</p> <p>100 CERAMIC CONDENSERS. Ass'd. types, top makers. 30 values, color-coded. Discs, too. Reg. \$15.
\$1</p> <p>CRYSTAL DIODES. Most commonly used—1N34, 1N56, 1N58, 1N69 poly bag. Reg. \$1.
\$1</p> <p>180 COIL FORMS. 15 types. Assorted sizes. Insulation. Reg. \$15.
\$1</p> <p>20 TUBULAR CONDENSERS. 30 types, .0005 to .05mf to 1500. Wt. 1 lb. Reg. \$12.
\$1</p> <p>70 TERMINAL STRIPS and boards. 15 types. 1 to 30 screw and solder points. Wt. 1 lb. Reg. \$1.
\$1</p> <p>70 RESISTORS. Insulated IRC, A-B, etc. 5 ohms to 10 meg. 1/2" x 1/2" x 1/2". Wt. 1 lb. Reg. \$10.95.
\$1</p> <p>70 MICRA CONDENSERS. 30 values: .00001 to .01 mf to 1000V. Silver. Wt. 1 lb. Reg. \$1.
\$1</p> <p>70 STANDARD KNOBS. Ass'd. colors, bakelite & plastic. Wt. 3 lbs. Reg. \$8.
\$1</p> <p>RADIO PARTS! Wide variety resistors, condensers, pots, plugs, strips, tubes, forms & more! Reg. \$10.
\$1</p> <p>30 POPULAR BULBS. 1 to 6V, acwv & bayonet types. miniature. Wt. 1/2 lb. Reg. \$2.40.
\$1</p> <p>25 PORCELAIN CONDENSERS. tubular. 10 values: .001 to .03 mf to 1000V. Wt. 1/2 lb. Reg. 25¢ each.
\$1</p> <p>40 MINIATURE CONDENSERS. Ass'd. miniature, subminiature, printed circuit types; Centralab, Sprague. Reg. \$1.
\$1</p> <p>30 POWER RESISTORS. W. candohm, sand coated, vitreous. 15 values. 5 to 50W; 1/2 to 1100 ohms. Wt. 1 lb. Reg. \$1.
\$1</p> <p>30 PRECISION RESISTORS. W. 7 candohm. 30 values, 50 ohms to 1 meg. 1/2" x 1/2" x 1/2". Wt. 1/2 lb. Reg. \$1.
\$1</p> <p>30 TUBE SOCKETS. 4 to 11-pin miniature, subminiature, octals, alphas. Tube shields. Wt. 2 lbs. Reg. \$5.50.
\$1</p> <p>15 SUBMINIATURE CENTRALAB TRIMMERS. Assorted values. Printed circuits, etc. \$1. Reg. 79¢ each.
\$1</p> <p>15 CERAMIC VARIABLE CONDENSERS. Erie, Elenco, up to 300mmf. Reg. \$1.
\$1</p> <p>12 VOLUME CONTROLS. Single, concentric, TV, some w/switch. 8 1/2" shaft. Up to 1 meg. Some \$1. \$2.50 each.
\$1</p> <p>12 ROTARY SWITCHES. ceramic & bakelite. 1, 2, 3 gangs. 8 1/2" shafts. Shop mail Wt. 3 lbs. Reg. \$10.
\$1</p> <p>20 AC/DC LINE CORDS. for clocks, motors, etc. 2-conc. w/ molded plugs. Wt. 1 lb. Reg. \$5.
\$1</p> <p>10 "POLY" BOXES. Assorted sizes, screw & pin-tied hinged boxes w/ snap locks. Reg. \$2.50.
\$1</p> | <p>10 ELECTROLYTICS. PP. Assorted sizes, 8 to 500 mmf to 450V. Wt. 3 lbs. Reg. \$15.
\$1</p> <p>8-PC. NUTDRIVER SET. Plastic handle, 3/16, 7/32, 1/4, 5/16, 11/32, 3/8, 7/16, steel socket wrenches in plastic case. Weight 1 pound. \$3 value.
\$1</p> <p>18-PC. TWIST DRILL SET. 1/16 thru 1/4" by 60th in graduated plastic holders. Regular \$1 \$4.
\$1</p> <p>8-PIECE MAGNETIC SCREWDRIVER SET. Magnetic, tempered steel blades, shockproof handles, UL approved. Phillips \$1 \$4.
\$1</p> <p>8 TRANSISTOR SOCKETS. For sub-miniature tubes. 8. \$3.50 each. Reg. \$3.
\$1</p> <p>40 SILICON DIODES. 2N1, 1N23, 1N24, 1N25, 1N26, 1N27, 1N28, 1N29, 1N30, 1N31, 1N32, 1N33, 1N34, 1N35, 1N36, 1N37, 1N38, 1N39, 1N40, 1N41, 1N42, 1N43, 1N44, 1N45, 1N46, 1N47, 1N48, 1N49, 1N50, 1N51, 1N52, 1N53, 1N54, 1N55, 1N56, 1N57, 1N58, 1N59, 1N60, 1N61, 1N62, 1N63, 1N64, 1N65, 1N66, 1N67, 1N68, 1N69, 1N70, 1N71, 1N72, 1N73, 1N74, 1N75, 1N76, 1N77, 1N78, 1N79, 1N80, 1N81, 1N82, 1N83, 1N84, 1N85, 1N86, 1N87, 1N88, 1N89, 1N90, 1N91, 1N92, 1N93, 1N94, 1N95, 1N96, 1N97, 1N98, 1N99, 1N100.
\$1</p> <p>50 OHM RELAY. Allied Control, 4FDT, for plate and control circuit. 15 ma. Reg. \$1. \$6.50.
\$1</p> <p>500 TRANSFORMERS. COILS. IF, RF, ant. slug-tuned coils, chokes, 25 types. Wt. 3 lbs. Reg. \$15.
\$1</p> <p>MINI-METER BUY! 154", round. 0 to 6 amps. AC. Chromed. For model r/c, port. supplies, mobile. Reg. \$5.
\$1</p> <p>5 ROLLS TAPE. electrical, plastic, friction rubber. For home, shop or lab. Reg. \$50.
\$1</p> <p>TRANSISTOR SCOOP! Hermetically sealed PNP transistor (cannot advertise mfr's name). Guaranteed satisfaction. Reg. \$5.
\$1</p> |
|--|--|---|

HOW TO ORDER
Check items wanted. Return entire ad w/ check or money order, including sufficient postage. Excess returned. C.O.D. orders, 25% down. Rated, not 30 days. Print name, address and amount of money enclosed, in margin. RTN-2

LEKTRON SPECIALTIES

131-133 Everett Ave. Chelsea 50, Mass.

ENGINEERING
Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. degree in 27 months at Indiana Technical College. Intensive, specialized course. Comprehensive training in electronics, television, advanced radio theory and design, math and electrical engineering. Modern laboratories. Low rate. B.S. DEGREE IN 27 MONTHS in Aero, Chem., Civil, Elec., and Mech. Engineering in 36 MO. in Math, Chem. Physics. Also preparatory courses. G. I. appor. Enter March, June, Sept., Dec. Earn part of your expenses in Fort Wayne while studying. Catalog.

INDIANA TECHNICAL COLLEGE
927 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

☐ Electronics ☐ Chemical ☐ Aeronautical
☐ Civil ☐ Mechanical ☐ Electrical

Name _____
Address _____

QUALITY ELECTRONICS
HI-FI Amplifier Kit \$28.50
Tuner Kit \$28.50
And they have the finest features and specs. Fully illustrated step-by-step 28-page manual makes assembly a snap!
WRITE FOR FREE CATALOG! *100% Federal Tax. QUALITY ELECTRONICS, Dept. T-3, New York 13, N. Y.
319 Church Street.

CODE SENDING SPEED
Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through Famous Candler System. Used by best operators. Quality for Amateur or Commercial License. Write for FREE BOOK.
CANDLER SYSTEM CO., Dept. 2-8, Box 928, Denver 1, Colo., U.S.A.

designed to speed jobber sales and technician repairs.

Included in the new service is an "exact replacement manual," which catalogues the complete line of TV coils, yokes, and flybacks hermetically sealed in plastic containers. The subscription service consists of supplement sheets mailed periodically to manual users.

TV technicians, dealers, and shop owners may obtain the manual service free from the firm's local distributors or for 75 cents from the company direct.

"VARIAC" BULLETIN

General Radio Company, 275 Massachusetts Ave., Cambridge 39, Mass. has just issued "Bulletin O" covering its line of "Variacs."

This 24-page publication lists several new models, portable types with overload protection, motor drives, completely enclosed units, and ball-bearing models. Each of the models is pictured and described in considerable detail. Electrical and mechanical specifications are included.

A tabulation of single and ganged "Variacs" is included on the back cover of the catalogue.

G-E RADIO SERVICE GUIDE

A service guide covering all of its radios manufactured from 1946 to 1956 has been issued by the radio receiver department of General Electric Company.

The 275-page, spiral-bound service guide contains schematic diagrams, replacement parts catalogue numbers, descriptions and list prices, tube complements, voltage measurements, and sensitivity and stage gains in order to provide the service technician with a condensed single source of reference for all postwar radios.

Write the division at 1285 Boston Ave., Bridgeport, Conn. for details on how to obtain a copy of this service guide.

CLOSED-CIRCUIT TV DATA

The Broadcast and TV Equipment Department of Radio Corporation of America, Camden, N.J. has issued a comprehensive, illustrated "guidebook" covering its latest broadcast equipment and systems for color and black-and-white closed-circuit TV service in medical, educational, industrial, and business fields.


Entitled "RCA High-Fidelity Television," the 28-page booklet uses color and monochrome photographs, diagrams, and sketches to describe the nature and applications of the company's line of such gear.

The booklet is available on letterhead request from Department TV-1056, Building 15-1 of the company in Camden.

TUBE DATA BOOKLET

A 44-page booklet for service technicians, amateurs, and engineers containing essential data on its "Reliatron" line of receiving tubes is now

Loran APN/4 Oscilloscope

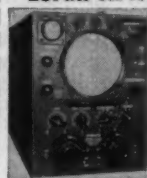

Easily converted for use on radio-TV Service Bench!

BRAND NEW
Completely Assembled
Supplied with 5" Scope
type 5CP1
and RCA
100 Kc.
Crystal
Unit **\$14.95**

I-95-M FIELD STRENGTH METER

Tunes 100 to 155 Mc. Made for Signal Corps. **\$34.50**

Like New Complete installation comprises:
BC-605 INTERPHONE AMPLIFIER. Easily converted to intercom set—ideal for office, home or factory! BRAND NEW, with original schematic. **\$4.45**

MN26Y BENDIX DIRECTION FINDER
150 Kc. to 1 Mc. Complete with tubes, motor. **\$26.95**

BRAND NEW..... **\$2.25**
Used, like new, incl. installation and dynamotor. **\$18.95**

BENDIX DIRECTION FINDER

MN-26-C, 12-tube remote control Navigation Direction Finder and communications receiver. 150 to 1500 Kc in 3 bands, 28 V. DC input. Ideal for commercial navigation on boats and planes. Complete installation comprises:
MN-26-C Receiver, used, with **\$16.50**

MN-20-E Rotatable Loop. **\$2.25**

MN-52 Azimuth Control Box. **2.95**

TS-16/APN TEST SET. BRAND NEW, complete with all cables. **\$12.95**

JUST ARRIVED!

MODEL 040-2 NAVAL RADIO TEST EQUIPMENT
FREQUENCY METER. 110 V. 60 cycles.
AC. 105 to 127 Mc. Mfd by LIEBEL-FLAR-SHEIM CO. BRAND NEW, Export Packed **\$44.50**

TS51/APN-4 TEST SET, 13-26 Volts DC. Including all cables, complete with operating manual. BRAND NEW in original packing. **\$49.50**



BC-906 FREQ. METER—SPECIAL!

Cavity type, 145 to 255 Mc. BRAND NEW in original factory packing, complete with antenna. Manual included.
OUR LOW PRICE **\$8.88**

BC-221 FREQ. METER..... \$129.50

BC-221 FREQ. METER CASE

Aluminum Case for BC-221 or TS-164 Freq. Meters. Shock Mounted. BRAND NEW (add 50¢ for packing).
Original 1000 Kc Crystal for BC-221. BRAND NEW **\$8.45**

TG-5-B TELEGRAPH SET

Made for USA Army Signal Corps. A dandy little field set for 2-way communication. Sturdy metal container, 6 3/4" x 4 1/2" x 4", with hinged covers, complete with telegraph key and headset. BRAND NEW, in carrying case **\$9.95**
Used, exc. Cond. **\$7.95**

BRAND NEW SELSYNS

Operates from 57 1/2 volts, 400 cycles. New tested. Conversion diagram for 110 volts AC included.
2101 Selsyn Control Transformer. Each **\$2.95**
Cups for Above. **50¢**

DYNAMOTOR VALUES!

Type	Input	Output	Used	BRAND NEW
DA-19-A	28V 11A	400V .400A	\$4.99	\$6.95
DM-28	28V	224V .07A	1.95	4.95
DM-32A	28V 1.1A	250 V .05A	2.95	5.95
DM-33A	28V 5A	575V .16A		
	28V 7A	540V .25A	1.95	3.95
DM-34D	12V 2A	220V .080A	4.25	5.50
DM-37	25.5V 9.2A	625V .225A	5.95	8.95
DM-40	14V 3.4A	172V .138A	1.75	3.45
DM-53A	28V 1.4A	220V .080A	3.95	5.95
DM-64A	12V 5.1A	275V .150A		7.95
PE-73C	28V 20A	1000V .350A	8.50	11.50
PE-86	28V 1.25A	250V .050A	2.95	5.24
PE-103	6V	500V .160A		
	12V	500V .160A	19.50	34.50
PE-186	28V 11A	400V .400A		6.95




2 VOLT BATTERY "PACKAGE"

1—2V. 20 Amp. Hr. Willard Storage Battery. **\$2.45**
1—2V. 7 prong Synchronous Plug-in Vibrator **1.49**
1—Quart Bottle Electrolyte (for 2 cells) ... **1.45**
ALL BRAND NEW!
Combination Price. **\$4.99**

Willard 6-Volt Midport Storage Battery
8 Amp. Hour. BRAND NEW. 8 1/2" x 1-13/16" x 2 1/4". Uses Standard Electrolyte. Only **\$2.22**

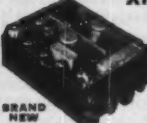Ham Special! Famous BC-645 XMITTER-RECEIVER



With MANUAL for Easy Conversion to CITIZENS' BAND!

Makes wonderful mobile rig for 420-500 Mc. Easy to convert for phone or CW 2-way communication. This swell rig originally cost over \$1000—yours for practically a song! You get it all, in original factory carton, BRAND NEW, complete with 17 tubes, less power supply. Conversion instructions included. **\$29.50**

Shpg. wt. 25 lbs. **\$7.95**

PE-101C DYNAMOTOR for BC-645, has 12-24V input (easy to convert for 6V Battery) **\$7.95**

only **\$2.45**

UHF ANTENNA ASSEMBLY, for BC-645. **\$5.50**

Complete set of 10 Plugs **\$2.25**

CONTROL BOX for above. **1.25**

SHOCK MOUNT for above. **\$2.50**

CONVERSION BOOKLET, Instructions for most useful surplus rigs. **\$2.50**

ASB-5 RECEIVER FOR 420 Mc BAND!

As featured in "CQ" for October 1935. Easily converted, makes a marvelous receiver for 420 Mc band, with RF amplifier! Supplied complete with all tubes. OUR LOW PRICE. **\$16.95**

ASB-5 INDICATOR **\$16.95**

SCR-522 2-METER RIG!

Terrific buy! VHF Transmitter-receiver, complete with all accessories. 100% V. 2, 4 Xtal-controlled. Amplitude modulated voice. They're going fast! Excellent condition.

SCR-522 Transmitter-Receiver, complete with all 18 tubes. **\$33.33**

COMBINATION Special

Receiver Only, with all tubes. **\$19.50**

Transmitter Only, with all tubes. **\$22.25**

ARC-5/T-23 TRANSMITTER

100-156 Mc. Includes 2-832A, 3-1625 Tubes. **\$14.95**

Excel. Used. BRAND NEW **\$21.50**

ARC-5 MARINE RECEIVER-TRANSMITTER

Navy Type Comm. Receiver 1.5 to 3 Mc BRAND NEW with 6 tubes. **\$16.95**

Navy Type Comm. Transmitter 2.1-3 Mc BRAND NEW with 4 tubes and Xtal. **\$12.45**

NAVY RECEIVER TYPE ARB

Four Band. 195 to 9050 Kc. Low Freq., Ship, Broadcast—40 to 80 meters. Includes tubes and dynamotor, for 24 volt operation. Easily converted for 110 V. 12 V. or 6 V. Schematic Included. Excellent Condition. Overall: 8 1/4" x 7 1/4" x 15 1/4". Wt. 30 lbs.
COMPLETE WITH ALL TUBES, **\$21.50**
Special.

AN/ARR-2 RECEIVER

BRAND NEW—A Terrific Value! Tuning Range 234 to 258 Mc. Tubes: T-9001, 3-6AK5, 1-12AG. Only 2 lbs. at this low price! Complete. **\$8.99**

With 28 V. 1.6A Dynamotor, complete. **\$18.95**

110 VOLT AC POWER SUPPLY KIT for above. **\$7.95**



LORAN APN-4 FINE QUALITY NAVIGATIONAL EQUIPMENT

Determine exact geographic position of your boat or plane! Complete, BRAND NEW installation consists of: ID-6B/APN-4 Indicator; R-9B/APN-4 Receiver; PE-206 Inverter; Set of Plugs; Visor for Indicator; Operation manual; Brand New, Export packed. **COMPLETE**. **\$129.50**

SPECIAL APN-9A LORAN Receiver Indicator, less tubes, NEW (demilitarized) **\$29.50**

WRITE FOR FREE CATALOG!

Please include 25% Deposit with order—Balance C.O.D. MINIMUM ORDER \$3.00. All shipments F.O.B. Our Warehouse N.Y.C.

G & G Radio Supply Co.

Dept. N-2

51 Vesey St., New York 7, N. Y. CO 7-4605


Branch: 5007 N. Nava Ave., Chicago 31, Ill.

R24-ARC/5 NAVY TYPE

(Similar to BC-946)

BROADCAST RECEIVER

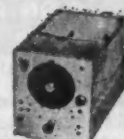590 to 1500 Kc. 6 tubes: 2-12SK7, 12SK7, 12A6, 42K5. For dynamotor operation. Easily converted to 110 or 92 Volt. 2-IF stages, 3-gang tuning cond. Complete with all tubes, in original sealed carton. **\$19.95**



BRAND NEW.....

BC-457 TRANSMITTER—4-5.3 Mc. complete **\$7.88**

BC-454 Receiver 3-6 Mc. **\$7.88**

BC-458 TRANSMITTER—5.3 to 7 Mc. Complete with all tubes and crystal. **\$7.88**

BC-459 TRANSMITTER—7-9.1 Mc. complete with all tubes and crystal. **\$11.95**

BC-456 TRANSMITTER—3 to 4 Mc. BRAND NEW complete with all tubes & crystal. **\$8.88**

SCR-274 COMMAND EQUIPMENT

ALL COMPLETE WITH TUBES. Excellent Brand Type Description Used Used NEW

BC-453 Receiver 190-550 KC. **\$9.95** **\$11.55** **\$14.85**

BC-454 Receiver 3-6 Mc. **7.19** **8.29** **11.55**

BC-455 Receiver 6-9 Mc. **5.25** **7.95** **9.95**

BC-456 Modulator. **2.24** **2.75** **4.24**

BC-450 3-Receiver Control Box **1.49** **1.95**

BC-451 Transmitter Control Box **1.25** **1.49**

BC-458 Xmttr 3-4-Mc (like new) **6.95** **8.88**

Only

110 VOLT AC POWER SUPPLY KIT

For All 274-N and ARC-5 Receivers


Can be assembled quickly and easily, on pre-drilled chassis. Plugs into the rear of any model 274-N receiver and delivers 24 volts as well as "B" voltage. Complete kit of parts with metal case, instructions, **\$7.95**

SPLINED TUNING KNOBS for 274-N RECEIVERS. Fits BC-453, BC-454 and others. **49¢**

Only

BC1206-C BEACON RECEIVER

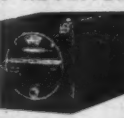195 to 420 Kc. made by Satchel-Carson. Works on 24-28 volts DC. 135 Kc. IF. Complete with 5 tubes. Size 4" x 4" x 6". Wt. 4 **\$8.88**
the BRAND NEW. **\$5.95**
Brand New, less tubes. **\$5.95**
USED, with tubes. **\$5.95**
USED, less tubes. **2.95**



BRAND NEW SPECIAL PURPOSE TUBES

In Original Individual Packing

JAN CRP-730A WAGNETRON, Raytheon. **\$3.45**

Type Each Lots of 12 Lots of 100

6J6W **\$4.45** **\$5.15** **\$41.00**

1025 **.16** **1.75** **13.50**

1025B **.16** **1.75** **13.50**

826 **.44** **4.95** **39.50**

2J724B **.35** **3.95** **29.50**

NEW! Cathode Ray Tubes NEW!


3CP1 **.98** **SBP4** **\$2.23**

3FP7 **.88** **SCP1** **2.45**

8SP1 **5.23** **SLP7** **1.88**

BUBBLE SEXTANT

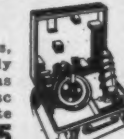Made for U. S. Armed Forces, by AGFA ANSCO. Actually worth \$150 or more! Has illuminated averaging disc for nighttime use. Complete with carrying case. **\$9.95**



DYNAMIC HANDMIKE, with "Press-to-talk" Switch, cord and plug—BRAND NEW, only..... \$2.95

DYNAMIC HEADPHONES, 600-ohm impedance, with large earphone cushions, cord and phone plug. BRAND NEW, special. **\$2.95**

SOUND POWER Headphone with Dynamic Mike, BRAND NEW **\$3.95**

HI-FI DYNAMIC HEADSET with Cushions Free Range: 40-14000 CPS. No Distortion. **\$5.95**

BRAND NEW

MICROPHONES

Model Description Excellent BRAND Used NEW

T-17 Carbon Hand Mike. **\$5.45** **\$7.95**

T-30 Carbon Throat Mike. **.33** **.69**

T-45 Navy Lip Mike. **.99**

RS-38 Navy Type. **2.45** **4.95**

T-24 Carbon Mike. **3.95**

TS-9 Handset. **4.95**

HEADPHONES

Model Description Excellent BRAND Used NEW

HS-23 High Impedance. **\$2.25** **\$4.35**

HS-33 Low Impedance. **1.99** **4.95**

HS-30 Low Imp. (featherweight). **1.49** **2.25**

H-16/U High Imp. (2 units). **2.75** **7.95**

CD-307A Cords, with PL55 plug and JK26 Jack. **.99**

BC-442 ANTENNA RELAY

Wonderful Value! Consists of 84 amp 2" RF Ammeter antenna current indicator, 0-10 scale, Transmitter-Receiver Switching relay, in aluminum case with associated components. BRAND NEW. **\$2.24**



FINEST TUBES FOR SIGHT AND SOUND!

Save ON RADIO, CAR & TV Tubes **RAD-TEL!** Buy

RAD-TEL Tubes Are Brand New Direct from Tube Factory • Same Day Service • Full Year Guarantee • Individually Boxed

Type	Price	Type	Price	Type	Price	Type	Price
0A2	.74	6AN4	.78	6SN7GT	.59	12K5	.65
0B2	.81	6AN4	.95	6SQ7	.53	12J7	.49
0C3	.72	6AN8	.78	6SR7GT	.45	12K6	.59
0D3	.70	6AQ5	.50	6SS7GT	.75	12L6	.51
024M	.45	6A07	.70	6T4	.99	12Q7	.59
1A5	.49	6ARS	.45	6T8	.80	12S6GT	.62
1A7GT	.61	6AS6	1.49	6U4	.70	12SA7	.65
1AB5	.54	6AT6	.41	6U5	.57	12SC7M	.63
1A22	.62	6AT8	.72	6U7	.48	12SF5	.50
1B3GT	.73	6AU4GT	.68	6U8	.78	12SF7	.69
1C5	.43	6AUG	.46	6V6GT	.50	12SH7	.49
1H5GT	.54	6AU7	.61	6V8	.86	12SJ7M	.67
1W6	.59	6AUB	.83	6W4GT	.47	12SK7GT	.63
1L4	.46	6AV6	.40	6W6GT	.57	12SL7GT	.57
1LA4	.59	6AW8	.83	6X4	.37	12SN7GT	.59
1LA6	.69	6AX4GT	.65	6X5GT	.37	12SQ7	.64
1LB4	.59	6AX7	.64	6X8	.75	12SR7M	.49
1LC5	.59	6B4	.54	6Y6G	.65	12SV6GT	.46
1LC6	.79	6BA6	.49	7A4	.47	12W6	.63
1LD5	.59	6BA7	.57	7A5	.59	12X4	.38
1LE3	.59	6BC5	.54	7A6	.69	14A4	.59
1LG5	.69	6BC7	.82	7A7	.69	14A5	.59
1LH4	.69	6BC8	.95	7AD7	.79	14B6	.63
1LNS	.69	6BD5	.85	7A8	.69	14AF7	.59
1NSGT	.67	6BD6	.45	7AF7	.53	14B8	.63
1PSGT	.57	6BE6	.51	7AG7	.69	14C5	.79
1Q5GT	.58	6BF6	.37	7AH7	.70	14C7	.79
1R5	.59	6BG6G	1.25	7AU7	.61	14E6	.75
1S4	.59	6BH6	.53	7B4	.44	14E7	.88
1S8	.51	6BJ6	.49	7B6	.69	14F7	.65
1T4	.58	6BK5	.80	7C4	.59	14F8	.69
1T5	.59	6BK7	.80	7C7	.59	14H7	.59
1U4	.57	6BL7GT	.91	7E5	.59	14K7	.84
1U5	.50	6BN4	.57	7E7	.59	14R7	.79
1V	.43	6BN6	.74	7F7	.79	14S7	.89
1X2B	.96	6BQ/CU	1.25	7F8	.79	14W7	.49
2AF4	.96	6BQ6GT	.96	7G7	.89	14X7	.69
2D21	1.20	6BQ7	.90	7H7	.59	14Y4	.69
3A3	.45	6BR8	.78	7J7	.79	19AU4	.76
3A4	.45	6BS8	.90	7K7	.69	19B6G	1.39
3A5	.85	6BY6	.94	7L7	.59	19C8	.90
3AL5	.42	6BZ6	.94	7M7	.66	19T8	.69
3AU6	.41	6CZ7	.90	7N7	.89	19V8	.79
3AV6	.41	6C4	.40	7S7	.79	24A	.39
3BC5	.54	6C5	.39	7Y6	.54	25AV6GT	.98
3BE6	.52	6C6	.58	7Z4	.59	25CA5	.56
3BZ6	.52	6CA5	.56	12A4	.60	25CD6	1.44
3BY6	.55	6CB6	.54	12A6	.59	25CUG	1.01
3CB5	.54	6CD6	1.11	12ABGT	.61	25DQ6	1.06
3CF6	.60	6CE5	.54	12AB5	.50	25L6GT	.81
3C56	.52	6CF6	.54	12AC6	.49	25W4GT	.59
3D76	.50	6CG7	.60	12AD6	.51	25Z5	.66
3LF4	.69	6CL8	.75	12AE6	.43	25Z6	.49
3Q4	.59	6CR6	.51	12AF6	.49	26	.45
3S4	.59	6CM7	.56	12AN7	.66	27	.47
3V4	.58	6CS6	.51	12AJ6	.46	35R5	.82
4BC8	.96	6CUG	1.08	12AL5	.37	35C5	.51
4BQ7	.90	6DG6	.59	12A27	.52	35L6GT	.81
4BZ7	.41	6DE6	.54	12AT6	.41	35W4	.47
5A8B	.75	6DG6GT	.51	12AT7	.72	35Y4	.54
5AN8	.78	6DQ6	1.03	12AU6	.46	35Z3	.59
5AQ5	.52	6DT6	.49	12AV7	.39	35Z4	.47
5AT8	.75	6E5	.48	12AV6	.39	35Z6GT	.47
5BK7A	.82	6F5GT	.39	12AV7	.73	36	.39
5BR8	.79	6F6	.59	12AW6	.67	45	.55
5C09	.76	6F8	.59	12AX4	.67	45Z3	.54
5CL8	.76	6H6GT	.41	12AX7	.63	45Z5	.49
5J6	.64	6J5GT	.48	12AY7	.69	46	.69
5T4	.79	6J6	.64	12AZ7	.59	50B5	.52
5T6	.81	6J7	.43	12B4	.51	50C5	.51
5U4G	.55	6K6GT	.45	12BA6	.49	50L6GT	.61
5U4GB	.60	6K7	.44	12BA7	.60	50X6	.49
5UB	.78	6L5	.79	12BD6	.45	50Y7	.50
5V4	.71	6L6	.84	12BE6	.55	50Z	.49
5V6	.50	6L7M	.68	12BF6	.39	56	.49
5X5	.75	6R7	.69	12BH7	.63	57	.58
5Y3GT	.37	6S4	.48	12BK5	.70	58	.60
5Y4	.51	6S7M	.79	12BL6	.49	70L7	.97
6A6	.46	6SV7	.90	12BQ6GT	.99	71A	.62
6AB4	.46	6S6GT	.93	12BY7	.65	76	.44
6AC5	.86	6SA7GT	.55	12BZ7	.65	77	.57
6AC7M	.90	6SD7GT	.41	12C5	.56	78	.47
6AF4	.56	6SF5GT	.46	12C8M	.56	84/6Z4	.46
6AG5	.67	6SH7GT	.49	12C6	.51	85	.59
6AG7M	.45	6SJ7GT	.50	12C8	.99	117L7	1.89
6AH4	.45	6SK7GT	.53	12DQ6	1.04	117P7	1.89
6AK5	.42	6SL7GT	.67	12M6	.56	117Z3	.45
6ALS	.42			12J5	.42	866A	1.39

NO GADGETS! NO GIMMICKS!

6" PM SPEAKER
With filter choke and resistor. Use as extra speaker for TV or as rear car speaker.

99¢

Rad Tel TUBE CO.
Not ARI, With Any Other Tube Mail Order Co.

115 COIT ST., IRVINGTON II, N. J.

WIRE KIT
3 to 15 inch. Stranded, solid-hook-up wire, plastic, etc. Covered ends cleaned and some tinned. All usable lengths.
1 lb. 50¢
2 lbs. 75¢ 5 lbs. \$1.50

PACKAGE OF 100 ASSORTED RADIO TUBES \$11.89

EXPORT INQUIRIES INVITED

Write Dept. RN-2 for FREE Catalog of Parts

being offered by the electronic tube division of Westinghouse.

The booklet presents more than 450 of the company's receiving tubes representing more than 95 per-cent of the tubes involved in radio and television servicing. Features incorporated in the booklet are: large, clear tube socket diagrams on the same page as the associated data; bold tube type numbers for quick location; and open style data for easy readability.

Priced at 35 cents a copy, the booklet (RU-020A) can be ordered from Dept. T-286 of the division at Route 17, Elmira, N. Y.

ENGINEERING DATA SHEETS

International Instruments Incorporated, P. O. Box 2954, New Haven 15, Conn., has issued two new engineering data sheets of interest to designers and industrial product engineers.

One sheet describes the firm's Model 104 line of 1" round flush-mounting panel meters. Details are given on both electrical and mechanical specifications along with a tabulation of the ranges and types in which the line is being offered. The second sheet covers the Series L7000 lever and the Series SRL7000 spring-return lever switches. Full details are provided on both of these subminiature components.

Either or both of these data sheets are available on request to the manufacturer.

SEMICONDUCTOR CONVERTERS

Power Sources, Inc., 8 Schouler Court, Arlington 74, Mass., has just issued a four-page brochure describing its newly developed d.c.-to-d.c. converters using semiconductor devices to replace the usual vibrator or dynamotor conversion.

The text included with Catalogue 56P is directed to the designer of mobile systems including missiles, beacons, airborne systems, and other items where severe operating conditions place a premium on efficient, rugged, and reliable operation.

The brochure is extensively illustrated and includes useful tables and circuit information. Write M. Comins in care of the company for a copy.

ACCESSORIES AND COMPONENTS

The Component Parts Sales Dept. of the Allen B. Du Mont Laboratories' Technical Products Division has issued a compilation of its complete line of accessories for electronic test equipment and components for electronic circuitry.

More than 200 items associated with CR oscillographs, oscillograph record cameras, and other electronic test equipment are described in the 20-page catalogue. Among these accessories are knobs, test probes, magnetic shields, viewing hoods, photographic developing equipment, CR tube and multiplier phototube base clamps, base sockets and connectors, movable tables, and rack mounting adapters, etc.

Requests for this catalogue, titled "Du Mont Catalog of Components and Accessories," must be made on company letterhead and be addressed to the department.

GUIDE TO INDUSTRIAL TV

Graybar Electric Company, Inc., 420 Lexington Ave., New York 17, N. Y., has issued a new 64-page booklet entitled "Graybar Guide to ITV—with Equipment Selector" of interest to industrialists.

The publication describes not only a wide selection of video, audio, lighting, transmission, and distribution equipment for industrial television systems but also contains a 15-page guide to the types and uses of such equipment and accessories, procedures for the servicing and maintenance of such gear, as well as several pages of engineering data permitting approximate layouts and system costs to be determined.

Equipment manufactured by Diamond Power, Ampli-Vision, Altec Lansing, and Benjamin Lighting is covered, among others. Write the distributor for full details and a copy of this guide.



"CIRCUIT THEORY AND DESIGN"
by John L. Stewart. Published by John Wiley & Sons, Inc., New York. 474 pages. Price \$9.50.

This work applies modern network theory and pole-zero design methods to the understanding of vacuum tubes and feedback systems. In doing so it assembles a great deal of information which has previously been scattered throughout the literature in relatively incomplete form. Extensive circuit analysis and network synthesis are included along with examples of practical system design.

In order to understand the author's presentation, a background in calculus and differential equations is required. The book is written at the level of the senior undergraduate or graduate engineering student.

"PICTURE BOOK OF TV TROUBLES"
by Rider Staff. Published by John F. Rider Publisher, Inc., New York. 49 pages. Price \$1.50. Paper bound. (Vol.

7, Sound Circuits & L-V Power Supplies)

This is the seventh in this publisher's current series dealing with circuit faults as reflected in the picture tube and on the scope screen. This particular volume deals with the low voltage circuits of the TV set, faults in a Foster-Seeley FM discriminator, sound i.f. amplifier troubles, ratio detector malfunction, and faults in gated-beam FM detectors.

As with the previous volumes, scope patterns and picture tube photos are used extensively to illustrate the effects of the troubles.

"TEACHING TYPEWRITING THROUGH TELEVISION" by William R. Pasewark. Published by Michigan State University, East Lansing, Mich. 53 pages. Price \$1.50. Paper bound.

In an experimental test, with rigid scientific controls, the author demonstrates the relative effectiveness of television typing instruction and conventional instruction. Results show that superior speed and at least equal accuracy are achieved by television students compared with students in the conventional classroom.

"RADIO VALVE DATA" compiled by the "Wireless World" staff. Published by Iliffe & Sons, Ltd., London. Available from British Radio Electronics, Ltd., 1833 Jefferson Place, N.W., Wash-

ington 6, D. C. 126 pages. Price \$1.50 postpaid. Paper bound. Fifth Edition.

This handy reference book will be of interest to engineers and service technicians who have occasion to work on electronic gear using British tubes. The book gives in tabular form the characteristics and base connections of approximately 2500 British and American receiving tubes, over 300 CR tubes, and 37 transistors. There is also a section devoted to voltage stabilizers.

A complete index and a table of British-American equivalents are provided.


"RADIO" by J. D. Tucker & D. F. Wilkinson. Published by The English Universities Press, Ltd., London E.C. 1. 244 pages. Price 12/6. Vol. 3.

This is the third in the publisher's series of training manuals prepared for the instruction of would-be radio engineers in England. Coverage of the subject is based on the material included in local licensing examinations.

This volume covers aperiodic amplifiers, r.f. power amplifiers, v.h.f. and u.h.f. amplifiers, oscillators, modulation, radio transmitters, antennas and transmission lines, transmission of electromagnetic waves, receivers, measurements, power supplies, direction finding, and the principles of picture transmission.

Although the treatment is mathematical and the terminology British, many radio students in this country

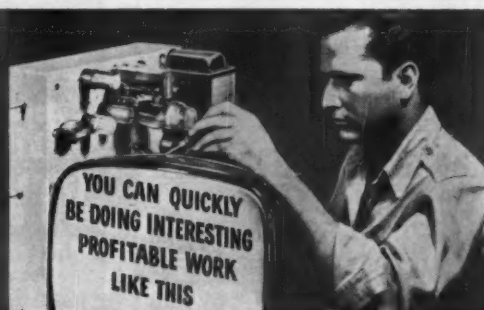COYNE QUALITY TELEVISION RADIO - COLOR TV Home Training at Unbelievably Low Cost



The future is YOURS in TELEVISION!
A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you MODERN-QUALITY Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—no costly "put together kits." Not an old Radio Course with Television "tacked on." Here is MODERN TELEVISION TRAINING including Radio, UHF and Color TV. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—**make money early in course**. Free Life-time Employment Service to Graduates.

COYNE
ELECTRICAL SCHOOL
A TECHNICAL TRADE INSTITUTE OPERATED
NOT FOR PROFIT
500 S. Paulina Street, Chicago 12, Dept. 27-MT5



Send Coupon for Free Book

and full details, including easy Payment Plan. No obligation, no salesman will call.



COYNE Television Home Training Division
500 S. Paulina St., Chicago 12, Ill.
Dept. 27-MT5

Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name _____
Address _____
City _____ State _____

THE SCOOP OF THE YEAR!!! SAVE 75% on KAY ELECTRIC TEST EQUIPMENT

KAY MODEL RF-P MARKA-SWEEP
Wide sweep, switchable, with crystal markers for aligning TV tuners, receivers. All 12 VHF channels. \$795.00 value.
Special price.....ea. **\$195.00**

KAY MODEL MEGA-PIX
Output signal frequencies: TV RF picture and sound frequencies. Maximum picture and sound carrier output: 250 MV across 72 ohms. All 12 VHF channels. \$495.00 value.
Special price.....ea. **\$125.00**

COLOR TV CHASSIS
Here's a tremendous deal for you experimental color TV chassis mfg. by Scott, using many genuine RCA parts. These are brand new and about 75% complete. Worth at least \$150.00 in replacement parts alone! While they last you get can type condensers, H.V. condensers, H.V. transf., yoke, power transf., output transf., controls, I.F.'s, coils, resistors, condensers, etc. (no tubes).....All for **\$39.50**

4.5 MC GENERATOR
Used to align sound I.F.'s. These are used but in wonderful condition. Bought at auction from Capehart. Worth much more than our low price **\$39.50**

TV CHASSIS
Mfg. by American Television, using string chassis, completely wired, less tubes and yokes. Buy them for replacement parts: flyback, tuner, 3-segment, condensers, resistors, controls, etc. All brand new, ideal for experimenting on latest type circuits. **\$15.95 ea.**

Schematics are not available for these chassis, however, with some knowledge of TV these can be put in operation. These require tubes, yoke and alignment.

SAVE 75% ON KAY ELECTRIC TEST EQUIPMENT - AT THIS EQUIPMENT WAS SPECIALLY PURCHASED AT AUCTION FROM KAYTHEON AND CAPEHART

ELECTROLYTIC BARGAINS

Cardboard insulated, with wire leads.			
Mfd.	Volts	ea.	per 10
30-30	150	3.99	34.95
20	450	.39	2.95
500	150	.39	2.95
12	475	.39	2.95
50	250	.39	2.95
20-100	490-25	.39	4.95
4	400	.19	1.95
4	300	.19	1.49

B & J ELECTRONICS INCORPORATED

COLLINS TRANSCEIVER—Model MBF. 115 V. AC-DC. 14 x 7 x 8. 25 lbs. JUST ARRIVED. Not checked, fair condition. 25 **\$19.95**
tubes. AS IS.....

COMMUNICATIONS RECEIVER—Type RBL-5—
Mfd by National for U.S. Navy and Merchant Marine—Frequency 15-600KC in 6 bands. Perfect for hams, distress band listeners, ships, etc.—Works from 115 volt 60 cycle. Gov't cost over \$600—Brand new with Tech manual (A perfect gift for ANY Radio Ham)..... **\$59.95**

CAPACITY RESISTANCE BRIDGE
Capacity Range 10 Mmfd-100 Mfd.
Resistance Range 1 Ohm-10 Meg.
Sloping Front Panel, Eye Tube and meter indicator. 12 x 10 x 10; 12 lbs.
Used, but OK..... **\$22.50**

VTVM—6 Resistance Ranges, AC Volts, DC Volts, DC Mils. Mfgd. for U.S. A lab. instrument for less than the price of a kit.
Checked out..... **\$24.95**

ARC-5 TRANSMITTERS
3-4 Mc. Exc. cond. w/tubes..... **\$5.95**
5.3-7 Mc. Exc. cond. w/tubes..... **4.95**

ARC-5 RECEIVER
3-6 Mc. Autotune Head w/tubes..... **\$6.95**

FRA—Frequency Shift Receiver Converter. RCA. Good Condition..... **\$59.95**

DYNAMOTOR—6 VDC Input; 425 VDC 375 MA. Output. 3 1/2" D. x 7" L. Elcor..... **\$25**
\$12.95, 2 for.....

RECEIVER—3 Band RCA RADIOMARINE 240-205Kc. Input 115 V. 60 cy. Part of DAE Direction Finding Equip.
Exc. Cond..... **\$39.95**

1% MIRROR SCALE—0.1 Mil. 4 1/2" Sq. Meter. Roller Smith Wht. Dial.
New..... **\$9.95**

807W/5938 Ruggedised 807. Reg. Net \$12.50
Special \$1.59 ea. Dugen..... **15.00**

DUMONT—224A Scope, Good Cond..... **\$79.95**

082 Min. VR Tube 69—Dosen..... **\$7.00**
SA5 (Radio Control tube)—3 for..... **1.00**
Telephone Dial Mechanism..... **2.95**
3" Rd. 100 Mil. Dejur..... **3.49**
2. Mfd. 600 V. B'tub S.T.—3 for..... **1.00**
MS-53 Antenna Rods—Bundle of 10..... **2.00**
Noval Sockets (9 Pr.) Lo-Loss—Dosen..... **1.00**
Resistor Bds. 12". Mt. 40 Res.—4 for..... **1.00**
Meter 1 1/2" Sq. 200 u/a. Dejur..... **5.95**
Modul. Xform 20 Watts Cased—Closeout..... **1.00**

Rex Radio Supply

88 Cortlandt Street, New York 7, N. Y.

THIS EQUIPMENT WAS SPECIALLY PURCHASED AT AUCTION FROM KAYTHEON IN CHICAGO AND CAPEHART IN FORT WAYNE.

KAY MODEL MEGA-SWEEP, CALIBRATED
Displays band-pass, single dial tuning from 50 KC to 950 MC. Dial indication of approximate output freq. \$495.00 value.
Special price.....ea. **\$125.00**

SPECIAL SMALL PARTS BAG
Over 500 usable radio and TV parts. This is not a surprise package; no junk included. Many parts have been removed from new chassis and sub-assemblies, many are brand new. Contains condensers, resistors, knobs, sockets, switches, etc.
A terrific value for only..... **\$3.95** per asst.

DOOR KNOB CONDENSER SPECIAL
500 MMFD 20KV.....49c ea. 10 for **\$3.95**
500 MMFD 10KV.....29c ea. 10 for **\$1.95**

TWIST LOCK CONDENSER SPECIALS
40-20-20 MPD @ 150V.....49c ea. 10 for **\$3.95**
50 MPD @ 450V, 40-20 MPD @ 350V.....69c ea. 10 for **\$4.95**

MIDGET IF
485 KC Broadcast band IF. 1/2" sq. x 3" high. Used for input or output..... **\$2.95** per pair 10 for **\$2.95**

ASSORTMENTS

CERAMICS. 100 asst. tubular and disc type ceramic cond. all std. values. Stk. #101..... **\$2.95** per asst.

BY-PASS. 50 asst. paper tubular by-pass condensers. Wide range of std. values; guaranteed fresh. Stk. #102..... **\$2.95** per asst.

MICAS. 50 asst. std. value mica condensers. Wide range of std. values. Stk. #103..... **\$2.95** per asst.

RESISTORS. 100 asst. carbon 1/4, 1/2, 1 watt imported resistors. Stk. #104..... **\$1.00** per asst.

RESISTORS. 100 asst. carbon 1/4, 1/2, 1 watt std. American mfg. AB, Blackpole, ETC. etc. Stk. #105..... **\$2.95** per asst.

WIRE-WOUND RESISTORS. 50 asst. 5, 10, 20, 25, 50W in wide range of values. Stk. #106..... **\$2.95** per asst.

TERMINAL STRIPS. 100 asst. Wide range of sizes and shapes from 1 lux to 8 lux. Stk. #107..... **\$1.95** per asst.

BATHUB CONDENSERS. 25 asst. Great for building hi-fi amps. 4 ham equip. Stk. #108..... **\$2.95** per asst.

CONNECTORS. 100 asst. battery plugs and small connectors. Stk. #110..... **\$2.95** per asst.

TUBE SOCKETS. 50 asst. 7 pin, 9 pin, octal, etc. Stk. #115..... **\$1.95** per asst.

TWIST LOCK COND. 10 asst. twist lock. Sell one and get your investment back! Stk. #114..... **\$2.95** per asst.

HOOKUP WIRE. 500 ft. in various sizes and colors. Stk. #119..... **\$2.95** per asst.

TOGGLE SWITCHES. 10 asst. Another great money saver for the builder. Stk. #113..... **\$2.95** per asst.

KNOBS. 50 asst. radio & TV knobs..... **\$1.95** per asst.

Stk. #111..... **\$1.95** per asst.

5335 1/2 W. DIVERSEY CHICAGO, ILL. Phone BE 7-1660

Terms: F.O.B. Chicago, Ill. Cash with order or 25% deposit on C.O.D. orders. All merchandise subject to prior sale. Prices subject to change without notice.

BUY DIRECT FROM FACTORY

THE **New** Transistorized **VTVM-VOM KIT**

NO AC source required **\$29 KIT**
Has long battery life because of Transistors **\$49 assembled**
Only gets you started

PRECISION Lab & Service Instruments in 1

Combines a transistorized VTVM with a precision VOM (Voltmeter-Ohmmeter-Milliammeter) giving you: (1) additional vital functions... (2) instantaneous checking of VTVM readings... (3) eliminates doubtful results often obtained with a VTVM.

Completely self-contained. No AC power required; no vacuum tubes to go bad. Turn of switch converts to VOM. Double check readings (VOM against the VTVM). Over 50 in precision parts in kit, such as 1% Resistors, Shunts, Microammeter, etc. Anyone can assemble in a few hours. Only \$10 gets you started; balance in easy payments. Rush order direct to factory!

TRANSVISION, INC. • NEW ROCHELLE, N. Y.

Transvision, Inc., New Rochelle, N. Y. RN-2
Enclosed find \$..... please send..... Transistorized VTVM-VOM kits.

Name.....
Address.....
City.....Zone.....State.....

will find this a worthwhile addition to their reference shelves.

"SERVICING TV AFC SYSTEMS" by John Russell, Jr. Published by John F. Rider Publisher, Inc., New York. 113 pages. Price \$2.70. Paper bound.

This book is written to help technicians locate and correct circuit faults involving the a.f.c. sections of television receivers.

The theory, waveforms, components, and common faults and their diagnosis are all covered in this handy volume. The presentation is clear and concise with the text material further enhanced by the use of 75 illustrations.

"THE RADIO-ELECTRONIC MASTER" compiled and published by United Catalog Publishers, Inc., 106 Lafayette St., New York 13, N. Y. 1546 pages. \$2.95. 21st Edition.

Once again this publication lives up to its industry reputation as the "Master" handbook of radio and electronic components. In addition to expanded coverage in almost every category, this newest edition provides a new and valuable section which lists the complete corporate name and main and branch office addresses of the manufacturers whose products are included in the catalogue. The thumb indexing of sections is another valuable time saver for the user.

Distribution of this book is being handled by local parts jobbers.

"REFERENCE DATA FOR RADIO ENGINEERS" compiled and published by International Telephone and Telegraph Corporation, New York. 1121 pages. Price \$6.00. Fourth Edition.

So much has happened in the electronics field since the Third Edition of this valuable reference manual made its appearance in 1949 that there was a real need for this improved and expanded edition.

Not only has the basic material of the earlier edition been brought up to date but new material has been added on the network design of filters, magnetic amplifiers, feedback control systems, semiconductors and transistors, scattering matrices, digital computers, nuclear physics, information theory, and probability and statistics.

A complete and cross-indexed listing of the book's contents makes this one of the easiest reference volumes for the engineer to use.

"MAN OF HIGH FIDELITY: EDWIN HOWARD ARMSTRONG" by Lawrence Lessing. Published by J. B. Lipincott, Philadelphia. 315 pages. Price \$5.00.

This is an interesting and sympathetic biography of Major Armstrong, whom the radio industry recognizes as one of its greatest inventors. He is credited with the development of the superheterodyne circuit and frequency modulation broadcasting as well as numerous other circuit improvements. The biographer points out that Ma-

40¢ FOR ANY TUBE

We Have
OVER 1000
USED
TV SETS

At all Times
in Our Huge
Warehouse

Buy one or more of these WORKING TV's to sell or use as your own second set! All Sets in GOOD WORKING condition!

Your Choice—Console or Table Model

10"\$23.00 19"\$58.00
12"\$28.00 20"\$64.00
14"\$33.00 21"\$72.00
16"\$40.00 24"\$99.00
17"\$46.00

When ordering TV's, state whether table model or console is desired. Also preference on make of set. All TV's sent railway express P.O.B. Newark. On any quantity WIRE or CALL today!

FREE BONUS AN-
TENNA GIVEN
WITH ANY TV SET
ORDER!!

FREE RCA
"CHEATER" CORD

GIVEN WITH ANY TUBE ORDER OF \$7.00 OR MORE!!

SEND for our FREE
complete TUBE &
PARTS LIST and order
blank.

WE WILL NOT BE UNDERSOLD
PROMPT SHIPMENT ON ALL ORDERS

\$3700
Per
Hundred

DON'T PAY MORE FOR SET TESTED LONG
LIFE DEPENDABLE RADIO & TV TUBES •
BUY VIDEO INDIVIDUALLY BOXED • ALL
GUARANTEED FOR ONE YEAR OR YOUR
MONEY BACK

Some Standard Brand—Others With Famous VIDEO Brand

0A2	2X2	6AC7	6BK5	6SG7	7F8	12V6GT
0A3	3A4	6AG5	6BK7	6SH7	7N7	12X4
0A4	3A5	6AF4	6BL7GT	6SJ7GT	7Q7	14A7
0B2	3AL5	6AH4GT	6BN6	6SK7GT	7Y4	14B6
0C3	3AU6	6AK5	6BQ6GT	6SL7GT	7Z4	14Q7
0Z4	3BC5	6AL5	6BQ7	6SN7GT	12A6	19B6GT
1A7GT	3CB6	6AM8	6BY5G	6SQ7	12AH7GT	19T8
1B3GT	3Q4	6AN4	6BZ7	6SS7	12AT6	24A
1C7G	3Q5GT	6N8	6C4	6SV7	12AT7	25AV5GT
1F4	3S4	6AQ5	6CB6	6T8	12AUG	25BQ6GT
1H4	3V4	6AQ7GT	6CD6G	6U4GT	12AU7	25OD6G
1H5GT	4B27	6AS5	6CF6	6U7G	12AV6	25CU6
1J6GT	4B97	6AS7G	6CS6	6U8	12AV7	25L6GT
1L4	5AM8	6AT6	6CU6GT	6V3	12AX4GT	25W4GT
1L6	5AN8	6AU4GT	6E5	6V6GT	12AX7	25Z6GT
1LA6	5AQ5	6AU5GT	6H6GT	6W4GT	12AZ7	35L6GT
1LC5	5AT8	6AU6	6J4	6W6GT	12B4	35W4
1LH4	5AW4	6BU5GT	6J5GT	6X4	12BA6	35Y4
1LN5	5AZ4	6AV6	6J6	6X5GT	12BE6	35Z3
1N5GT	5J6	6AX4GT	6K6GT	6X8	12BH7	35X5GT
1S4	5T4	6AK5GT	6L6	6Y6G	12BY7	50A5
1S5	5T8	6BA6	6N7GT	7A5	12CUG	50B5
1T4	5U4G	6BC5	6S4	7A7	12SA7	50C5
1U4	5U8	6BC7	6STG	7B5	12SG7	50L6GT
1U5	5V4G	6BE6	6SA7	7B7	12SH7	80
1V2	5V6GT	6BF5	6SB7Y	7C5	12SJ7GT	117N7GT
1X2	5Y3	6BG6G	6SC7	7C6	12SK7	117P7GT
2A7	5Y4G	6BH6	6SF5	7C7	12SN7GT	117Z3
2D21	6AB4	6BJ6	6SF7	7F7	12SQ7	

FREE POSTAGE in U.S.A. and Territories on orders over \$5.00. 25c handling charge on orders under \$5.00. 25% deposit required on C. O. D.s. Please send approximate postage or freight on Canadian and foreign orders. Subject to prior sale.

VIDEO ELECTRIC COMPANY

79 CLINTON PL. NEWARK, N. J. Phone HU-boldt 4-9848

FREE 3-in-1 PRECISION
SCREWDRIVER SET WITH EVERY ORDER

take your pick
any assortment

100
receiving
tubes
\$38

On orders of less than
100 tubes — 41¢ each

ALL TUBES UNCONDITIONALLY GUARANTEED FOR 1 YEAR


BRAND NEW TV PICTURE TUBES		PRETESTED TUBES—INDIVIDUALLY BOXED	
Type	T.M. Price	Type	T.M. Price
100P4	\$10.95	024	183GT
12LP4	12.95	040G	185GT
12QP4	10.00	045V	185GT
14CP4	15.25	045V	185GT
15DP4	14.95	045V	185GT
16DP4	18.50	045V	185GT
16QP4	19.25	045V	185GT
18KP4	17.00	045V	185GT
16RP4	\$17.00	045V	185GT
17BP4	19.00	045V	185GT
17QP4	21.00	045V	185GT
17LP4	18.00	045V	185GT
19AP4	23.00	045V	185GT
20CP4	24.00	045V	185GT
21ALP4	24.00	045V	185GT
21EP4	24.00	045V	185GT

Picture tubes
F.O.B. PASSAIC, N. J.
via Railway Express

TUBE MART
DISCOUNT HOUSE

Phonelt 3-8330 The Leiper Bldg. Passaic, N. J.

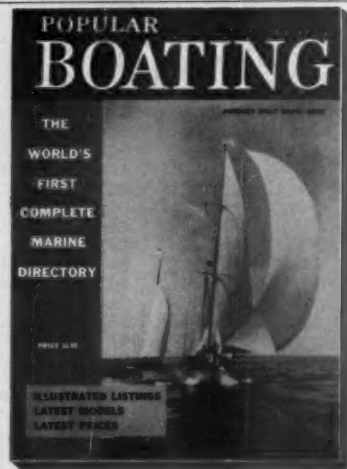FIRST COMPLETE
MARINE DIRECTORY
IN JANUARY
POPULAR BOATING!



The world's first complete Marine Directory is yours as a big extra bonus in the January Boat Show Issue of **POPULAR BOATING**, now on sale.

If you now own a pleasure boat . . . or plan to buy one soon . . . here's your guide to all craft, equipment and accessories on the market. It contains over 1000 illustrations . . . manufacturers' names and prices in full.

Be sure to buy your copy of the Giant 300-page January issue of **POPULAR BOATING**. Now on sale at your favorite newsstand—only \$1.00.

for Armstrong's "rugged individualism" in the age of industrial giants was both his strength and his weakness. Some three years have elapsed since Armstrong ended his life in New York and the biographer feels that time alone will restore the luster that by rights belongs to Edwin Howard Armstrong.

"ANALYSIS OF BISTABLE MULTI-VIBRATOR OPERATION" by P. A. Neeteson. Published by *Philips Technical Library*, Eindhoven, Holland. 82 pages. Price \$2.15 postage prepaid direct from the publisher.

This is volume ten in this publisher's series on tubes and covers the Eccles-Jordan flip-flop circuit. The careful and complete analysis of this useful circuit will be of particular interest to those working with electronic computers and allied equipment. The text material is divided into twelve chapters with mathematical calculations of the various circuit constants contained in five separate appendices.

"PICTORIAL MICROWAVE DICTIONARY" by Victor J. Young & Meredith W. Jones. Published by *John F. Rider Publisher, Inc.*, New York. 110 pages. Price \$2.95.

This is a specialized volume for both technical and lay persons interested in microwave techniques. Like a dictionary, terms are listed alphabetically and relatively concise definitions of the words given in italics but unlike usual dictionaries, explanations and circuit diagrams are included to amplify the term being defined. —30—

"Presence" Equalizer
 (Continued from page 42)

at 3000 cycles when the choke is shunted by the 100 μ fd. capacitor. If another make of choke is used, the value of C_2 may have to be changed to produce the required resonant frequency.

The location of the parts is not critical, and any other convenient arrangement can be used if desired, but as is usual with high-impedance, low-level devices, the leads should be kept as short as possible. The equalizer shown in the photographs was assembled in a 2½" x 4" x 1½" ICA aluminum "Flexi-mount" case. The 2½" x 3½" x 1½" size case could also be used without difficulty.

The insertion loss varies between 4.8 db and 10.5 db, depending upon the amount of boost. The usual type of equipment used in home high-fidelity installations has enough spare gain to compensate for this loss.

As the choke is subject to hum pickup from the magnetic fields of power transformers and tape machine and record player motors, the equalizer should not be mounted permanently until it has been determined that its position in relation to such hum-producing fields is correct for minimum hum.

—30—

Component Checking (Continued from page 66)

current allowed, and when the capacitor has reached its nominal charged voltage, it can then be removed from the charging arrangement. Then, after discharging the capacitor for the sake of safety, the capacitor is ready for installation in its intended circuit. Discharge should preferably be accomplished through a fairly large resistor. The common practice of short-circuiting a fully charged capacitor results in a very high discharge current that may damage the capacitor.

Sometimes a capacitor which has been in stock a long time will deteriorate in the quantity of electrolyte present, so the capacitance will fall low in value, even after it has been adequately reformed.


If it is not convenient to build a capacitance measuring arrangement incorporating the polarizing supply, a fairly legitimate result can usually be achieved by ensuring that the capacitor is correctly formed using the polarizing jig of Fig. 8, then discharging the capacitor and finally measuring it immediately with the aid of one of the conventional capacitance bridges without polarizing voltage.

If the electrolytic capacitor is reasonably stable, a null will be obtained which will not vary at a perceptible rate. If the capacitor is not sufficiently stable to be reliable in use, the null may be observed to vary perceptibly while the measurement is being taken. If the capacitance varies at a rate that can be noticed while making the measurement, then the capacitor should be discarded as insufficiently stable for reliable operation.

The foregoing discussion has covered the more common measurements necessary on resistance, inductance, and capacitance. Sometimes much more precise methods of measurement are necessary, especially where the equipment is for some kind of standard operation such as a precision oscillator. In this kind of application it is often necessary to make measurements, not only as to the precise value at room or ambient temperature, but to determine the effect of temperature on the component. To make such measurements, only precision bridge apparatus is satisfactory, and the component should be measured under carefully controlled conditions of temperature and the measurements repeated at different temperatures, to discover what temperature coefficient the component possesses.

—M—

Fig. 8. Details for constructing a simple jig for forming electrolytic capacitors up to their working voltage. See article.

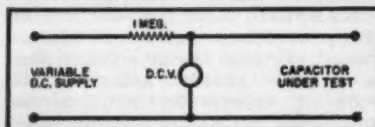

ADDS INCOME 2 WAYS

1. Tests and Repairs Picture Tubes
2. Makes New Tube Sales Easier

CATHODE REJUVENATOR TESTER

Quickly Spots and Corrects TV Picture Tube Troubles Without Removing Tube From the Set

TESTS the picture tube for all the important factors which determine the quality of the tube.

RESTORES emission and brightness.

REPAIRS inter-element shorts and open circuits. Stops leakage.

LIFE TEST checks gas content and predicts remaining useful life of the picture tube.

GRID CUT-OFF reading indicates the picture quality customer can expect.

QUALITY DESIGN makes it easy to use. Provides quick reading at a glance.

CRT 400 PROVES REAL MONEY-MAKER

Here's what Joe Driscoll of TV Trouble Shooters, St. Paul, Minnesota says: "It has made more money for us than any other instruments, with the possible exception of tube checkers. We make an additional charge each time we use the instrument in the home to check or correct picture tube conditions. We have been able to convince customers much easier that their old tubes need replacing and have enjoyed a nice profitable business from the sale of new picture tubes without leaving any doubt whatever in the customer's mind that he needed a new tube."

This is typical of the experience of thousands of servicemen using the CRT 400. It cuts service-operating costs...brings new profits...builds customer good-will...quickly pays for itself. Also saves money on TV set trade-in reconditioning. Has 4 1/2-inch plastic meter. Easily portable. **NET \$54.95**

See Your Distributor today or Write for Bulletin No. 400-N

Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR

B & K MANUFACTURING CO.
3726 N. Southport Ave. · Chicago 13, Illinois



BEST SURPLUS VALUES



RT-34/APS-13 TRANSCIVER

for 430 mc. use. Less tubes and dynamotor.

\$3.50 each, 2 for \$6.00.

T-20-ARC-5 TRANSMITTER

4-5.3 mc. Brand new with all tubes and calibrating crystal. Only.....**\$6.00**
POWER TRANSFORMER: Primary 110 vac, 60 cycle. Secondary 700 v, c. t. @ 100 ma; 6.3 v @ 7.5 a; 6.3 v @ .3 a; 5.0 v @ 2 a. Only.....each **\$3.95**

FILAMENT TRANSFORMER: Primary 110 vac, 60 cycles. Secondary 6.3 v @ 1 a. Only.....each **89c**
FREE! Send for our bulletins of hundreds of quality surplus items.

All items shipped FOB our warehouse. On C.O.D.'s include 25% with order. Ohio residents add 3% sales tax. All items subject to prior sale.

KOPELOVE ELECTRONICS COMPANY
Dept. RM 257, 1919 East First Street, Dayton 3, Ohio

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

ISOLATION TRANSFORMER BARGAIN

(110V-110V.)

Fully shielded with line cord and receptacle.

200 WATTS.....\$4.75 2 for \$8.95

POWER TRANSFORMER BARGAIN

Primary 115 V. 60 cy. Sec. 425-0-425V @ 200 ma., 5.3 V. @ 5 amp., 5 V. @ 4 amp. Standard mounting. 2 for \$7.50

\$3.99 ea.

POWER SUPPLY KIT

Transformer as described above plus 1-shielded 500K 200 MA choke and 2 oil condensers 10 MFD, 600 VDC.....\$6.75 ea.

G.E. MIDGET POWER SUPPLY

115V. 60 cy. input. Delivers 138 VDC @ 50 MA and 5.3 V @ 1 amp. Well filtered. Ideal for 8 eliminator for periscope, pre-amps, etc. Complete with rectifier and line cord.....\$3.95 ea.

OIL CONDENSER

4x4x4 MFD 500 VDC.....95c

.001 15,000 VDC

Ceramic Condenser Low-loss 2 for \$9.95

WESTERN ELECTRIC

Stepping relay 44 steps. 5-15 Volt.....\$4.95

6 VOLT DYNAMOTOR

400 Volts @ 175 Mils. out. Small size.....\$9.95

6 VOLT DYNAMOTOR

500V @ 150 ma.\$9.95

OIL CONDENSER

4 MFD. 3000 VDC Ceramic Inc.\$3.95

4" PM SPEAKER

BRAND NEW.....\$1.19 ea.

DM-350 DYNAMOTOR BRAND NEW

12 Volt DC Input 625 V. @ 325 Mill. Output.....\$14.95

Write for quantity prices.

Visit Our Store for Unlisted Bargains

G. E. RELAY CONTROL

(Ideal for Model Controls, Etc.)

Contains a sigma midget 3,000 ohm. relay (trips at less than 2 MA), high impedance choke, bimetal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total low price of.....\$1.10 Each 10 for \$9.25

FREE Model Control Book with Purchase of 10.

SENSITIVE PLUG-IN RELAY

DPDT 14,000 OHM COIL Plugs into Gatal Socket \$1.99 each

WESTON

0-1 MILL METER 270° SCALE 2" CASE MODEL #1329.....\$4.95

12-14 VOLT DYNAMOTOR

375 Volt at 150 Ma. with Filter.....\$4.95

ANTENNA RELAY

12 Volt DC. DPDT plus extra SPST 10 amp contact. Low loss Inc.\$1.39

POWER SUPPLY

HEAVY DUTY—HIGH VOLTAGE

Delivers 5,000 volts at 500 MA continuous duty. Input single phase 115/230 volts 60 cy. Variacs in high voltage primary and rectifier fil. mounted in cabinet with dolly. Equipped with blower motor, circuit breakers and other protective devices. HV and Filament transformer, metered plus running time meter. HV oil filters and chokes. Complete with 4 GL451 rectifier tubes.....\$295.00

USN Surplus. Priced at.....\$295.00

WESTON MODEL #799

PORTABLE INSULATION TESTER

0-50,000 Megohms Complete with 3LM4 Tube

In Wood Carrying Case Reg. \$75.00. Our Price

Only \$18.50 ea.

OIL CONDENSER BARGAINS

1 mfd 500 VDC .35 2 mfd 500 VDC .45 4 mfd 500 vdc. .75 8 mfd 500 vdc. .95 10 mfd 500 vdc. .99 1 mfd 1000 vdc. .60 2 mfd 1000 vdc. .75 4 mfd 1000 vdc. 1.25 8 mfd 1000 vdc. \$1.35 12 mfd 1000 vdc. 1.50 6 mfd 1500 vdc. 1.95 2 mfd 2000 vdc. 1.50 3 mfd 2000 vdc. 2.25 4 mfd 2000 vdc. 2.75 6 mfd 2000 vdc. 3.45 8 mfd 2000 vdc. 4.25 10 mfd 2000 vdc. 4.95 2 mfd 3000 vdc. 1.85 4 mfd 3000 vdc. 2.75 6 mfd 3000 vdc. 3.45 8 mfd 3000 vdc. 4.25 10 mfd 3000 vdc. 4.95 2 mfd 4000 vdc. 2.75 4 mfd 4000 vdc. 3.45 6 mfd 4000 vdc. 4.25 8 mfd 4000 vdc. 4.95 10 mfd 4000 vdc. 5.65

BIG BARGAINS IN LITTLE TYPE

KIT of 25 WIRE WOUND RES. 5 to 50 watt. \$1.95 KIT of 10 TRANSMITTING MICAS.....1.00 1 amp. MERCURY SWITCH.....95c ea. 2 for 1.00 500 MFD CERAMIC CONDENSERS.....10 for .50 15 REG 1% METER MULTIPLIER.....10 for .50 2 MFD 400VDC OIL COND.....10 for .99

Min. Order \$3.00—25% with order F.O.B. New York 10 DAY GUAR. PRICE OF MDSE. ONLY

ADVANCE ELECTRONICS COMPANY

6 WEST BROADWAY, NEW YORK 7, N. Y. Phone REctor 2-0270

Miniature Scope

(Continued from page 69)

Whether you build this device or one employing a larger tube, remember that the electron beam is quite sensitive to the presence of alternating-current fields. Be sure to use a galvanized sheet-metal shield, or one of the commercially available CRT shields! Always keep transformer and a.c. wiring fields well behind the CR tube.

Component placement is shown in Fig. 3. Midget pots R_2 , R_3 , and R_4 are secured to the front panel directly beneath the 913. Due to space restrictions, R_4 is screwdriver-adjusted through a hole in the front panel's center.

When doing miniaturized construction, wiring becomes easy, due to tricks of soldering one part to another and making "sandwiches" of components. Using short connections and clamping an occasional part to the chassis, this method of construction results in a solid non-vibrating package.

If you prefer to build a larger instrument than the one shown, the schematic of Fig. 1 may be applied to other CR tubes such as the 2AP1A, 2BP1A, etc. Proper operating voltages for such tubes may be determined by experimenting with the values of R_1 , R_2 , and R_3 .

Applications

Fig. 4 illustrates the method of connecting the trapezoidal scope to a transmitter. The connection between vertical plate (4) and the transmitter should be made with coaxial cable, using the outer shield as common ground return for one side of the r.f. pickup link and the ground side of the audio voltage. If shielded links are not used, you will probably encounter 60-cycle distortion on the spot trace.

After application of a.c. power, allow the tube to warm up. Advance intensity control R_2 until the spot appears; it may be large and fuzzy at first, so adjustment of focus control R_3 should bring it to a sharp, bright pinpoint. Do not allow the spot to remain in one position for more than a moment at a time. The concentrated beam will burn a permanent mark into the fluorescent screen. Run the intensity setting at a level just sufficient to produce a clearly visible trace.

Couple the r.f. link to the transmit-

Fig. 4. Connections for modulation check.

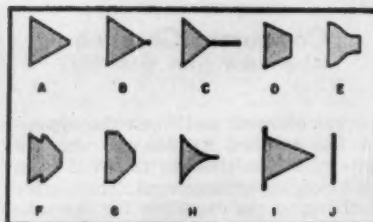
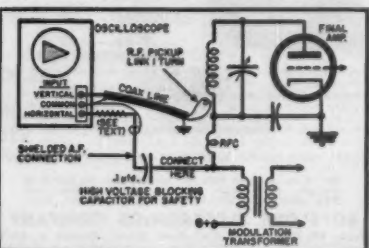


Fig. 5. Typical modulation patterns. Refer to the article for a complete discussion.

ter final tank. Too much coupling will result in a vertical line too long for the tube's screen. Decouple the link until the vertical deflection occupies about four-fifths of the screen. Using this line as a guide, rotate the tube into final operating position, and lock the clamp.

By whistling into the microphone while adjusting horizontal gain control R_1 , you'll see a triangle like that shown in Fig. 5A if your rig is properly adjusted. Once the vertical r.f. amplitude is fixed, adjust R_2 so that an even, three-cornered triangle is visible. Note: If your modulator delivers over 20 watts, better add two or three megohms in series with the a.f. lead as shown in Fig. 4. This scope will monitor a full kilowatt transmitter's output, but audio voltage to the device must be attenuated in proportion to modulator power.

You'll probably be primarily interested in modulation percentage. If you're overmodulating, the triangle's apex will extend outward in a thin line. By percentage interpolation, it's easy to ascertain approximately how much you're overdoing it, as shown in Fig. 5B.

Heavy overmodulation splatter due to severe negative peak clipping elicits a pattern such as Fig. 5C. If the rig is undermodulated, the triangle will not fill completely, interpolation showing by what approximate amount below 100%.

If the modulator isn't properly matched to the final (due to incorrect antenna loading, wrong impedance ratios, etc.) you'll get a pattern similar to Fig. 5E. If the modulator is regenerative, Fig. 5F results. With insufficient grid drive to the final, you'll see Fig. 5G.


Supposing the final isn't properly neutralized? Fig. 5H shows up. And when your transmitter develops parasitic oscillations only on modulation peaks, you'll see the pattern of Fig. 5I as well as hear about it. Fig. 5J shows the straight line produced by the unmodulated r.f. carrier.

It's very difficult to interpret all of the foregoing conditions when looking at a wave-envelope pattern. Therefore this scope was designed to use the triangular pattern, resulting in minimum parts but maximum utility.

WARNING! Note that one side of the power line connects to chassis ground. Be sure that the power plug is correctly inserted, otherwise 117 volts a.c. appears between the case and "house" ground.

-30-

What's

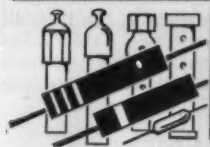

New in Radio

FERRITE YOKE CORES

Allen-Bradley Company, 136 West Greenfield Ave., Milwaukee 4, Wis. has developed a new ferrite "full-round" deflection yoke core for use in TV picture tube assemblies.


The yoke core is pressed as a ring of perfectly uniform section and circularity. It is then "cracked" into two halves for later assembly over deflection coils and fitting to the tube. The mated halves are shipped held together mechanically to avoid damage in transit. These yokes eliminate the grinding, fitting, and setting necessary with quarter-round sections.

Full details on this new component are available from the company or from the firm's distributors.

NEW "REJUVA-CHECK"

Century Electronics Co., Inc., 111 Roosevelt Ave., Mineola, N. Y. has added a new instrument to its line of service test gear.

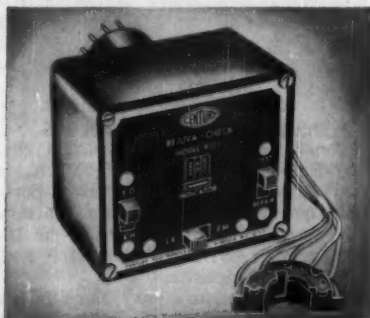Known as the "Rejuva-Check" Model RJC-1, the new unit is a compact, low-priced item that checks cathode emission, indicates shorts and leakage between elements, estimates the remaining useful life of the CRT, clears interelement shorts and leakage, re-



moves cathode surface contamination, and restores emission to give new life to weak and dim tubes.

Price information and additional data on this unit are available from the manufacturer.


TRANSISTOR CODE OSCILLATOR

Jackson Electrical Instrument Company, 16-18 S. Patterson Blvd., Dayton 2, Ohio has announced the availability of a transistorized code practice oscillator, which is compact and easy-to-operate.

Employing a *p-n-p* junction transistor, the new unit utilizes external magnetic phones and a key. The oscillator also includes special jacks for interconnecting two units to simulate station-to-station operation. With a few minor circuit changes, the instrument

may also be used to monitor a c.w. transmitter.

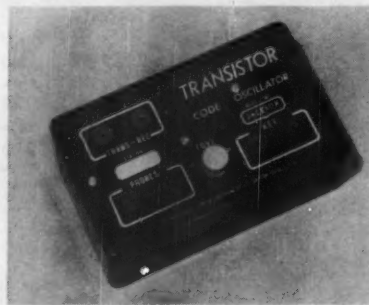The unit weighs 1½ pounds, less battery, and measures 6¼" x 3¾" x 2".



The case is of molded Bakelite. The unit is being merchandised through regular parts jobbers.

VOLTAGE DROPPING RESISTORS

G-C Electronics Mfg. Co., 400 S. Wyman St., Rockford, Ill. is now merchandising a pair of voltage dropping resistors which enables service technicians to connect 6-volt electrical accessories to the 12-volt ignition systems found in most new cars.

Two units are available, the No. 5225 is designed specifically for use with car radios while the No. 5226 is for wider voltage dropping requirements. Additional information on either of these units is available from the company.

V.H.F. SWEEP GENERATOR

Community Engineering Corporation, P. O. Box 824, State College, Pa.



is now in production on a new wide-band v.h.f. sweep generator for laboratory and field use.

The Model 100-T is a fixed frequency unit which can be specified for any

HARVEY's famous hi-fi consultants RECOMMEND

... the DYNAKIT MARK II 50-WATT Power Amplifier Kit

This is the amazing do-it-yourself package that audio perfectionists have been choosing for over a year now in preference to more expensive amplifiers. Incorporating an ingeniously simple, unprecedentedly stable and utterly reliable circuit by David Hafler (of "Ultra-Linear" fame), plus premium-quality components such as the superb Dynaco A-430 output transformer, the DYNAKIT delivers 50 watts at any audible frequency with incredibly low distortion—harmonic, intermodulation, square-wave, phase, pulse or any other kind. Listening quality is unsurpassed; construction time is around three or four hours thanks to the pre-wired printed circuit board; price is still only \$69.75

... the W/B STENTORIAN

Model HF 1214

12-Inch

Extended-Range Loudspeaker

A HARVEY Special!




Despite widely different tastes in loudspeakers, this beautifully made 12-inch single-cone unit has the virtually unanimous vote of critical high-fidelity enthusiasts as an exceptionally smooth and natural-sounding transducer. The 5½ lb. Alcomax magnet system, the specially designed cone, the unusually low bass resonance (39 cps) all contribute to the de luxe performance of the HF 1214, which even at its regular price is easily the equal of many more costly loudspeakers. At the present limited-offer price, it is a bargain without a rival.

Regularly \$49.50... HARVEY SPECIAL \$34.50

... and the GARRARD 301

3-speed

Transcription Turntable

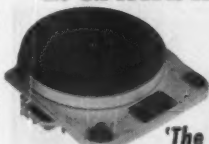

'The Professional'

Among the many top-quality wow-and-rumble-free turntables available today, the GARRARD 301 seems to be the first choice of a large number of hi-fi authorities. The famous Mr. G. A. Briggs, for example, has been using it exclusively in all of his celebrated concert-hall demonstrations throughout the world. The variable + or - fine-speed control, operative on all 3 speeds, may have something to do with the 301's exceptional success—and the Swiss-watch-like precision construction, combined with components of the very highest quality, is quite irresistible.

So is the price—only \$89.00

MAIL ORDERS SHIPPED SAME DAY AS RECEIVED

Include with your payment a generous allowance for shipping charges—the excess will be promptly refunded.

HARVEY Estab. 1927
RADIO CO., INC.

1123 Avenue of the Americas JU 2-1500
16th Ave. at 43rd St. N.Y. 36, N.Y.

Radio experts solve your engineering problems

Save \$6.50 on newly revised
RADIO ENGINEERING LIBRARY

At your fingertips in one convenient source—facts, standards, practices, data for the whole field of radio engineering. Highlights current developments in transistors, other semi-conductors, microwave tubes, pulse techniques, color TV, and more. Covers everything from tube and circuit fundamentals through essentials of major fields of application.

OVER 4000 PAGES OF PRACTICAL MATERIAL!

Five fact-packed volumes of data, graphs, charts and tables give information quickly. Includes material on UHF, frequency modulation, instruments and methods for measuring high frequency, etc. Selected by radio specialists as most helpful material for engineers, designers, and others in communication, broadcasting, aircraft radio, and related fields, this library is yours at a special price on easy terms.

10-DAY FREE TRIAL!

McGraw-Hill Book Co., Dept. RTN-2
327 W. 41 St., New York 36, N. Y.

Send for 10 days' FREE trial, the Radio Engineering Library. In 10 days I will send (check one) ☐ \$49.50; or ☐ \$7.50 in 10 days and \$7.00 a month until \$49.50 is paid—a savings of \$6.50 over regular price of \$56. Otherwise, I will return books postpaid.

Name

Home Address


City & State

Employed by

For price and terms outside USA, RTN-2 write McGraw-Hill Int'l., N.Y.C.

ELECTRIC BRAIN KIT

Can you think faster than this machine?

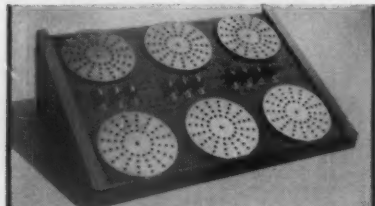

Control Panel of GENIAC set up to do a problem in check valve research.

Be careful before you answer. GENIAC the first electrical brain construction kit is equipped to play tic-tac-toe, cipher and encipher codes, convert from binary to decimal, reason (in syllogisms) as well as add, subtract, multiply and divide. Specific problems in a variety of fields—actuarial, policy claim settlement, physics, etc., can be set up and solved with the components. Connections are solderless and are completely explained with templates in the manual. This covers 33 circuits and shows how new ones can be designed.

You will find building and using GENIAC a wonderful experience; one kit user wrote us: "this kit has opened up a new world of thinking to me." You actually see how computing, problem solving, and game play (tic-tac-toe, nim, etc.) can be analyzed with Boolean Algebra and the algebraic solutions transformed directly into circuit diagrams. You create from over 400 specially designed and manufactured components a machine that solves problems faster than you can express them.

Schools and colleges, teachers of science or math, engineering, philosophy or psychology will find these excellent demonstrators of circuitry, solutions in symbolic logic, theory of numbers, cybernetics, and automation.

SEND for your GENIAC kit now. Only \$19.95 with over four hundred components and parts, fully illustrated manual and wiring diagrams. We guarantee that if you do not want to keep GENIAC after one week you can return it for full refund plus shipping costs. Add \$1 west of the Miss. \$21.95 outside U.S.

Dept. RT-27, Oliver Garfield Co.
126 Lexington Ave., N. Y. 16, N. Y.

frequency sweep width ratio of 1.7 to 1 in the frequency range from 30 to 220 mc. One popular range is from 52 to 90 mc. to sweep TV channels 2 to 6 in equipment of community antenna TV systems. Output is greater than .5 volt r.m.s. and flat to less than $\pm .5$ db. The unit is highly portable, weighing only eleven pounds.

Details and specifications are available on request to the manufacturer.

CAPACITOR CHECKER

The Barjay Co., 145 W. 40th St., New York, N. Y., is now in production on a new "Capacitest" unit, the Series 11.

The new test instrument not only checks all types of capacitors but also offers a positive test of selenium rectifiers. With an applied voltage of 150 volts, approximating the working voltage of the components in the set, the instrument will show up open, inter-




mittent, shorted, or leaky capacitors. It will also indicate a faulty selenium rectifier.

The unit measures 4" x 4" x 2" and comes complete with test leads and full instructions.

MONITOR RECEIVER

Industrial Radio Corp., 428 N. Parkside Ave., Chicago 44, Ill., has designed a new monitoring receiver especially for police and fire department, utility, government, and industrial radio applications.

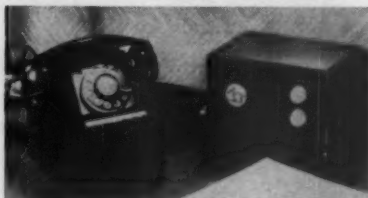The small set, known as the "Volunteer," uses miniature tubes and transistors, an improved dual conversion superhet, and crystal control. A squelch circuit silences the receiver be-



tween calls. Because the set is designed for single channel use, the only adjustments are for volume and squelch setting.

The a.c. models use 15 tubes and have built-in speakers and power supplies. The mobile models are available for 6 or 12 volt electrical systems and use power transistors in the output to


reduce battery drain to a minimum. The antenna terminals are designed to accommodate ordinary car radio antennas.

There are six models in the line, all moderately priced. The crystal is extra. These receivers will be merchandised by two-way radio service organizations.

TRANSISTOR OSCILLATOR

Kay Electric Company, 14 Maple Ave., Pine Brook, N. J., has announced the availability of a new portable, crystal-controlled transistor oscillator, the Model 125A.

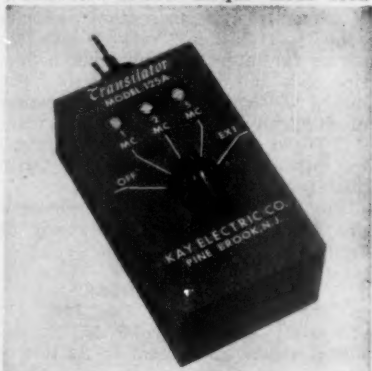The "Transilator" employs a pair of transistors and a unique diode feed-



back system in a battery-operated unit. Output frequencies of 1, 2, and 5 mc. are available by rotating a selector switch. An external crystal jack is provided to furnish other frequencies falling between 1 and 5 mc.

The output is .25 volt at 1000 ohms impedance level. The entire instrument measures 2" x 1 1/4" x 4 1/2" and weighs 12 ounces. The company will supply any additional information required.

PLUG-IN BATTERY CHARGERS

American Television & Radio Co., 300 E. 4th St., St. Paul 1, Minn., is now offering a complete line of portable automobile plug-in type battery chargers for operation with 6- or 12-volt storage battery systems for 4, 6, and 10 amp capacities.

The units feature easy charging by simply plugging into cigarette lighter receptacles. Complete information is available directly from the factory.


COMMUNICATIONS MONITOR

The Monitor Radio Division of I.D.E.A., Inc., 7900 Pendleton Pike, Indianapolis 26, Ind., is now offering two new FM receivers which have been designed especially for police, fire, civil defense, etc. applications.

The "Minute Man" is a tunable unit which is available in two models. The MR-10 will monitor all frequencies on the 152-174 mc. band while the MR-33 is designed to cover the 30-50 mc. band. This 7-tube FM receiver includes a built-in electronic squelch, fully tuned r.f. stage, a 5" PM speaker, a transformer-type power supply—all housed in a rugged metal cabinet.

A fixed-frequency version of this

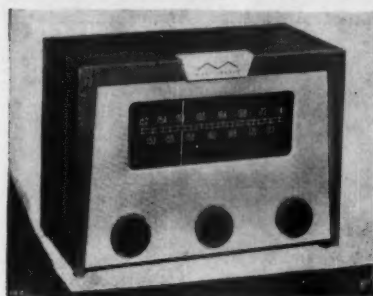receiver is available as the "Signal Master." It, too, is available in two



models and comes with the crystal custom-ground and the circuit aligned.

WHITE DOT GENERATOR

The Special Products Division of Admiral Corporation, Chicago, Ill., is now offering a low-cost, compact white-dot generator which is designed for setting up color receivers during installation and servicing and for adjusting linearity on black-and-white sets.

The new instrument contains only three tubes and two semiconductor diodes. It features an a.c.-operated transformer-type power supply.

DIODE-TRANSISTOR TESTER

Fretco Incorporated, 406 N. Craig St., Pittsburgh 13, Pa., is now offering




a new diode and transistor tester for service applications.

The new unit will measure and test characteristics of diodes, *p-n-p*, and *n-p-n* transistors. The instrument is battery powered and comes complete with test leads.

Full details on this moderately priced unit are available from the manufacturer.

VARIABLE AIR CAPACITORS

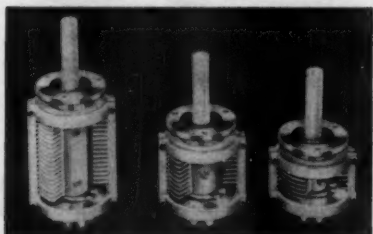General Radio Company, 275 Massachusetts Ave., Cambridge 39, Mass., is



now offering a new line of variable air capacitors whose improvements in electrical and mechanical properties have been effected by machining them from solid metal.

With the Type 1420 units both ro-

NEW

HICKOK

CRYSTAL CONTROLLED WHITE DOT-BAR COLOR DISPLAY GENERATOR

Model 660



The 660 is ideal for the proper alignment of color TV receivers. It is accurate and unusually easy to use. Preset channels allow easy selection through a built-in switching arrangement. Provides either of the following patterns on any color TV receiver:

White Line Crosshatch; 20 vertical and 15 horizontal, less those in blanking.

White Dot (small size); 300 dots, less those in blanking.

Crystal Accurate Color Display Pattern; in a blended sequence of orange, red, magenta, blue, cyan, green.

The 660 features the necessary high degree of stability not found in variable white-dot generators. In the 660, the white dots are "locked" together to assure stability. This locking is achieved through the extremely stable (crystal controlled) timer circuit. Frequency of chrominance (color) signal is exactly crystal controlled to reduce possibility of alignment errors. This feature permits increased accuracy over ordinary color generators which use a free running oscillator. RF output frequency is in preset channels, 2 thru 6, to allow easy selection through a built-in switching arrangement. Small dot and crosshatch size down to two lines in both horizontal and vertical planes. Ratio of sync to video is variable from 10 to 90%.

• The circuit of the 660 is such that the instrument will be useable regardless of future color TV receiver design.

TECHNICAL SPECIFICATIONS:

VIDEO OUTPUT: 0 to 4 volts Peak-to-Peak. 300 ohm output impedance. Black positive or negative. 300 white dots, less those in blanking. Crosshatch white lines, 20 vertical and 15 horizontal, less those in blanking. Sidelock color frequency crystal is 3.563795 MC output 1 volt Peak-to-Peak.


RF OUTPUT VOLTAGE: .05 volts maximum. .001 volts minimum.

RF modulated by all video outputs (60% modulation).

★ The Model 660 is especially designed for Home service calls.

★ Light weight portable with detachable cover... weighs only 15 pounds.

ORANGE RED MAGENTA BLUE CYAN GREEN

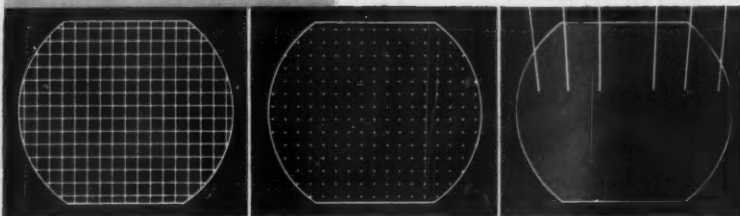

White line crosshatch pattern. 20 vertical and 15 horizontal, less those in blanking.

Small size white dot pattern. 300 white dots, less those in blanking.

Color display pattern with crystal accuracy. Color sequence: Orange, Red, Magenta, Blue, Cyan and Green.

THE HICKOK ELECTRICAL INSTRUMENT CO.

10524 Dupont Avenue • Cleveland 8, Ohio

"ONE DOLLAR"

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.

- 3 - 20KV—500 mmfd H. V. Cond.\$1
- 100 - ASSORTED 1/2 WATT RESISTORS.\$1
- 100 - FUSES 1 AMP. standard also 1 1/4" x 1/4"\$1
- 4 - SETS SPEAKER PLUGS wired\$1
- 100 - ASSORTED WHITE TUBE CARTONS.\$1
- 5 - HI-VOLT. ANODE LEADS with 10" leads\$1
- 1 - 21" TV OPEN MASK soft gray color\$1
- 100 - FINEST NYLON DIAL CORD.\$1
- 300 - SELF TAPPING SCREWS #8/32 x 3/4"\$1
- 400 - ASST. SCREWS, NUTS, WASH, RIVETS.\$1
- 50 - ASST. TUBULAR CONDENSERS 85"\$1
- 70 - ASST. 1 WATT RESISTORS.\$1
- 35 - ASST. 2 WATT RESISTORS.\$1
- 35 - ASST. RADIO KNOBS screw end push-on\$1
- 50 - ASST. SOCKETS arial and miniature\$1
- 50 - ASST. MICA CONDENSERS come in 50p\$1
- 50 - ASST. CERAMIC CONDENSERS.\$1
- 10 - ASST. VOLUME CONTROLS less switch\$1
- 5 - ASST. VOLUME CONTROLS with switch\$1
- 20 - ASST. PILOT LIGHTS #4, 46, 47, 51\$1
- 50 - ASST. TERMINAL STRIPS 1/2, 3, 4 bar\$1
- 10 - ASST. RADIO ELECTRO. CONDENSERS.\$1
- 5 - ASST. TV ELECTROLYTIC CONDENSERS.\$1
- 10 - 6 FT. ELEC. LINE CORDS with plug\$1
- 5 - TV CHEATER CORDS with both plugs\$1
- 10 - ASST. WIREWOUND RES. 5, 10, 20 watts\$1
- 200' - HOOK-UP WIRE & SOLDER KIT.\$1
- 100' - TWIN 3000' LEAD-IN heavy duty\$1
- 5 - TV CRT. SOCKETS with 18" leads\$1
- 10 - AC-DC ANTENNA HOOKS each 20 feet\$1
- 25 - ASST. MICA TRIMMER CONDENSERS.\$1
- 50 - TUBULAR CONDENSERS 1-300v\$1
- 50 - TUBULAR CONDENSERS .02-400v\$1
- 50 - TUBULAR CONDENSERS .001-600v\$1
- 25 - TUBULAR CONDENSERS .01-600v\$1
- 20 - TUBULAR CONDENSERS .25-600v\$1
- 20 - TUBULAR CONDENSERS .047-600v\$1
- 15 - H.V. CONDENSERS .018-1600v\$1
- 10 - H.V. CONDENSERS .008 or .003-800v\$1
- 10 - H.V. CONDENSERS .008-3000v or .001-6000v\$1
- 5 - H.V. CONDENSERS .005-6000v\$1
- 3 - I.F. MINIATURE TRANSFORMERS 450Kc.\$1
- 3 - ELECTROLYTIC COND. 80/50 - 450v\$1
- 3 - ELECTROLYTIC COND. 40/10 - 450v\$1
- 3 - ELECTROLYTIC COND. 40/40 - 450v\$1
- 3 - ELECTROLYTIC COND. 50/30 - 150v\$1
- 4 - OVAL LOOP ANTENNAS 1/2, 1, 2, 3 ft. gain types\$1
- 3 - LOOPSTICK ANT. new ferrite, adjustable\$1
- 12 - RADIO OSCILLATOR COILS 450Kc.\$1
- 3 - 1/2 MEG VOLUME CONTROLS with switch\$1
- 1 - BEST 4" PM SPK. 1.47 oh. alnico #5 magnet\$1
- 1 - 5" PM SPEAKER alnico #5 magnet\$1
- 2 - 32.50 SAPPHIRE NEEDLES 4000 playings\$1
- 2 - SELENIUM RECTIFIERS 1-65ma. 1-100ma\$1
- 2 - DIODE CRYSTALS 2-IN23, 2-IN23, 1-IN64\$1
- 1 - \$4 INDOOR TV ANTENNA bi-gain 3 elec.\$1
- 50 - 100 OHM 1/2 WATT RESISTORS 5%\$1
- 75 - 680 OHM 1/2 WATT RESISTORS 10%\$1
- 75 - 470K OHM 1/2 WATT RESISTORS 10%\$1
- 50 - 3.3 OHM 1 WATT RESISTORS 10%\$1
- 50 - 3900 OHM 1 WATT RESISTORS 10%\$1
- 50 - 15K OHM 1 WATT RESISTORS 10%\$1
- 50 - 27K OHM 1 WATT RESISTORS 10%\$1
- 50 - 120K OHM 1 WATT RESISTORS 10%\$1
- 50 - 150K OHM 1 WATT RESISTORS 5%\$1
- 50 - 470K OHM 1 WATT RESISTORS 10%\$1
- 50 - 2.2 MEG OHM 1 WATT RESIST. 10%\$1
- 25 - 2.2 OHM 2 WATT RESISTORS 5%\$1
- 25 - 3.3 OHM 2 WATT RESISTORS 5%\$1
- 25 - 270 OHM 2 WATT RESISTORS 10%\$1
- 25 - 470 OHM 2 WATT RESISTORS 10%\$1
- 25 - 100K OHM 2 WATT RESISTORS 10%\$1
- 3 - AUDIO OUTPUT TRANSFORMERS 50L4 type\$1
- 3 - AUDIO OUTPUT TRANS. 6X6 or 6V6 type\$1
- 1 - SET TV KNOBS standard type, incl. escutcheon\$1
- 1 - 53 CRT BOOSTER new life to old tubes\$1
- 1 - LB SPOOL ROSIN CORE SOLDER 40/60\$1
- 6 - SPIN TIGHT SOCKET SET 3/16" to 7/16"\$1
- 3 - TV ALIGNMENT TOOLS 7", 12", 18"\$1
- 1 - WIRE STRIPPER AND CUTTER.\$1

FEBRUARY SPECIALS

- 1 - 10" CARBONEAU PM SPKR. 8 oh. mag \$ 1.78
- 1 - 6x7 OVAL SPKR. 1.47 mag 2.49
- 1 - 12" PM SPEAKER Alnico #5 Mag 3.95
- 1 - SONORA AC-DC RADIO 10.95

3 TUBE PHONO-AMPLIFIER

complete with 35Z5-125Q7-90L8 ready to plug-in.\$4.94

TV CONVERSION KIT

Matched 70" Def. Yoke and Flyback Transformer with Instruction Manual to Convert any Small TV to 21" Picture.\$9.78

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted, enclose with money order or check. No letter needed, envelope address is sufficient. You will receive a new copy of this ad for re-orders. ON SMALL ORDERS—Please include stamps for postage, excess will be refunded. Larger orders will be shipped express collect.

Send for Free Catalog of Amazing Bargains

CAPITAL ELECTRONICS

218 FULTON ST., N. Y. 7, N. Y. CO-7-7842

tors and stators are gang milled from shaped extruded aluminum rods. This method of manufacture allows close mechanical tolerances to be held and makes a sturdy structure with high mechanical stability.


At the present time, three sizes are available with 70, 130, and 250 μ fd. maximum capacitance. Write the manufacturer direct for full specifications on these air capacitors.

"KNIGHT" SWEEP GENERATOR

Allied Radio Corporation, 100 N. Western Ave., Chicago 80, Ill. has begun marketing a new r.f. sweep generator kit under its "Knight" label.

Designated as the 83-YX-123, the new unit can be used wherever coils or circuits must be adjusted for resonance and proper bandpass. It can be used on the production line, for repair work, incoming inspection, quality control, etc.

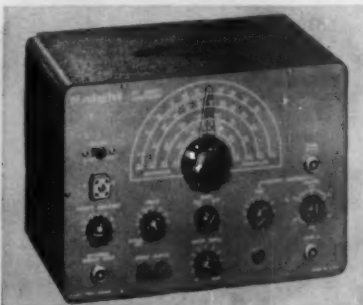The circuit incorporates an exclusive electro-mechanical wobblator system designed to provide good sweep linearity. Frequency range is 300 kc. to 250 mc. on four fundamental ranges and sweep is fully variable from 0 to 13



mc. on any frequency within this range. A built-in crystal-controlled marker, accommodating any two crystals, is included in the kit.

The kit comes complete with tubes, punched chassis, all parts, wire, solder, "step-and-check" instructions and giant-size pictorial diagrams.

FILTERS FOR SSB

The RCA Electronic Products Division, Camden, N. J. has developed a small, 7 ounce electro-mechanical filter which is designed to reduce requirements for electron tubes and components in radio communications systems, especially SSB.

The new bandpass devices are designed to provide the extreme selectivity required for SSB and include a 250 kc. upper sideband type (MFU-250-1) and a 250 kc. lower sideband unit (MFL-250-1).

The filters, which measure a mere 1 1/2" x 1 1/4" x 3 3/4", will operate over a temperature range of -40 to +85 degrees C.

PRECISE "POWER-LAB"

Precise Development Corporation of Oceanside, Long Island, N. Y., has developed a new item of service test equipment, the "Power-Lab."

The new instrument is a combination

battery eliminator and d.c.-a.c. high-power supply that is said to do the work of at least eleven pieces of equipment. Among its functions are that of




a battery eliminator, battery charger, high-current variable line voltage supply, a.c. line voltage meter, a.c. line ammeter, a.c. line wattmeter, a.c. line isolation transformer, low-voltage high-current a.c. supply, d.c. line variable voltage supply, d.c. high-current ammeter, and a.c. bias box.

The unit is available in two models, each of which is offered in kit or factory-wired form. Write the company for complete specifications.

HICKOK AM GENERATOR

The Hickok Electrical Instrument Company, 10524 Dupont Ave., Cleveland 8, Ohio has released a new high-speed, low-cost AM generator which has been especially designed for radio service work.

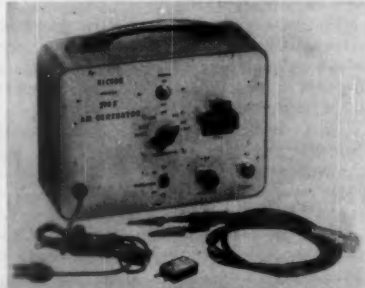The Model 290X provides an accurate and stable source of r.f. power for alignment of AM broadcast receivers. Five calibrated frequencies (262, 455, 465, 600, and 1400 kc.) are available by means of a selector switch on the front panel and r.f. output is modulated or unmodulated. The r.f. output is variable from 2 microvolts to 200 microvolts and audio output is 400 cps. If



desired, crystal accuracy may be obtained through the addition of a crystal in the holder provided.

Literature on the Model 290X is available on request.

REPLACEMENT CAPACITORS

Sprague Products Company, North Adams, Mass., has recently introduced a new capacitor kit in which just four of its new "Universal" ceramics will take the place of forty-two conventional ceramics rated from 400 μ fd. to .15 μ fd.

Although the new "Universal" line is available in individually packaged

bigger BETTER BARGAINS at VIDEO



EICO TUBE TESTER

Model 625K

- Illuminated gear-driven "Speed Rollchart"
- New lever-action switches for individual testing of every element
- Tests all conventional and TV tubes

\$49.95 wired

Kit, **34⁹⁵**



NEW INDOOR ANTENNA

Both UHF and VHF. Brings better reception than most outdoor antennas. Use on top of TV. List price \$9.95.

YOUR PRICE

\$3.99 each

3²⁹

Lots of 3



Brand New PICTURE TUBES

- RCA Licensed
- One Year Unconditional Guarantee

Type	Price	Type	Price
108P4	\$11.90	178P4	\$20.63
121P4	\$14.38	19AP4	\$24.81
148P4	\$16.86	21AP4	\$28.79
168P4	\$19.38	21EP4	\$28.79
176P4	\$19.38	24AP4	\$42.50

Picture tubes shipped F.O.B. Harrison, N.J. Above types are most popular. However, you may order any equivalent size at the same price!



TV TUBE BRIGHT- ENER

Fits all makes of picture tubes, AC parallel circuits. Completely automatic. Easy to install.

99c each, single

89¢
Lots of 3 each

FREE POSTAGE in U.S.A. and Territories on orders over \$5.00. 25c handling charge on orders under \$5.00. 25% deposit required on C.O.D.'s. Please send approximate postage or freight on Canadian and foreign orders. Subject to prior sale.

ELECTRIC COMPANY

79 CLINTON PL.

NEWARK, N. J.

Phone HUmboldt 4-9848

Abraham Markus, co-author of famous best-seller
"Elements of Radio" makes amazing offer!



TRY MY TV and RADIO REPAIR COURSE FREE FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."



Here it is! The most amazing guarantee offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-copy best-seller. Second, because these books get right to the point—tell you what to do in 1-2-3 fashion. For example, once you master the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls.

DON'T WAIT! You risk nothing when you send the coupon below. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.

WHAT YOU GET IN THESE 3 GIANT VOLUMES

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete, step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned-radio-frequency tuner—AC-DC superheterodyne receiver—etc.

RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair, replacement, and readjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers; shortwave, portable, automobile receivers, etc. Explains how to use testing instruments such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.

MAIL THIS COUPON

Prentice-Hall, Inc., Dept. 5741-B1

Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$5.60. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. Or I will keep the course and send you two more payments of \$5.60 a month for two months.

Name

Address

City..... Zone..... State.....

SAVE 1/2 — PAY PART-BY-PART — HAVE FUN
Assembling the Schober

ELECTRONIC ORGAN in KIT form



**NO SPECIAL
SKILLS
NEEDED**

Now you can afford a real, full concert organ, just like those made by the foremost organ manufacturers. Because over 1/2 the cost is saved when you assemble it yourself. And it's REALLY EASY: only 24 separate units, all with printed circuits, and detailed-to-the-smallest-step instructions. In addition, you purchase each of the 24 kits when you are ready for it — and can afford it.

You'll get a real kick out of putting the "Schober Electronic Organ" together — and then sitting down and pulling out the stops for Strings, Trumpets, Clarinets, Diapasons, Flutes, etc.

Compact CONSOLE

One of the many exclusive features of this exceptional offer is the handsome console, made by hand in Old World Craftsman manner. It is equally at home in a traditional or modern setting, and takes little more space than a spinet piano.

Free Literature

Complete descriptive booklet and price list are available on request. And, if you wish to hear the glorious pipe organ tone of the Schober Electronic Organ, a 10" long playing recording by Dr. C. A. J. Parmentier, renowned organist, is available for \$2. This is refundable when you order. Write today and see what a fine instrument you can get at such a great saving.

The SCHOBBER ORGAN CORPORATION


2248-A Broadway, New York 24, N. Y.

* Designed by Richard H. Dorf.

a TERRIFIC BARGAIN in a

SOLA CONSTANT-VOLTAGE TRANSFORMER
Ends fluctuating line voltage!

OVER 60% OFF...

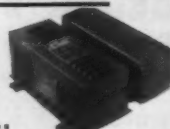

the factory price at a 1-input 2,000 VA unit! And here's another bonus! This Air Forces 2,000 VA overstock, Sola Cat. No. 30788, has 4 inputs! 90-125 V., 190-250 V., 50 cy. or 60 cy. Isolated secondary is constant 115.0 V. $\pm 1\%$ from no-load to full-load of 17.4 amp. So, if you choose, use it as a 220-115 V. step-down. And slash \$167.50 off the factory 3-input price!

Brand new in original wood box. 4
cu. ft. Ship. wt. 254 lbs. F.O.B. **\$97.50**
Pasco, Wash. Only.....

THE M. R. COMPANY
P. O. Box 1220-A Beverly Hills, Calif.

CONVERT TO COLOR TV

COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any-size black-and-white TV, direct view or projection, to receive compatible color TV. **COLORDAPTOR** is simply attached to TV set, does not affect normal operation and can be built from parts experimenters have on hand.

Complete specifications including theory of operation, complete simplified construction plans, schematic and sample color filters..... **\$1.95**


Essential parts kit containing all special parts—coils, delay line, crystal, color filters—

Up to 16" sets— **\$19.95** 17" and larger— **\$20.95**

All other **COLORDAPTOR** parts, kits, motors, etc. available. Write for information and prices.

COLORDAPTOR, 3471 Remona, Palo Alto, Calif.

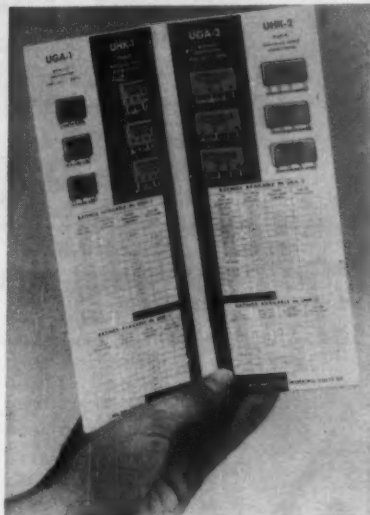form, the kit provides a good opportunity for the technician to become acquainted with the many uses to which the new capacitors can be put. Tables packed with the capacitors and



printed on the kit tell which unit to use for the desired capacitance, which of the four leads to use as terminals, which leads to solder together or clip off. No arithmetic is involved.

Kits and additional details are available from the company's distributors.

EXPANDED-SCALE VOLTMETERS

Phaotron Instrument and Electronic Co., 151 Pasadena Ave., South Pasadena, Cal. is now in production on a new line of expanded-scale voltmeters. The units can be supplied in either a.c. or d.c. models. They are available in a wide variety of ranges and case styles to meet production requirements.

Write the Products Development Department of the company for a data sheet and additional details on this new line.

RIGHT-ANGLE TUBE SOCKETS

A new alkyl-base tube socket that mounts tubes horizontally to reduce space requirements has been designed especially for use with printed circuits. Marketed by **Aerovox Corporation**, 2724



S. Peck Road, Monrovia, Cal., the new sockets permit greater miniaturization and more compact packaging and allows tubes to be placed closer to heat sinks.

Contacts are silver-plated beryllium copper while the mounting bracket, support, and shield are tin-plated steel. Write the manufacturer for full details and specifications on this new tube socket line.

DRIFT TRANSISTORS


The Semiconductor Division of **Radio Corporation of America**, Harrison, N. J. has announced the commercial availability of two new drift transistors for high-frequency applications.

The **RCA-2N247** and **RCA-2N267**, of the germanium *p-n-p* type, are intended for use as r.f. amplifiers in military and commercial equipment and in entertainment type receivers operating at frequencies covering the AM broadcast band and up into the short-wave bands. They are also useful as i.f. amplifiers or as mixer-oscillators.

TV-FM SWEEP GENERATOR

Eico, 84 Withers St., Brooklyn 11, New York is now offering a new TV-FM sweep generator which is designed to speed and improve the alignment of FM, monochrome, and color television receivers.

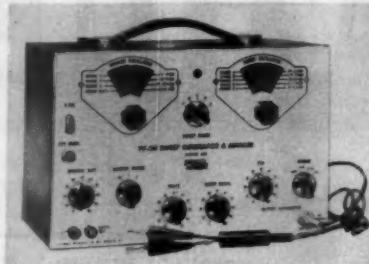The entirely electronic sweep circuit, with accurately biased Incredutor, provides good linearity on both



sides of the center frequency. The newly designed a.g.c. circuit automatically adjusts the oscillator for maximum output on each band with minimum amplitude variations. The resonance-free r.f. choke eliminates "suck-out" points anywhere in the r.f. spectrum.

The sweep generator range is 3-216 mc. in five overlapping fundamental bands with the sweep continuously variable from 0-3 mc. lowest maximum deviation to 0-30 mc. highest maximum deviation. The variable marker generator range is from 2-75 mc. in three fundamental bands plus a calibrated harmonic band.

The Model 368 is being offered in both kit and factory-wired form. Write the manufacturer for full details.


VIDEO GENERATOR

American Scientific Development Company, 336 South Main, Ft. Atkinson, Wis., is marketing a low-priced, test pattern and picture generator, the Model TV-10.

Generating a 525-line, fully-interlaced picture or test pattern with a usable frequency response of over 4.5 mc., the TV-10 contains a multiplier-type phototube and high voltage power supply, video amplifier and high-fre-

quency compensator, and a modulator operating on the standard low-band TV channels.

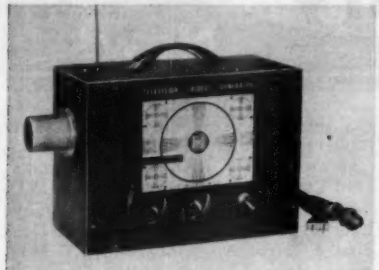This unit is actually the "second half" of a flying-spot TV system. The other half can be any inexpensive, sec-



ond hand 10" or 12" TV receiver. This economical "sweep section" provides the fully interlaced 525 line picture. This interlace is available only with systems using a complete TV set as a raster generator which can be interlaced by a signal from a local TV broadcasting station.

The manufacturer will supply additional details and a data sheet on the television video generator upon written request.

PRINTED CIRCUIT MODULE

Arthur Ansley Manufacturing Co., New Hope, Pa., is now offering a line of new plug-in modular units which are compact, rugged, flexible, and easily interchangeable.

Known as the "Plus Module," the standard size is approximately 1 1/2" square and 2 1/2" high, either with an octal plug-in base which makes the unit directly interchangeable with many hand-wired modules or with a new type of plug known as the "Plus" base that provides up to 32 contacts. A 7- or 9-pin tube socket is incorporated in the top of the unit or it can be adapted to transistors or subminiature



tubes. Other sizes and shapes can be supplied, supporting two or more tubes.

The manufacturer offers engineering assistance in solving special circuit problems. Firms are invited to write for additional information on the printed circuit module.

MEASUREMENTS CORP.

SIGNAL GEN. MODEL 70B

Gov't. Avg. Cost \$300.00
Used for alignment of radio I.F. freq. stages of radio receivers and other test operations requiring a C.W. or modulated R.F. voltages. 15 to 25 Mc and 195 to 225 Mc will actually cover 125 Mc to 245 Mc signal may be unmodulated or modulated at approx. 30% by an audio frequency of 400 or 8200 CPZ.

Brand New..... \$395.00
Used Exc..... \$29.50

COMMAND ARC-5 TRANSMITTER

T-20... 4 to 5.3 MC New \$595

T-21... 5.3 to 7 MC

Used..... \$3.95

New..... \$13.95

Used..... \$9.95

3 to 4 mc. like new..... \$5.95

RECEIVERS

190-530 KC

1.5-3.0 MC

Excellent

Used

\$9.95

7.95

RCA MOBILE RECEIVER

30-41 mc. AM Crystal Controlled. \$14.95

each.

DYNAMOTOR FOR ABOVE

6V DC Input-250 V DC Output. \$6.95 each.

RCA MOBILE TRANSMITTER

30-41 mc. AM Crystal Controlled. \$14.95

each.

DYNAMOTOR FOR ABOVE

6V DC Input-375 Volts 250 ma Output. \$9.95 each.

ALL 4 ABOVE USED UNITS \$39.50

FM WOBULATOR CAPACITOR

Frequency modulation unit with a permanent magnetic field and a moving coil mechanism driving a metal diaphragm supported at the rim. This diaphragm sets as a moving plate of the frequency modulator capacitor. W/instructions. Build TV sweep \$2.75

size gear BRAND NEW..... \$4.95

2 for only..... \$4.95

Sweet Oscilloscope Deals

INDICATOR UNIT. For conversion to test scope, pandapter, analyzer, etc. Double deck chassis. 5CP1 mounted in tube shield. Less small tubes and crystal, but complete with 5CP1. \$9.95

Exc. Cond..... each

ASB-7 Radar Indicator Unit: For conversion to test scope or for use as modulation monitor. Has standard test-scope CR tube, H Cent, V Cent, Brill, Foc, Gain, and range selection switch. External power source was used. Tubes: \$9.95

4-6AC7, 3-6H6, Less 1-6BP1. New.....

BC929 RADAR, \$9.95

BC-929 A Radar Indicator Scope. This unit could be rebuilt into a fine test scope. It is an ideal also. 8x3x14 priced with tubes 2-6SN7, 2-6H6, 6G5, 6X5 and 2X2. This is a red hot buy. Scope Price, New..... \$9.95

LORAN APN-4

FINE QUALITY NAVIGATIONAL

EQUIPMENT

Determine exact geographic position of your boat or plane! Complete. BRAND NEW installation consists of: 1D-6B/APN-4 Indicator; R-9B/APN-4 Receiver; PE-206 Inverter; Set of Plugs; Visor for Indicator; Operation manual; \$129.50

Brand New, Export package.....

104B INDICATOR, R9B RECEIVER, \$69.50

Excellent.....

UHF TRANSCIVER, APG-5

2500 Mc complete with 2C43, 2C40, 3E29, 1B27, VR105, 5Y3, 6AL5, 2 each \$39.50

2X2 and 8 each 6AK5.....

PE109 INVERTER

12VDC Input, 115 VAC, 1 1/2 amp, single phase, 400 cycle output. \$34.50

Brand New.....

Exc. used..... \$27.50

WRITE FOR NEW BULLETIN

ALL ITEMS F.O.B. CHICAGO 25% Deposit required with orders

R W ELECTRONICS

Dept. N 2430 S. Michigan Ave. Chicago 16, Ill.
PHONE: CAIumet 5-1281-2-3

BEWARE OF IMITATIONS

There is Only One Original Dependable NO-NOISE

Volume Control and Contact Restorer with Perma-Film

2 oz. bottle. Net to servicemen. 1.00

Cleans, lubricates, protects... not a carbon-tet solution. Still available in the new 6 oz. spray can. Net to servicemen—\$2.25

"NO NOISE"

Also available in 8 oz. bottles and quart cans. At your nearest distributor.

TUNER-TONIC with PERMA-FILM

Cleans, lubricates, restores all tuners including water type. Won't change or affect capacitance, inductance or resistance. Won't harm insulations or precious metals, nor attack plastics. For television, radio and FM. Eliminates all noise, oxidation and dirt indefinitely. Non-toxic. Net to servicemen. \$3.25

ELECTRONIC CHEMICAL CORP.

813 Communipaw Avenue

Jersey City 4, N. J.

\$45.00 HI-FI Headset for only \$7.95

Uses annular grooved plastic fibre cones with voice coils as in speakers, and chamois ear pads to obtain spacing for correct acoustical load. GIVES FINEST MUSIC REPRODUCTIONS! Imp.: 300 Ohms per unit or 600 Ohms when wire series.

USED, EXC. COND..... \$4.95

WITH BRAND NEW CHAMOIS

CUSHIONS..... \$6.19

APG 5 or 15 CAVITY

10 Cm. 2C43 osc Xmitter, 2C40 Loc. Osc. Rec. 1B27 TR; tunes 2400 to 3000 MCS, less tubes.

Price..... \$4.95

Radio Receiver 11-tube UHF tunable 234-258 MC receiver with schematic.

Complete with tubes, 3 ea. of 6AK5, \$6.95

7 ea. of 9001, 1 ea. of 12A6, Like new

Less Tubes..... \$2.95

SCOPE TUBES

2AP1 \$1.95
3BP1
3CP1
3EP1
3HP1
5AP1
5CP1
ea. 4 for \$7.00

DYNAMOTORS

Type Input Output Excellent New

BD-77 12 VDC 1000 VDC 350 MA \$14.95

BD-83 12 VDC 375-150 MA..... 1.95

DM-37 24 VDC 625 VDC 225 MA..... 2.95 9.95

DM-34 12 VDC 220 V 80 MA..... 2.95 4.95

DM-65 12 VDC 440 VDC 400 MA..... 14.95 19.95

DM-14 24 VDC 230 VDC 100 MA..... 4.95

DM-28 24 VDC 230 VDC 100 MA..... 4.95

DM-32A2 12 VDC 250 VDC 60 MA..... 4.95

MOBILE HEAVY DUTY DYNAMOTOR: 14 V. IN-PUT-OUTPUT: 1030 VDC 260 MA, Tapped 516 V.

215 MA, use or 6 V DC INPUT-500 V, 175 MA. While they last—DM-42-Excel. Condition, \$4.95

Brand New..... \$9.95

MG-149F Inverter, 24 VDC input, 115AC, 400 cycles, 500 VA single phase. \$15.95

Exc.....

Used..... \$9.95

RS-38 Navy Carbon Hand Brake.

Exc..... \$2.45 ea.

I-98A Signal Generator 100-156 Mc, complete w/cords and cables, like new \$69.50

Variac General Radio—Model 200 1100-130V, 1 Amp. Brand new..... \$5.95 ea.

MN-26-C—Remote Control Navigational Direction finder and communication receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC. 24V. Self contained dynamotor supply. Complete installation, including receiver, control box, loop, azimuth control, Left-Right Indicator, plugs, loop transmission line and flex. shafts, oper. & main. manual. Ideal for use in boats, etc.

BRAND NEW..... \$39.50

MN-20-E Loop..... 4.95

MN-52-CRANK Drive, New..... 2.50

MN-28-C..... New 4.95


MN-26-C Rcvr., New..... 19.95

MN-40-E Azimuth Indicator, New..... 9.95

DYNAMOTORS for above, 12VDC, MN-26 9.95

METER—3"-0-5 Ma. 270° Indication—By Pass Shunt and add scale. Excellent Condition..... \$1.25

Five for..... \$5.00

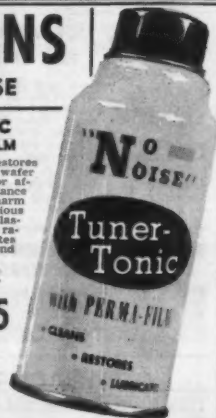

KITS! KITS!

HERSHEL'S KITS ACCLAIMED BEST!


ALL KITS CONTAIN THE FINEST ASSORTMENTS. OVER 10,000 SOLD!

- 30 TUBE SOCKETS
- 2 1/2-lbs. of HARDWARE
- 15 ROTARY SWITCHES
- 10 Electrolytic Condensers
- 40 Radio & TV KNOBS
- 40 BY-PASS Condensers
- 60 CARBON RESISTORS
- 60 MICA CONDENSERS
- 100 SET SCREWS
- 8 1N22 XTAL DIODES
- 50 Ceramic Condensers
- 15 Variable Condensers (Air & Wire)
- 50 RF CHOKE
- 20 POWER RESISTORS
- 1 Phone Motor 115 Vac.
- 50 TERMINAL STRIPS
- 200 ft. HOOK-UP WIRE
- 1 TRANS. 6.3V-110 Vac.
- 5 Meissner Plug-In COILS
- 5 PILOT PANEL LITES
- 50 FUSES 3AG UP
- 1 Motor Rectifier Q-IMA.
- 1 ION. COIL 3V-15,000 VSEC.
- 25-Ft. Phono-Mike Cable
- 3 SELENIUM RECTIFIERS (65 MA. 110V.)
- 1 PHOTO Electric CELL

YOUR CHOICE ANY KIT LISTED IN THIS AD 97c


- 10 STRAIN INSULATORS
- 1 TELEGRAPH KEY
- 5 MICRO SWITCHES
- 75-Ft. 300 OHM TV LEAD-IN
- 25 TV STAND OFFS
- 24 SHOCK MOUNTS
- 1 PHONO XTAL with NEEDLE
- 1 PIX TUBE BRIGHTENER
- 3 CONDENSERS (500 MMFD 20,000 Volts)
- 100 Ft. of SPAGHETTI
- 1 RCA Flyback Trans.
- 10 BATHTUB CONDENSERS
- 10 GRAIN WHEAT LAMPS
- 3 RADIO-PHONO CHASSIS
- 4 LOOP ANTENNAS (RADIO)
- 1 PHANTOM ANTENNA A-42
- 100 SPRINGS (RADIO-PHONO)
- 3 RADIO NOISE FILTERS
- 25-Ft. RG-38/U COAXIAL CABLE with PLUGS
- 2 Powerful ALNICO 3 Magnets

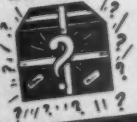All New MYSTERY PACKAGE of ELECTRONIC PARTS



Worth \$40.00
Our Price \$3.95
It's the surprise of your life! 20 pounds of BRAND NEW usable GOVT. surplus. The ideal gift for RANTS, etc.

OIL CONDENSER

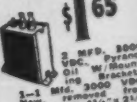

ARC-5 COMMAND TRANSMITTER



TERMS: Cash with order or 25% DOWN—BALANCE C.O.D. ALL PRICES NET F.O.B. DETROIT MINIMUM ORDER \$2.00

HERSHEL RADIO CO.
TYler 8-9400
5249 GRAND RIVER Detroit 8, Michigan

110V. AC POWER SUPPLY FOR 274N RECEIVERS

Just plug it into the rear of your 274-N RECEIVER... any model. Complete kit and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. Only \$8.95.
Filament trans. for 274N receivers. Pri. 110V, 60 cy. AC. Sec. 24V @ .6A. An excellent buy at \$1.95 ea.

SPLINED TUNING KNOB FOR 274N RECEIVERS

An exclusive O-R item manufactured for us. Fits BC-453, BC-454 and other 274N receivers. This is a really hard-to-obtain item. Only .89c ea.

OFFENBACH-REIMUS
1564 Market Street, San Francisco, Calif.

Service Industry

RADIO SERVICE



News

AN IMPORTANT series of association meetings were held in the Hotel Roosevelt in New York City during the first week of December.

The first of these sessions was a conference of delegates representing associations in seven of the northeastern states. The major objective of this luncheon was to discuss a dual 10-point program toward the improvement of Distributor-Service relations with members of the National Electronic Distributors Association. This plan was outlined in an article by William Leonard in the January issue of RADIO & TELEVISION NEWS. Because of some difficulties in making arrangements, the distributors were unable to meet with the association delegates.

The conference, under the chairmanship of Frank Silverman, president of the Television Service Association of Connecticut, officially formed a regional federation of service associations to embrace the New England States, New York, New Jersey, and Pennsylvania. The Federation, which is made up of associations affiliated with one or the other of the national organizations and including non-affiliated local associations, is primarily concerned with the problems of service peculiar to the heavily populated areas on the eastern seaboard. It will operate as a loosely knit, cooperative organization with delegates meeting at regularly scheduled intervals.

Following the regional conference, the first annual Electronics Fair to be sponsored by the Radio Television Guild of Long Island was held at the New York State Agricultural College at Farmingdale, L. I. The Fair, termed an outstanding success by Murray Barlowe, president of the RTG, including a comprehensive program of technical and business lectures presented by nationally known speakers. With attention focused primarily on the operation and servicing of color TV receivers, a wide range of service equipment and replacement products was shown and demonstrated at booths maintained by parts distributors and manufacturers.

The Guild Fair terminated in a panel discussion on captive service held at the Hotel Roosevelt, following a meeting of the Empire State Federation of Electronic Technicians Associations.

Termed by the Guild as a "fact-finding" forum, the purpose of the panel discussion was to develop information which could be presented to the Guild Board of Directors for consideration in recommending a stand for the organization on captive service.

Members of the panel included Mur-

ray Barlowe, president of the RTG, as moderator; John F. Rider, publisher of *Rider's* service manuals and books; Dan Creato, vice-president of the *RCA Service Company*; John Miller, manager of product service for the *General Electric Appliance and TV Division*; Pete Langer, national service manager for *Sylvania Electric Products*; Frank Moch, executive director of *NATESA*; John Wheaton, secretary of *ESFETA*; Sam Marshall, editor of *Service Dealer*; Paul H. Wendel, editor of *Service*; and Sidney C. Silver, service editor of *RADIO & TELEVISION NEWS*.

The panel discussions developed a clear line of demarcation between "captive" service and "factory" service, terms that have been widely confused in the discussions of the two plans used by manufacturers to provide their own service to consumers.

After opening statements by eight members of the panel, written questions directed to them were answered by individual members of the panel. The bulk of the questions were directed to Mr. Miller and to Mr. Creato for detailed information on their companies' policies in providing consumer service.

In his opening statement, Mr. Miller had pointed out that *G-E's* main reason for entering the service field was to "give maximum support to the sale of our sets." He emphasized that it was not the result of poor servicing on the part of the independent service dealers in any of the areas.

Mr. Miller also differentiated between the direct factory service depots, such as his organization has established in Fort Wayne, Indiana, and Toledo and Columbus, Ohio, and the consumer service activities of the *General Electric* appliances and television receivers in the retail trading areas surrounding the 107 U. S. cities with a population of 100,000 or more. Outside of these metropolitan markets, *G-E* recommends that its distributors provide for service through authorized and trained dealers and also independent servicing establishments.

Referring to their distributors' acceptance of these recommendations, Mr. Miller said: "On major appliances (white goods), retail service is presently being provided by our distributors in less than 70 per-cent of the 107 large metropolitan markets."

In his opening statement, Mr. Creato, of the *RCA Service Company*, traced the gradual loss of business to independent service dealers from the time television was introduced postwar in 1946. He pointed out that, during the 1946-47 period the *RCA Serv-*

ice Company handled service on all RCA TV sets. Since then, it has steadily lost ground to independent service dealers to the extent that it now handles consumer service on less than 10 per-cent of RCA sets now in use.

Mr. Creato pointed out that, while his service company was not "happy" about the trend, loss of business to independent service shops has been substantial since 1951. Answering a question relative to the servicing of color TV sets, he said that RCA encourages independent shops to service color receivers.

John Rider urged service dealers to diversify their activities so they do not have to rely entirely on consumer television service for their business. He pointed out that shop owners should take a leaf out of the book of big business by merging with other shops to provide for greater operating efficiency.

Mr. Rider said the independents must adopt the promotional tools that are used effectively by big companies. As an illustration he said that a dozen similar service trucks on the streets of a city from a single organization look like a much bigger service operation than several hundred trucks operated by independents, but with different company names on each. He urged service dealers to adopt a common identifying name that could be advertised nationally to make the public aware of the great industry of independent service businesses.

Frank Moch, executive director of NATESA, outlined the difference between "captive service" and "factory service." He said, "Captive service is a scheme foisted upon the public whereby they are led to believe they are getting something for nothing, and thus they are deprived of getting better service, quicker, more personal, and more economically."

Bert Bregenzler, chairman of the FRSA, said that television technicians do not fear a clean fight for business in competing with captive service. He said that certain types of ads which have appeared in newspaper and magazine advertising have tended to "degrade the independent serviceman."

The NEW YEATS "Shorty" STATION WAGON & PANEL PICK-UP appliance dolly



YEATS Model No. 5

Aluminum alloy
Height 47"
Weight 32 lbs.

Only 47" tall, this new YEATS dolly is designed for TV and appliance men who make deliveries by station wagon or panel truck. No need to detach appliance for loading into the "wagon" or pick-up... the YEATS "Shorty" will slide into your vehicle with ease. Has aluminum alloy frame with padded felt front, quick fastening (30 second) strap ratchet, and endless, rubber belt step glide. New YEATS folding platform attachment, at left, saves back-breaking work handling TV chassis or table models. Call your YEATS dealer today!



Folding platform is 13 1/2" x 24 1/2" —attaches instantly. (Platform only) \$9.95.

"Everlast" COVERS & PADS

YEATS semi-fitted covers are made of tough water repellent fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes—Write,



Furniture Pad

SEND postcard for full information on our complete line TODAY!



TV Cover

YEATS appliance dolly

2101 N. 12th St.

sales co.
Milwaukee, Wis.

February, 1957

Mullard AUDIO TUBES DESIGNED FOR HIGH FIDELITY

Many years of research and development have been spent in producing a range of

Audio Tubes to meet the requirements of High Fidelity sound

reproduction in all respects. This is why MULLARD Audio Tubes are accepted in Great Britain as a standard by which others are judged, and why leading High Fidelity manufacturers in the United States also use MULLARD tubes in their equipment.



EL-34—Recognized as the finest high power output pentode, up to 100 watts in push-pull. Exceptionally linear, requires low input voltage.



EL-44—9-pin miniature AF power pentode, combining high gain and linearity. Up to 18 watts in push-pull.



EL-37—Specialized manufacture of Mullard High Fidelity tubes, particularly the EL-37 assures longer life and increased balanced power output. Equivalent to 6L6, 5881, KT66.



***ECC83/12AX7**

***ECC82/12AU7**

***ECC81/12AT7**

Mullard quality double triodes with low hum, noise and microphonics.



***EF-86**—High gain pentode with low hum, noise, and microphonics. Especially designed for input stages of tape recorders and pre-amplifiers. Equivalent to the 2729 and the 5879.



***6Z34**—Indirectly heated full-wave rectifier with 5v, 1.9 amp heater, 250 ma output. Equivalent to 5U4G/6A without circuit changes with the advantage of lower tube voltage drop due to unipotential cathode.

*Maximum levels specified and guaranteed

MULLARD TUBES are available at leading audio distributors throughout the United States. For detailed technical data and application information, write to:

INTERNATIONAL ELECTRONICS CORP.

81 Spring Street, New York 12, N. Y.

TRADE MARK MULLARD, LTD., LONDON



MULLARD TUBES DEVELOPED FOR HIGH FIDELITY

STAN-BURN

CATHODE RAY TUBE SPECIALS

ONE YEAR GUARANTEE			
G.E.	Type	STAN-BURN	G.E.
\$15.00	10BP4	\$30.00	17CP4
19.10	12LP4A	13.95	17GP4
12.00	12BP4	18.50	17LP4
18.75	12UP4	15.00	19AP4A
28.75	14CP4	13.75	28.35
15.00	15DP4	14.50	20CP4B
33.75	16AP4	18.75	21AP4
32.20	16DP4A	15.25	21EP4A
23.50	16KP4	15.75	21EP4B
27.20	16KP4A	10.75	21FP4
33.75	16UP4	18.75	21MP4
31.50	16LP4A	15.25	21VP4
31.50	16WP4	15.25	100.00
23.50	17BP4	15.75	24CP4A
27.50	17BP4B	18.75	24DP4A

Aluminized—INQUIRE FOR ANY TUBE TYPE NOT LISTED
STAN-BURN CRT TUBES RCA LICENSED—MFD. BY LINCOLN
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

530 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: Permalloy anodes, coils, speaker, transformers, resistors, condensers, etc. ONLY \$1.95 (plus shipping postage).

TAPE RECORDERS—Famous Brand
List Pr. \$249.95, \$169.00 List Pr. \$129.95, \$79.95
List Pr. 109.95, 129.00 List Pr. 79.95, 59.95
Write for complete details.

RECORDING TAPE—TOP QUALITY
Plastic based, 200 Feet on 3" Reel—Free. Response: 50-15,000 cps. Red oxide base. Lots of 12, ea. \$3.49
Same—500 Feet on 5" Reel. Lots of 12, ea. .99

KITS! We stock the following manufacturers complete line of kits—see Index
RICO • QUALITY • ARKAY • PRECISE • KARLSON
JENSEN • CABINET • ELECTRO-VOICE • DYNA.

All domestic orders will be shipped prepaid for a limited time. Please allow your order by Manufacturer and Model Number of item.

VM 4 SPEED HI-FI CHANGER—Model 1210 with Ronette, Sonotone or Astatic flip-over cartridge. \$22.95
RC 450 4-speed Collaro, BRAND-NEW, Special. \$35.81
45 RPM SPINDLE for above. 2.95

4 SPEED PORTABLE RECORD PLAYER with MONARCH CHANGER—Ronette cartridge—Two Tone Case. \$33.95
VM 4 SPEED portable changer ampl. with 2 tube amplifier. \$39.95

WESTER 4-speed "Magic Mind" automatic Ronette, Sonotone or Astatic flip-over cartridge. \$24.95
MONARCH Model UAGU 4 SPEED AUTO. INTERMIX CHANGER with crystal cartridge. \$22.95

Same with GOLD RING 500 S.S. 25.95
Same with G.E. RFX050A. 25.95
Same with G.E. RFX050A-B. 25.95

45 RPM SPINDLE. 1.95
TV-8 MONARCH 3 Speed MOTOR with TUBE TABLE UNIT (less arm) NEW LOW PRICE. 3.95
SONORA—4 TUBE SUPER HET-AC/DC-EBONY \$11.50
Above in RED, WHITE, MAHOG. 12.50

RCA-21 "ADAM" TABLE MODEL TV. \$159.95
AUTO ANTENNAS AND SPEAKERS
UNIVERSAL 3 sec.-40 sec. load. ea. \$2.25
Lots of 10 ea. 2.00

UNIVERSAL 2 sec.-84" load. ea. 1.75
Lots of 10 ea. 1.50
REAR SEAT SPEAKER KITS complete with grille, wiring switch, matching speakers. 8 x 6. \$8.00
8 x 7. 4.50

PACKAGED KITS ANY PACKAGE ONLY..... 98c

25 RADIO KNOBS	5 ROLLS (25 ft. ea.)
50 TERMINAL STRIPS	500 YD. WIRE
30 TUBE SOCKETS	1 PLASTIC BOX
1 LB. HARDWARE	25 ASST'D SPRINGS
100 SET SCREWS	25 BATTERY PLUGS & SOCKETS
10 VOLUME CONTROLS	12 WIRE WOUND RE-ISTORS
25 FT. SHIELDED WIRE	30 ASSORTED TRIMMERS
25 CHOKES & COILS	80 TV & IF TUNER SLUGS
25 MICA CAPACITORS	15 ROTARY SWITCHES
40 TUBULAR CAPACITORS	50 CERAMIC CAPACITORS
100 INS. RESISTORS (STANDARD)	20 METER TYPE RESIST. W/ WOUND
100 INS. RESISTORS (Deluxe)	
100 KNOB SPRINGS	

SPEAKERS—ALNICO V

SIZE	Lot of 10 (ea.)	Each
4"	99c	\$1.08
5"	\$1.09	1.19
6" x 7"	1.88	2.00
6"	1.80	1.98
6" x 9"	1.98	2.18
8"	2.75	2.95
12"	3.75	3.98

DEALERS: Write for low cost prices and complete catalogs on 58 models—MALL-CARTERS, SUPERIOR, NATIONAL, PRECISION, HICKOK, TUNING, G.E., WESTINGHOUSE, TUNG-SOL, MAJESTIC, GRUNDIG, ARKAY KITS, DELCO, GEN. MOTORS, BOOMER ELECTRO-VOICES, HARMON-KARDON, GARRARD, KARLSON, UNIVERSITY, N. H. SCOTT. Address all inquiries to Dept. 100, STAN-BURN.

COMPLETE HIGH FIDELITY DEPARTMENT. SEND US YOUR LIST FOR LOWEST QUOTATIONS ON ANY ITEM. We invite expert inquiries and orders. Our expert department will give special attention to expediting foreign orders, minimum quantities, and complete electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations. authorized distributors for United Motors, all Delco and Gen. Motors Auto Radio parts in stock. We also carry a complete line of superior makes of Radio Tubes at 50/10 discount. Also many other special purpose and transmitting tubes, and all electronic 200c. with order. Balance C.O.D. All electronic P.O.B., NEW YORK Warehouse. Minimum order \$9.99. Write for our latest price list and Hi-Fi Catalog No. 2. ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

STAN-BURN RADIO and ELECTRONICS CO.
558 CONEY ISLAND AVE • B'KLYN 18, N. Y.

Service Diversification (Continued from page 60)

erating from a central location in the city.

The partners in the new Consolidated Services, Inc., are Forrest L. Baker, A. R. "Al" Niehaus, Paul W. Carter, W. L. Lehmborg, and H. M. Willman. Each of these men has operated his own independent TV service business for many years.

The partners all stress the fact that no one of them could afford or even obtain the supervisory ability and experience necessary to operate a business of the caliber of Consolidated. Neither was it economically advisable to develop a warehouse stock of parts sufficient to supply an operation of this magnitude. The same thing applied to testing and other technical equipment. After months of planning, they developed a physical plant that is a service technician's dream and accomplished a division of supervisory responsibilities that utilizes the maximum capabilities of each of the partners.

The managerial responsibility is divided roughly among Baker, vice-president of the corporation, in the capacity of business manager, Niehaus, secretary-treasurer of the firm, and Carter, dividing the duties of shop superintendent so that each heads an eight-hour shift in the 16-hour working day observed by the firm. Outside service, with four radio-dispatched mobile units, each fully equipped to do shop repair work, is also divided into eight-hour shifts with Lehmborg and Willman supervising.

The combined organization provides many operational advantages. The departmentalization of the organization enabled the partners to add a number of related electronic service activities and to handle factory warranty contract service for Vornado room air conditioners. By March, they will also be ready to assume the installation and maintenance work on Vornado's new automobile air conditioner. For the present, at least, Consolidated will confine its activities to radio and television with the exception of the Vornado contract service and hi-fi record player service.

From the standpoint of providing the top skills and employing the most advanced techniques, the consolidation is expected to have a remarkable effect. Although all five members of the firm do active supervisory work and turn out a sizable amount of personal servicing, they now have more freedom for attending factory schools and taking other advanced training. With the increase in personnel and the stepped-up individual efficiency, they plan to have key men in regular attendance in trade and factory schools and to foster a perpetual on-the-job training program for their experienced personnel.

A

.... Always

B

.... Buy

C

.... Columbia

TCS REMOTE CONTROL BOX

Contains many parts plus JENSEN SPEAKER with a mammoth slug. This speaker makes terrific 25-30 Watt tweeter for hi-fi. It alone is worth \$10.00. Complete unit, new.....

\$7.95

MBF TRANSCEIVER

Late model, ideal 6 and 10 meter set-up. 115 VAC and DC. Good condition.....

\$22.95

2 Meter 19" Whip Antenna

Like you see on police cars. With cord and base. Brand new, boxed. Only.....

\$2.95

ARB RECEIVER

190-9050 Kc. 4-band continuous tuning. Excellent condition.....

\$19.95

YOUR OWN CRYSTAL BANK!

Assorted FT-241 & FT-243. Brand new U.S. Gov't surplus. Good, useful, popular frequencies. Special.....

\$9.95

COMMAND GEAR—EXCELLENT COND.

RC-453 RECVR. 10-55 MC Q 5'er..... \$12.95
RC-454 RECVR. 3-6 MC. 50 meters. ONLY..... 4.95
RC-455 RECVR. 9-9.1 MC. 40 meters..... 4.95
RC-457 XMTTR. 4-5.3 MC. Special..... 2.95
RC-458 XMTTR. 5-5.7 MC. It's a steal..... 2.95
4-5.3 MC. XMTTR. Brand new, boxed. Only..... 4.95
5-5.7 MC. XMTTR. Spanking new! Boxed..... 4.95
RC-456 MODULATOR. Excellent cond..... 4.95
RC-442 ANTENNA SWITCHING RELAY: with vacuum capacitor. New, low price mount..... 3.49
TRIPLE RECEIVER RACK. With shock mount..... 2.95
DOUBLE XMTTR. RACK. With shock mount..... 2.95
ALL PLUGS: For RC-3743N or ARC-5. Ea. 1625 TUBES: For spares. New, boxed, Ea..... 1.00
TRIPLE RECEIVER CONTROL BOX..... .25
RC-450..... .95
TRANSMITTER CONTROL BOX. Only..... .95
18 FT. FLEX CABLE TACH SHAFTS. To control receiver remotely. Special..... 1.95

All orders FOB Los Angeles. 25% deposit required. All items subject to prior sale. MINIMUM ORDER \$3.00.
OPEN FRIDAY NITE TILL 10 P.M.

Columbia ELECTRONICS
2251 W. WASHINGTON BLVD.
LOS ANGELES 18, CALIFORNIA

DUOTONE IN ESQUIRE MAGAZINE GET YOURS FREE

Get your free DFF* Kit and start cashing in. *Duotone Fidelity Focus

Write: DUOTONE CO., INC. KEYPORT, N. J.

TV-ELECTRONICS

WTI GRADUATES IN BIG DEMAND

Take your pick and hold a key top paying job in Television, FM and AM Radio, Broadcasting, Radar, Automation, Computers, Missiles, etc. Over 35 job classifications open to WTI graduates. FCC license coaching included.

Complete, Modern Resident Facilities

You work with the latest laboratory equipment in Los Angeles. Non-essential math and engineering theory omitted. Approved for veterans. Free Placement Service. Complete information in our FREE Booklet. Write Dept. R-257.

WESTERN TELEVISION INSTITUTE

341 W. 18th Street Los Angeles, Calif.

Mac's Service Shop

(Continued from page 76)

"Laying off the kidding," Barney said, "I think I see what you're driving at. You're saying it behooves a technician to be alert to the little dangers in his work as well as the big ones."

"That's it exactly," Mac applauded. "You don't need to tell a fellow clinging to the side of a TV tower to be careful; neither do you have to warn him about the dangers of implosion when he's handling picture tubes—at least not if he has deliberately broken a couple of burned out ones under controlled conditions just to see what happens. Most of us are pretty alert to the danger of being electrocuted by the sets we work on or the equipment we use. If we are not completely stupid, we guard ourselves against these serious, ever-present dangers; but where most of us fall down is in getting careless about the apparently little threats to our well-being such as we have been discussing. We just don't seem to realize that lockjaw developing from an infected burn can kill us just as dead as a fall from the top of a seventy-foot TV tower."

"The independent service technician has to think of such things more than people do who work in radio factories, and so on," Barney mused. "In a factory, there would be safety engineers constantly studying each job for hidden dangers and warning the worker against them. He would have to attend safety meetings, and safety slogans would be plastered all over the place. The independent in service, on the other hand, has to look out for himself and be his own safety engineer. That makes it a little tough since many of these independent technicians are already their own several-other-things. For example, many are their own office force, their own janitor, their own purchasing agent, their own advertising manager, and their own public relations department."

"Very true," Mac commented with a grin; "but just don't forget that they also have their own businesses." —50—

PHOTO CREDITS

Page	Credit
37, 38, 39, 61.....	Raytheon Mfg. Co.
46, 47.....	Alecric Mfg. Co.
49, 54, 78.....	Sylvania Electric Products Inc.
56.....	Simpson Electric Co.
67.....	Inland Broadcast Co.
70.....	IBM
71 (top).....	Burroughs
71 (bottom).....	Underwood
94.....	Jerrold Electronics Corp.
100.....	Sperry Gyroscope
110, 111.....	CBS
116.....	Northrop Aircraft, Inc.
124.....	Minneapolis-Honeywell Regulator Co.
150, 151.....	U. S. Recording Company

SAMS BOOKS keep you ahead in ELECTRONICS

SAMS books cover every phase of Electronics for the service technician, engineer, student or experimenter. Listed below are a few of the many valuable SAMS books available at electronic parts distributors and leading book stores.

2 GREAT NEW BOOKS

"HI-FI HANDBOOK"

by
William F. Boyce

Invaluable for audiophiles and technicians interested in Hi-Fi design, selection and installation. Chapters cover: Fidelity, Sound Theory and Distortion; Loud-speakers; Baffles and Enclosures; Amplifiers, Pre-amplifiers and Controls; Program Source Equipment; Systems Design, Selection and Installation. Really covers the whole subject of high-fidelity from a practical point of view, with invaluable hints on equipment selection, operation of program sources, speaker location and system installation. 240 pages; 5½ x 8½"; fully illustrated. Order today, postpaid only... \$3.00

"METALLIC RECTIFIERS

Principles and
Applications"
by Leonard R. Crow

This book clearly presents theory, principles and applications of the three most commonly used metallic rectifiers: the copper-oxide, the magnesium-copper sulfide, and the selenium. Also includes a chapter on the new silicon type rectifiers. Illustrates interesting rectifier circuits, applications of power and small current rectifiers, instrument rectifiers and how rectifiers are used as electric valves. Includes electrical and metallic rectifier terminology, bibliography and list of metallic rectifier manufacturers. 286 pages; 5½ x 8½"; illustrated. \$3.00
Order today, postpaid only.....

USE THIS ORDER FORM

☐ HI-FI HANDBOOK.....\$3.00

☐ Transistor Circuit Handbook. This authoritative book completely covers all phases of transistor circuits, types, construction, characteristics, applications, techniques for wiring and testing. 430 pages, 6 x 9"; illustrated.....\$4.95

☐ Scatter Propagation Theory and Practice. Covers the installation, operation and maintenance of Scatter Propagation Systems. Describes theory, design and construction of parabolic antennas, characteristics, equipment used. 204 pages, 5½ x 8½"; illustrated.....\$3.00

☐ Color TV Training Manual. Prepares the Technician for Color TV service work. Covers principles of the Color TV system; Color receiver circuits; installation and servicing steps. Includes color blocks outlining the use of color test equipment. 260 pages; 8½ x 11"; 300 illustrations.....\$6.95

☐ TV Test Instruments. Revised and enlarged to include latest data on instruments used in Color TV servicing. Tells clearly how to operate each type of test instrument used in TV service work. 180 pages; 8½ x 11"; illustrated.....\$3.50

☐ Key Checkpoints in TV Receivers. Prepared by the Howard W. Sams engineering staff. Provides many applications for general TV service work, including time-saving information on how to make quick tests at key points to determine where trouble lies, and how to check overall performance of the receiver after repair, to insure against callbacks. 182 pages; 5½ x 8½"; illustrated.....\$2.00

☐ Servicing TV Sweep Systems. Describes the operation, circuit function and circuit variations of vertical and horizontal sweep systems common to most TV receivers. Tells how to analyze circuits; troubleshoots for you. 212 pages; 5½ x 8½"; illustrated.....\$2.75

☐ METALLIC RECTIFIERS.....\$3.00

☐ So You Want to Be a Ham. Tells you what you need to know about getting your license and acquiring equipment. Covers such subjects as: Conquering the Code; Getting Your Ticket; Going on the Air; Electronics as a Career; etc. 196 pages; 5½ x 8½"; illustrated.....\$2.50

☐ Tape Recorders—How They Work. Explains recording theory, tape characteristics, motorboard mechanisms, drive motors, amplifiers, magnetic heads, volume indicators, equalization circuits—covers everything you want to know about recorders. 176 pages; 5½ x 8½". \$2.75

☐ Servicing AGC Systems. Describes the operation and circuit variations of the various types of AGC systems and explains the servicing techniques that can be applied. Illustrated by actual case histories and photographs of symptoms. 132 pages; 5½ x 8½"; illustrated.....\$1.75

☐ Servicing & Calibrating Test Equipment. Shows you how to keep your test instruments in reliable working order, how to determine proper operation and avoid erroneous indications. Explains calibration procedures; gives method for performance record-keeping; shows simple ways to check instrument accuracy; describes proper maintenance and servicing of instruments. 192 pages, 5½ x 8½".....\$2.75

There is an authoritative Sams book on virtually any Electronic subject in which you're interested. Check below for FREE Book List describing all Sams books.

☐ Send Book List



...HOWARD W. SAMS & CO., INC.....

Order from your Parts Jobber today, or mail to Howard W. Sams & Co., Inc., Dept. 1-B7 2201 East 46th St., Indianapolis 5, Indiana.

Send books checked above. My (check) (money order) for \$..... is enclosed.

Name.....

Address.....

City.....Zone.....State.....

(outside U.S.A. priced slightly higher)

Look
for
SAMS BOOKS
on
the "Book Tree"
at your
Parts Distributor

WRITE FOR BONUS CATALOG

New, Unused • Individually Boxed
TUBES FULL RETMA WARRANTY

No Electrical or Mechanical Rejects

02A	.48	8AV5	.80	8B6	.45	12AX7	.35
1A3	.75	8AV6	.45	8B7	.45	12BA6	.50
1B2	.85	8AX4	.80	8B7A	.30	12BE6	.45
1B5	.50	8AX5	.75	8B7B	.30	12BH6	.50
17A	.50	8B6S	.48	8B7C	.50	12BY7	.47
1U5	.48	8B6S	.48	8B7D	.55	12CA7	.54
1X3	.85	8B7A	.48	8B7E	.55	12CW7	.50
3V4	.75	8B7B	1.15	8B7F	.55	12DN7	.46
5U4	.48	8B7C	1.11	8B7G	1.15	12EQ7	.50
5V4	.80	8B7D	.90	8B7H	.75	23Q6	.90
5Y2	.85	8B7E	1.10	8B7I	.55	23L6	.45
6AC7	.85	8B7F	.90	8B7J	.35	23RA6	.45
6AG5	.48	8B7G	1.30	8B7K	.40	25L6	.40
6AK5	.50	8B7H	.22	8B7L	.45	31B6	.50
6AL5	.40	8B7I	.50	8B7M	.88	32X5	.45
6AQ5	.48	8B7J	1.08	12AT6	.40	50B5	.70
6AT6	.40	8B7K	.12	12AT7	.68	50C5	.82
6AU4	.09	8B7L	1.85	12AU6	.41	50L5	.85
6AU6	.50	8B7M	.40	12AU7	.50	75	.85
6AV6	.48	8B7N	.45	12AX4	.90	83V	1.22

INFRARED SNOOPSCOPE

See in Dark Tube

Selected, GTD & Tested for resolution. 1st class image converter viewing tube. Hi-sensitivity, simplified design. 3" dia. Willemite screen. Hi Resolution. Tube & Data. Special @ \$4.75; 2/59

NEW IMPROVED "TAB" HI-FI SPEAKERS

With Inbuilt Network Tantalum Alesis S Plus Magnet, & 50 Ohm V.C.
15" TRIAX, 25 Watt/30-20,000 Cycles. \$37.50
12" TRIAX, 20 Watt/40-20,000 Cycles. \$32.50
MODEL F12H35
12" COAX, 20 Watt/30-18,000 Cycles. \$32.50
MODEL F12H2X

"TAB" SPECIALS!

MILLEN 1 1/2" Chrome Knob, 180° CW ±10007, Reg. 75¢ @ \$1.00. SPECIAL 35¢ @ 3 for \$1
TRANSFORMER, 115 VAC/RC, sec'd 0-5 for \$1
Amps, tap @ 0.3V & 18V or 24V, wgt 8 lbs.
SPECIAL 90¢ @ 3 for \$1
COMBO PC Power Parts Package 18 VDC @ 8 amp, incl above transformer & F. W. Bridge Rectifier, \$20 Value.
CRYSTAL SET \$1.40; with socket, \$2.40
DIENL miniature PM motor 10,000 RPM, "TAB" \$1.85
VDC Reg. \$30.
CRYSTAL DIODES (IN38 @ 5¢; 10/95; IN31 @ 9.5¢)
VOLTMEETER 2N Type 246 "TAB" \$2.25
SPECIAL @ \$3.
S.E. 314A Precision 50,000 ohm Pot, reg. 60¢, "TAB" @ \$4.
Electrometer CKB697/570AK, mini tube, Raytheon @ \$3.
IMA DE JURE 3" Rod White Cad 2310 meter, "TAB" @ \$4.
800MA DE JURE Rod White Cad 2310 meter, "TAB" @ \$3.
Fountain Pen, Precision Dial or Carbon 2 for \$5
CRYSTAL @ \$3.
NEW PHOTOFLASH 55mm/450VDC/55 Watt sec'd, gtd low leakage, famous reg. \$15; late 59 prod. "TAB" @ \$6; 2/52; 5/53
C.N. 350T Toggle 10 amp 1/2 to 24 HP, \$2.40 reg. SPECIAL @ 2 1/2 for \$5
0-1MA New Miniature Sq. Precision Jweeled D'Arsenal Mtr., better 2nd accy, Special @ \$4. 3 for \$7
Phone-CW-Filter, Cord, Plug & Jack 1020 w/ filter, reg 80¢, URN. "TAB" @ \$1.56

FAMOUS BRAND PHONO CARTRIDGES

Original Boxed, Money Back Gtd.
RPX050A .001 & .003 (58).....\$6.75
RPX052A Golden Treasure (UD).....\$2.25
RPX053A Golden Treasure (DD).....\$3.00
Replacement Needles "TETRAD" Diamond
RPJ013A Dual (DB) .001 & .003 "TETRAD".....\$10.95
RPJ012 or RPJ013 Single (D) "TETRAD".....\$6.95
RPJ015 or RPJ013 Single (S).....\$1.65
RPJ003 or RPJ004 Single (D) "TETRAD".....\$5.95
RG or 78 Single (D) "TETRAD".....\$5.95

FINEST HI-FI RECORDING TAPE

1200 Ft.—7" Reel \$1.45 Lots of 12

Famous makers quality tape. Precision coated & SH. Gtd. Constant 1/100 sec'd. Splice Free. Preg. 7 1/2 IPS 40-15KC. Oxide Wnd In. 3 FOR \$1.50 EACH; SINGLY @ \$1.50 EA.

"TABLITE" ELECTRONIC FLASH KITS

AC & Battery Inbuilt All in One Camera Case
Uses new low cost voltage super circuit constant bright lightoutput; light duration 1/100 sec'd. 1/200 sec'd. 1/8000; cost per flash less than \$4. 1000 to 2000 flashes per set of batteries. All kits with inbuilt AC Pack. (Kit less battery \$9)
MODEL 400S, 60W sec'd color 25+ & W 255+ Recycles 2 sec'd, less than 4 lbs.....\$25.95
MODEL 600S, 120W sec'd color 100+ & W 300+ Recycles 3 sec'd, less than 5 lbs.....\$39.95
2-340V Battery.....\$10.95
SOLD WITH "TAB" MONEY BACK GUARANTEE

KITS! KITS!

All Kits Contain Most Popular Values & Sizes

EXTRA: ONE FREE KIT WITH EACH \$10 KIT ORDER.

25 Precision Resistors	25 Power Resistors
10 Switches	65 Minu Cond's
25 Knobs	5 Crystal Diodes
75 Carbon Resistors*	250 ft. Hookup Wire
100	10
10 Electrolytic Cond's	35 Ceramic Cond
10 Volume Controls	10 Rotary Switches
25 Tube Sockets	5 Crystals
50 Tubular Cond's	60 Inductors & Coils
500 Lugs & Eyelets	5 On-Off Switches
10 Bathing Oil Cond's	10 Wheat Lamps
5 lbs. Surprise Kit	5 Insulators
10 Kmit Minu Cond's	5 Plastic Boxes

ONE KIT EACH.....only 99¢

"TAB"

TERMS: Money Back Gtd (cost of mfg only) \$5 min order P.O.S. N.Y.C. Add ship charges or for C.O.D. 25% Dep. Telco. gtd. via R-Exp Only. Prices shown subject to change.

Dept. 3077, 111 LIBERTY ST., N. Y. 6, N. Y. PHONE RECTOR 2-6345-CABLE "TABPARTS"

INDEX OF Advertisers

FEBRUARY 1957

[While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.]

ADVERTISER	PAGE	ADVERTISER	PAGE
Advance Electronics Company.....	186	McGee Radio Company.....	148, 149
Airex Radio Corp.....	138	McGraw-Hill Book Company.....	188
Alliance Manufacturing Co.....	133	M. R. Company, The.....	192
Allied Radio Corp.....	9, 98,	Mallory & Co., Inc., P. R.....	4th Cover
113, 117, 118, 119, 120, 121, 122, 123, 133		Madison-Fielding Corp.....	169
Altec Lansing Corporation.....	165	Milwaukee School of Engineering.....	116
American Elite, Inc.....	132, 167	Moss Electronic Distributing Co.....	143, 144
American Television & Radio Co.....	108	Musicraft.....	172
Amperex Electronic Corp.....	170		
Argos Products Company.....	26	Natco Aviation.....	104
Arrow Sales, Inc.....	146	National Radio Institute.....	3, 19, 20
Atlas Sound Corp.....	162	National Schools.....	7, 161
Arkay Kts, Inc.....	161	Nel-Kaye Records, Inc.....	27
Ashe Radio Company, Walter.....	34	Neshaminy Electronic Corp.....	146
Audel Publishers.....	188	North American Phillips Co., Inc.....	10
		Northronics.....	112
B & J Electronics, Inc.....	182		
B. & K. Manufacturing Co.....	107, 168,	Offenbach-Reimus.....	194
185		Olson Radio Warehouse.....	175
Baltimore Technical Institute.....	168		
Barry Electronics Corp.....	199	Peak Electronics Company.....	134
Belden.....	24	Perma Power Company.....	174
Bell Telephone Laboratories.....	77	Pickering & Co., Inc.....	95
Bendix Radio.....	142	Pilot Radio Corp.....	164
Bozak Sales Co., R. T., The.....	160	Popular Boating.....	184
British Industries Corp.....	155, 163	Precision Apparatus Company, Inc.....	103
Burstein-Applebee Co.....	112	Precision Elec. Mfg. Co.....	168
		Prentice-Hall, Inc.....	191
Cabinart.....	114	Presto Recording Corp.....	11
Candler System Co.....	178	Progressive "Edu-Kits," Inc.....	108
Capital Electronics.....	190	Proto Tools.....	12
Capitol Radio Engineering Institute.....	101, 182		
CBS-Hytron.....	21, 78	Quality Electronics.....	178
Century Electronics Co., Inc.....	94	Quetrolco Company, Inc.....	174
Channel Master Corp.....	15		
Chicago Standard Transformer Corporation	104	R.C.A. Institutes, Inc.....	109
Cleveland Institute of Radio Electronics	29, 28	RW Electronics.....	193
Colordaptor.....	192	Radiant Corp., The.....	8
Color Television.....	115	Radio Corporation of America.....	14, 32, 173
Columbia Electronics.....	196	Radio Ham Shack, Inc.....	200
Columbia LP Record Club.....	13	Radio Shack of Boston.....	126, 127, 128, 129
Cornell-Dubilier.....	6	Radio-Television Training Association.....	25
Coyne Electrical School.....	101, 132	Rad Tel Tube Co.....	180
		Rauland-Berg.....	146
DeLoe Radio.....	22	Raytheon Manufacturing Company.....	Second Cover
DeVry Technical Institute.....	5	Company.....	
Dressner.....	112	Rex-O-Kut Company.....	158
Duotone Co., Inc.....	168, 196	Rex Radio Supply.....	182
		Rider Publisher, Inc., John F.....	79
Editors & Engineers, Ltd.....	152	Rinehart & Co., Inc.....	136, 137
Electronic Chemical Corp.....	193	Rockbar Corporation.....	166
Electronic Instrument Co., Inc. (EICO).....	35, 36	Rohn Manufacturing Company.....	75
Electro-Sonic Laboratories, Inc.....	155		
Electro-Voice.....	17, 8	Sams & Co., Inc., Howard W.....	99, 197
Eric Resistor Co.....	152	Schober Organ Corporation, The.....	192
		Scott, Inc., H. H.....	16
Fair Radio Sales.....	131	Service Instrument Co.....	142
Fairchild Recording Equipment Company.....	167	Shure Brothers, Inc.....	153
Fisher Radio Corporation.....	156, 157	Sprayberry Academy of Radio.....	23
Flying.....	177	Stan-Burn Radio & Electronics Co.....	196
		Stanley Electronics Corp.....	125
G. & G. Radio Supply Co.....	179	Superec Electronics Corp.....	172
Goodheart, R. E.....	94		
Garfield Company, Oliver.....	188	"TAB".....	198
Grance Products.....	169	Tematic Industries.....	114
		Teraco Company.....	132
Harjo Sales Co.....	104	Texas Crystals.....	124
Hartley Products Co.....	154	Transvision, Inc.....	182
Harvey Radio Co., Inc.....	187	Tri-State College.....	104
Hawkins Co., P. E.....	94	Tube Mart.....	184
Heald Engineering College.....	176	TV Trend.....	142
Heath Company.....	80, 81,		
62, 83, 84, 85, 86, 87, 88, 89, 90, 91, 92, 93		United Radio Co.....	161
Hershel Radio Co.....	194	University Loudspeakers.....	159
Hickok Electrical Instrument Co.....	145		
Hi-Fi Guide & Yearbook.....	130	V. S. I. Television School.....	94
Hi-Lo TV Antenna Corp.....	189	Valparaiso Technical Institute.....	112
Hughes Research & Development Laboratories.....	18	Van Nostrand, D. Co., Inc.....	105
		Video Electric Co.....	183, 191
Indiana Technical College.....	178	Viking of Minneapolis.....	Third Cover
Instructograph Company.....	185		
International Business Machines Corp.....	30, 31	Wall Manufacturing Co.....	106
International Electronics Corp.....	195	Weiler Electric Corporation.....	135
International Rectifier Corporation.....	163	Western Radio.....	176
International Resistance Co.....	96, 97	Western Television Institute.....	196
Jackson Electrical Instrument Co.....	108	Xcelite, Incorporated.....	176
Jones & Laughlin Steel Corporation.....	147		
		Yeats Appliances Dolly Sales Co.....	195
Kester Solder Company.....	174		
Kopelove Electronics Co.....	185	Zenith Stamp Co.....	176
Krylon, Inc.....	114	Zyttron Tube Company.....	163
Lafayette Radio.....	139, 140, 141		
L. M. B. Box Chassis.....	168		
Lampkin Laboratories, Inc.....	106		
Lansing Sound Inc., James B.....	173		
Lektro Specialties.....	178		

Classified

RATE: 50¢ per word. Minimum 10 words. April issue closes February 11th. Send order and remittance to: RADIO & TELEVISION NEWS, 366 Madison Ave., N. Y. C. 17.

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice; television; broadcasting; servicing; aviation, marine, police radio, 18 or 21 months. Catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

DESIGN—Construction Service or Consultation on any type of Electronic Device. Electronic Service Engineers, Poteau, Oklahoma.

FOR SALE

DIAGRAMS! Repair Information! Radios—amplifiers—recorders \$1.00. Televisions \$1.50. Give make, model, chassis. Norelco-Philips and Amperex tubes in stock! TV Miltie, Box 101RA, Hicksville, New York.

DIAGRAMS for repairing radios \$1.00. Television \$2.00. Give make, model. Diagram Service, Box 672-RN, Hartford 1, Conn.

TUBES—TV, Radio, Transmitting And Industrial Types At Sensibly Low Prices. New, Guaranteed, 1st Quality, Top Name Brands Only. Write For Free Catalog or Call Walker 5-7000, Barry Electronics Corp., 512 Broadway, New York 12N, N. Y.

DIAGRAMS—Radios, Amplifiers, Changers, \$1.00 Each. Television Service Data \$2.00. Unknown Models, Give Tube Layout And Part Numbers. Kramer's Radio Service, Dept. 656, 36 Columbus Ave., New York 23, N. Y.

COMPLETE Television Sets \$11.95. Jones TV, 1115 Rambler, Pottstown, Pa.

BUILD your own television test instrument from old TV set. Complete instructions \$2.00. Sterling Electronic Co., 129 W. Long Ave., New Castle, Pa.

ONE of the original General Electric FM receivers covering the old band 44-48 mc. \$10.00. Box 51 % RADIO & TV NEWS.

TUBES 40¢ each. High emission, clean, boxed, thoroughly checked, reprocessed. Most types Radio, TV, 7 day money back satisfaction. Prepaid 50¢ handling. 20% C.O.D., F.O.B. R & M TV, 234 Morris Ave., Elizabeth, N. J.

TV ANTENNAS—Taco Shark Model 1845—Box of 2—\$13.95; 1847 or 1848 Stacking Kits \$1.00; Trio Z26A (ANT) \$9.95; Trio Z26H (AN8H) \$4.95; 10 Element Conical Kit Model 5A or 5D with lead, Masts, Standoffs and Hardware, a high quality Kit, \$4.95. Allied Electronics, 111 North 41st, Omaha, Nebraska.

TUBES 40¢ Each. High emission, clean, boxed, thoroughly checked, reprocessed. Most types Radio, TV, 7 day money back satisfaction. Prepaid 50¢ handling. 20% C.O.D., F.O.B. R & M TV, 234 Morris Ave., Elizabeth, N. J.

POCKET vacuum cleaner \$5.95 World-Export, Box 929, Indio, California.

WANTED

CYLINDER and old disc phonographs. Edison Conqueror, Idella, and Oratorio models. Berliner Gramophones and Zono-phones, Columbia cylinder Graphophones, and coin-operated cylinder phones. Want old catalogues and literature on early phones prior to 1919. Will pay cash or trade late hi-fi components. Box 50 % RADIO & TELEVISION NEWS.

AN/APR-4, AN/APR-9, other "APR," "ARR," "TS," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. Engineering Associates, 434 Patterson Rd., Dayton 9, Ohio.

WANTED: Receiver R5/ARN-7, MN-62A Transceivers, RT18/ARC-1, AN/ARC-3, BC-788C, I-152C, Collins, Bendix equipment, Test Sets, Dynamotors, Inverters. We pay highest prices. Advise quantity, condition, price first letter. Aircraft Radio Industries, Inc., 15 East 40th St., New York City, telephone LEXington 2-6254.

ART-13/T47A Transmitters, \$175.00; **ART-13/T47** Transmitters, \$125.00; **BC-788 C** Altimeters, \$175.00; **ARC-3** Transceiver Complete, \$325.00; **R5/ARN-7** Radio Compass, \$175.00; **BC-348** Rec'r Modified, \$25.00; **BC-348** Rec'r Unmodified, \$30.00; **ARC-1** Transceiver, \$300.00; **BC-342** Rec'r, \$50.00; **BC-312** Rec'r, \$40.00; **I-152-C** Indicator, \$50.00. Ship Via Express, C.O.D. Subject To Inspection To H. Finnegan, 49 Washington Ave., Little Ferry, N. J.

WILL pay for operating Manual or Diagram Scott Marine Radio S.I.R.M. Dr. E. F. Miller, 344 A St., Idaho Falls, Idaho.

OLD Cone Type Loudspeakers: Collector wants all makes and models manufactured before 1927. In reply write make, model, condition, location, price. Box 554, RADIO & TV NEWS.

BC221's WANTED—Highest cash price for BC-221's paid even more if the unit has modulation and hasn't been tampered with. Original Book needed. Write giving Model No. to Bolton Laboratories, Inc., Bolton, Mass.

WANTED: ART-13 transmitters and parts—also ARC-1, ARC-3, and ARN-7. Have requirement for ARN-6 material, Iron Core Loops, need all types Collins and Bendix Aircraft Radio equipment. Florida Aircraft Radio & Marine, Inc., P.O. Box 205, International Airport Branch, Miami 48, Florida.

CASH Paid! Sell your surplus electronic tubes. Want unused, clean transmitting, special purpose, receiving, TV types, magnetrons, Klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: Barry, 512 Broadway, New York 12, N. Y. Walker 5-7000.

BEFORE You Sell—Check With Rex! Wanted: Surplus military and commercial aircraft electronics. BC-788, I-152, ARN-7, ARC-1, ARC-3, BC-221, RTA18, ART-13, DY-21, APN-9, transmitters, receivers, test equipment, etc. Also Want Electronic Tubes: broadcast, transmitting, receiving, Magnetrons, Klystrons, miniature, sub-miniatures, ruggedized, etc. For Top Prices Contact: Bob Sanett, W6Rex, 1524 S. Edris Dr., Los Angeles 35, Cal. Phone: REpublic 5-6215.

WANTED One TN 54 Tuning Unit for APR 4. We will pay \$275 for unit in good condition. Reply to: Wlaky, 15 Primrose Ave., Brantree, Mass. U. S. A.

WILL pay for operating Manual or Diagram Scott Marine Radio S. L. R. M. Dr. E. F. Miller, 344 A St., Idaho Falls, Idaho.

REPAIRS AND SERVICING

HIGH Fidelity Speakers Repaired. Amprite Speaker Service, 70 Vesey St., N. Y. 7, N. Y. Ba. 7-2580.

TV TROUBLES? Send Model Symptoms and \$2.00 for Analysis. Electronic Service Engineers, Poteau, Oklahoma.

HEATH Kit Computers Wired-Tested. Electronic Service Engineers, Poteau, Oklahoma.

TAPE RECORDERS

RECORDERS, Tape, Hi-Fi. Wholesale Prices. Catalogue. Klarston, 215 E. 88th St., N. Y. C. 28.

PRE-RECORDED Tapes, Recorders, Accessories. Unusual Values, Catalog. Efsco Sales, 270-E Concord Avenue, West Hempstead, N. Y.

TAPE Recorders, Tape. Unusual Values. Free Catalog. Dressner 69-02 R, 174 St., Flushing 65, N. Y.

WHOLESALE Catalogue: Recorders, Tapes, Radios, Records, Phonographs, Towers—155, Philadelphia 5.

CORRESPONDENCE COURSES

USED Correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

USED Correspondence Courses, Educational Books Bought, Sold, Rented, Catalog Free. Vernon, 624 Mohawk, Rossville, Ga.

INSTRUCTION

ENGINEERING Degrees earned by home study. (Residential courses also available.) Pacific International University, (American College of Engineering), Box 27724-C, Hollywood 27, Calif.

LEARN While Asleep! Details free. Research Association, Box 610-RT, Omaha, Nebraska.

MISCELLANEOUS

DECALS—Trademarks, Service, Sales, etc. Write Allied Decals, Inc., 8375 Hough, Cleveland, Ohio.

EAVESDROP with a pack of cigarettes, miniature transistorized radio transmitter. Complete Diagrams and Instructions. \$1.25. C. Carrier Co., 734 15th St., N.W., Washington, D. C.

TELEPHONE Extension in your car. Answer your home telephone by radio from your car. Complete diagrams and instructions. \$1.25. C. Carrier Co., 734 15th St., N.W., Washington, D. C.

HQ for the 5 TOP QUALITY brands of

TUBES

AT SENSIBLE PRICES!

• 90-Day RETMA guarantee • Brand New
• Individually boxed • First quality only
WRITE FOR LATEST RECEIVING AND TV TUBE
PRICE LIST, FREE!

1835	.. 93.80	6L200	.. 83.00	6X102B	.. 2.35
1023	.. 80.00	304TH	.. 8.75	1820	.. 83.00
CL-2	.. 10.00	304TL	.. 16.50	1824	.. 1.25
2C39	.. 2.00	307A	.. 8.00	1828	.. 3.75
2C39A	.. 11.00	355A	.. 12.00	2050	.. 1.00
2C51	.. 2.50	357A	.. 15.00	2051	.. .55
2C53	.. 9.95	371B	.. .90	5817	.. 1.35
2C51	.. 2.70	403A	.. .75	5836	.. 2.05
2824	.. 2.35	403B	.. .75	5836A	.. 2.95
2K28	.. 15.80	404A	.. 12.50	5843	.. 1.00
2K45	.. 35.00	418A	.. 39.00	5843	.. 5.00
2K35	.. 15.00	418B	.. 39.00	5848	.. 4.50
3824	.. 1.50	417A	.. .75	5851	.. 1.40
3824W	.. 1.50	417A	.. .75	5854	.. 1.40
3829	.. 5.50	5843	.. 12.50	5856	.. 4.50
3829	.. 1.40	5850T	.. 44.00	5870	.. 1.50
3C23	.. 4.00	KU-510	.. 3.50	5875	.. 8.00
3C45	.. 1.45	WL68S	.. .50	5878	.. 2.75
3C45	.. 6.00	558	.. 90.00	5887	.. 2.75
3130	.. 30.00	6L673	.. 13.00	5891	.. 4.75
3K0000K	.. 16.50	701A	.. 1.10	5893	.. 4.75
4-125A	.. 30.25	723A/B	.. 7.85	5718	.. 2.50
4-250A	.. 35.00	725A	.. 3.50	5719	.. 2.00
4-600A	.. 55.50	730T	.. 38.00	5723	.. 3.40
4B24	.. 4.50	800	.. .90	5726	.. .80
4C36	.. 13.50	803	.. 2.00	5749	.. 1.25
4E27	.. 5.50	805	.. 8.00	5763	.. 1.20
4F80A	.. 40.00	807	.. .50	5812	.. 1.00
5C22	.. 19.10	807W	.. 1.50	5814	.. 1.00
5C22	.. 19.10	807W	.. 1.50	5840	.. 8.00
6AK5W	.. 1.40	813	.. .85	5879	.. 3.40
6C4	.. 20	814	.. 2.75	5881	.. 2.95
6E5	.. 10.20	818	.. .50	5910	.. .45
614	.. 1.90	816	.. 1.50	5910	.. .45
615W	.. 1.00	836	.. 1.25	5911	.. 2.00
15E	.. 1.25	837	.. 1.25	6111	.. 4.95
6F32	.. 4.50	838	.. .70	6112	.. 4.95
6F32	.. 2.45	840	.. .50	6130	.. .50
VC30	.. 3.00	889A	.. 1.25	6135	.. 6.00
6C4	.. 20	873A	.. 1.00	6161	.. 60.00
RG60	.. 1.35	917	.. 2.00	6189	.. 2.50
RG65	.. 7.00	918	.. 1.00	6201	.. 2.50
RG65	.. 2.50	927	.. .50	6239	.. 9.00
RGK72	.. 40	930	.. 1.80	6308	.. 3.25
73	.. .40	955	.. .35	6308	.. 3.25
F123A	.. 8.00	956	.. .35	6309	.. 2.00
VX8-130	.. 1.75	956	.. .35	9001	.. .85
203A	.. 2.50	958A	.. .35	9002	.. .85
211	.. .50	951	.. .35	9003	.. 1.35
250R	.. 2.95	CK100S	.. .35	9004	.. .50
HK353	.. 5.00	CK1007	.. .75	9006	.. .50

and many, many others. Over 1000 types in stock. WRITE! (SURPLUS)

2 COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partition prevents breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity 100 of any one size. Write for case lot prices.

SIZE	FOR TUBE PER 100
Miniature	.. 5AUS, etc. \$1.00
GT	.. 68N7, etc. 1.25
Large	.. 68N7, etc. 1.50
Large	.. 68N7, etc. 2.00

WHITE GLOSSY BOXES
Completely blank. No printing or color. Otherwise same as above. Same high quality same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

TUBE STACKERS
White glossy only. Mini-stacker holds 10 Mini tube cartons; "GT" stacker holds 10 "GT" cartons.

SIZE	PER EACH
Mini-stacker	.. 1.15
GT	.. 1.75

5" DUMONT SCOPE MODEL 274A AT LESS THAN HALF PRICE!

Genuine Dumont model 274A, 5" oscilloscope, regularly sold for \$150, now available for LESS THAN HALF PRICE! Look at these features: Frequency response within 50% from 20 to 200,000 cps with recurrent sweeps from 5 to 30,000 cps. Similar X and Y amplifiers and provision for intensity modulation. Portable, light weight. Shpg. wgt. only 35 lbs. Used, clean, checked out and guaranteed. SPECIAL! F.O.B. N.Y.C. \$65.00

TEST EQUIPMENT BARGAINS!

Absorption Wavemeter, GEN'L. Radio type 788A 95-400 MCS. (Worth \$40.00) NEW! \$ 12.50
5" OSCILLOSCOPE, Dumont 274A. Vg. 75.00
5" OSCILLOSCOPE, Dumont 205B. Vg. good. 110.00
5" OSCILLOSCOPE, RCA WD-88A. Vg. good. 95.00
TV XTAL 15 CHANNEL MARKER, Ray "Mega-marker" incl. all 13 chals. Vg. good. \$49.50
SIGNAL GENERATOR, Measurematic Corp. model 78FR. 85-310 Mcs. 30 Mc. deviation. Excellent condition. \$175.00

TV Sweep Generators RCA MODEL WR-59A SPECIAL COND. \$75

TRANSFORMER SPECIAL!
 3100-0-3100 volts @ 1/2 amp
 PRIMARY: tapped for 95-104-110-115-125 volts, 60 cps.
 SECONDARY: 3100 volts each side of center @ 500 mA. 15 KV impregnated mica insulation. Generatively rated. Meas. 9" L x 3" H x 7 1/2" W. C.O.D. New, guaranteed. Shpg. wgt. 60 lbs. \$34.50

WRITE FOR "BARRY'S GREEN SHEET." FREE!

TERMS: 25% deposit with order, balance C.O.D. All merchandise guaranteed. F.O.B. N.Y.C.
 Subject to Price Variation & Stock Depletion


BARRY ELECTRONICS CORP.

512 Broadway, Dept. RN, N.Y. 12, N.Y.
 Call Day or Night—24 Hour Phone Service
 Phone: Walker 5-7000

TUBE

SPECIALISTS to the WORLD

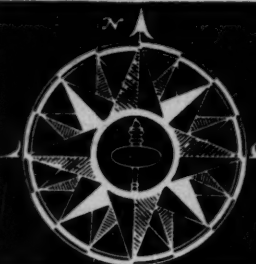SELECT THE TUBES YOU NEED FROM ONE OF THE MOST COMPLETE TUBE INVENTORIES IN THE WORLD



First Quality — Fully Guaranteed — No Seconds

RECEIVING TUBES

0A2	.65	6AD7G	1.50	6L6G	.95	12BF6	.60
0A4B	.95	6AF4	1.25	6L7	.95	12BH7	.69
0B2	.65	6AF6G	.85	6N7	.99	12BK5	.95
0Z4	.40	6AG5	.72	6Q7	.95	12BQ6GT	1.35
1A3	.40	6AG7	.60	6Q7GT	.79	12BY7	.90
1A7	.52	6AH4	.85	6R7	.85	12C7	.95
1AD4	1.20	6AH6	.65	6R7GT	.68	12C8	.69
1AE4	.92	6AJS	1.49	6S4	.57	12CUG	1.35
1AX2	.95	6AK5	.60	6S6GT	1.05	12H6	.89
1B3GT	.79	6AG6	.75	6SA7	.79	12H6GT	.60
1C5GT	.52	6ALS	.58	6SA7GT	.79	12K7GT	.89
1G4	.65	6AL7	.95	6SB7Y	.87	12K8	.69
1G6GT	.40	6AN4	1.50	6SC7	.72	12Q7 GT	.75
1H6GT	.58	6AN6	1.10	6SF5	.72	12S7	.89
1HGT	.60	6AN4	1.50	6SF5GT	.69	12SA7GT	.69
1L4	.74	6AN5	2.75	6SF7	.92	12SC7	.75
1L6	.79	6AN6	1.15	6SGT	.65	12S6GT	.79
1L4A	.79	6AQ5	.57	6SH7	.74	12SN7	.85
1L4B	.85	6AQ6	.57	6SH7GT	.59	12SJ7	.65
1L84	.85	6AQ7	1.15	6SJ7	.69	12SK7	.69
1LC5	.79	6ARS	.70	6SJ7GT	.69	12SL7	.85
1LC8	.79	6AR6	2.15	6SK7	.59	12SN7	.75
1LD6	.85	6ASS	.70	6SK7GT	.59	12ST7	.59
1LE3	.79	6AS6	1.95	6SL7GT	.75	12SR7	.59
1LG5	.85	6ASTGT	2.35	6SN7GT	.75	12TGT	.59
1LH6	.85	6ASS	1.15	6SQ7	.59	12V6GT	.73
1LH8	.79	6AT6	.52	6SH7GT	.59	12W6GT	.87
1N5GT	.59	6AT8	1.05	6SR7	.55	14A4	.95
1Q5GT	.95	6AU4	1.05	6SS7	.75	14A5	1.30
1R4	.65	6AUS	1.10	6ST7	.95	14A7	.75
1R5	.65	6AU6	.85	6T8	.95	14A7	.95
1S4	.65	6BA7	.85	6U5	.95	14B6	.69
1S5	.65	6AV5	1.20	6V8	.95	14C7	.95
1T4	.65	6AV6	.53	6V3	1.25	14E6	1.05
1T5	.69	6AX4	.70	6V6	1.10	14E7	1.15
1U4	.67	6AX5	.69	6V6GT	.89	14F7	.85
1U5	.69	6BA4	.65	6W4GT	.85	14F7	.85
1V	.65	6B8	.67	6W6GT	.79	14F8	1.10
1V2	.59	6BA6	.83	6X4	.48	14H7	.85
1V6	1.40	6BA7	.85	6X5GT	.48	14H7	.85
1X2A	1.05	6BC4	1.80	6X8	.98	14H7	1.20
2A3	.95	6BC5	.68	6V6G	.89	14Q7	.85
2A6	.59	6BC7	1.20	7A4	.79	14S7	1.10
2X2	.40	6BD5	1.35	7A5	.99	14W7	1.25
2X2A	1.35	6BD6	.73	7A6	.78	14W7	1.25
3A3	1.00	6BE6	.85	7A7	.75	19B6GT	1.09
3A4	.50	6BF5	.82	7A8	.75	19T8	.95
3A5	.64	6BF6	.82	7A7	1.65	25AV5	1.25
3A5A	.80	6BG6G	1.75	7AF7	.89	25AX4	1.05
3AU6	.70	6SH6	.79	7AG7	.95	25BK5	.95
3AV6	.60	6BJ6	.69	7AH7	.95	25BQ6GT	1.25
3B4	2.95	6BK6	.95	7B4	.75	25CD6G	1.75
3B7	.39	6BK7	1.05	7B5	.85	25CUG	1.30
3BC5	.90	6BL7	1.05	7B6	.75	25LGT	.65
3BN6	1.05	6BN6	1.10	7B7	.75	25W4GT	.72
3BY6	.75	6BQ6GT	1.15	7B8	.65	25Z5	.75
3CB6	.80	6BQ7A	1.15	7C5	.75	25Z6	.62
3CF6	.65	6BX7	1.20	7C6	.75	25Z6	.62
3D6	.39	6BY6G	1.25	7C7	.79	30	.65
3FLA	.65	6BZ7	1.20	7E7	1.15	32L7	.85
3Q4	.65	6C4	.38	7F7	.88	35A5	.69
3Q5	.73	6C5	.48	7F8	1.10	35B5	.68
3S4	.65	6CSGT	.46	7G7	1.10	35C5	.68
3V4	.69	6C6	.49	7H7	.79	35L6	.65
4BQ7A	1.30	6C8G	.85	7J7	1.25	35W4	.44
4BZ7	1.35	6CB5	4.40	7K7	1.15	35Y4	.65
5A6	1.05	6CB6	.68	7L7	1.10	35Y4	.65
5AN6	1.10	6CD6G	1.75	7H7	.85	35Z3	.59
5AQ5	.75	6CF6	.90	7Q7	.95	35Z5	.59
5AS6	1.10	6CG7	.85	7R7	.95	41	.75
5AT8	1.10	6CL6	1.10	7V7	.95	42	.69
5AV8	1.15	6CM6	.85	7W7	.88	43	.79
5AW4	1.10	6C56	.75	7X7	.90	43	.79
5AZ4	.60	6CUG	1.30	7Y4	.65	50A5	.68
5J6	.90	6D6	.59	7Z4	.85	50B5	.68
5R4GY	1.45	6DC6	.95	12A4	.85	50C5	.68
5T4	.90	6E5	.75	12A6	.57	50L6	.62
5U4Q	.58	6F5	.59	12ABGT	.79	50X6	.85
5U5	1.10	6F6	.85	12AN7GT	1.05	50Y6	.78
5V4G	.89	6F6GT	.69	12AL5	.85	50Y7	.78
5V6GT	.70	6F7	.85	12AQ5	.70	53	1.20
5W4GT	.95	6F8G	.72	12AT6	.48	70L7	1.15
5X4G	.75	6G6G	.72	12AUG	.62	75	.65
5X5	1.05	6H5	.89	12A7	.92	77	.47
5Y2GT	.49	6H6GT	.49	12A7	.92	77	.47
5Y4G	.65	6J4	2.85	12AV6	.52	78	.57
5Z3	.69	6J5	.48	12AV7	.95	80	.59
5Z4	.89	6J5GT	.47	12AW6	.95	81	1.85
6A3	.95	6J6	.68	12AX4	.85	83	1.10
6A6	.82	6J7	.82	12AX7	.78	83V	.95
6A7	.67	6J7GT	.85	12AY7	1.15	84/8Z4	.49
6AB	1.05	6K6GT	.85	12AZ7	.95	85	.85
6ABGT	.95	6K7	.74	12B4	.60	117L/M7	2.45
6AB4	.59	6K7GT	.59	12BA6	.60	117N/P7	2.45
6AB7	.69	6K8	1.10	12BA7	.89	117Z	.68
6AC5	1.05	6K8GT	.95	12BD6	.70	117Z4	1.05
6AC7	.85	6L6	1.60	12BE6	.65	117Z6	.95

TRANSMITTING TUBES

6A3/VR15	.86	5J2	6.35	876	.72	56B7	2.65	6099	1.35
6B3/VR105	.73	5J5	9.95	878	.48	56B2	8.10	6101	1.45
6C3/VR105	.68	5LP1	7.40	884	.95	56B3	4.65	6113	1.25
6D3/VR150	.88	5NP1	4.95	885	.95	56B6	.90	6146	4.75
1B22	1.25	6AC7W	1.48	902	2.45	5702	1.95	6161	89.50
1B23	2.68	6AK5W	1.45	918	1.65	5703	.95	6187	3.95
1B24	4.85	6AL5W	.95	923	1.25	5704	1.85	6189	2.25
1B27	12.95	6AQ5W	1.70	925	1.50	5718	2.75	6263	11.45
1B35	3.45	6AS5W	2.69	927	.95	5718A	4.75	6264	11.45
1B36	35.50	6BFTW	3.45	930	1.19	5719	2.15	6539	2.95
1B40	3.45	6C4W	6.75	931A	2.95	5725	1.45	8005	4.75
1B41	14.95	6C21	14.95	984	.25	5726	.60	8008	3.95
1C21	1.89	6F4	2.65	985	.35	5727	1.25	8012	.98
1C23	.39	6I4WA	4.45	986	.35	5732	2.95	8013	2.65
1N21B	1.45	6J5WGT	3.90	957	.35	5744	1.75	8013A	3.75
1N23	.68	6J6W	2.20	958A	.35	5781	1.45	8014	67.80
1N23B	1.40	6J6WA	3.90	959	1.32	5782	99.50	8020	1.25
1N34	.42	6K4	2.20	991	.20	5783	1.25	8025	1.45
1N34A	.48	6SN7WGT	1.85	1803	2.95	5793	4.45	9001	.82
1P21	25.50	6X4W	1.20	1616	.80	5787CK	4.05	9002	.60
1P22	13.25	6X5W	1.35	1619	.30	5794	5.95	9003	1.20
1P23	1.85	7BP7	4.45	1622	1.45	5812	2.70	9004	.38
1P24	1.45	12DP7	14.95	1624	.95	5814	.95	9005	1.39
1P25	64.50	18E	1.45	1628	.25	5819	32.50	9006	.25
1P28	1.95	18R	.49	1626	.19	5820	495.00	C1A	10.95
1P30	1.95	28D7	.95	1633	.85	5823	1.35	9007	7.95
1P32	.95	100TH	6.25	1635	1.48	5829	1.35	CK1005	.32
1P39	1.45	100TL	8.25	1641	1.35	5843	4.40	CK1006	3.45
1P40	1.25	211	1.45	1654	1.75	5841	7.40	CK1007	.65
1P41	2.45	249B	2.95	2050	1.25	5844	.95	CK1038	4.70
1P42	2.35	249C	1.95	2051	.65	5851	3.45	CK1039	4.70
2AP1	4.95	250TH	18.95	5816	6.45	5876	12.80	F123A	2.75
2B22	1.95	250TL	14.75	5817	1.65	5879	1.35	F127A	22.50
2C21	.39	262B	4.95	5834	6.95	5881	2.95	F128A	14.95
2C34	.25	274A	3.45	5836	2.90	5886	3.25	FQ17	4.95
2C36	21.50	274B	.85	5837	4.95	5894	18.95	FQ27A	10.90
2C38A	10.95	304TH	9.95	5838	7.45	5896	4.45	FQ32	3.95
2C40	9.45	304TL	12.50	5839	8.95	5899	3.95	FQ95	17.50
2C43	10.25	307A	1.10	5841	8.95	5902	5.95	FQ105	12.95
2C52	2.95	350A	2.65	5842	.95	5905	8.75	FQ172	17.95
2C53	10.75	350B	2.35	5843	8.95	5906	14.95	FG172	17.95
2D21	.85	371B	.85	5847	3.95	5908	7.85	HF100	6.95
2D21W	1.95	393A	.45	5851	1.35	5922	3.95	HF200	6.95
2E23	14.00	WL417A	2.95	5854	1.2L	5933	2.25	HF300	17.50
2E24	2.40	WL417A/5842	6.70	5856	7.90	5963	8.45	WL616	47.50
2E26	3.25		14.95	5870	1.10	6021	4.45	WX65	7.50
2E30	1.55	434A	2.95	5875	10.95	6080WA	7.95	RK65	7.50
2E31	2.45	450TH	47.50	5876	1.25	6096	1.45	RK72	7.50
2J31	14.00	500TL	35.00	5878	1.25	6097	1.45	RX21	5.50
2J32	12.50	575A	12.50	5886	1.95	6098	1.85	TX40	4.95
2J33	14.00	705A	.68						
2J34	14.00	707A	4.95						
2J36	14.95	707B	3.95						
2J51	97.50	715B	2.95						
2J55	38.50	715C	10.95						
2J61	12.95	717A	.35						
2J62	12.95	721A	.65						
2K23	15.25	723A/B	8.45						
2K25	11.95	725A	2.95						
2K28	37.50	726A	4.95						
2K29	27.50	726B	32.50						
3AP1	2.95	860C	26.50						
3B24	1.50	750TL	65.00						
3B24W	4.95	801A	.38						
3B25	4.95	802	2.45						
3B26	7.45	803	1.85						
3B27	4.45	804	8.85						
3B29	5.95	805	3.95						
3B31	2.95	806	4.85						
3C22	59.50	807	1.15						
3C23	3.45	808	1.25						
3C24	1.48	809	2.20						
3C25	1.85	810	19.00						
3D21A	2.95	811	2.75						
3D1	3.25	811A	3.25						
4E27	9.50	812	2.75						
4E55A	12.95	812A	3.95						
4-128A	22.50	813	10.50						
4-280A	3.45	814	1.95						
4C25	15.95	815	1.95						
4C28	17.45	816	1.95						
4C35	18.95	816A	.65						
4E27	9.50	826	7.45						
4E28	13.45	828	7.45						
4E29A	12.95	829B	7.95						
4X1500	31.95	830B	7.95						
5BP1	2.35	832	5.75						
5BP4	1.95	832A	7.95						
5C22	27.50	834	42.50						
5CP1A	8.45	837	1.25						
5CP7	7.95	838	.68						
5D21	7.45	845	4.85						
5F27	8.81	846	1.95						
5J29	25.50	840	2.75						
5J30	17.25	841	12.95						
5J33	6.95	846A	1.15						

CASH for YOU!

We urgently need for government contracts military electronic equipment, such as: BC312, BC342, BC348, ART13, APR4, ARC1, ARC3, ARN6, ARN7, BC221, BC788, BC610, and many others. State conditions, type and best price.


2" SIZE METER SPECIALS

— 10 D.C. VOLTS	2.95
— 40 D.C. VOLTS	2.95
— 100 D.C. VOLTS	2.95
— 150 D.C. VOLTS	2.95
— 250 D.C. VOLTS	2.95
— 500 D.C. VOLTS	2.95
— 25 D.C. MILLIAMMETER	2.95
— 50 D.C. MILLIAMMETER	2.95
— 100 with 300 mill SCALE	2.95
— 500	2.95

TERMS: cash with order or 25% deposit—balance C.O.D. 10 days net to rated accts. All prices F.O.B. our warehouse.

Special Quantity Discounts.


All Inquiries Answered Promptly





STEREO RECORDING!

*you can have it
now with
viking*

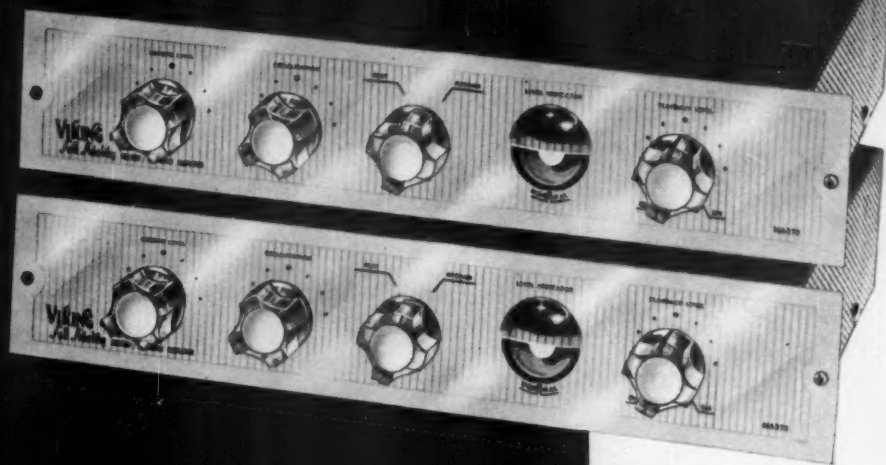

SOME OF THE BEST THINGS COME IN PAIRS

A pair of matching RP61 and RP61S Record Playback Preamplifiers for *stereo recording* as well as playback of stereo tapes — plus conventional erase-record operation.

A pair of in-line heads on the Viking "SR" Tape deck for *stereo realism*, plus the conventional erase and record/playback heads.

Viking tape system components and recorders are sold through dealers. Further technical information may be obtained by writing directly to Viking of Minneapolis.

ALL VIKING DECKS

frequency response: 30 to 14,000 cps plus, at 7½ ips. 40 to 7,000 cps plus, at 3½ ips.

signal-to-noise: 50 db or better.

flutter: 0.2 percent average.

long term speed regulation: ½ of 1.0 percent.

capstan drive: belt driven from full-floated motor platform.

capstan flywheel: 1½ lb.

tape speed: 7½ ips (3½ ips available by changing belt to smaller groove on motor pulley).

maximum reel size: 7".

motor: 4-pole, 60-cycle, (50-cycle motors available at \$2.00 additional charge.)

supply reel brake: mechanically actuated. Felt pad braking surface. Adjustable.

take-up reel brake: mechanically actuated. No adjustment required. Cork pad braking surface.

record/playback head characteristics: track width .090 inch. Gap width .00015 inch. Impedance 2000 ohms at 1000 cycles. Double coil hum bucking winding. Mu-metal shielded. Output 2.5 mv.

recommended bias current: .8 ma. at 68 kc.

erase head characteristics: track width .125 inch, double gap (each .005 inch), inductance 53 mh. at 1 kc, erase 60 db at 68 kc.

RP61 SERIES PREAMPLIFIERS

frequency response, playback: 30 to 14,000 cps \pm 2 db.

frequency response, record-playback cycle: 30 to 12,000 cps \pm 2 db.

distortion (tapes recorded 12 db below saturation): less than 2% within specified frequency range.

internal signal-to-noise ratio: 60 db minimum all units.

equalization: modified NABT

output: 1 volt, high impedance.



Viking OF MINNEAPOLIS


9600 Aldrich Avenue South, Minneapolis 20, Minnesota

EXPORT DIVISION: 23 Warren Street, New York City 7, New York
Cable: SIMONTRICE, NEW YORK (All Codes)

... another
MALLORY
service-engineered
product

New, long lasting switch
with "floating rings"

stops
control job
call-backs

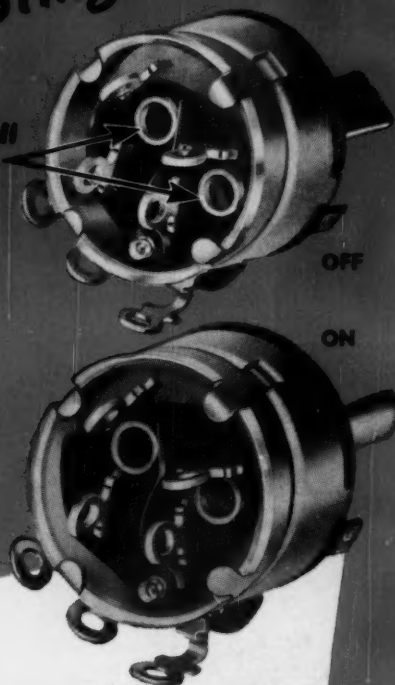

There's something new on Mallory volume controls—a line switch with unique contact action. Make and break is accomplished by spring-snapped motion of "floating" rings of special Mallory contact alloy. Rings rotate with each switch operation . . . presenting a constantly changing contact surface . . . providing these performance extras:

Far Longer Life . . . cleaner make and break . . . less wear and arc erosion.

Overload-proof . . . Snap spring carries no current . . . won't soften when overloads occur.

Positive snap action "feel" . . . with minimum torque.

These extra features come at no extra cost to you. On your next replacement job . . . insist on Mallory controls with these new switches . . . put extra value into every control replacement!

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

• Capacitors • Vibrators • Resistors • Controls • Switches • Filters
• Rectifiers • Power Supplies • Mercury and Zinc-Carbon Batteries